

DISCOVER THE BENEFITS OF THIN SPEAKERS

audioXpress

THE AUDIO TECHNOLOGY AUTHORITY

DECEMBER 2002

US \$7.00 Canada \$10.00

Continuing *Audio Electronics*, *Glass Audio* & *Speaker Builder*

The Zen Amp:
BETTER THAN EVER


BLUEPRINTS to Build
Your Own 100W Amp

TRIODE AMP REDUX:
An Improved French Design

Rules for PERFECT Crossovers

TOP Tube Performers


SOUND ADVICE
For Power Supplies

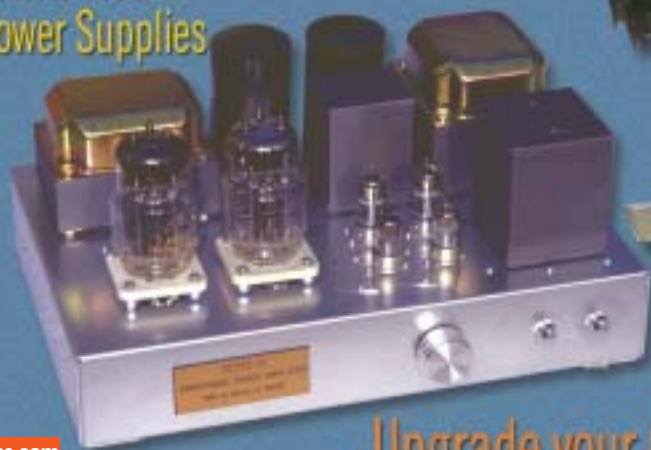

Upgrade your CD
with **SUPER AUDIO**



www.audioXpress.com

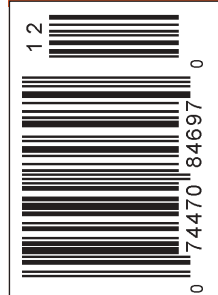



the real deal, Not a cheap imitation

WBT®

THE ART OF CONNECTION

801-621-1500 □ www.wbtusa.com


WATTGATE ⚡
PURE POWER



www.wattgate.com

801-621-1501

SUPRA[®] *Cables*

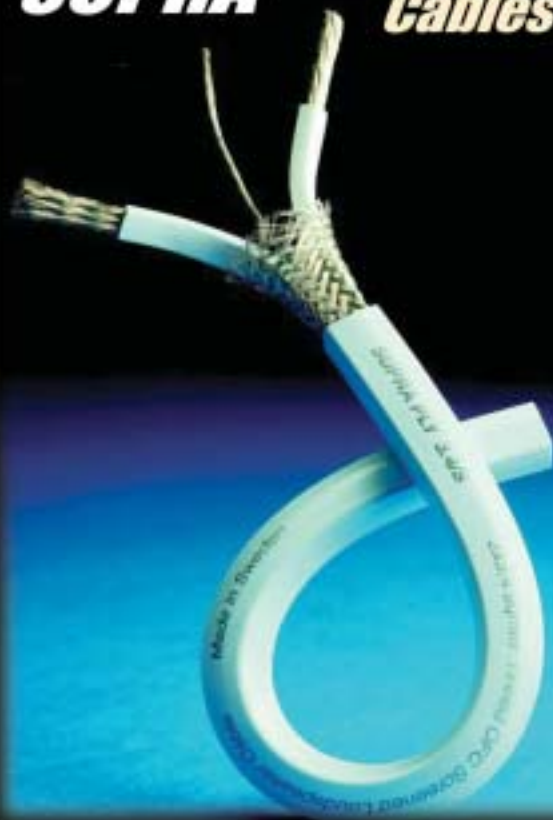

AER



TONIAN LABORATORIES specialty Audio Imports & Distribution

Phone: 818.848.9881
Fax: 818.848.9090
www.TONIANLABS.COM

PHY-HP



*PHY-HP (Next generation) **

PARTS
EXPRESS
ELECTRONICS & MORE
www.partsexpress.com

**1 HOUR
KIT!**

**TITANIC
SERIES**

Designed By

Vance Dickason

NEW

GOT BASS?



Textured Black Polymer Coating



Black Chrome Spikes

10" Titanic Subwoofer System



ASK FOR #300-739



Perfect For Any Room



Complete Kit

BUILD THIS KIT AND YOU WILL!

This system was designed by Vance Dickason and is featured in the 6th. Edition Loudspeaker Design Cookbook. It produces quick, accurate and powerful bass. Perfect for small to medium size home theater or listening rooms. It comes in kit form and can easily be assembled in less than 1 hour. The 3/4" MDF cabinet is finished in a durable textured black polymer coating and is rigidly coupled to the floor using our "black chrome" spikes set. The 10" Titanic driver is precision crafted using only the finest components and features a build quality that rivals the best European drivers. Coupled with our (#300-794) 250W amplifier, this system produces a maximum output of 112dB and yields an F3 of around 24Hz when room loaded. The amplifier contains variable phase, 30Hz bass boost and other high-end features. ♦Frequency response: 24-160 Hz ♦Exterior dimensions: 14-1/4" W x 14-1/4" H x 14-1/4" D ♦Net weight: 46 lbs.



**FREE CATALOG
CALL FOR YOURS
TODAY!**

1-800-338-0531

www.partsexpress.com

Check us out online or give us a call
for all of your audio electronic needs.

725 Pleasant Valley Dr., Springboro, OH 45066-1158

Phone: 937/743-3000 ♦ FAX: 937/743-1677

E-Mail: sales@partsexpress.com

SOURCE CODE: AXM

CONTENTS

VOLUME 33

NUMBER 12

DECEMBER 2002

FEATURES

A 100W/CHANNEL AB DIFFERENTIAL INPUT AMPLIFIER, PART 2

You know you'll learn a lot about amp design when this teacher/astronaut/doctor/audio veteran takes command of the class.

By Norman Thagard 6

ZEN VARIATIONS PART 4: THE PENULTIMATE ZEN

Improvements to the original design produce optimal performance in this single-stage amp.

By Nelson Pass 16

AN AGAINST THE WALL SPEAKER

Here's a flat-speaker project that offers several advantages over more conventional designs.

By John Mattern 24

DESIGN AN ACTIVE TRANSIENT-PERFECT SECOND-ORDER CROSSOVER

Follow this author's simple guidelines to help make designing second-order crossovers a snap.

By John Kreskovsky 36

6C33C-B PUSH-PULL POWER AMPLIFIER II

Some things are better the second time around. In this case, improvements to this original design is time well spent, resulting in increased listening pleasure.

By Daniel J.F. David 40

THAGARD'S POWER SUPPLY REVISITED

Towards a greater understanding of power-supply design.

By Tom Perazella 46

HIGH G_M SMART POWER TUBES, PART 2

This report unveils the features of three vacuum tubes that are gaining popularity among audio enthusiasts.

By Stefano Perugini 50

REVIEWS

SONY SACD PLAYER MODIFICATION

Should you modify your CD player to take advantage of the new SACD format? Our reviewer gives you the answer.

Reviewed by Gary Galo 55



page 40




page 6

audioXpress (US ISSN 0004-7546) is published monthly, at \$34.95 per year, \$58.95 for two years. Canada add \$12 per year; overseas rates \$59.95 per year, \$110 for two years; by Audio Amateur Inc., Edward T. Dell, Jr., President, at 305 Union St., PO Box 876, Peterborough, NH 03458-0876. Periodicals postage paid at Peterborough, NH, and additional mailing offices.

POSTMASTER: Send address changes to: audioXpress, PO Box 876, Peterborough, NH 03458-0876.

ETF5.X SOFTWARE FEATURES

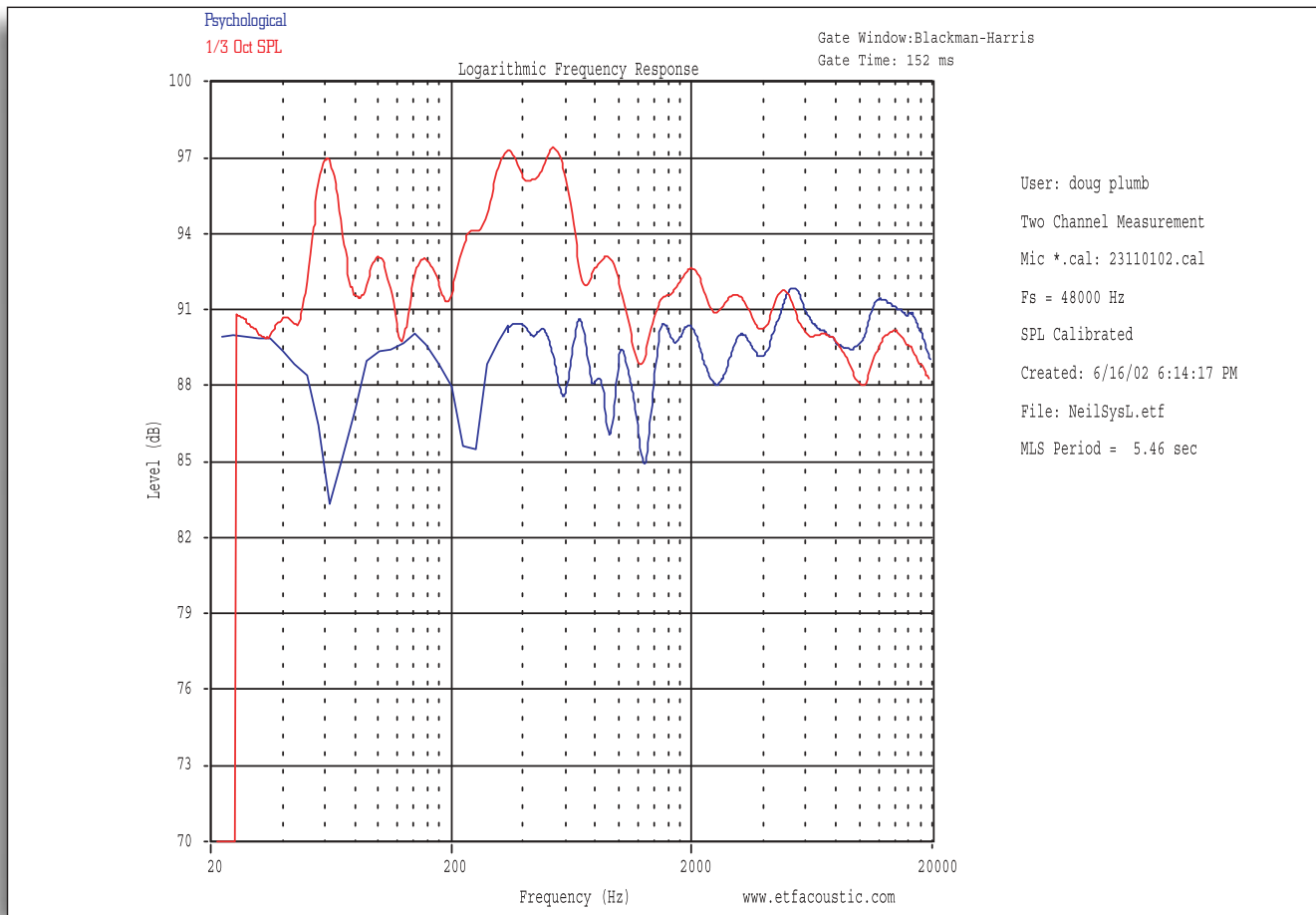

ETF5.x is a software packaged designed to evaluate and set up multichannel sound systems for music playback in small to medium sized rooms ($RT/60 < 3$ sec in valid $RT/60$ frequency range). ETF5.x was designed for recording studios & control rooms, AV presentation rooms, home hifi, theaters, clubs and small churches to trouble shoot acoustical problems and to verify solutions. It incorporates a number of innovations designed to make these measurements easier, cheaper, faster and more relevant to today's thinking on sound systems engineering. Join the PC revolution in sound and take accurate sound measurements using your existing PC that would normally cost thousands of dollars for dedicated hardware.

Innovative features make it easy for both novices and pros to take MLS based measurements for loudspeaker response measurement and for room response measurements. ETF5.x runs on Win 95/98/NT/2000 & XP as well as Mac emulators. Two channel measurements means that one channel (right) is used to measure and the other (left) is used only for measuring the sound card so that the sound card response can be removed from the measurements. Flat 20 Hz - 20 KHz ± 0.1 dB measurements possible on almost any sound card. Download the ETF demo today to test how well your low cost "game" card can be used to take accurate professional quality measurements and save hundreds on "high end" hardware. Use our on line procedure for checking your sound card for accuracy of measurement (included in the free downloadable demo). Check out our web site discussion group for tips, tricks & comments on ETF from other users.

Measurements provided include all typical small/medium sized room parameters such as: Band filtered Energy/Time curves, Fractional octave smoothing for 1/2, 1/3, 1/4, 1/6, 1/8 & 1/10 octave selection, Reverberation time, impulse response, frequency response, phase response and high resolution low frequency resonance finding.

Features such as AutoRanging and the TestSignal CD make it easy & fast for anyone to take accurate measurements using a PC. No complex setup or graphical mic/ speaker distance finding involved. The Multiple Document user interface and graphic overlays make it easy to view & compare results. Graphic metafile export makes it easy to place ETF measured results in presentations requiring any screen resolution.

The basic ETF5.x is only \$149.95 USD and provides all standard measurements for set up and optimization of sound systems.

It can be ordered from our web site at www.etfacoustic.com.

- MLS and tone sweep measurements provide a greater level of sophistication and relevance to today's sound system technicians and engineers over "Real Time" analyzers. The use of your existing hardware makes these measurements substantially cheaper than dedicated hardware systems.
- Test Signal CD - wireless operation with laptop computers. Great for car audio systems.
- Psychological modeling - ETF has an optional add on to more closely model how human beings hear spectral balance in the presence of room reflections. The model used in ETF is the most sophisticated yet used for commercial audio analyzers and makes otherwise difficult or impossible EQ setting an easy procedure. See our online discussion group for user opinions as well as technical explanations. (add on = \$75.00 USD)
- PSD optimized sweep test signal. - This new innovation provides the highest possible dynamic range in measurement over any test signal in existence today. Obtain useful low frequency measurements, even in noisy environments with this add on component. (add on = \$75.00 USD)
- Multi-tone and two tone distortion measurements. ETF5.x gets useful and musically relevant distortion measurements by using new multitone measurement methods to simulate real music. A computer optimized B weighted 16 frequency test signal is used to generate over 600 distinct distortion components for analysis. The two tone measurement provides accurate high order distortion measurements for loudspeakers for benchmarking

- **Fast complete support - expect answers from email questions within hours, not days.**

Check out our web site for a free discussion group, free downloadable demo of the software, a room project example and over 40 pages of textual support literature to answer almost any question. Take free measurements with our demo version and enjoy bug free operation from an extremely well tested body of code. Don't let the price fool you, ETF is highly sophisticated and powerful and compares favorably with much more expensive hardware and PC based software.

Accurate reliable measurements can be taken using the Radio Shack SPL meter. For those in need of accuracy that is only available on individually calibrated mics, the ETF mic/preamplifier is available. Each individual mic and preamp is hand made and calibrated by its designer in Germany. Compare with other units costing much more. The new model provides SPL calibration for actual SPL measurement as well as relative SPL measurements.

AcoustiSoft Inc
465 King St
Upper Peterborough Ont.
K9J2T1
www.etfacoustic.com
www.acoustisoft.com



A 100W/Channel AB Differential Input Amplifier Part 2

Part two concludes our look at this 100W/channel amp, with information about the power supply, construction, and more.

By Norman Thagard

POWER SUPPLY

The voltage doubler/regulator schematic is shown as *Fig. 4*, while the raw power supply schematic is drawn as *Fig. 5*. The power supply of the prototype uses the same type of 200VA toroidal power transformers that were used in my 100W monoblocks. These are transformers that I picked up as surplus for \$15 each. They have two independent 20V RMS windings rated at 5A. As in the monoblocks, two are used in series to provide approximately $\pm 50V$ DC of unregulated, but filtered voltage.

As is my established practice with MOSFET output stages, the DIFF 100 uses a voltage doubler/regulator in order to provide the input stages with a regulated power supply whose voltage is about 5V higher than that for the output stage. This allows the output to nearly “swing the rails” and isolates the output supply from the input stages. Since the supply is bipolar with a center-tapped transformer secondary, it is possible to use full-wave voltage doublers.¹⁰ However, I incorporated half-wave voltage doublers, with which I have long experience, into the DIFF 100.

Regulator outputs were measured at $\pm 56.4V$, but the value of R107 in the positive regulator differs from its counterpart, R108 of the negative regulator. R107/R109 on the upper and R108/R110 on the lower half of the regulator circuit set the positive and negative regulator output voltages, respectively. The greater base current draw of the pnp MPSU60—used as Q104 as opposed to the npn MPSU10 used as Q103—would otherwise cause Vreg(–) to be a couple of volts higher than Vreg(+).

VR101 and VR102 are zener-connect-

ed Motorola pnp transistors. Since currently sold units may not give the desired 7V reference when so used, it is perfectly acceptable to substitute 6.8V zener diodes. Check the regulated output voltages to be sure that they remain around 55V magnitude.

Little further elaboration on the operating principles of the voltage doubler/regulator is necessary, because it is almost identical to that described in a previous article.¹¹ However, please note that the voltage doublers reference one end of C103 and C104 to the positive and negative unregulated rails, respectively. In other amplifiers, I have referenced these capacitors to ground.

The advantage to the approach here is that the required voltage rating of these capacitors is reduced by almost half. The disadvantage is that any ripple on the unregulated rails is applied to the input of the voltage regulators that immediately follow the doubler circuitry. Since I pre-regulate doubler output with zener shunt regulation, this should have little impact.

If you desire the more conventional technique, *do not* connect either the Vunreg(+) or the Vunreg(–) outputs

from the unregulated DC rails to the voltage doubler/regulator PC board. Instead, interconnect the Vunreg(+), Vunreg(–), and star ground traces on the input side of that board together with jumpers. Star ground itself is the midpoint of a heavy brass bus bar that spans the common terminals of the unregulated power-supply filter capacitors.

Of course, C103 and C104 should be 150V DC-rated units if this modification is made. Otherwise, the voltage rating of C103 and C104 may be as low as 63V. A rating of 80V is shown on the schematic and in the parts list because similarly rated components were incorporated into the prototype due to availability.

If you take this option (and even if you don't), you may omit the pre-regulator. This will increase power dissipation in pass transistors Q5 and Q6, so larger heatsinks may be required for these devices. These power BJTs could dissipate several watts in the absence of pre-regulation.

PARTS AVAILABILITY

It is unusual when no suitable alternative to a discontinued component is available, but can occur. The DIYer may experience some difficulty obtaining some existing parts. Although I attempt to use readily available components, other considerations sometimes supersede this priority.

An example of this would be the



PHOTO 1: Amp front.

high- g_m JFETs used in my phono preamp.¹² In that case, I knew of no alternative device that would be comparable. However, the fact that these devices allowed realization of a discrete topology otherwise unrealizable took precedence. I believed it possible that if the article attracted sufficient interest, *audioXpress* might step in and secure the transistors for sale to builders.

Also, in that particular case, I knew that those JFETs were readily available in small quantities by purchase over the Internet from Erno Borbely, albeit at a price significantly in excess of that obtained through quantity purchase. A reader has subsequently sent an e-mail indicating that Match-A-Knob of 170-30 Jamaica Avenue, Jamaica, NY 11432 (800-321-5662) has plenty of these devices in stock for about \$1.25 each with a minimum order of \$25.

Employment of replacement-series parts may not be a panacea for the builder. I found one of four channels of my phono preamp to be unusually noisy, and traced it to the negative voltage regulator, a device from one of the several popular replacement-series

manufacturers. A quick look showed a second such part to be noisy as well. None of the several standard brand regulators that I subsequently purchased suffered from this defect.

While this could be a fluke, it is one reason I prefer standard brand components rather than replacement-series devices. On the other hand, some of my designs have specified replacement-series devices, so my reluctance is admittedly not absolute.

When I offer designs for publication, I am at least as much interested in the presentation of concepts as I am in the presentation of a DIY project. My hope is that a DIYer might gain sufficient knowledge of principles to modify my designs or even effect an entirely new design. It is very satisfying when former students of my "Feedback Amplifier Principles" course write or e-mail me to say that they've successfully built their own preamp or amp; some have even boasted that their design was better than anything that I presented. Surprisingly, I find that pleases rather than offends me. My further hope is that my articles have enough socially redeem-

ing value to justify publication, even if the design is not practical for the average DIYer.

It would be dangerous to speak for the editor, but I suspect that the purpose of *audioXpress* is broader than presentation of a collection of DIY projects. My impression is that the magazine generally serves the interest of technically minded devotees of sound reproduction. There certainly have been a number of purely tutorial articles over the years, so I am satisfied if purported design articles adequately serve this function, even though centered on a design rendered unrealizable through component unavailability.

I do acknowledge that the author has an obligation to apprise the reader of any known availability problems. This is something that I have done in my articles. It should be understood, however, that the author doesn't always know that availability problems exist at the time of article submission and certainly cannot know whether manufacturers will discontinue components afterwards.

Bear in mind, too, that *audioXpress* is not a peer-reviewed journal. In fact,

www.audiokits.com

DIY AUDIO

www.audiokits.com

Hi-End Tube Kits

- Phono Preamp
- Lineamp
- 15W SE Power Amp & Power Supply

Accessories

- Cables
- Capacitors
- Chassis
- Connectors
- Potentiometers
- Stepped Attenuators

All-FET Amps

- All-FET Line Amp
- All-FET DAC
- All-FET Ribbon 20/40W
- All-FET Millennium
- Headphone Amp
- Super Buffer

Audiokits.com is the Internet's best source for hi-tech, hi-end audio kits and components. We offer a variety of options including fully-assembled and tested kits.

audiokits.com

Audiophile Euphoria™

FIGURE 4: Voltage doubler/regulator schematic.

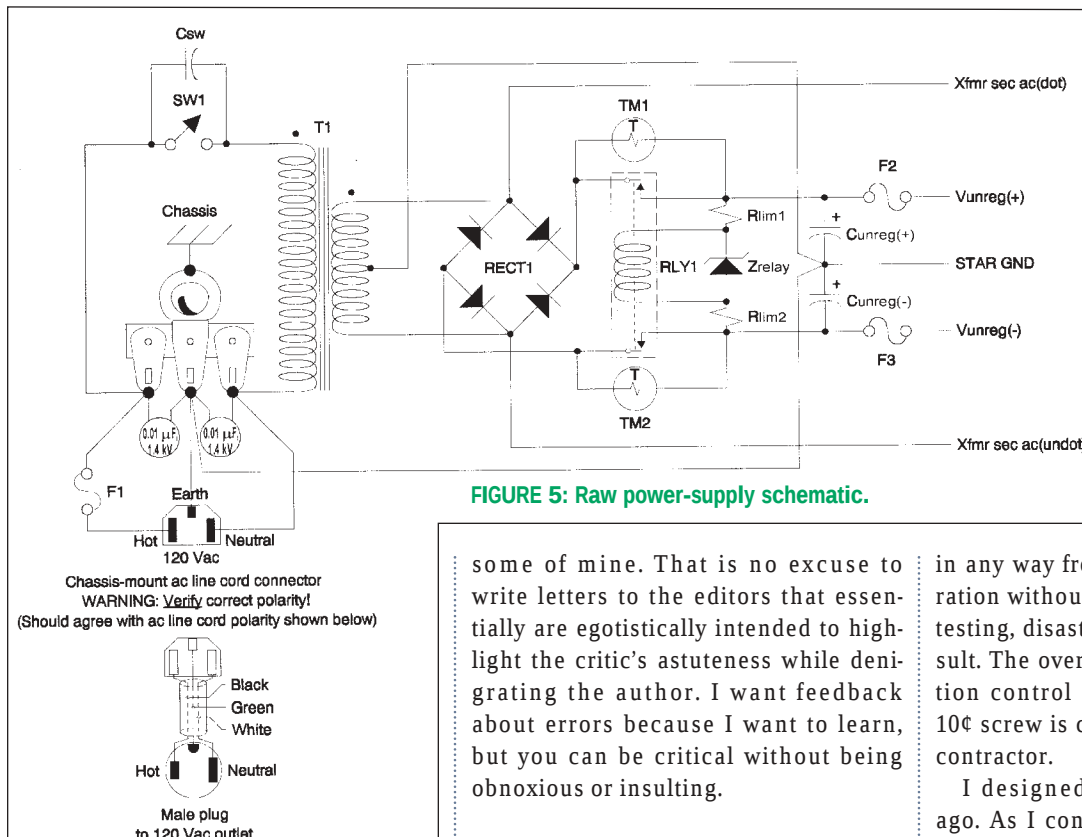
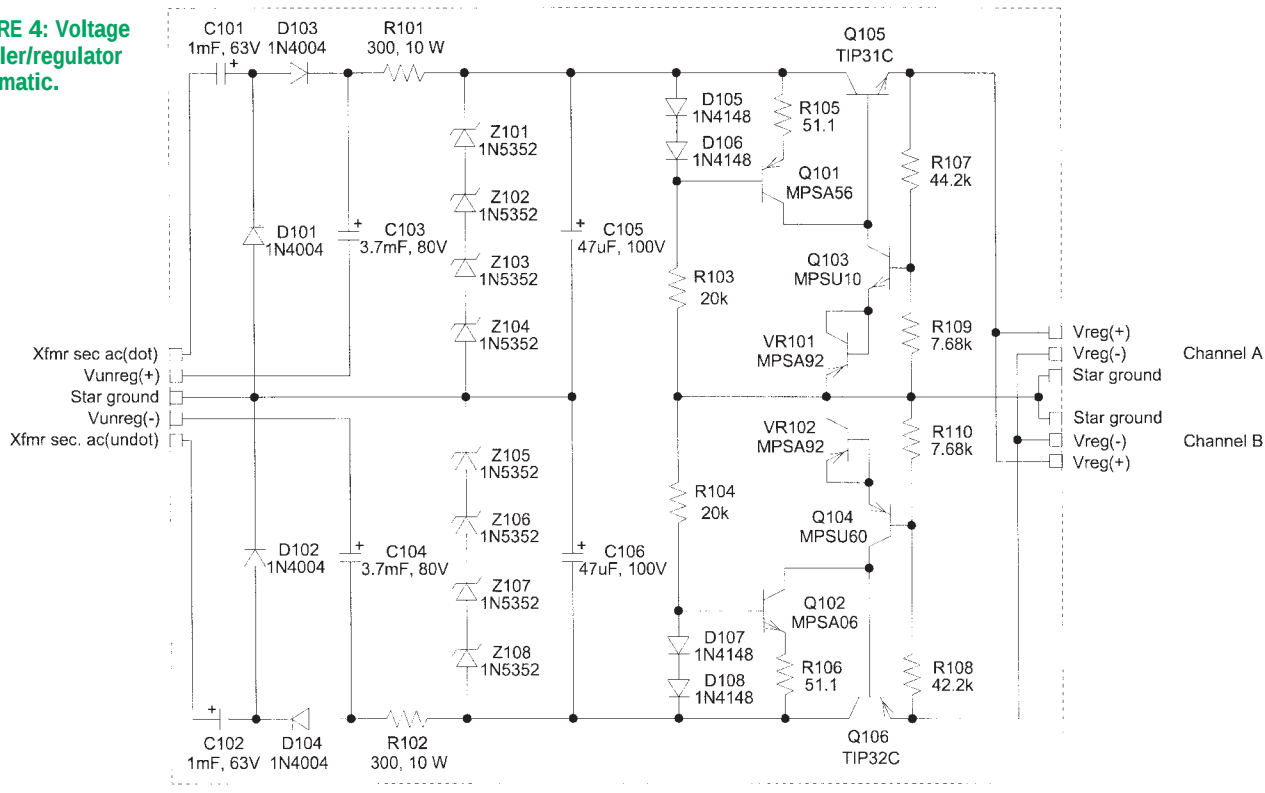


FIGURE 5: Raw power-supply schematic.

fier front-end and voltage regulator/doubler are provided as Fig. 6 and 7, respectively.

I have developed a much more sympathetic attitude concerning quality assurance issues since I began writing articles. There is a reason why NASA human space flight costs are high. If every last thing is not well-documented and if the final product changes

some of mine. That is no excuse to write letters to the editors that essentially are egotistically intended to highlight the critic's astuteness while denigrating the author. I want feedback about errors because I want to learn, but you can be critical without being obnoxious or insulting.

CONSTRUCTION DETAILS

You can infer many of the recommended construction details from the amplifier schematic (Fig. 1, Pt. 1), voltage doubler/regulator schematic (Fig. 4), and raw power-supply schematic (Fig. 5). In addition, the PC board patterns for the ampli-

ifier front-end and voltage regulator/doubler are provided as Fig. 6 and 7, respectively.

I designed this amp several years ago. As I confirmed the actual component types and values, I realized that potential builders would need a "heads-up" since some of those component values and types would ideally be different. Also, I am more experienced now, and some of my design and construction preferences have changed.

while authors are paid for accepted submissions, the pay does not justify the expense of even proofreaders, let alone independent technical review prior to publication. There may be mistakes in articles; there certainly have been in

Over the Top

Music performance and craftsmanship that exceed your expectation in every way

Compass DANCER SERIES

Compass DANCER SERIES DESIGN HIGHLIGHTS:

- Carbon-paper woofer cone
- Silk-fabric soft dome tweeter; Ceramic type on some models
- Innovative magnet flux design with corrective cooper elements on all drivers, resulting in significantly reduced third and second harmonic distortions
- Cast aluminum driver frame
- Hand picked, matched-pair drivers on all models
- Phase coherent crossover designed by world renowned master of speaker design, built with components of the highest quality and thoroughly tested with digital-based measuring equipment
- Massive, sonically dead front baffle which places drivers in a time-coherent physical arrangement
- Multi-chamber reinforced cabinet with solid wood side panels, handcrafted to the highest furniture grade



Behind the Scene

Dr. Joseph D'Appolito has been working as consultant for Usher Audio since early 2000. A world renowned authority in audio and acoustics, Dr. D'Appolito holds BEE, SMEE, EE and Ph.D. degrees from RPI, MIT and the University of Massachusetts, and has published over 30 journal and conference papers. His most popular and influential brain child, however, has to be the MTM loudspeaker geometry, commonly known as the "D'Appolito Configuration," which is now used by dozens of manufacturers throughout Europe and North America.

Dr. D'Appolito designs crossover, specifies cabinet design, and tests prototype drivers for Usher Audio, all from his private lab in Boulder, Colorado. Although consulting to a couple of other companies, Dr. D'Appolito especially enjoys working with Usher Audio and always finds the tremendous value Usher Audio products represent a delightful surprise in today's High End audio world.

With an abundance of original concepts in loudspeaker design, backed by thirty years experience in manufacturing and matched with an eye for fashion and unparalleled attention to detail, is USHER the ideal original design manufacturer you've always been looking for? Find out the answer today by talking to an USHER representative.

USHER

USHER AUDIO TECHNOLOGY

67, Kai-Fong Street, Sec.1, Taipei 100, Taiwan

Tel: 886 2 23816299 Fax: 886 2 23711053

Web site: www.usheraudio.com E-mail: usher@ms11.hinet.net

These concerns about configuration control notwithstanding, there was an awful temptation to offer a modified design for this article that would differ from the as-built amplifier. Thus, Q1–Q10 are specified here as MPSA06/MPSA56 complementary devices. However, the actual amplifier is populated with MPSA05/MPSA55 BJTs.

There is no difference in the AC parameters, but the '06/'56 pairs have an 80V DC collector-base breakdown voltage, while the '05/'55 pairs are rated at only 60V DC. Given the voltages involved, the former are to be recommended for a new design, but again, they are not the devices actually in the prototype. Given that there have been no failures of any of these particular transistors, I am not inclined to retrofit my amplifier at this point.

Similarly, protective zener diodes Z3–Z6 are specified as 1N4739A units. The amplifier had 1N5242Bs in these positions. Again, no failures have occurred with the former devices, so I did not change the prototype per my current recommendation. The 1N4739A, whose V_z is 9.1V, affords better protection to its associated MOSFETs and is also a sturdier device due to its 1W power rating. Since, as previously mentioned, the 2SJ49/2SK134 Hitachi power MOSFETs can be damaged if gate-source voltage (V_{gs}) exceeds 14V, the 12V V_z of the 1N5242B added to the forward drop of a diode limit is too close to (V_{gs})_{max} for comfort.

Z5 and Z6 were added after the fact when MOSFET M5 failed.¹³ Since the PC board pattern did not provide for installation of Z5/Z6, I soldered them to the foil side of the board. Per the cited reference, which was a letter to the editor from Nelson Pass, a signal diode such as a 1N914 or 1N4148 can be oriented in the same polarity as a zener and used in lieu of a zener. Unfortunately, I had made this modification before I saw the recommendation contained therein. As I recall from conversation with Nelson, the failure mode was discovered when a storage scope documented the condition that

caused the failures.

Some components were selected simply because they were in my parts bin. For example, I used a TIP31C for Q11, but a more cost-effective choice is the TIP29, since the (V_{ce})_{max} = 100V and (I_c)_{max} = 3A ratings of the former are ridiculously in excess of the requirement.

The amplifier schematic (Fig. 1) depicts a single channel. Duplicate the circuitry for a stereo (two-channel) configuration. The exception is the balanced/unbalanced mode switch, which appears on the schematic as a SPST type. If you construct the DIFF 100 as a monoblock, this is the appropriate type. However, as a stereo unit, only a single DPST mode switch is required to accommodate both channels, unless you plan to operate one channel in balanced and the other in unbalanced mode.

The original schematics and PC

board patterns were manually drawn. There lurks a danger that the newly produced electronic versions submitted to the publisher contain errors despite my careful attempts to verify exact equivalence. I made some minor changes to the patterns that should have no effect, but new boards were not etched, populated, and tested from the modified patterns. No doubt, letters will ensue quickly and will be welcomed if mistakes are found.

I have tried to provide sufficient detail in the schematics to make physical construction and interconnections obvious. I use quick disconnects (QDs) liberally in my prototypes and recommend them for beginners who are more likely to make a failure-producing mistake requiring board removal. Were I to construct this amplifier anew, I would omit them due to the proven reliability of the prototype. The PC board patterns


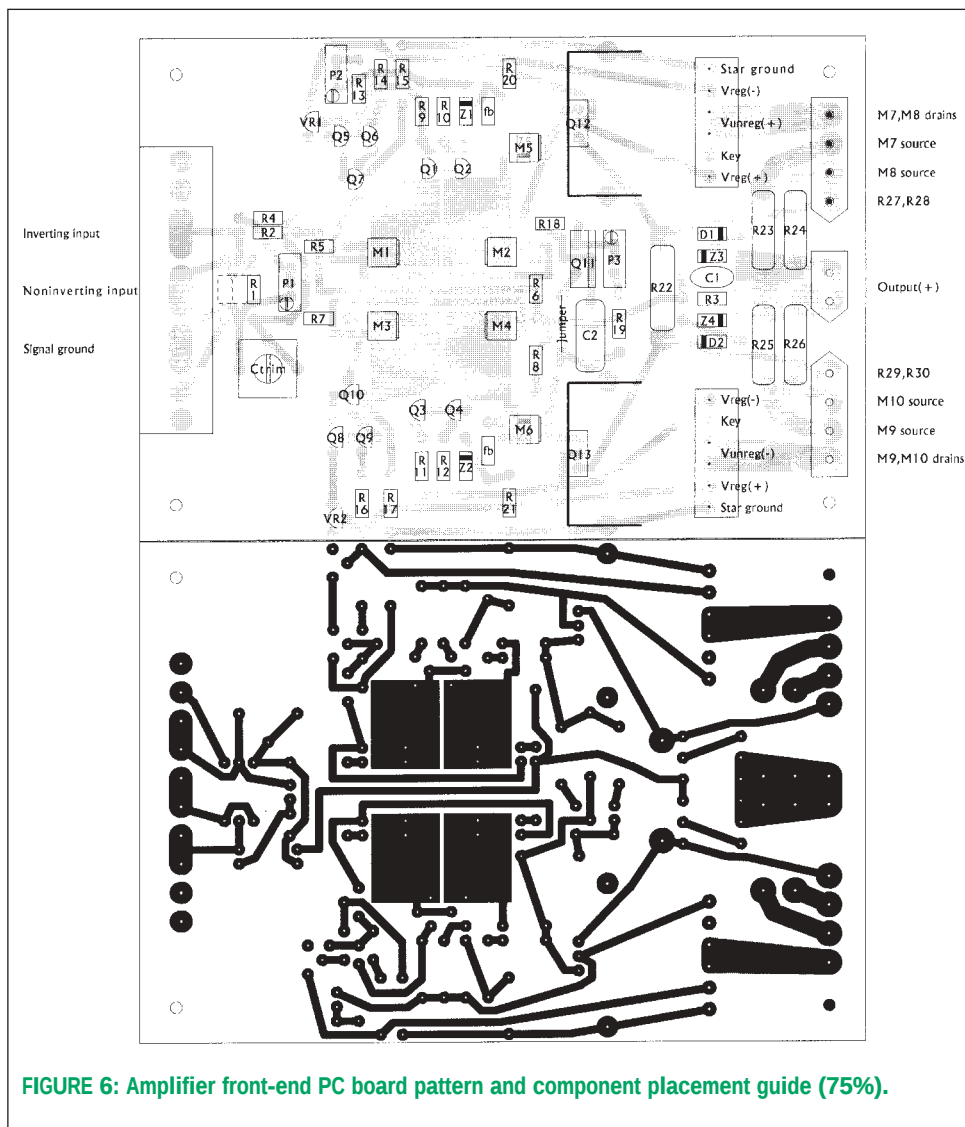


FIGURE 6: Amplifier front-end PC board pattern and component placement guide (75%).

PARTS CONNEXION

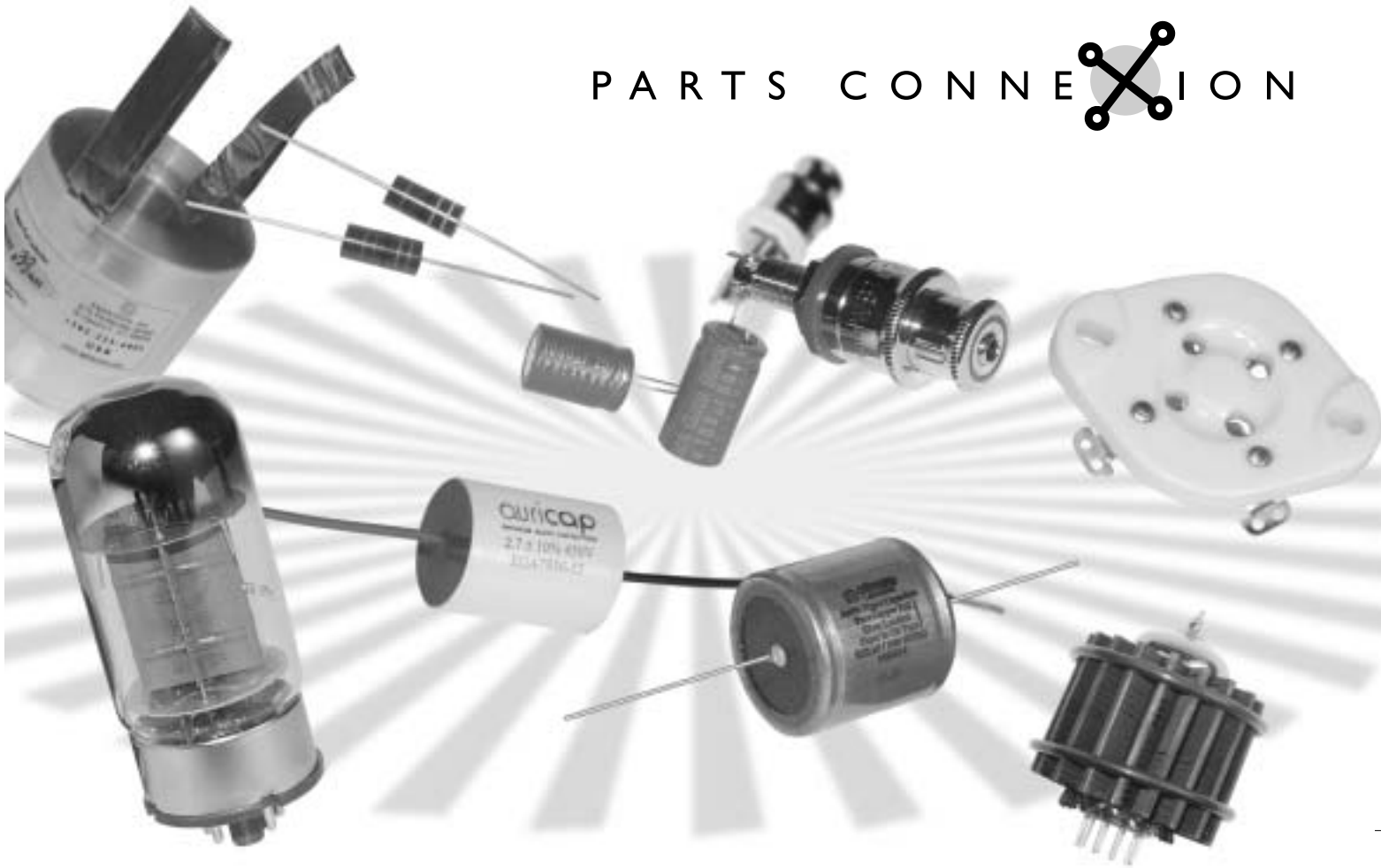

the authority on hi-fi DIY

pcX is adding a number of new lines including... AUDIO NOTE Copper and Silver Foil Capacitors; RIKEN Ohm 2-watt carbon resistors; NICHICON electrolytic capacitors; AZUMA premium gold-plated/ceramic tube sockets; TRT DynamiCap film capacitors (updated/revised InfiniCap); TKD conductive plastic potentiometers... as well as a greatly expanded collection of N.O.S. and O.S. vacuum tube offerings.

Check out our catalog online, then sign up for our eCONNEXION newsletter so you'll never miss a thing!



Subscribe to **eConnexion**, a monthly email newsletter featuring the latest happenings at pcX - including great specials, clearance items & new product introductions.

toll free
order line

1-866-681-9602 US & Canada only

www.partsconneXion.com

Tel: 905-681-9602 Fax: 905-631-5777 info@partsconneXion.com

Visa, MasterCard, American Express, Paypal, BidPay, Money Order/Bank Draft/Cashier's Check, Personal Check (after clearance)

PARTS CONNEXION, 2885 Sherwood Heights Drive, Unit #72, Oakville, Ontario, CANADA L6J 7H1

IMPORTANT NOTE: No "on-site/walk-in" business at this time



reflect the particular QDs actually used right down to the mix of male/female headers that prevent inadvertent interchange of cables.

Transistors Q12/Q13 require heatsinks. Please note that the heatsinks are grounded by the PC board foil pattern, making it necessary to insulate the BJT collectors from the heatsink in the usual manner.

WARNINGS

Two warnings are in order. The first involves power-supply connections to the standard 3-wire, 120V AC-line cord. The power-supply schematic (Fig. 5) shows the connection via a standard chassis-mount male QD receptacle, which would receive 120V AC power through a standard detachable power cord. I actually use AC line filters that are integrated with a male, chassis-mount AC line connector. These filters may be labeled to indicate “hot” and “neutral” connector pins. The “earth” connection to chassis may be via a similarly labeled “earth” or “ground” connector, via a wire with green insulation that must be bolted to the chassis, or may automatically be accomplished through the metal screws that attach the filter/connector unit to the chassis.

The best approach for verification of proper connection of any chassis-mounted AC connector is accomplished with the AC line cord plugged into the connector but unconnected to the AC wall outlet. Use an ohmmeter to check continuity between the plug (AC wall outlet) end of the line cord and the three chassis-mounted connector pins in turn. The smaller of the two parallel spades plugs into the

“hot” terminal of the AC wall outlet, the larger into the “neutral,” and the circular middle prong contacts the “earth” terminal. If you use an integral filter, it should be rated at least 3A. You may omit the two 0.01 μ F, 1.4kV disc ceramic capacitors shown on the power-supply schematic if you use a filter.

Second, the 10 Ω resistor shown connected between the outer (shield) connection of the RCA jack and chassis in Fig. 1 is prone to fail open. The placement of this resistor in this manner is very effective at eliminating a potential ground loop, but any voltage difference between ground potential of preamplifier and amplifier will cause current flow through this resistor. This scheme has been employed in all of my amplifier

designs, and resistor failures have occurred in every one of them.

I am not the first to use this technique for ground loop prevention. Recently, I found that the signal ground to chassis (and hence to earth ground) resistor used in my Krell preamplifier measured 1.5k Ω instead of its marked value of 10 Ω . I have not determined whether these resistors fail due to excessive current flow or voltage spikes, but I suspect the latter since measurements taken in normal circumstances have failed to show significant steady-state voltage across them.

In the A75, Nelson elected to isolate chassis from circuit ground at the power supply with a 5.1 Ω , 1W resistor. This resistor was in parallel with two

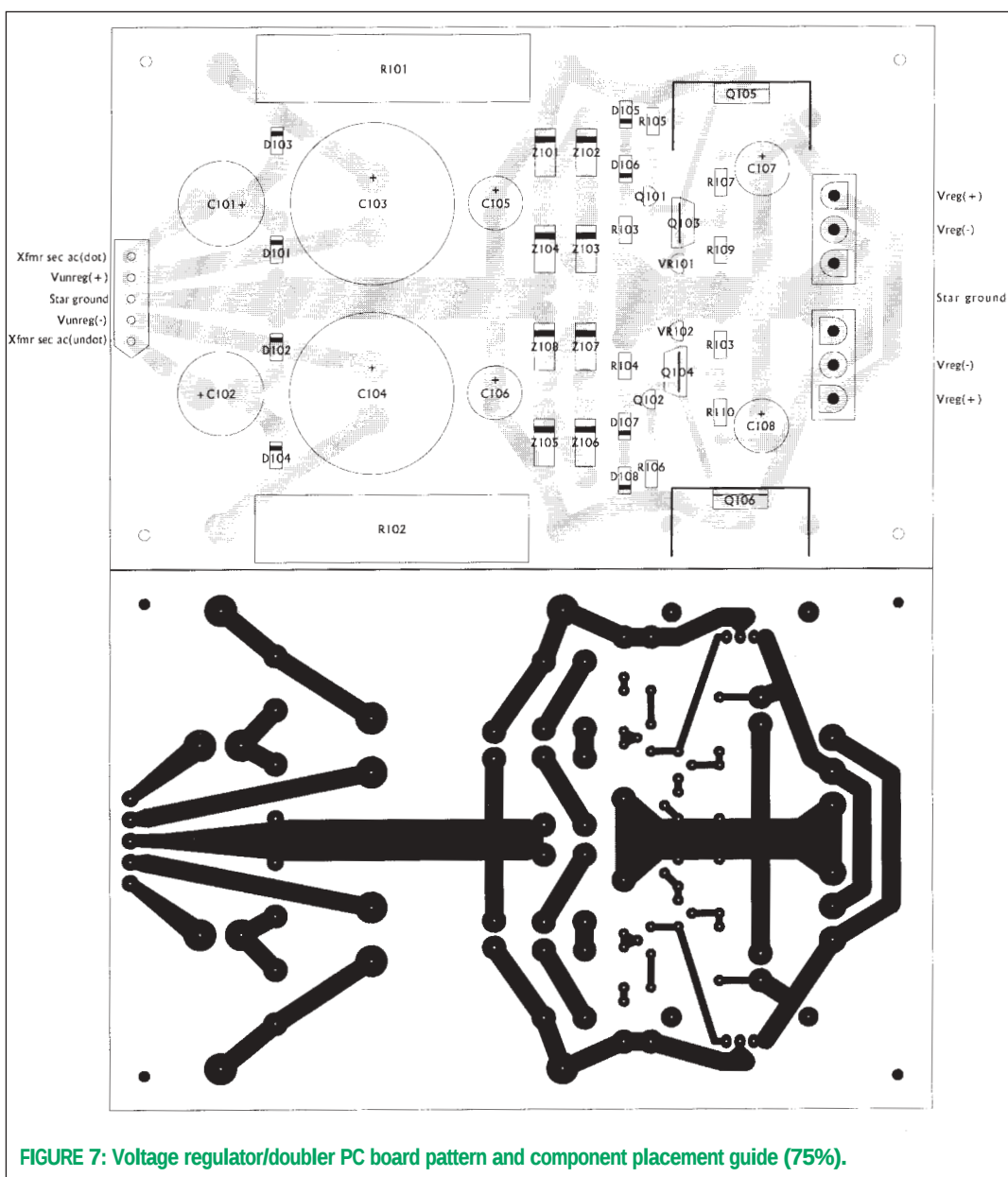


FIGURE 7: Voltage regulator/doubler PC board pattern and component placement guide (75%).

Transformers & Enclosures

In Stock...





Torodial Power:

13 sizes (15 - 1500 VA)
6 VAC - 240 VAC

"Classic" Tube Output:

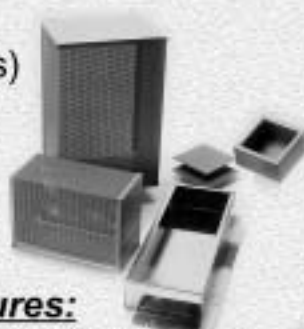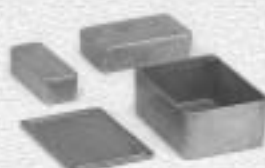Single Ended (up to 75 watts),
Push-Pull and Potted (up to 280 watts)



Enclosures:

Aluminum & Steel Chassis,
Diecast Aluminum, Plastic
and Rack Mount



Filament & Low Voltage Power Transformers:

Open & Enclosed

"Classic"

High Voltage Transformers:
Plate, Plate/Filament Combo
& Filter Chokes (Open & Enclosed)

Contact us for free catalogs & a list of stocking distributors



HAMMOND MANUFACTURING™

256 Sonwil Dr. - Cheektowaga, NY 14225 USA

Phone: (716) 651-0086 Fax: (716) 651-0726

394 Edinburgh Rd., N. - Guelph, Ontario N1H 1E5 Canada

Phone: (519) 822-2960 Fax: (519) 822-0715

www.hammondmfg.com



oppositely oriented 1N5401 diodes. This suggests that he was protecting against failure due to voltage spikes, although the diodes are rated at 3A continuous. You may similarly choose to parallel the 10 Ω resistors with diodes as do (some of) the prominent commercial designers. In general, the higher the resistor's wattage rating, the higher is its maximum voltage rating.

INITIALIZATION

The initial operation requires two to four adjustments and should be made with no load attached. P1 sets the low-frequency common-mode rejection ratio (CMRR), and Ctrim sets the high-frequency CMRR. P2 is used to null any DC offset at the output. Finally, P3 sets the DC bias current of the power MOSFETs in the output stage.

The initial adjustment should be to P3, but if two voltmeters are available, you should use the second to monitor output offset. Before power-on, place P3 at its maximum resistance. Measuring voltage across any of the four resistors R23–R26 affects monitoring of output MOSFET source current. With a resistor value of 0.5 Ω , current (mA) is twice the measured voltage (mV). Adjust for a reading of 50–60mV, which corresponds to a bias current of 100–120mA.

Next adjust P2 for 0V DC at the output. This voltage will vary over the short run, but should stabilize at no more

than 60mV magnitude. Both P2 and P3 should be readjusted after at least 30 minutes of continuous operation to allow for the inevitable thermal effects.

Adjustments of P1 and Ctrim are not critical since, as I mentioned earlier, each can be replaced with a fixed value component. I used my oscilloscope to

make these adjustments. With the balanced/unbalanced switch in the balanced position and driving both inverting and non-inverting inputs with the same 1kHz signal, I adjusted P1 for *minimum* output. Then, with 20kHz input, I adjusted Ctrim for *minimum* output. Using the highest driving signal

TABLE 2
POWER SUPPLY PARTS LIST

(ALL RESISTORS ARE 1%, 1/4W METAL FILM UNLESS OTHERWISE SPECIFIED)

SCHEMATIC REFERENCE	PART #/VALUE	DESCRIPTION	MANUFACTURER
C101, C102	1m, 63V	electrolytic	
C103, C104	3.7m, 80V	electrolytic	
C105, C106	47 μ , 100V	electrolytic	
Csw, AC hot, neutral to gnd (2)	10n, 1.4kV	disc ceramic	
Cunreg(+), Cunreg(-) (3)	10m, 63V	electrolytic	
R101, R102	300, 10W	wirewound	
R103, R104	20k		
R105, R106	51.1		
R107	44.2k		
R108	2.2		
R109, 110	7.68k		
Rlim1, Rlim2	470, 5W	wirewound	
Q101	MPSA56	pnp BJT	Motorola
Q102	MPSA06	nnp BJT	Motorola
Q103	MPSU10	nnp BJT	Motorola
Q104	MPSU60	pnp BJT	Motorola
Q105	TIP31C	nnp power BJT	TI
Q106	TIP32C	pnp power BJT	TI
VR101, VR102	MPSA92	pnp BJT	Motorola
D101–D104	1N4004	1A, 400 PIV Diode	
D105–D108	1N4148	diode	
Z101–Z108	1N5352B	15V, 5W zener	
Zrelay	1N5359B	24V, 5W zener	
RECT1	600 PIV, 25A	bridge rectifier	
TM1, TM2	KC011L	NTC thermistor	Keystone
F1	3A slow-blow	line fuse	
F2, F3	3A fast-blow	DC rail fuse	
T1	80Vct, 5A	power transformer	
RLY1	76R4-24DC-SCO	DPDT relay	Sigma
Chassis-mount male AC power connector, 3-conductor AC line cord, SPST on/off switch rated 120V AC @ 10A, fuse holders, TO220 heatsinks, standoffs, enclosure			


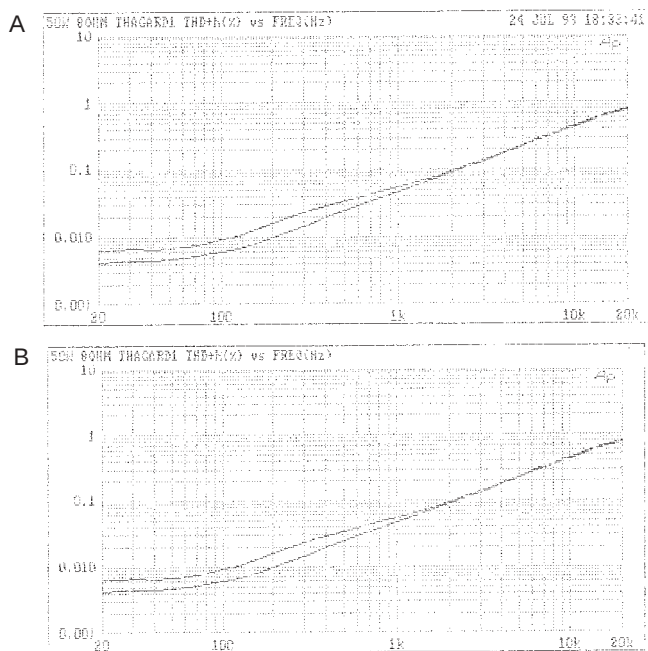


FIGURE 8A–D: THD curves.

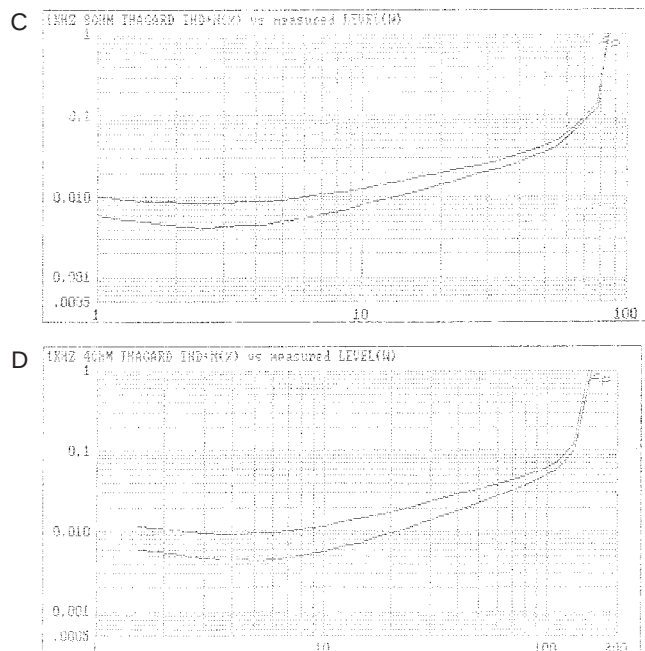

not to exceed clipping or obvious distortion gives the maximum sensitivity since even in the 2mV/division scope vertical sensitivity position the trace can be nearly flattened.

I measured a high-frequency CMRR of over 60dB with these adjustments. The CMRR is just the ratio of differential-mode gain to common-mode gain. The differential-mode gain is about 20, and the common-mode gain will be the observed output voltage from the test divided by the input voltage that produced it. CM gain will be much less than 1, so CMRR should be much greater than 20 (26dB).

PERFORMANCE

The THD curves supplied (*Fig. 8, a-d*) were generated on PASS Lab's Audio Precision analyzer. They show that the prototype could not achieve more than about 85W into an 8Ω load. Since I can achieve slightly more than 100W at clipping on my test bench, I assume the published curves were for both channels driven simultaneously. The limitation is due to the power supply. Rail voltage drops rapidly as the output

power increases.

Again, the power transformers were surplus units with only 10,000μF filter capacitors used. A common power supply powered both channels. A stiffer supply should achieve 100W/channel with little trouble, even with both channels driven simultaneously.

Note that at the 50W output level, distortion ramps up smoothly with increasing frequency to 0.75% at 20kHz. My goal is usually no more than 0.1% even at this frequency at or near full-rated output. This level of high-frequency distortion reflects the high impedance in the feedback network. Recall that this was a necessary condition to keep input impedance at a reasonably high level in balanced input mode. At lower output levels or frequencies, THD is quite low.

In no event should anything close to 50W at 20kHz be output in normal use. There is very little energy at the upper end of the audio band and high-frequency drivers; i.e., tweeters are seldom designed to accommodate more than a few watts without damage. In listening tests, highs are smooth. There is no audible

concomitant to the THD. Indeed, it is not unusual for tube amplifiers to have such levels of THD at even lower frequencies.

It is interesting that a friend of mine who has been using a pair of my 100W class A monoblocks for ten years in a pretty good system thought that this was the best sounding of the four amplifiers with which I have been associated. This, despite the fact that this amp is class AB using a common power supply, whereas the others were operated class A and constructed as either monoblocks or as dual mono units.

I am currently working on a balanced mode preamp. Until then, I cannot comment on the sonic quality of this amplifier when driven by differential sources. With unbalanced inputs, the DIFF 120 is a solid performer, even in a system with a Krell preamplifier and Martin Logan ReQuest speakers. ♦

REFERENCES

10. Joe Berry, "Letters," *Audio Electronics*, 5/00, p. 42.
11. Norman E. Thagard, "A Case Study in Audio Amp Design, Part 5," *Audio Electronics*, 3/00, pp. 33-37.
12. Norman E. Thagard, "A Phono Pre-Preamplifier for the CD Era, Part 1" *audioXpress*, 1/01, p. 25.
13. Nelson Pass, "Letters," *TAA*, 2/93, p. 38.

Sophia Electric

Presents "S.E.T."
high end line of tubes,
tube amplifiers,
cables and parts

www.sophiaelectric.com

Call: 703-204-1429

Fax: 703-560-3502

e-mail: sophiaelectric@yahoo.com

S.E.T. Tube Amplifiers:

205D drive 845 Single-ended amp
with Litz wire transformer, call.

300B amplifier, KT66 drive 300B.
Artistic beauty, glorious single
ended performance (see photo,
right). \$3500

6P3 Push and Pull, 35 watts of
sweet tube sound (same looks as
the above 300B amp). Amazing
performance/price ratio

Dealers wanted worldwide



S.E.T. 300B single-ended amp
Beauty with amazing voice.

Mesh Plate 300B

S.E.T. tubes (known as Sophia)

S.E.T 300B mesh plate tubes, per-
haps the world's best sounding

S.E.T. 300B/2.5V mesh plate for 2A3
Amplifiers. Huge upgrade.

S.E.T. 274B/274A rectifier tube,
killer performance at cost.

S.E.T. 205D mesh plate tubes.
More tubes to come.



Pre-assembled tube phono stage
board. Introduction special:
\$199-\$299

Soft start delay action board for
300B/845/211/2A3 tube filament
warm up. \$29-\$35 each

Cute Gold-plate all metal knob: \$9.95

High-end performance speaker cable,
interconnection cable and power
cables.

Tube sockets and transformer covers

Zen Variations Part 4: The Penultimate Zen

Much spit and polish has been applied to this Zen amp design to maximize its efficiency. **By Nelson Pass**

The Penultimate Zen is the sum of several incremental improvements to the original Zen amplifier of 1994 ("The Pass Zen Amplifier," TAA 2/94). Eight years just flies by, doesn't it? These improvements are contained here and in Parts 2 through 3 (July and Aug. '02) of the Zen Variations, and is likely the last version of this amp, although by no means the end of the variations on the theme of single-stage amplification.

In Part 2 we developed an improved active current source load for the single gain device, which is at the heart of the amplifier. Originally designed for the Aleph amplifier series, this current source doubles the output current and significantly lowers the distortion of the circuit over the original constant-current source. Because the original Zen amplifier is limited in both power and fidelity, this is a welcome improvement.

The original Zen amp is also limited in its rejection of power-supply noise, and benefits from having a quiet, stable power supply. In Part 3 we discussed some possibilities for power-supply regulation for this and other Zen amplifiers.

The final shortcoming to address in the Penultimate Zen is the low input impedance. Depending on the version and the desired gain and distortion figures, the original Zen amp has an input impedance that varies from 600 Ω to a couple thousand ohms. For many audio sources, this input impedance is simply too low to give optimal performance. The ideal input impedance would be something up around 47k Ω .

We will address this fault here and

now, and then go on to present a final circuit with a nice finished printed circuit board design.

UPPING THE INPUT IMPEDANCE

The issue of increasing the input impedance of the Zen amp is a delicate one. There is no way around the need to add circuitry to accomplish this, but in the spirit of the Zen amp, we wish to do it minimally.

The input junction of the gain MOSFET of the amplifier is operated at virtual ground, so that previous Zen amps have an input impedance that is the value of the input resistor between the input connector and the Gate of the MOSFET. You could simply increase the values of the input and feedback resistor, but then you bump into the non-ideal nature of the MOSFET.

The Gate of the MOSFET has essentially an infinite input impedance at

DC, but offers capacitance between the Gate and Source and the Gate and Drain pins. The amount of the capacitance is not so great and by itself does not impose serious limits on the resistor values. The problem is that this capacitance varies under differing voltage and current conditions, and is thus nonlinear in character, producing distortion at higher frequencies. You can clearly see this effect on the distortion versus frequency curves of the previous Zen amplifiers, where somewhere above the midrange the harmonic distortion begins increasing with frequency. The higher the resistance at the input, the earlier this effect starts.

To have a high input impedance while maintaining low distortion at high frequencies, the amp needs a buffer. The most obvious approach is to use an input follower (*Fig. 1*). Here a small N channel MOSFET is biased up to serve as a Source follower, presenting a very high input impedance, and a fairly low output impedance while following the input voltage. Since we use a small MOSFET for this purpose, the input capacitance is tiny enough not

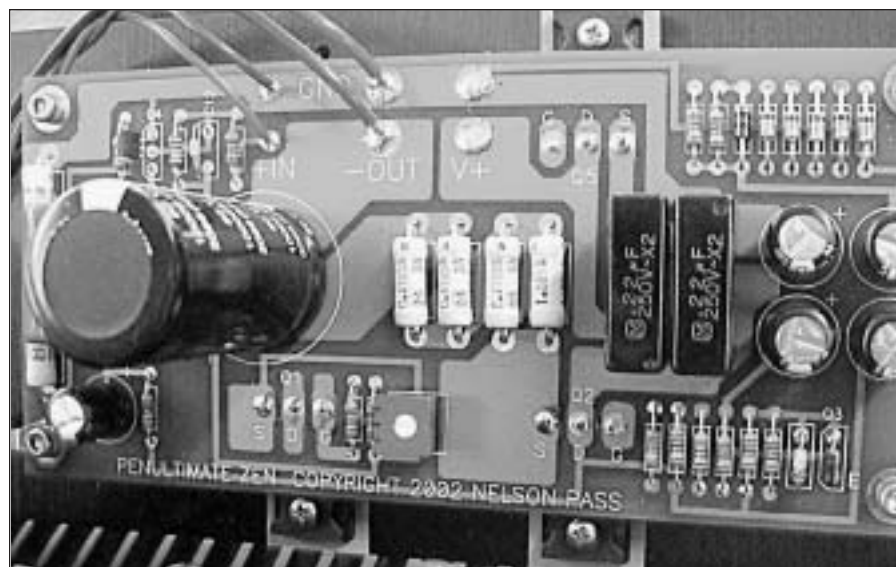


PHOTO 1: The loaded PC board.

to have a significant effect at audio frequencies.

There is another, more clever way to accomplish this follower (Fig. 2). Here we use a P channel MOSFET with the Drain connected to ground and the Source biased up by a current source, in this case just a resistor. There are several advantages to this approach.

First, the input can be direct cou-

pled, because it operates at ground potential, eliminating the input capacitor and bias circuit.

Second, it is self-adjusting in the sense that the Source will operate at $+V_{gs}$, where V_{gs} is the Gate to Source voltage for the MOSFET, or about 3.5V. The amount of current the resistor supplies is not critical, and can be quite high if desired, as the MOSFET will

only dissipate that current times the V_{gs} value. For the ZVP3310 you will be using, you could run it as high as 50mA, which is a lot.

Third, the P channel nonlinearity will tend to operate in opposition to the N channel distortion of the gain MOSFET, giving some distortion reduction due to cancellation. You can alter this cancellation a bit by adjusting the bias current and loading the P channel device.

Fourth, because the input system is at virtual ground, you can swing all the drive current you want without being concerned about the voltages across the input device, since it will be held very close to the constant V_{gs} of the P channel input. No Miller effect, hardly any gain or capacitance modulation, better performance.

Talk among yourselves. I'll give you a topic: Is this still considered a single-gain-stage circuit? If a differential pair or Darlington or a cascode is considered single-stage, would this be considered one also?

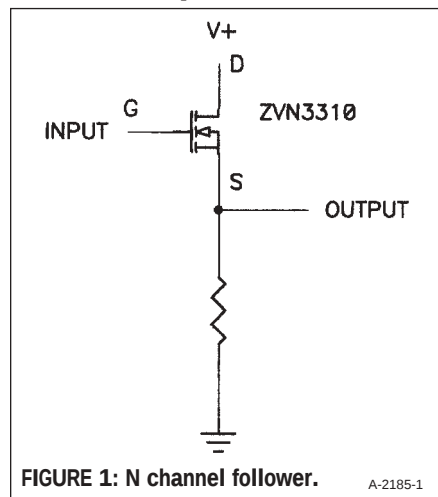


FIGURE 1: N channel follower.

A-2185-1

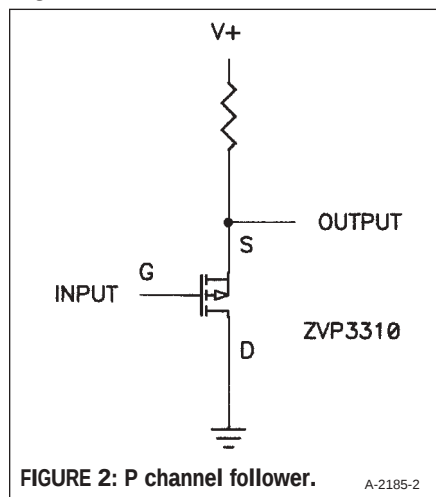


FIGURE 2: P channel follower.

A-2185-2

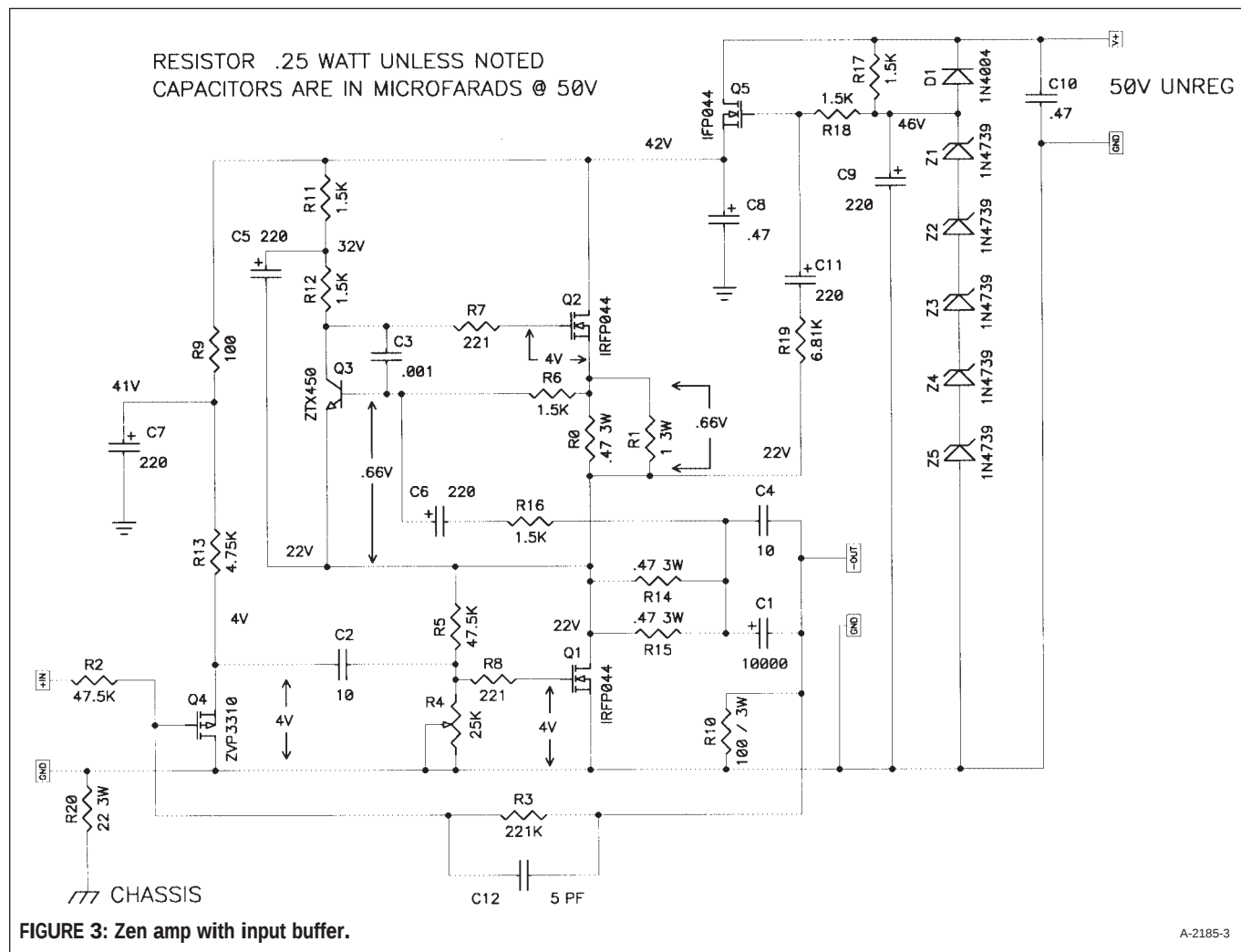


FIGURE 3: Zen amp with input buffer.

A-2185-3

THE CIRCUIT

Figure 3 shows the circuit of Fig. 2 incorporated into the Zen amp with the regulated power supply. Q4 is the added buffer transistor, and it is biased by R13. R9 and C7 filter the voltage provided to R13. The feedback loop of R2

and R3, which previously connected to the Gate of Q1, is now connected to the Gate of Q4 and have values two orders of magnitude higher, giving the amp an input impedance of 47k Ω .

This circuit was designed to idle at 2A, which is more than it actually needs

to achieve the desired 25W into 8 Ω figure. R0 and R1 together form a .33 Ω resistor, and if you leave R1 out, the bias figure drops to 1.3A. With both R0 and R1 and a 50V rail, the amplifier will dissipate 100W, and with R1 removed, the circuit dissipates 67W at idle.

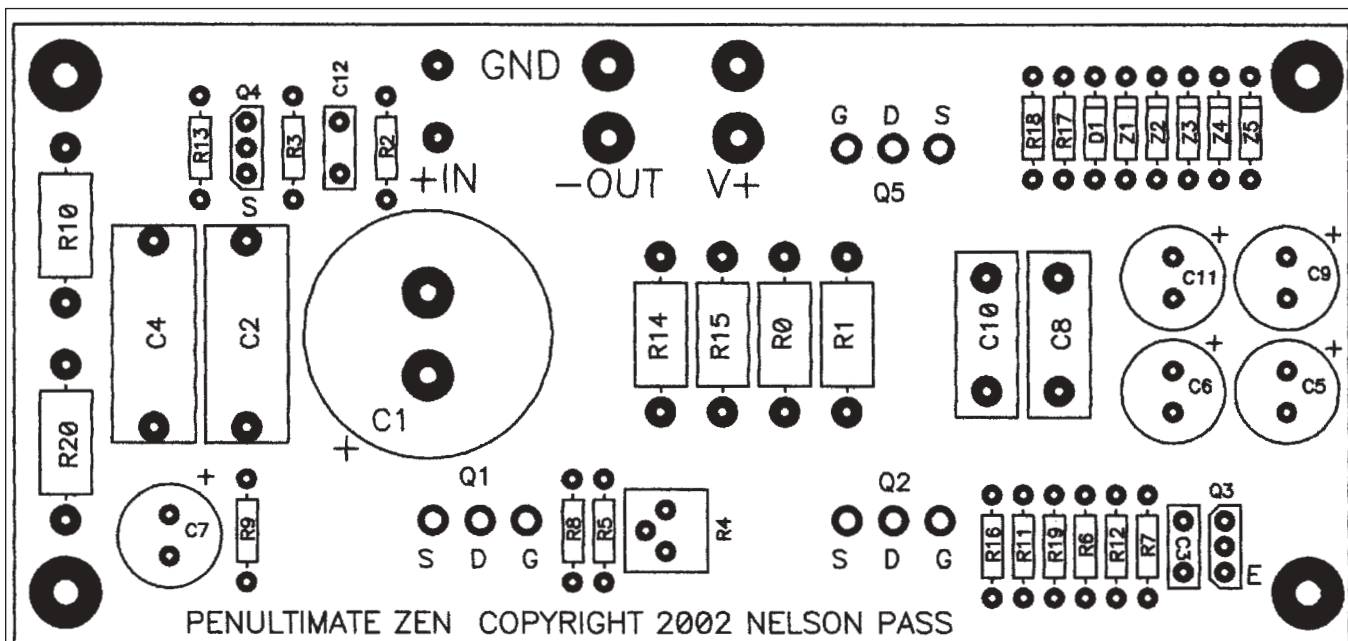


FIGURE 4: PC board component placement.

A-2185-4

LANGREX SUPPLIES LTD

DISTRIBUTORS OF ELECTRONIC VALVES, TUBES & SEMICONDUCTORS AND I.C.S.

1 MAYO ROAD, CROYDON, SURREY, ENGLAND CR0 2QP

24 HOUR EXPRESS MAIL ORDER SERVICE ON STOCK ITEMS

E-MAIL: LANGREX@AOL.COM

PHONE
44-208-684-1166

FAX
44-208-684-3056

A SELECTION OF OUR STOCKS OF NEW ORIGINAL VALVES/TUBES MANY OTHER BRANDS AVAILABLE

STANDARD TYPES			AMERICAN TYPES			SPECIAL QUALITY TYPES		
ECC81	RFT	3.00	5R4GY	RCA	7.50	A2900/CV6091	G.E.C.	17.50
ECC82	RFT	6.00	5U4GB	SYLVANIA	15.00	E82CC	SIEMENS	7.50
ECC83	RFT	8.00	5Y3WGT	SYLVANIA	5.00	E83CC	TESLA	7.50
ECC83	EI	4.00	6BX7GT	GE	7.50	E88CC G. PIN	TESLA	8.50
ECC85	RFT	5.00	6FQ7	EI	5.00	E188CC	MULLARD	20.00
ECC88	BRIMAR	6.00	6L6GC	SYLVANIA	20.00	ECC81/6201	G.E.	5.00
ECC88	MULLARD	10.00	6L6WGB	SYLVANIA	15.00	ECC81/CV4024	MULLARD	6.00
ECL82	MULLARD	5.00	6SL7GT	USA	7.50	ECC81/M8162	MULLARD	7.50
ECL86	TUNGSRAM	10.00	6SN7GT	USA	7.50	ECC81/6201 G. PIN	MULLARD	10.00
EF86	USSR	5.00	6V6GT	BRIMAR	7.50	ECC82/CV4003	MULLARD	15.00
EF86	MULLARD	15.00	12AX7WA	SYLVANIA	7.50	ECC82/M8136	MULLARD	17.50
EL34	EI	6.00	12BH7	BRIMAR	12.00	ECC83/CV4004	MULLARD	40.00
EL37	MULLARD	30.00	12BY7A	G.E.	7.00			
EL84	USSR	3.00	211/VT4C	G.E.	85.00			
EL519	EI	7.50	807	HYTRON	7.50			
EZ80	MULLARD	5.00	5687WB	ECG	6.00	B7G	CHASSIS	0.60
EZ81	MULLARD	10.00	6072A	G.E.	10.00	B9A	CHASSIS	1.00
GZ32	MULLARD	25.00	6080	RCA	10.00	OCTAL	CHASSIS	1.00
GZ33/37	MULLARD	20.00	6146B	G.E.	15.00	OCTAL	MAZDA	2.00
PL509	MULLARD	10.00	6922	E.C.G.	6.00	LOCTAL	B8G CHASSIS	2.50
UCH81	MULLARD	3.00	6973	RCA	15.00			
UCL82	MULLARD	2.00	7308	SYLVANIA	5.00			
			SV6550C	SVETLANA	20.00			

MANY OTHER BRANDS AVAILABLE

These are a selection from our stock of over 6,000 types. Please call or FAX for an immediate quotation on any types not listed. We are one of the largest distributors of valves in the UK. Same day dispatch. Visa/Mastercard acceptable. Air Post/ Packing (Please Enquire). Obsolete types are our specialty.

Depending on your heatsinking and power needs, you can include R1 or not. If you are planning on driving 4 Ω , you will definitely want it. If you leave R1 off, you should also change the value of R16 from 1.5k Ω to 1.0k Ω .

As with all the Zen amps, very few of the component values are critical; in fact, none of them are, so if you have resistors and capacitors that come close to these values, feel free to use them.

As discussed previously, many substitutions will work for the transistors. You can choose Q2 and Q5 from a wide array of IRF-type N channel devices as long as they have the power and current rating to do the job, which would be around 150W and 10+A. They do not have very much influence on the sound compared to Q1 and Q4.

In the case of Q1, the IRFP044 is the preferred part, but you can achieve almost as good performance from the IRFP140 and 240 parts, and pretty much anything else that is similar in character.

In the case of Q4, the Zetex ZVP3310 performed the best among the parts tried. The IRF9510, 9610, and similar parts worked, but have higher capacitance, and thus higher distortion at the top end with these input impedances. You can improve this by lowering the values of R2 and R3. If you can accept a 10k input impedance, you could consider using these alternate P channel MOSFETs.

While we're talking about the input, note that the input of this amplifier is not protected against high voltage transients. Input voltages in excess of 20V will have some chance of damaging the input MOSFET Q4. If this occurs, it should not damage other parts, so if you plan on being careless when connecting the amp, keep a couple of spare ZVP3310s lying around.

Q3 works well with the Zetex ZTX450 NPN transistor, but note that any decent NPN signal device will work here, as you are primarily using it for the .66V junction voltage to control the current through Q2. Like most of the parts here, it was chosen because it is available through Digi-Key.

C4 is simply a bypass capacitor for C1. You may omit it altogether or replace it with your favorite bypass part. C2 can be electrolytic or film (film

being preferred) but should be at least 10 μ F to avoid low-frequency rolloff. If C2 is an electrolytic type, the polarity will not usually be important, as the DC values on either side are approximately the same. If you find that they are not, you will know where to point the positive side, won't you? For more commentary on the main audio circuit, refer to "Zen Variations, Part 2."

C8 and C10 are simply high-frequency bypass capacitors. Usually the circuit will work fine without them, but they provide a nice margin for stability. Similarly with C12, which trims the high-frequency response so as to avoid peaking at high frequencies. Digi-Key no longer stocks 5pF caps, but I have listed 10pF parts in the parts list. You can buy two and put them in series to form a 5pF capacitor.



Alternatively, you can twist two fine insulated wires (like those used in wire-wrap construction) together at a length of about 1.5" and get about 5pF. This technique has the advantage that you can start out too long and trim it with a pair of scissors while watching the square wave of the amplifier.

Z1 through Z5 are 9.1V zener diodes, which produce a 45.5V reference for the regulator Q5. You can adjust these to different voltages or bypass any of them if you find yourself using a different rail voltage. You can leave them out altogether, in which case the regulated supply will be about 4V less than the unregulated supply, but with the AC ripple removed. This works just fine in practice, and is usually referred to as a capacitance multiplier. For more information on the other parts in the supply regulator, refer to "Zen Variations, Part 3."

CONSTRUCTION

Figure 4 shows the printed circuit board for this project. It measures about 6.5 $\times$ 3" and holds the circuitry shown in Fig. 3. The board is available for sale from www.passdiy.com, and you can also download the Gerber files to get your own made.

Photo 1 shows the stuffed board, which does not include the components for an unregulated 50V supply, but Fig. 5 shows a typical circuit for one channel and the grounding layout for a stereo

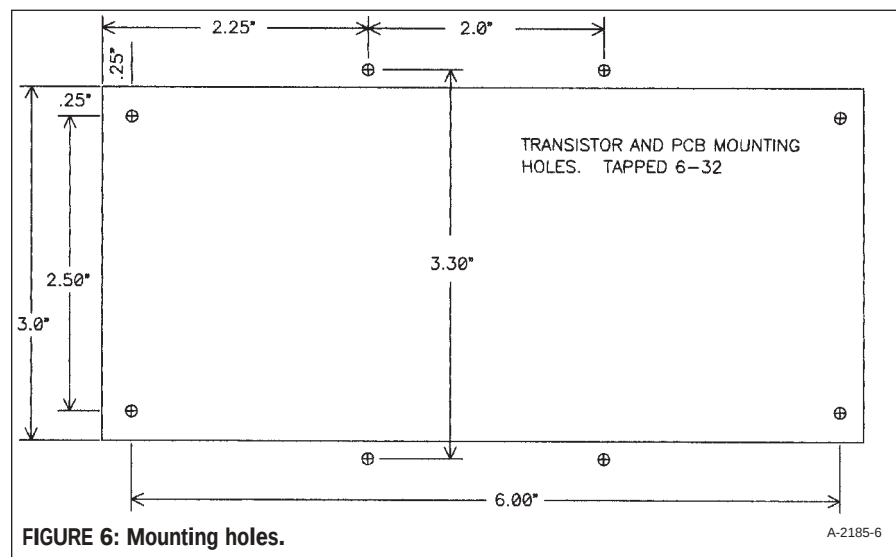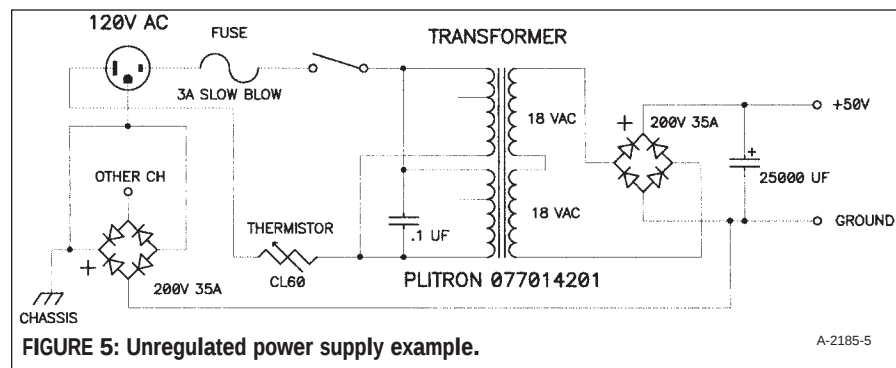

amplifier. The transformers are Plitron 077014201, with two 18V secondary windings and a 300VA wattage rating. While two transformers are recommended for two channels, we did build an amplifier using only one. It worked well enough, but ran hot and mechanically buzzed a bit at 200W draw.

Note in Fig. 5 that we have chosen to isolate the two channels through a rectifier bridge to ground, with each channel's ground appearing on one of the AC legs of the bridge. If you use a single transformer supply for two channels, tie both of their grounds together and to both AC legs of the bridge.

If you construct the amplifier with two separate transformers and decide to operate the amplifier balanced or bridged, be certain to tie the ground speaker outputs together with a heavy piece of wire to provide a good low impedance ground connection between both channels, otherwise speaker current will attempt to flow through the input ground cables.

Figure 6 shows the mounting hole dimensions for the board and power transistors. These holes are tapped 6-32

EarMax™ • EarMax Pro™

The most sought after miniature vacuum tube headphone amplifiers.

Since 1993



Contact us for details and a host of reviews.

**Analog Specialties: TURNTABLES by Amazon, Bauer, EuroLab (Golden Ear Award 2001)
TONEARMS by BelCanto, Golden Gate, Mørch (Golden Ear Award 2001), Schröder
CARTRIDGES by Allaerts, Benz, Decca, Denon, Empire
Loricraft record cleaning machine**

AUDIO ADVANCEMENTS LLC

973 875 8705 • audadv@earthlink.net • www.audioadvancements.com

Quieter than a computer mouse.

auto

home

marine

aero

industrial

studio

Zeronoize knows what it takes to enjoy the finest sound quality possible and with Cascade Audio Engineering's sound control products you're bound to feel the music!

CAE offers the most advanced dampers, barriers, absorbers, diffusers, traps and baffles available in the industry.

You'll be amazed how easy it is to restore lost midbass and achieve levels of sonic accuracy never thought possible.

Visit www.zeronoize.com today and view our complete selection of VBLOK sound control products.

Zeronoize.com, silence at the tip of your fingers.

Deflex PowerPads

These amazing speaker tuning pads will eliminate speaker backwave once and for all! Install them behind any speaker where a parallel wall exists to fragment speaker backwave and eliminate standing waves within a loudspeaker enclosure. Install a pair and discover accuracy, smooth response and realize a dramatic improvement in sound quality.

sizes:

5"

7"

9"

13"

VB1X

VB1X vibration damping compound works well when brushed onto the inside surfaces of a loudspeaker enclosure. When cured, the impedance mismatch created can improve output 1 to 1.5 db!

sizes:

1qt

1g

5g

ZERONOIZE
.COM



61580 American Lane Suite #3

Bend, Oregon, 97702

www.zeronoize.com

info@zeronoize.com

onto a flat surface of a heatsink. You must insulate the power transistors from the heatsink using thermal insulators—either silicone pads or mica and thermal grease. Use a washer between the head of the screw and the case of the transistor to spread the force across the package, and don't tighten them very tight. The ground on each board connects to the heatsink through R20, providing a resistive connection to the chassis.

The heatsinks must dissipate up to 100W per channel, and need to do so with a temperature rise of about 30°C, which gives them a rating of about .3°C/W. If you use smaller sinks, then a lesser bias (no R1) and/or fan cooling will be necessary.

If you manage to cool the amplifier very well, you can consider whether you can get more power out of it. I would say the practical limit to this will be Q1, which is run at about 44W with the 2A bias. Personally, I hesitate to operate this device at greater than 50W, but you can crank the supply voltage and bias up higher if you want.

With the IRFP044 I would not exceed 50V on the regulated supply. If you want to try higher, I suggest the IRF140 or 240 devices.

More bias is easily provided by replacing R1 with .47Ω, which will give

you 2.8A, enough to probably get 50W into 4Ω and 100W balanced into 8Ω. Beyond this, you can expect some excitement. If you do replace R1 with .47Ω, I suggest R16 at 2kΩ or so.

Table 1 shows the parts list. You can

TABLE 1
ONE-CHANNEL PARTS LIST FROM DIGI-KEY

REFERENCE	DESCRIPTION	PART #
Q1, Q2, Q5	IRFP044 N channel power MOSFET	IRFP044N-ND
Q3	Zetex NPN ZTX450	ZTX450-ND
Q4	Zetex ZVP3310 P channel MOSFET	ZVP3310A-ND
D1	1N4004 diode	1N4004GICT-ND
Z1-Z5	1N4739 9.1V zener diode	1N4739ADICT-ND
C1	10,000μF @ 50V electrolytic	P6939-ND
C2, C4	10μF polyester film	EF1106-ND
C3	.001μF film	4773-ND
C5, C6, C7, C9, C11	220μF @ 50V electrolytic	P1246-ND
C8, C10	.47μF polyester film	E1474-ND
C12	5pF film	399-1806-1-ND (2 in series)
R0, R14, R15	.47Ω 3W metal film	P0.47W-3BK-ND
R1	1Ω 3W metal film	P1.0W-3BK-ND
R2, R5	47.5k .25W metal film	47.5KXBK-ND
R3	221k .25W metal film	221KXBK-ND
R4	25k trim potentiometer	3386P-253-ND
R6, R11, R12, R16, R17, R18	1.5k .25W metal film	1.50KXBK-ND
R7, R8	221 .25W metal film	221KXBK-ND
R9	100 .25W metal film	100KXBK-ND
R10	100Ω 3W metal film	P100W-3BK-ND
R13	4.75k .25W metal film	4.75KXBK-ND
R19	6.81k .25W metal film	6.81KXBK-ND
R20	22Ω 3W metal film	P22W-3BK-ND

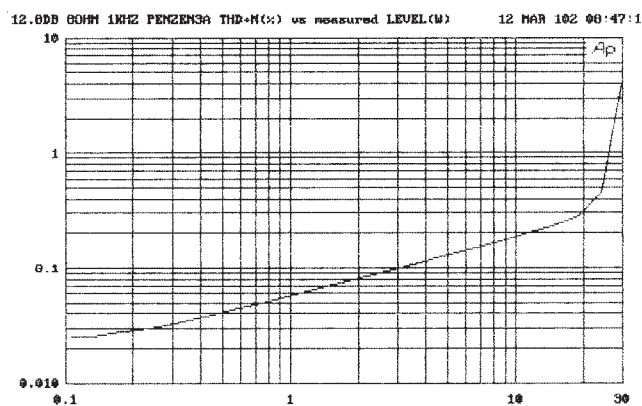


FIGURE 7: THD versus power with 2A bias.

A-2185-7

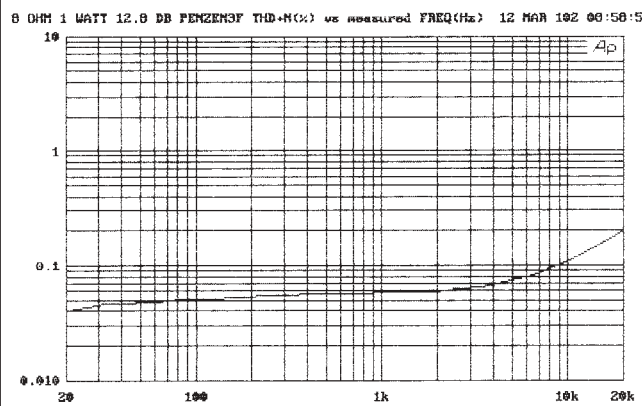


FIGURE 9: THD versus frequency at 1W.

A-2185-9

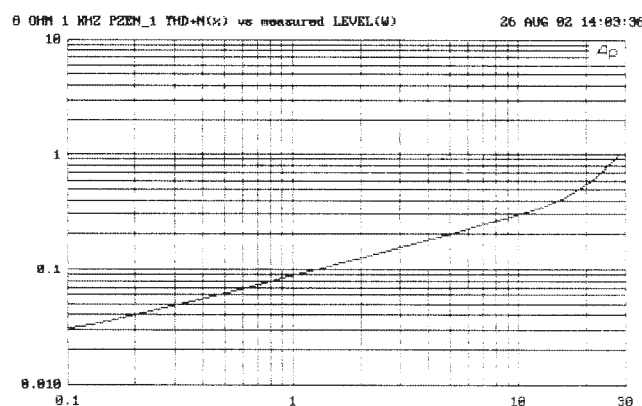


FIGURE 8: THD versus power with 1.3A bias.

A-2185-8

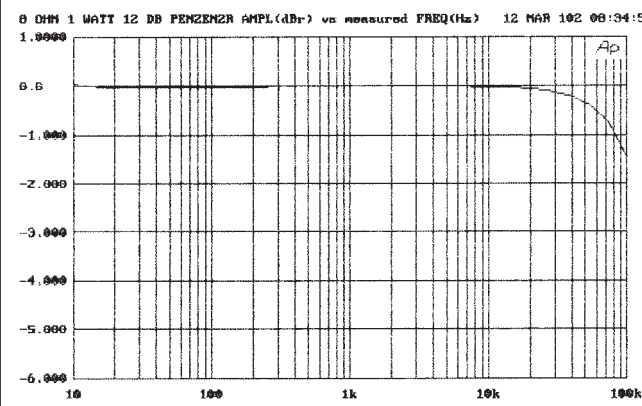


FIGURE 10: Frequency response.

A-2185-10

find all the parts except the transformer and mechanical package at Digi-Key (www.digikey.com).

The amplifier is not very susceptible to noise pickup, and you can achieve good results enclosing it in a wooden chassis. If you do, be certain to heatsink the rectifier bridges, which ordinarily get their heatsinking from the chassis. Placing them on the main sinks is OK.

ADJUSTMENT

Assuming that you have triple-checked your assembly work, it is time to "light this candle." Do so one channel at a time connected to unregulated V+. Wear safety glasses. Fuse the transformer at the minimum value, about 1.5A. Set R4 at maximum value, which is counter-clockwise.

Bring the amplifier up slowly using a Variac® and watch the voltage across R0. If it does not exceed .7V or so, then continue to increase the Variac. Adjust R0 so that the Drain voltage of Q1 is half the regulated voltage plus about 2V.

If you get this far without problems, then check for the other voltages called out in the schematic. Readjust R4 after the amplifier has warmed up for a couple of minutes. Now do the same thing for the other channel. Watch where you stick those probes!

If the voltages all check out, then you have a 95% chance that everything is proper. If not, it is time to start doing your detective work. This is best done slowly. Wait till the next day. The vast majority of problems are board stuffing and wiring errors. Look for those at length before picking up a soldering iron. Think about it twice.

When you have the bugs out, run both channels for an hour and check the temperature of the heat every few minutes. Check for burning smells. Readjust R4 after an hour.

PERFORMANCE

In addition to having the high input impedance, this circuit also measures better than the previous editions. Due to the regulated power supply, the noise is about 35µV at the output, a really excellent figure.

The distortion plus noise versus power into 8Ω at 1kHz is shown in *Fig. 7* with the 2A bias. *Figure 8* shows the

same curve at 1.3A bias with R1 removed and R16 at 1.0kΩ.

Figure 9 shows the distortion at 1W from 20 to 20kHz, which is dramatically better than any earlier Zen amp. *Figure 10* shows the frequency response, which is totally flat at 10Hz, and down about 2dB at 100kHz.

Like just about any other amplifier, the Penultimate Zen will drive 4Ω also, but at a higher distortion figure. If you include R1, you should get about 30W into 4Ω. If you decide to run a pair of the channels balanced (or bridged) with R1 installed, you can expect to see about 60W into 8Ω, and the performance is very good. As documented in Zen Variations 1 and 2, the distortion tends to drop due to cancellation of the second harmonic, which is the dominant distortion. This mode of operation is highly recommended if you need the most power possible into 8Ω.

CONCLUSION

Sonically, this is about as good as it's going to get for this topology, and I would match it up against an Aleph 3 without hesitation, and indeed the performance is quite similar. Its signature is relaxed and very easy to listen to, although it is not a powerhouse at the bottom end. It works best with 8Ω speakers, 90+dB sensitivity, which do not require a lot of control from the amplifier. In other words, a tube friendly loudspeaker.

Does it sound like a tube amp? It's a little bit of a cross between tubes and solid state, but it has its own character, the result of a very simple MOSFET circuit operated pure Class A.

So there you have it. The amplifier is called the Penultimate Zen because it represents how far we want to take this particular topology without getting medieval.

ACKNOWLEDGMENT

Thanks to Karen Douglass, Wayne Colburn, and Desmond Harrington for their help. ♦

Buy low. Sell hi-fi.

www.AUDIOGON.com
HIGH END AUDIO MARKETPLACE



An Against the Wall Speaker

Thin is in . . . for fashion models, laptops, and now speakers. This thin design suggests some interesting future applications. **By John Mattern**

I had three objectives in pursuing a thin speaker design. First, I believed that the effect of the wall on the diffraction step would be lowered by having the speaker hug the wall. In the limit as the thickness becomes very small, it satisfies the large flange assumption that is basic to the simulation software for both the cone and the port openings.

Second, I believe that there is a future in the thin LCD and plasma displays. They have a depth of about 3.5" at present. A speaker that had a depth of the same amount would harmonize with such a monitor. This particular thin design also has the advantage of placing the drivers at a good height.

The final objective was to verify the latest version of my software that simulates the performance of a back-loaded speaker with fiberglass stuffing. The software has been modified to eliminate the major discrepancies noted in my prior articles ("Another Look at TL Design," *SB* 3/99, and "More on TL

Speaker Design," *aX* Feb. '02). The latest simulation software is based on the acoustic treatment of the conical horn by Stewart and Lindsay.¹

The Stewart and Lindsay equation for velocity potential in a conical pipe defines the forward and backward velocity potential along the length of the pipe as a function of the distance from the apex. However, the equation does not provide for losses. To allow for losses I combined a loss term with the Stewart and Lindsay phase term yielding $e^{-(ikr-ar)}$, where $-ar$ is the loss term that I added ("a" is the loss exponent per meter and "r" is distance in meters). The loss, therefore, is introduced into Stewart and Lindsay's subsequent terms for pressure and velocity.

I used the same mathematics they used in the lossless case to develop acoustic pressure and velocity at any distance from the apex. This also required a major revision in my software. In the end this change allowed the cone and port outputs to cancel each other at



PHOTO 1: Bass speaker assembly with fiberglass installed before attaching front panels and top.

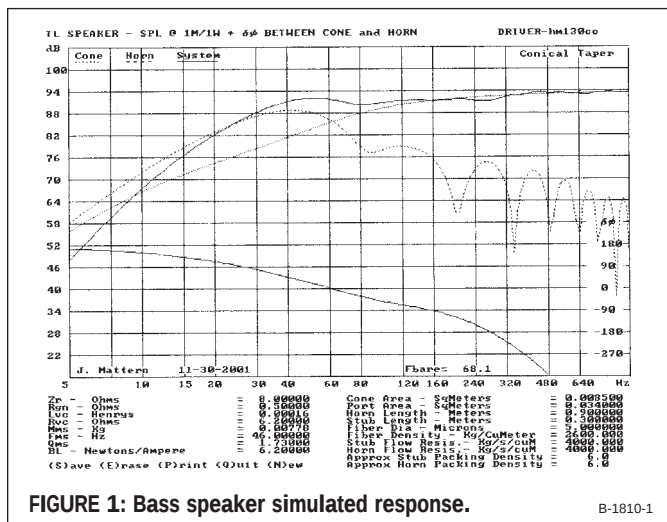


FIGURE 1: Bass speaker simulated response.

B-1810-1


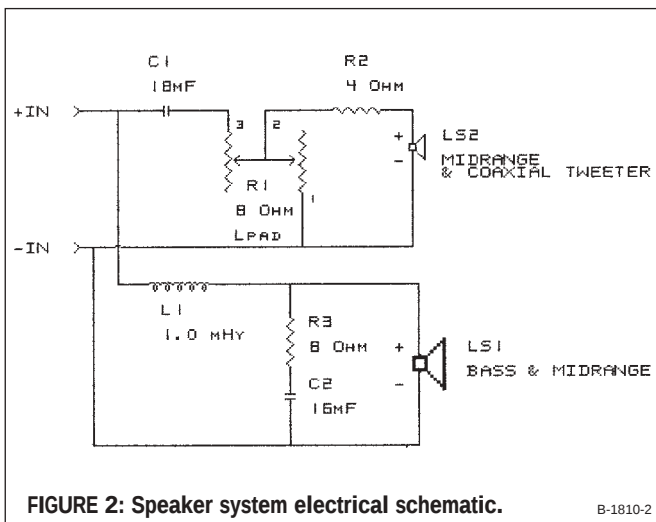


FIGURE 2: Speaker system electrical schematic.

B-1810-2

HI-VI RESEARCH®
you can hear the difference

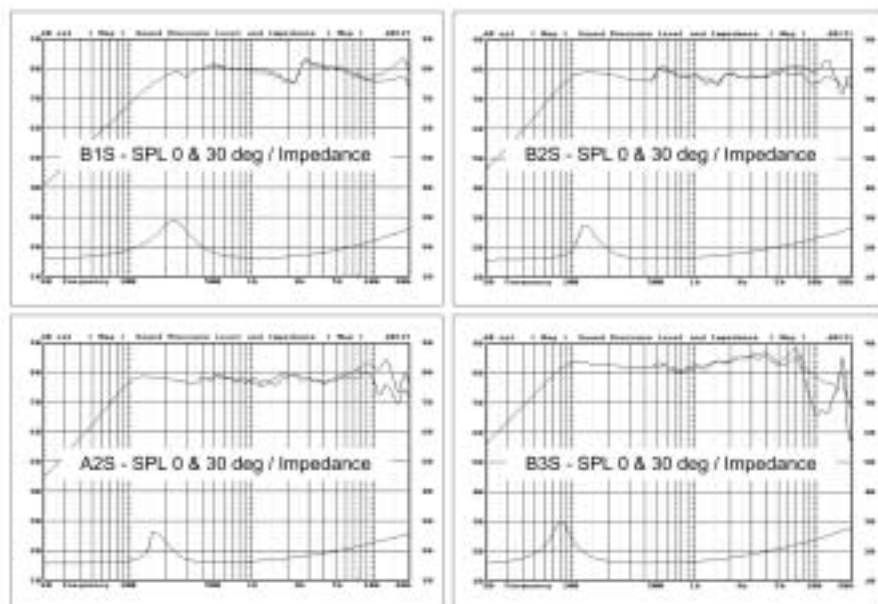The new *compact* drivers
full range and midrange woofers



- Aluminum-magnesium cone — an improvement over pure aluminum cone technology
- 100% shielded magnet system - home theater/computer ready
- Optimized T/S parameters for more flexible cabinet design



www.swanspeaker.com
www.dulcet.com

Distributed by
Parts Express
Tel: 1-800-338-0531
www.partsexpress.com

HI-VI RESEARCH(USA)

Swans Speaker Systems, Inc. 2550 Corporate Place, Suite C-103, Monterey Park, CA 91754 USA Tel: (323)-881-0806 Fax: (323)-881-0657 e-mail: jennie@swanspeaker.com

HI-VI RESEARCH(HongKong)

Hongo (Holdings) Ltd. Flat 1709, China Merchants Tower, Shun Tak Centre, 168-200 Connaught Road, Sheung Wan, Hong Kong Tel: (852)2587-6728 Fax: (852)2587-6768 e-mail: hongo@netvigator.com

HI-VI RESEARCH(China)

HI-VI RESEARCH ELECTRONIC CO., LTD. FuXing Building, 2/Fat / FL, East Tower, 163 HuangPu Ave, GuangZhou, Guangdong, China Tel: 86-20-34919808 Fax: 86-20-85201293 e-mail: yao@dulcet.com

©2002 Swans Speaker Systems, Inc. HI-VI RESEARCH and the Swan logo are registered trademarks of Swans Speaker Systems, Inc. or its subsidiaries in the United States and other countries. All right reserved

very low frequencies, a necessary condition brought to my attention in correspondence with G.R. Koonce. My early software based on Olson's conical horn treatment² did not lead to this result. My effort to introduce losses into Olson's conical horn formula was apparently unsuccessful.

THE TAPERED TRANSMISSION LINE

The acoustic transmission line may be used to control the back wave from a bass driver in a multiple driver system. A tapered transmission line uses a changing cross-section to achieve a particular characteristic. If the taper is flared outward (the mouth is larger than the throat), then there will be gain that can provide more bass output. If the taper is in the other direction, it saves space and diminishes the radiation from the port (should there be one). Whether tapered or not, the line will be filled with a tangle of fibers that selectively absorb the back wave.

The action is largely mechanical. According to Bradbury³, at high frequencies where the inertia of the fibers renders them stationary there is absorption of sound but little change in speed. At low frequencies where the inertia forces are small, the fiber tangle moves with the air causing a significant reduction in the speed of sound but with little attenuation. At some frequency there is a turning point causing a rolloff with increasing frequency similar to an L-R filter. But in this case the action is mechanical rather than electrical.

There are three factors that determine the filter action: fiber density, fiber diameter, and flow resistance. The flow resistance and packing density are interdependent. Increasing the packing density (compressing the fiber tangle) increases the flow resistance, and, conversely, specifying a higher flow resistance demands a higher packing density. A figure of merit for the fibers may be written as the fiber density divided by the fiber diameter. The greater this number the lower the turnover frequency and the greater the attenuation in the midbass region above the turnover frequency.

I have examined a number of materials, and of these the fiberglass tangle has the greatest figure of merit for use in the conical horn. Unfortunately, fiber-

TABLE 1
SPEAKER SYSTEM ELECTRICAL AND MECHANICAL PARTS LIST

PART	VALUE	SOURCE	DESCRIPTION	MFG PT#	SUPPLIER PT
C1	18.0mF	Parts Express—Solen	400V polypropylene		027-580
C2	16.0mF	Parts Express—Solen	400V polypropylene		027-578
R1	8.0Ω	Parts Express	50W Lpad		260-255
R2	4.0Ω	Parts Express	20W wirewound		017-4
R3	8.0Ω	Radio Shack	20W non inductive		271-120
L2	1.0mH	Parts Express	Air core .21Ω		266-350
LS1	8.0Ω	Parts Express	Carbon fiber midbass woofer	HT 130C0	296-063
LS2	4.0Ω	Boston Acoustics	Midbass and coaxial tweeter		CX3/FX3
QTY	DIMENSIONS	MATERIAL			
1	12 × 4 × .5"	Fiberboard (CO base—with cutout for Lpad)			
1	12 × 6 × .5"	Fiberboard (CO panel)			
12	#6-32 × 1.25"	Brass screws (3 nuts/screw)			


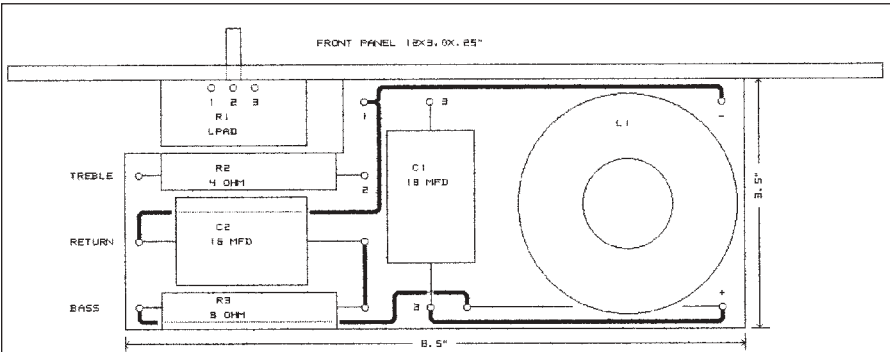


FIGURE 3: Crossover parts mounted on 3.5 × 8.5 × 3/8" plywood board with 1 × 3" cutout for Lpad.

B-1810-3

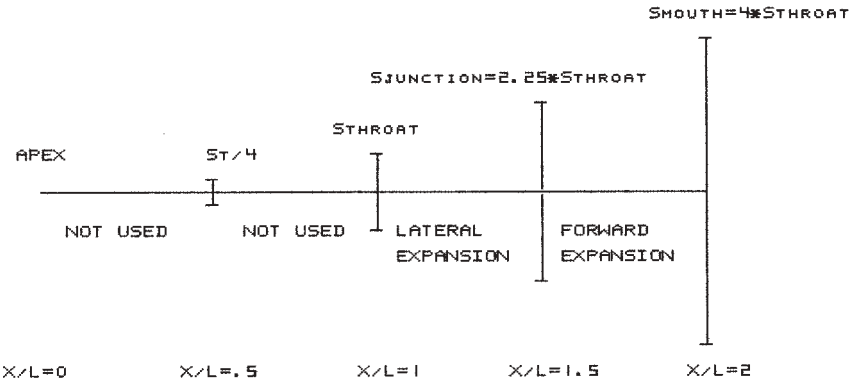CONICAL HORN APPROXIMATION USING TWO CASCADED PARABOLIC HORNS
Sx=STHROAT(X/L)^2 L= LENGTH HORN



LOCATION	DISTANCE FROM THROAT	AREA SQ IN	DIMENSIONS IN	AREA SQ IN
THROAT	0.000 L	ST	2.5 × 4.3	11.75
JUNCTION	0.500 L	2.25*ST	2.5 × 10.5	26.25
MOUTH	1.000 L	4*ST	4.522 × 10.5	47.5

WILL USE APPROXIMATIONS BETWEEN X/L=1 AND X/L=2

FIGURE 4: Calculation showing approximation to conical horn using two short cascaded parabolic horns.

B-1810-4

DRIVERS:

- ATC
- AUDAX
- ETON
- FOSTEX
- ILLUSION AUDIO
- LPG
- MAX FIDELITY
- MOREL
- PEERLESS
- SCAN-SPEAK
- SEAS
- VIFA
- VOLT

COMPONENTS:

SOLENEPTA-LITZ
AND STANDARD
INDUCTORS AND
CAPACITORS - THE
CHOICE OF MANY
HIGH-END SPEAKER
MANUFACTURERS.

HARDWARE:

POWER RESISTORS,
L-PADS, CABLE,
ABSORBING AND
DAMPING MATERIALS,
GOLD SPEAKER
TERMINALS, GOLD
BANANA PLUGS AND
BINDING POSTS, GRILL
FASTENERS, PORT
TUBES AND TRIM
RINGS, PAN HEAD
SCREWS, SPIKES
AND TEE NUTS WITH
ALLEN HEAD BOLTS
AND PLENTY MORE...

**CUSTOM
COMPUTER AIDED
CROSSOVER AND
CABINET DESIGN**

HOW TO BOOKS

The Process of Design.



When designing a loudspeaker, the initial driver considerations and final driver choice can make or break a project. To ensure your success - you want the most complete information and specifications at your finger tips - the Solen catalog.

Order the **FREE** Solen catalog and CD- containing a wide selection of quality drivers - with complete manufacturer's spec sheets, as well as applications in detail on woofers, with predicted response in different sealed and vented enclosures. It is a valuable resource that will bring out the possibilities in your designs.

Order the **FREE** Solen Catalog and CD.

Forward your request by
phone, fax, mail or email
- or fill in the online request
form at solen.ca.



Name: _____
Address: _____

State/Prov: _____
Zip/Postal Code: _____
Country: _____
Tel: _____
Email: _____



SOLENEPTA-LITZ

4470 Avenue Thibault
St-Hubert, QC J3Y 7T9
Canada

Tel: **450.656.2759**

Fax: 450.443.4949

Email: solen@solen.ca

WEB: <http://www.solen.ca>

glass is the least predictable, because the fibers are anything but uniform. Bradbury gives the diameter as .005mm. The fiberglass tangles I have examined appear to have a large spread in fiber diameter as well as length. Acousta-stuf, in contrast, is quite uniform but has a lower figure of merit as a result of its larger diameter and light weight.

The design of a tapered transmission (or horn-loaded speaker, if you prefer) will benefit from simulation software that predicts the approximate results to be expected. The simulation software I am now using is the result of many years of casual study backed up by system construction for experimental verification. Only now has the agreement between theory and practice been reasonably good.

SIMULATION

Since the simulation precedes the experimental phase, I will start with it first. Figure 1 shows the predicted performance for an optimized enclosure using the Audax HM130CO. This is an upscale 5.25" mid woofer featuring a fully ventilated woven carbon fiber cone. This figure shows the cone response, the port response, the phase difference between the cone and port, and the vector sum of the two responses.

I obtained the driver parameters from the data sheets in the Solen catalog, and the fiberglass diameter from Bradbury's paper. I obtained the fiberglass density from the *ITT Engineers Handbook*.⁴ It differs somewhat from that given by Bradbury.

The simulation suggests that, with a port-to-cone-area ratio of four or greater, the port response can look very much like that of a subwoofer. I have verified the predictions of Fig. 1 using the enclosure parameters listed on the lower right side of the figure.

CROSSOVER

I chose to stay with the simple 6dB per octave crossover for both the bass and treble speakers. It served me well in the previous design and I could see no reason to change it. The requirement that the bass and treble speakers have substantial overlap is still satisfied, and the treble speaker, a nearly full-range coaxial unit, can handle what little bass is fed to it. I do intend to try the Infinity

Kappa 3.5" car speaker, which has even more bass capability than the Boston Acoustics FX3, an upgraded version of the CX3.

There were more pressing issues to resolve, so I simply will repeat the earlier crossover (CO) design. I omitted the inductance and resistance used in the original CO to correct for the diffraction step because they were not needed. This is not to say that there are no diffraction edge effects because there still are. But I will cover this later.

Table 1 provides the CO parts list. The electrical schematic for the CO is shown in Fig. 2 and the mechanical arrangement is shown in Fig. 3. I did not enclose the CO this time but used a

wide front panel to hide the parts and, for convenience, placed the assembly on top of the treble speaker.

I have reservations about any speaker that uses a bipolar electrolytic as part of the CO. Both the CX3 and FX3 use a 3.3mF electrolytic capacitor in series with the tweeter. I have successfully modified the wiring of both types so a quality external capacitor replaces the original internal one. aX willing, I will report the details in a follow-up article.

CONICAL HORN APPROXIMATION

The simulation assumes a conical horn connecting the back of the cone to the port. This, of course, implies a smooth

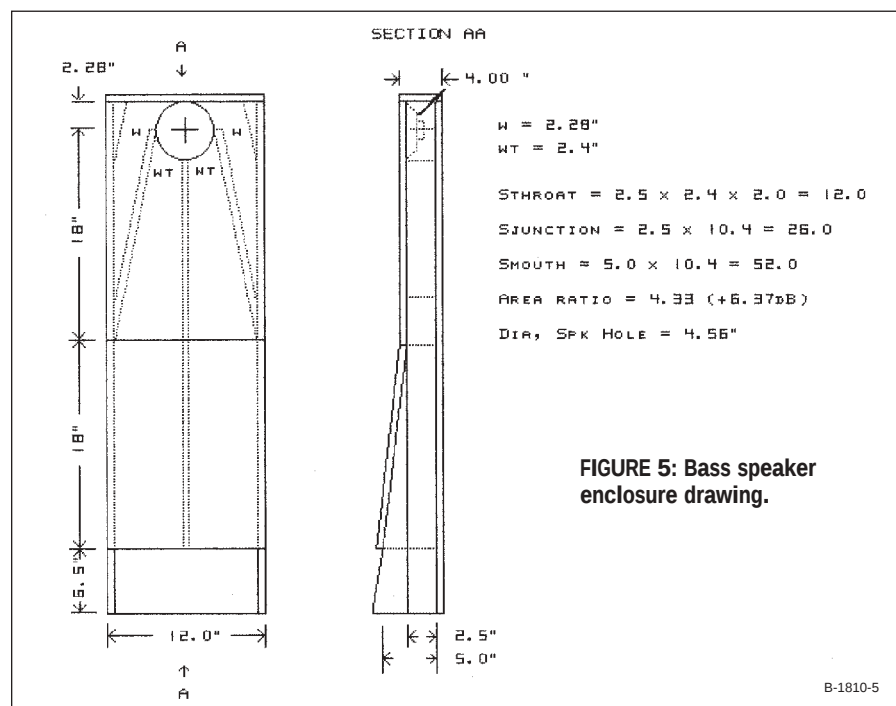


FIGURE 5: Bass speaker enclosure drawing.

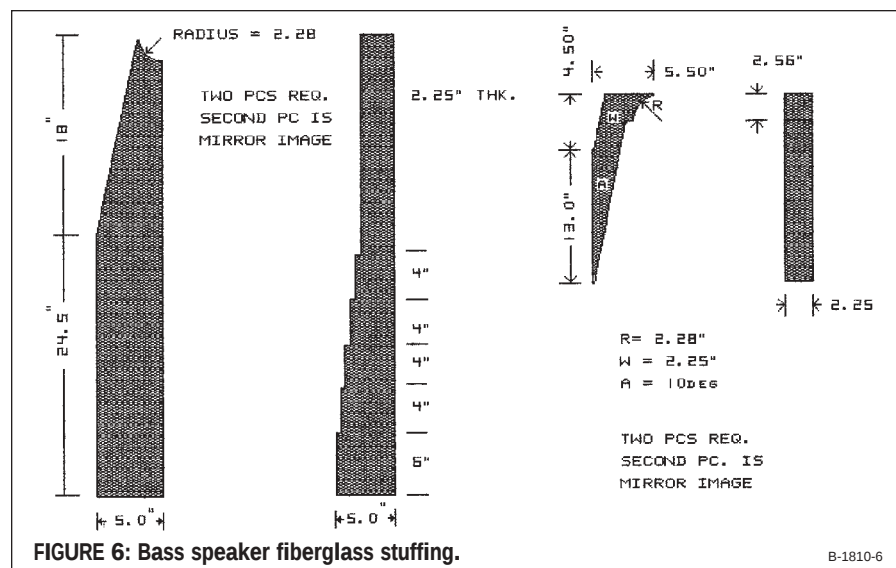


FIGURE 6: Bass speaker fiberglass stuffing.

change in dimensions in two directions, a difficult design to execute. For a 4:1 area ratio the difference between the conical horn and the parabolic horn is not great. The parabolic horn can be formed with a uniform change in one direction only.

Figure 4 shows how a conical horn can be approximated by cascading two parabolic horns to closely approximate a conical horn. Of course, were the area ratio much greater than four, this simple solution would not suffice. The example in the diagram approximates a conical horn between Sthroat and Smouth for an area ratio of four. This is the basis for the claim that the thin speaker is back loaded by a conical horn as assumed in the simulation.

BASS SPEAKER DESIGN

I took the bass speaker dimensions from the simulation plot of Fig. 1. I had difficulty meeting the requirement that the cone area, the stub area, and the horn mouth area be equal. The reason becomes apparent when you examine the speaker drawing of Fig. 5. Note that the position of the horn's mouth is not well defined. I did the best I could, and I think the discrepancy is less than 10%.

The front and back of this enclosure uses $\frac{3}{4}$ " particleboard shelving. It is called MDF but is more dense than what usually passes for MDF.

The outside pieces connecting the front and rear surfaces are $\frac{9}{16}$ " thick hardwood. Their depth is 2.5" in the top

half and linearly increases from 2.5" to 5.0" in the bottom half. The internal pieces are only $\frac{1}{2}$ " thick. The bottom halves are a composite of a straight piece and a wedge.

I use hardwood for two reasons. First, it is much stiffer than an equal sized piece of MDF. Second, the hardwood will hold the screws attaching the

lower front panel more securely.

I thought it was a good plan to make the lower front panel removable. I glued the upper front half trapping the stuffing, and fastened the lower front half with screws on 3" centers. Of course, you can glue the lower half once you have verified the performance of the stuffing. Photo 1 shows a partially constructed

Accuracy, Stability, Repeatability

Will your microphones be accurate tomorrow?



Next Week? Next Year? After baking them in the car???
ACO Pacific Microphones will!
 Manufactured to meet IEC, ANSI and ASA standards.
 Stainless and Titanium Diaphragms, Quartz insulators
 Aged at 150°C.

Try that with a "calibrated" consumer electret mic!

ACO Pacific, Inc.
 2604 Read Ave., Belmont, CA 94002

Tel: (650) 595-8588 FAX: (650) 591-2891 e-mail acopac@acopacific.com

ACoustics Begins With ACO™



Creative Sound Solutions

loudspeaker kits and components

www.creativesound.ca
sales@creativesound.ca

Introducing...

Criterion

Criterion - the first degree of Lucidity

- ▶ A reference-standard "bookshelf" or "mini-monitor" kit
- ▶ Stunning clarity from the ARG2 pure ribbon tweeter
- ▶ High-performance 5.25-inch woofer with a curvilinear treated paper cone
- ▶ Series crossover network at 3.5 kHz
- ▶ 12 x 8 x 11.75 reflex cabinet extends response to -3 dB at 55 Hz
- ▶ Complete kit with all components and plans
- ▶ Custom cabinets available in a variety of finishes

Lucidity - you can get there by degrees!

Watch for "Pursuit" - the second degree of Lucidity



bass speaker with the fiberglass stuffing installed. The final speaker uses stuffing surrounding the installed driver, not shown in the photo.

CONSTRUCTION OF THE BASS SPEAKER

The material list is provided in *Table 2*. Purchase shelving that is long enough



PHOTO 2: Treble speaker assembly with fiberglass installed before attaching back panel.

so you won't need a splice in the back. After cutting it to length, you will need to prepare the side pieces and internal partitions. I used scraps from Home Depot's scrap box for these pieces. You may prefer to salvage your parts from oak flooring. After cutting the back to size, I penciled in the plan from *Fig. 5* to the back panel for use in locating the five internal parts.

I used a jig to cut the slopes for the internal hardwood pieces. The jig itself required work with a saw followed by a plane to render it accurate enough for the task. With a radial arm saw, you might clamp the work at an angle and then move the saw through the work.

I made sure that the hardwood pieces were true and then brushed on a uniform coating of carpenter's glue. After clamping them to the back I wiped the excess glue away leaving a fillet of glue on the inside joints. I clamped the work in three places while the glue dried.

The three internal pieces should touch the 4.56 diameter speaker circle. Being careful to assure an airtight joint, you glue the three internal pieces to the back. This is a good time to fabricate the corner pieces and attach them. Remember this is the back and the only hole you will make is through the top for the wire.



I then made the 24.5" wedges that I glued to the bottom of the side pieces. I used a thinner ½" piece for the inside brace. I used a jig to fashion the bottom half of the outside pieces as well as the inside brace. Some ingenuity is required to construct this speaker, but, believe me, it is far more easily built than the first TL.

You will want to cut the 4 1/16" speaker mounting hole in the top front panel. I did this in two stages. First, I used a 4 1/2" hole saw and followed it with a drum sander to open the hole until the speaker fit.

I then used the router to cut a 45° chamfer on the back side, making the chamfer about ¼" deep. You will probably do this before cutting the top front panel to size. You may wish to leave a sliver of material at the top of the speaker cutout. The speaker fits on the outside of the front panel.

BASS SPEAKER STUFFING AND FINAL CONSTRUCTION

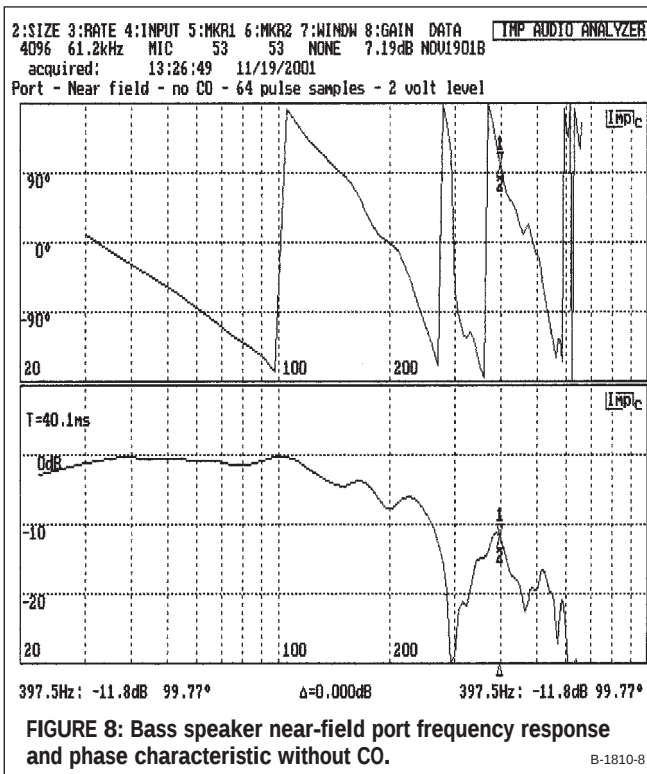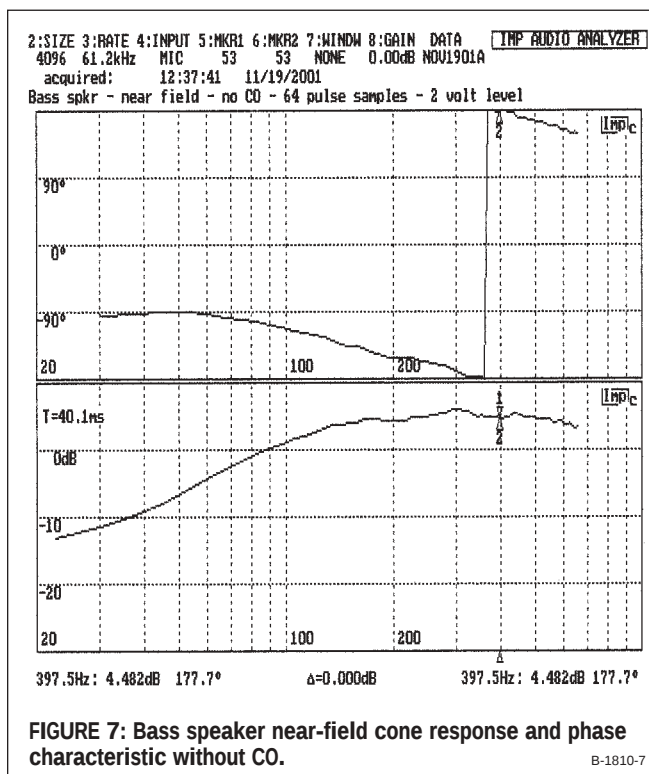The stuffing is a bit "iffy," because Radio Shack has discontinued their fiberglass blanket. I know of two other materials: the Home Depot ¾" pipe insulation and their 3 1/2" home insulation. In the first instance, you will need to attach three layers together with a very thin layer of spray adhesive to form a



2.25" laminate. In the second case, you will need to remove a 1¼" layer from the insulating blanket, but getting a neat result may be difficult.

You may want two patterns for cutting the four pieces of stuffing. Plans for the patterns are shown in *Fig. 6*. The speaker here used the Radio Shack fiberglass, so the steps you take will be somewhat different.

First, I used the pattern to make the two long pieces, which extend to the floor. I made the side pieces in two steps. I fabricated the uniform 42.5 × 2.0" piece and then glued it in place between the back and side pieces with a thin coat of carpenter's glue. Then I glued the top front panel in place with carpenter's glue with the chamfer on the inside, being careful to avoid air leaks.

Then I made the fiberglass "wedges" that fit under the lower front panel. I attached the fiberglass wedge with spray adhesive and attached the bottom front panel with screws on 3" centers using closed cell weather strip to seal the joints. When you are using thinner material you may want to use more pieces, but shorter ones. The idea is to not quite fill the space between the front and back panels.

Finally, I glued the top on and drilled a slanted hole through it close to the edge for the speaker wire. This allows you to place the speaker against the wall because the treble speaker box is not as deep as the bass speaker. I did not allow for the room's base board in the drawing of *Fig. 5*, since I will use my speaker in an area without one.

I used Home Depot pipe insulation in the second unit. This fiberglass comes in sheets that are 16 × 48 × .75". I cut out the pieces and then glued three pieces together with a very thin coat of spray adhesive, giving a nominal thickness of 2.25". The three-piece laminate at the back extends to the floor. This insulation also comes in a narrow ½" roll, which may be of some use.

MEASUREMENTS

I made all measurements using an early IMP audio analyzer on indefinite loan from G.R. Koonce. The test location was my one-car basement garage, with dimensions of roughly 8 × 10 × 24'. I placed the speaker against the inside of the closed door near its center. The

side walls near the door were covered with 7" thick fiberglass. I covered the floor near the speakers with 6" of foam

absorber. This was needed even when making near-field measurements to reduce nearby reflections.

TABLE 2
BASS ENCLOSURE MECHANICAL PARTS LIST

QTY	DIMENSIONS	MATERIAL
1	12 × 22 × ¾"	Fiberboard shelving (top front)
1	12 × 18¼ × ¾"	Fiberboard shelving (bottom front)
1	12 × 44¾ × ¾"	Fiberboard shelving (back)
2	44.8 × 2.5 × 9/16"	Hardwood (side)
2	24.5 × 2.5/0 × 9/16"	Hardwood (tapered side addition 7.91° slope)
1	33.7 × 2.5 × ½"	Hardwood (internal brace)
2	24.5 × 2.5/0 × ½"	Hardwood (tapered side addition 7.91° slope)
2	18 × 2.5 × ½"	Hardwood (partition with 10° taper)
2	4.25 × 2.5 × .8/0"	Wood (tapered corner piece with 10° taper)
1	12 × 4 × ¾"	Fiberboard shelving (top)

THE SCIENCE OF SOUND

Morel's R&D department continually researches the science of sound.

engineered to provide uncompromising sound, Morel is offering you top-of-the-line hybrid units with a diameter of either 4", 5 1/4", 6 1/2", 8" & 10".

Morel's Hybrid Range features:

- 2 1/4" or 3" Hexatech Aluminum Voice Coil
- Powerful Compact Hybrid Magnet Motor
- High Degree of Magnetic Shielding
- One-Piece Integrated Dome and Surround Cone

Morel's drive units are the choice of many of the world's high-end loudspeaker manufacturers.



Making a LoudSpeaker Music to Your Ears

USA Distributor:
Madisound Speaker Components
Tel: 608-831-3433
e-mail: info@madisound.com
Web Site: www.madisound.com

MOREL:
Tel: ++972-8-9301161
Fax: ++972-8-9301312
Email: info@morel.co.il

www.morelhifi.com

There is no longer any connection between Morel and morel acoustics u.s.a.

Morel name and logo is a worldwide registered trademark of Morel Israel. Reg USA No. 1549884



I set the analyzer window to 40ms to eliminate the rear wall reflection, which was very strong. With a steady 40Hz excitation I found the sound stronger in the center of the room than at the speaker cone! The 40ms window allowed the computation to go below 30Hz. I used the test probe to calibrate the system at the output of the DC-coupled amplifier that drove the speaker under test with a 2V test pulse.

BASS SPEAKER PERFORMANCE

Figure 7 shows the cone response of the Audax driver. The test was near-field with the speaker placed against the garage door. The cone response at 60Hz is down about 10dB. This is in good agreement with Fig. 1, which shows a 9dB loss. Figure 8 shows the port response at 40Hz to be down about 5dB. This is in good agreement with the prediction in Fig. 1, which shows about a 6dB loss at 40Hz.

I measured the port pressure at the exit opening that is somewhat larger than the horn mouth, hence the 7.2dB

area ratio gain correction rather than 6dB. The measurements pertain to the first speaker using the Radio Shack fiberglass stuffing. A comparison of Figs. 7 and 8 shows the port to be in phase with the cone at 60Hz. This also is in good agreement with the prediction in Fig. 1. The second speaker using Home Depot pipe insulation stuffing provided similar results.

TREBLE SPEAKER DESIGN

The mechanical design for the treble speaker is shown in Fig. 9. This is a true transmission line with a reverse taper and no port. I omitted the port because I wanted eventually to try other 3.5" car speakers and did not want to be tied to a length that depended on the treble unit's resonant frequency.

As you will see later, the sensitivity of the Boston FX3 is adequate

and the rise in impedance at resonance is well enough controlled so that a simple 6dB rolloff works well. I feared that the rise in impedance at resonance might be a problem with a simple 6dB per octave bass rolloff. Certainly the electrical damping would be compromised by the high impedance of the series CO capacitor.

In fact, I built an active CO and compared the treble unit's performance with the two types of COs. The measured and audible differences were negligible so I kept the passive CO.

I had several objectives to meet with this design. First, I wanted a thin enclosure to match the bass enclosure in width. Second, I chose to locate the tre-

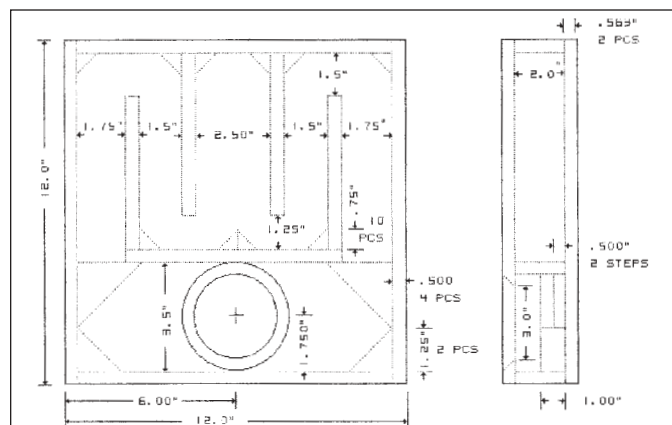


FIGURE 9: Treble speaker enclosure drawing.

B-1810-9

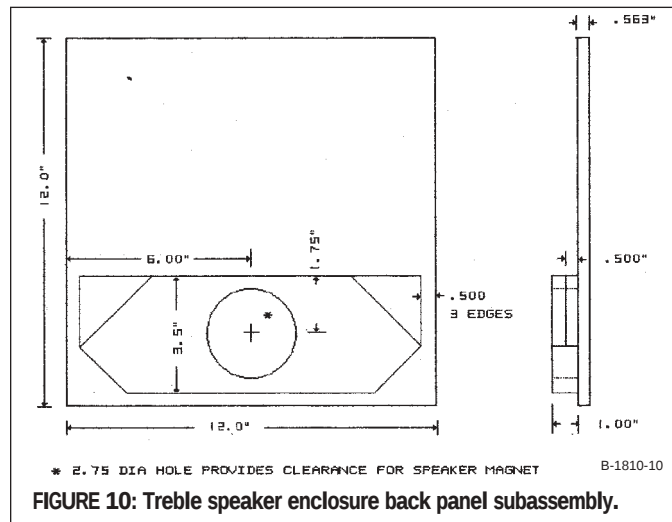


FIGURE 10: Treble speaker enclosure back panel subassembly.

B-1810-10

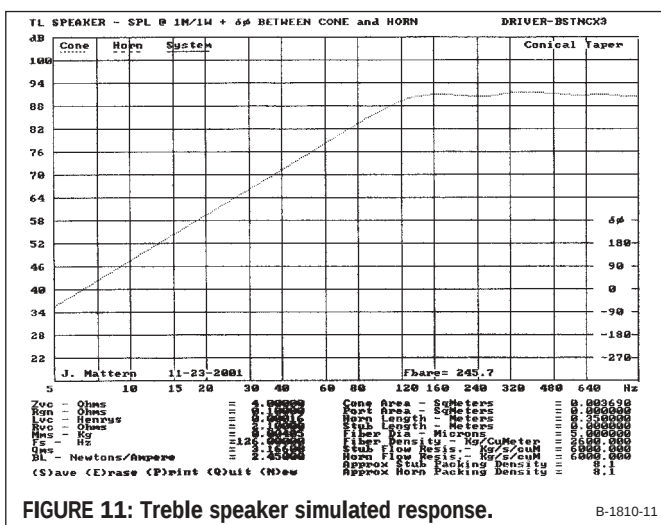


FIGURE 11: Treble speaker simulated response.

B-1810-11

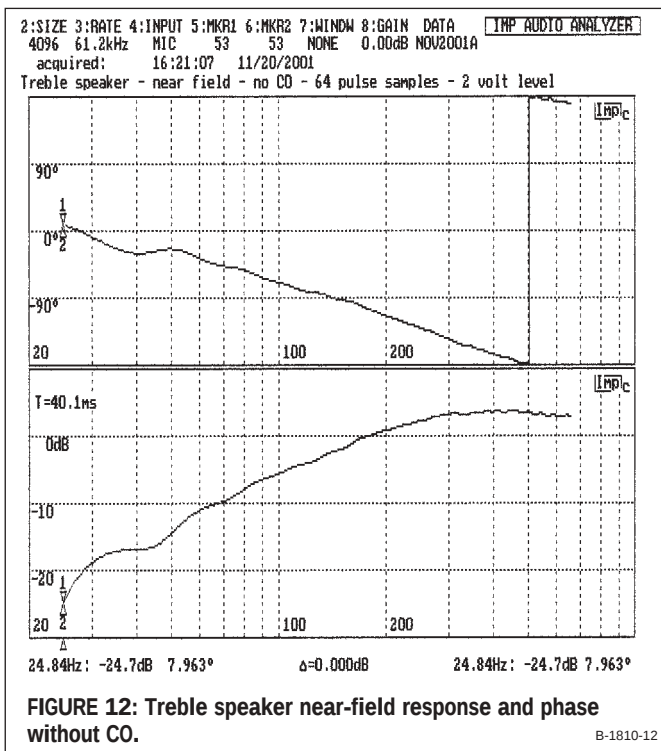


FIGURE 12: Treble speaker near-field response and phase without CO.

B-1810-12

ble driver as close as possible to the bass driver. Third, I wanted a balanced acoustic load on the back side of the driver. And fourth, I wanted the initial transmission line area to equal the cone area.

The last item required a 1" fill with a cutout for the magnet. The fill is at-

tached to the back panel as shown in *Fig. 10*. The shallow 1" TR feeds into a narrow TR having a depth of 2". The transition is accomplished by a 45° step, with a depth of 1.5". The remaining passages are narrower but deeper. Do not confuse this step with the 45° corner piece. There are two large cor-

ner pieces in the speaker section and ten other smaller corner pieces.

TREBLE SPEAKER CONSTRUCTION

The front and rear panels are made from $\frac{9}{16}$ " high density fiberboard. I used $\frac{1}{2}$ " fiberboard for the side pieces as well as the inside pieces, but I highly recommend using hardwood instead because the screws hold so much better. The gap between the front and rear panels is 2.0". Details of the major parts are provided in *Tables 3 and 4*.

I used the same procedure to assemble the treble speaker as I did with the bass speaker; that is, I made a drawing on the inside of the front panel locating all the 2" pieces and the driver cutout. The next step I should have done before but didn't—that is, make an identical drawing on the outside of the back panel as an aid in locating the screw holes. Since the speaker is mounted on the inside, it is desirable to have the back removable. I then cut the 3.0" hole for the driver in the front panel and cut a 45° chamfer with my router on the outside of the panel. You will want to leave an $\frac{1}{8}$ " section of wall without a chamfer.

TABLE 3
TREBLE SPEAKER ENCLOSURE PARTS LIST

QTY	DIMENSIONS	MATERIAL
1	12 × 12 × $\frac{9}{16}$ "	MDF (front)
1	12 × 12 × $\frac{9}{16}$ "	MDF (back)
2	12 × 2 × $\frac{1}{2}$ "	Hardwood (sides)
2	11 × 2 × $\frac{1}{2}$ "	Hardwood (top and bottom)
1	7.5 × 2 × $\frac{1}{2}$ "	Hardwood (internal horizontal)
1	11.0 × 3.5 × $\frac{1}{2}$ "	Hardwood (internal filler—see <i>Fig. 9</i>)
2	5.5 × 2 × $\frac{1}{2}$ "	Hardwood (internal outside vertical)
2	5.75 × 2 × $\frac{1}{2}$ "	Hardwood (internal inside vertical)
2	1.25 × 2 × $\frac{1}{4}$ "	Wood (45° corner piece)
10	.75 × 2 × .75"	Wood (45° corner piece)
14	#6 × $1\frac{1}{4}$ "	Steel wood screws

TABLE 4
TREBLE SPEAKER ENCLOSURE STUFFING—CORNERS PER *FIG. 9*


QTY	DIMENSIONS	MATERIAL
1	11 × 3.5 × 1"	Fiberglass blanket (2-.5" layers)
2	7.5 × 1.75 × 2.0"	Fiberglass blanket (2-.75 + 1-.5" layers)
2	7.0 × 1.5 × 2.0"	Fiberglass blanket (2-.75 + 1-.5" layers)
1	7.0 × 2.5 × 2.0"	Fiberglass blanket (2-.75 + 1-.5" layers)
1 pkg	.75 × $\frac{3}{16}$ "	Closed cell foam weatherstrip



CT2 6-gang
volume control for A/V Audio

General attenuator specifications

Number of steps:	24	
Bandwidth (10kOhm):	50	MHz
THD:	0.0001	%
Attenuation accuracy:	±0.05	dB
Channel matching:	±0.05	dB
Mechanical life, min.	25,000	cycles

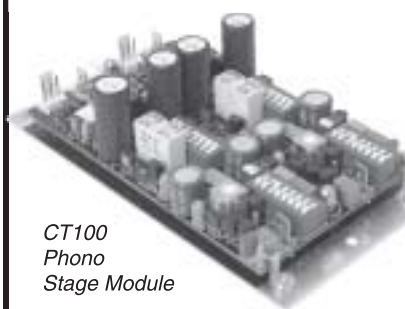

CT100
Phono
Stage Module

CT100 key specifications

Gain (selectable):	40 to 80	dB
RIAA eq. deviation:	± 0.05	dB
S/N ratio (40/80dB gain):	98/71	dB
THD:	0.0003	%
Output resistance:	0.1	ohm
Channel separation:	120	dB
Bandwidth:	2	MHz
PCB dimensions:	105 × 63	mm
	4.17 × 2.5	"



CT101 Line Stage Module
with a stereo CT1 attenuator added.

CT101 key specifications

Gain (selectable)	0, 6 or 12	dB
Bandwidth (at 0dB gain)	25	MHz
Slew rate (at 0dB gain)	500	V/uS
S/N ratio (IHF A)	112	dB
THD	0.0002	%
Output resistance	0.1	ohm
Channel matching	± 0.05	dB
PCB dimensions:	100 × 34	mm
	3.97 × 1.35	"

DACT
DANISH AUDIO CONNECT
DACT

Sales Dep.: Tel.: (+66) 2 260 6070
Fax: (+66) 2 260 6071
E-mail: info@DACT.com

<http://www.DACT.com>

High quality audio parts for upgrading existing equipment, DIY constructions and for audio equipment manufacturers. DACT audio components offer unusually large bandwidth, low distortion, high accuracy, low noise and long lifetime. DACT products:

- Stepped Audio Attenuators
- Stepped Balance Controls
- Audio Input Selector Switches
- Phono Stage Module
- Line Stage Module
- Different Accessories

Made in Denmark

I used the pencil layout on the front panel to place the parts, starting with the outside parts first. I glued all pieces including the ten small corner pieces and the two large corner pieces to the inside of the front panel a few pieces at a time because of the limited number of available clamps. The rear panel is attached with screws on 3" centers with closed cell weather stripping providing



PHOTO 3: Unfinished speaker system with CO at top, set up against garage door for tests.

the seal. *Photo 2* shows the entire assembly just before closing it. This enclosure is very sturdy and is virtually immune to speaker-induced vibrations, as is the bass speaker.

TREBLE SPEAKER PERFORMANCE

Figure 11 shows the predicted low frequency response using a modified simulation program that omits the parts that do not apply to a TL without a port. I obtained most speaker parameters using the IMP analyzer to measure the Thiele/Small parameters, which I converted to the alternate parameters, ex-

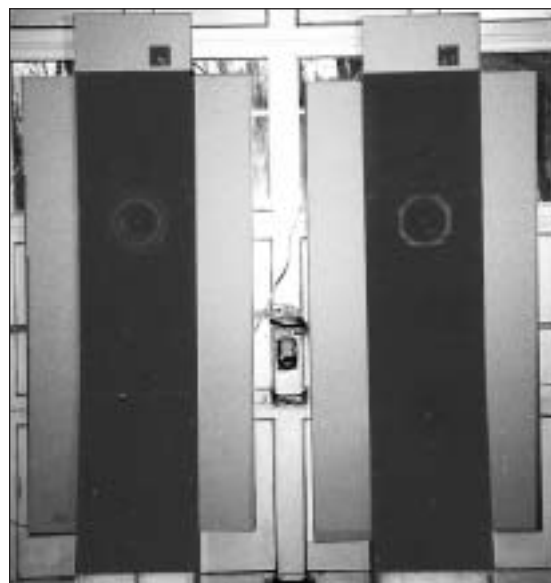


PHOTO 4: Stereo pair with diffraction-reducing side boards.

cept for BL, which I am able to measure directly at home. *Figure 12* shows the measured low frequency response of the treble speaker. The two are in good agreement at 40Hz.

COMBINED BASS AND TREBLE PERFORMANCE

Figure 13 shows the magnitude and phase of the bass speaker with the CO in the path. *Figure 14* shows the magnitude and phase of the treble speaker with the CO in the path. I made both measurements near-field with the window set to 6ms. The measurement system gains were equal and the Lpad setting was maximum. The design crossover is 1250Hz.

The phase difference at this frequency was 90° as required. The dip at 900Hz appeared to be related to edge diffraction, since the size was reduced with a window smaller than 6ms. *Photo 3* shows the completed speaker against the inside of the garage door. I abandoned outdoor testing because of the noisy environment.

EDGE DIFFRACTION

The stereo speaker configuration as tested is shown in

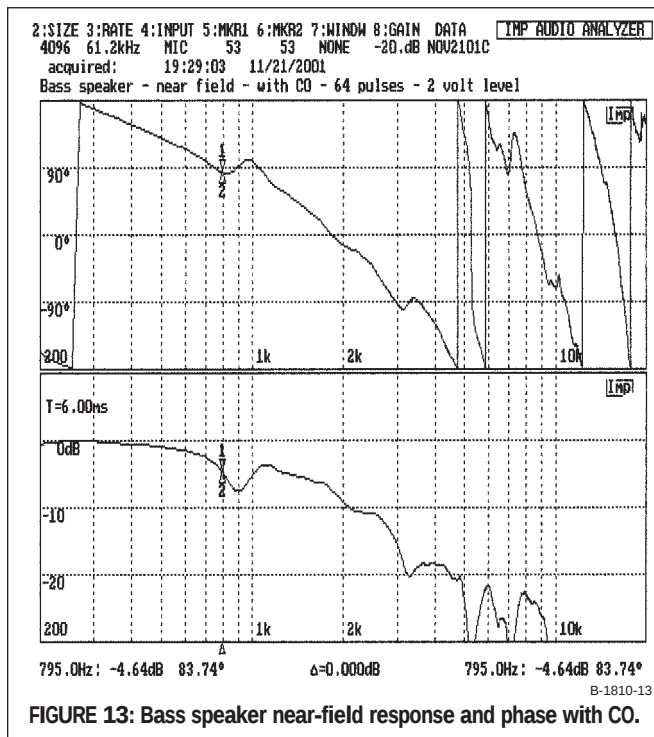


FIGURE 13: Bass speaker near-field response and phase with CO.

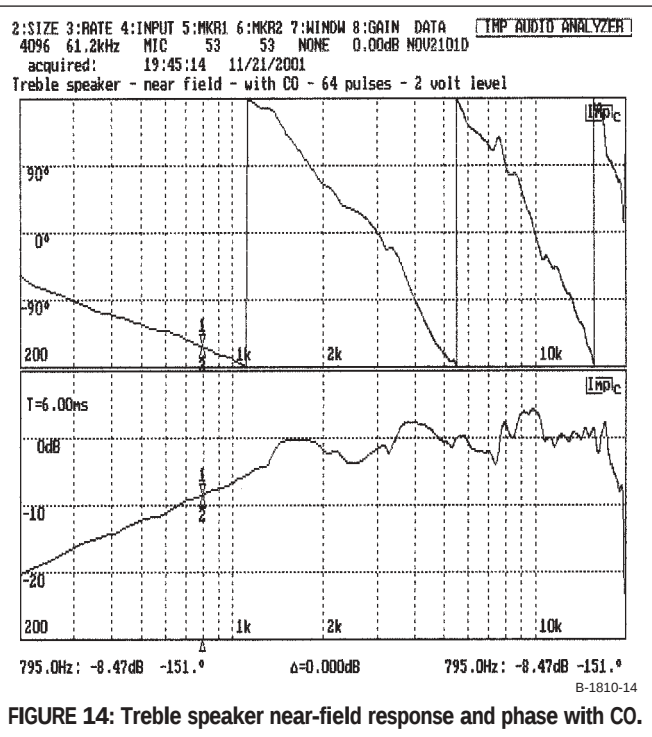


FIGURE 14: Treble speaker near-field response and phase with CO.

Photo 4. In Beranek's⁵ "acoustic measurements" his illustration of the diffracted wave from the edges of the speaker cabinet gave me an idea for canceling the wave with a second diffracted wave delayed 180° beyond the first. The measurements did show partial cancellation. The first peak and first dip, near 1000Hz, were reduced to half their value without the canceling panels. Of course, this works only if the outside panel ends are tight against the wall.

The panels are 6" in width and the front surface is set back 2" from the front surface of the main body of the speaker. There are two edge pieces giving the pieces a shallow U-shaped cross-section. The center contains fiberglass to suppress resonance. The depth of the panel and sidepiece is 2". I think sloping pieces might be more effective, but I was dissuaded by the greater construction difficulty.

SUBJECTIVE EVALUATION

Finally, I replaced the SB 3/99 speakers in the basement club room with the flat ones. I chose the following sources for the listening tests because I am familiar with the sound of a symphony orchestra and because it is difficult to reproduce.

1. The *Nutcracker* with the Kirov Ballet on a Philips DVD.
2. Beethoven adagio from piano concerto No. 5 on Silverline DVD Audio.
3. Murray Perahia's Mozart on Sony VHS.
4. Bruckner Symphony No. 8 by the Israel Philharmonic on Image DVD.
5. Excerpts from Tchaikovsky's Ballets on Silverline DVD Audio.

ACKNOWLEDGMENT

I would like to thank G.R. Koonce for the loan of the IMP audio analyzer as well as his invaluable comments on my earlier simulation mistakes.

REFERENCES

1. Stewart and Lindsay, *Acoustics*, Van Nostrand Co., 1930, pp. 79-83.
2. Olson, H. F., *Elements of Acoustical Engineering*, Van Nostrand Co., 1949, p. 20.
3. Bradbury, L.J.S., JAES, April 1976, volume 24, Number 3.
4. ITT, *Reference Data for Radio Engineers*, Howard W. Sams, 1977, pp. 4-45.
5. Beranek, Leo L., *Acoustic Measurements*, John Wiley & Sons, Inc, 1949, pp. 106-110.
6. Bailey A. R., "A Non-Resonant Loudspeaker Design," *Wireless World*, October 1965, p. 20.

In comparing the new speaker with the old one, I noted that the biggest difference was the cleaner highs. I attribute this to the changes in the FX3 and possibly to reduced diffraction effects. The bass was warmer than in the garage, but in the clubroom a tad more powerful than the old speaker. I have wondered about the effect of the garage door on the sound! In the clubroom the speakers are up against a 12" cement block wall. The new speaker's midrange definitely seemed more transparent.

In comparing the five sources, I would give the highest marks to the VHS and the lowest to the CD. The CD could not carry the peaks without audible distortion, particularly in the first ballet selection. All the DVDs produced fine sound even on peaks but lacked the polish of the VHS tape. ♦

Chat, browse, bid, buy, sell
or simply click 'til it hurts.

www.AUDIOGON.com
HIGH END AUDIO MARKETPLACE

It is not enough to put oil
into a Capacitor to make
it musical...

**KRISTALL
CAP**



Forget about resistive devices
for the volume setting.
We offer a silver wired
transformer approach

**Silver Rock
Transformer-
Potentiometer**



It is not enough
to use silver wire
for a good SE-OPT...

**Silver Rock
Output transformer**



**There is only one optimum solution
for a given problem.**

Audio Consulting / 14B chemin des Vignes / 1291 Commugny / Switzerland
Fax: 00-41-22-960-12-59 / e-mail: serge.schmidlin@span.ch
<http://www.audio-consulting.ch>



Design an Active Transient-Perfect Second-Order Crossover

After constructing and testing an active circuit, this author shares his design rules for actively implementing transient-perfect, second-order crossovers. **By John Kreskovsky**

In my article, "A Transient-Perfect Second-Order Passive Crossover" (May '01 *aX*), I presented the basic theory behind the development of transient-perfect second-order crossovers using symmetric, overlapped, low Q, second-order filters with equalization based on a simple second-order resonant circuit. The crossover yielded a summed response that had flat amplitude and zero phase shift, and hence was transient perfect. The design of the filters and equalization was based on a series of computer-optimized results from which a set of design graphs were presented.

In this installment I have returned to the analysis of the transfer functions and developed a set of design rules (equations) for determining the required filter and equalizer parameters as a function of the crossover frequency and overlap between the high-pass and low-pass filters. I have also developed a spreadsheet-based CAD tool for the design of active transient-perfect second-order crossovers that you may download from the web.

ANALYSIS

I begin with the assumption that a filter can be constructed such that

$$T_{EQ}(s) (T_{HP}(s) + T_{LP}(s)) = 1 \quad [1]$$

Here $T_{EQ}(s)$ is the transfer function of the equalization network, $T_{HP}(s)$ the transfer function of the high-pass filter, and $T_{LP}(s)$ the transfer function of the low-pass filter. I further assume that the transfer functions of high-pass and low-pass sections are those of symmetric,

overlapped second-order filters. Defining s as

$$s = j\omega/\omega_0 \quad [2]$$

where ω_0 is the crossover frequency, and an overlap parameter, γ , such that the corner frequencies of the high- and low-pass filters are given, respectively, as

$$\omega_{HP} = \omega_0/\gamma \quad [3a]$$

and

$$\omega_{LP} = \gamma\omega_0 \quad [3b]$$

The transfer functions for the high-pass and low-pass filters can then be expressed as

$$T_{HP}(s) = \frac{(\gamma s)^2}{1 + s\gamma/Q_f + (\gamma s)^2}, \quad [4]$$

and

$$T_{LP}(s) = \frac{1}{1 + s/(\gamma Q_f) + (s/\gamma)^2}, \quad [5]$$

Q_f is the Q of the filter section in the usual sense. Please note that the definition of γ is different here from that which I used in the original paper. The present γ is equal to the square root of gamma from the original work.

The transfer function of the equalization network is given as

$$T_{EQ}(s) = \frac{1 + sG/Q_{eq} + s^2}{1 + s/Q_{eq} + s^2} \quad [6]$$

In Equation 6 G is the gain at resonance and Q_{eq} is the Q of the resonant circuit.

Equations 4, 5, and 6 are then substituted into Equation 1. After some mathematical manipulation you end up with the rather ominous equation,

tuted into Equation 1. After some mathematical manipulation you end up with the rather ominous equation,

$$\begin{aligned} &[(\gamma s)^2 (1 + s/(\gamma Q_f) + (s/\gamma)^2) + (1 + s\gamma/Q_f + (\gamma s)^2)] [1 + sG/Q_{eq} + s^2] = \\ &(1 + s/(\gamma Q_f) + (s/\gamma)^2) (1 + s\gamma/Q_f + (s\gamma)^2) (1 + s/Q_{eq} + s^2) \end{aligned} \quad [7]$$

We can multiply this out and obtain an equation of the form

$$\begin{aligned} &a_0 + a_1 S + a_2 S^2 + a_3 S^3 + a_4 S^4 + a_5 S^5 + \\ &\quad a_6 S^6 = \\ &b_0 + b_1 S + b_2 S^2 + b_3 S^3 + b_4 S^4 + b_5 S^5 + \\ &\quad b_6 S^6 \end{aligned} \quad [8]$$

For the equality of Equation 8 to be satisfied, which will render Equation 1 satisfied with the transfer functions given by Equations 4, 5, and 6, the coefficients of like-order terms on the left- and right-hand side of Equation 8 must be equal. For example, a_0 must equal b_0 . The task at hand then is to determine values for Q_f , Q_{eq} , and G , for a specified value of γ that satisfies the necessary constraints. After a little effort the following relationships emerged:

$$Q_{eq} = \frac{1}{(\gamma^2 - 1)}, \quad [9]$$

$$Q_f = \frac{\gamma}{(\gamma^2 + 1)}, \quad [10]$$

$$G = 1 + 1/\gamma^2 + 2/(\gamma^2(\gamma^2 - 1)) \quad [11]$$

A plot of these relationships is shown in *Fig. 1*. Note the gain asymptotes to 1.0 as γ goes to infinity, and infinity as γ approaches 1.0. Q_{eq} also asymptotes to infinity as γ approaches 1.0, and 0.0 as γ approaches infinity. Q_f varies between 0.5 at $\gamma = 1.0$ and 0.0 as γ goes to infinity. I recommend that γ be restricted to between 1.5 and 2.0.

A schematic of an active circuit for the crossover is shown in *Fig. 2*. The

component values for the filter and equalizer sections are given as follows:

For the high-pass (HP) section, for a given value of C_{HP} ,

$$R1 = \gamma / (4\pi f_x C_{HP} Q_f)$$

$$R2 = \gamma Q_f / (\pi f_x C_{HP})$$

For the low-pass (LP) section, for a given value of R_{LP} ,

$$C1 = Q_f / (\pi \gamma f_x R_{LP})$$

$$C2 = 1 / (4\pi \gamma f_x R_{LP} Q_f)$$

and for the equalizer section, for a given value of R_e ,

$$Le = Q_{eq} R_e / (2\pi f_x)$$

$$Ce = 1 / (2\pi f_x Q_{eq} R_e)$$

$$Re1 = (G - 1) R_e$$

The inductor in the RLC resonate circuit can be replaced by an active inductor as shown in Fig. 3.

TESTING

I developed a spreadsheet-based CAD tool for designing the active crossover. A sample design, generated using the spreadsheet, is shown in Fig. 4 for the case where $\gamma = 2.0$ and the crossover frequency, f_x , is 1kHz. The low Q behavior of the HP and LP sections is evident. The filter section Q_f is 0.4. The equalization for this case has a Q_{eq} of 0.333 with 3dB gain. The equalized HP and LP responses are also shown.

The actual spreadsheet also shows the phase response of the filters, as well as reference first-order and second-order Linkwitz-Riley filter functions, and computes the required values for the filter components shown in Figs. 2

and 3. You can download it from the Internet at: <http://www.pvconsultants.com/audio/frdgroup.htm>.

When using the spreadsheet, the values of C_{HP} , R_{LP} , and Re are specified and values for $R1$, $R2$, $C1$, $C2$, Ce , Le , and $Re1$ are computed. You must also specify $Re2$, and the spreadsheet then calculates the values of $Re3$ and $Ce2$ for the active inductor. I chose values of 0.22μF for C_{HP} , 2.21kΩ for R_{LP} , 4.42kΩ

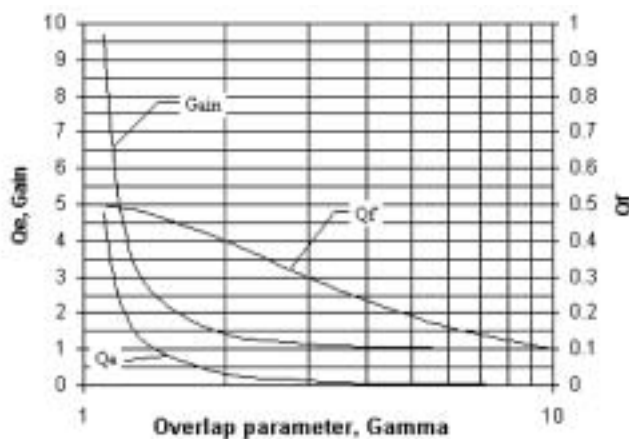


FIGURE 1: Variation of Q_{eq} , Q_f , and gain with γ .

B-2089-1

Hi-Fi Do Inc.

BUY & SELL

OVER A
MILLION
HITS/WEEK

USED AMPLIFIERS, SPEAKERS, BOOKS, ACCESSORIES etc.

www.hifido.co.jp

OSAKA(Overseas Dept.): 4-6-10 NIPPONBASHI NANIWA-KU OSAKA JAPAN

TOKYO: TOKUHARA BLD 5-5-7 SOTOKANDA CHIYODA-KU TOKYO JAPAN





NAGOYA: 3-11-30 OOSU NAKA-KU NAGOYA JAPAN

PHONE 816-4396-7611 FAX 816-4396-7621

for R_e , and $2.21k\Omega$ for R_{e1} . This yielded the following values for the remaining components:

$R1 = 1.809k\Omega$
 $R2 = 1.157k\Omega$

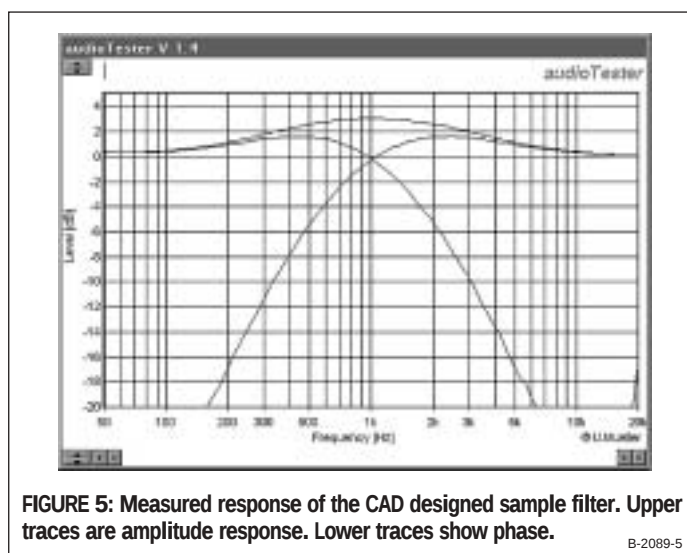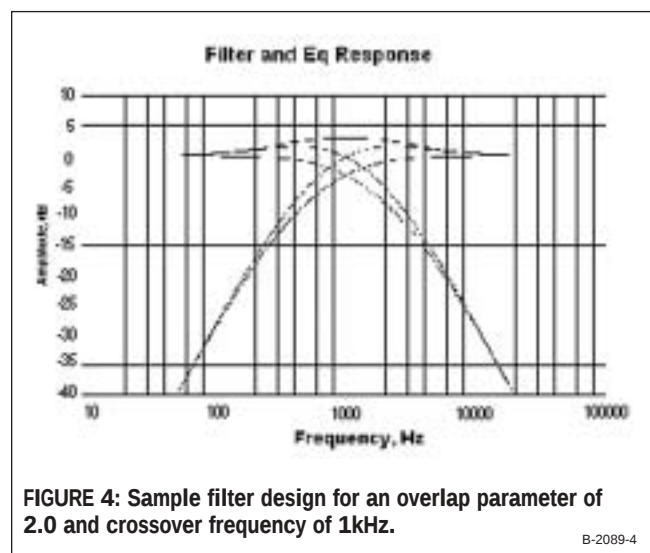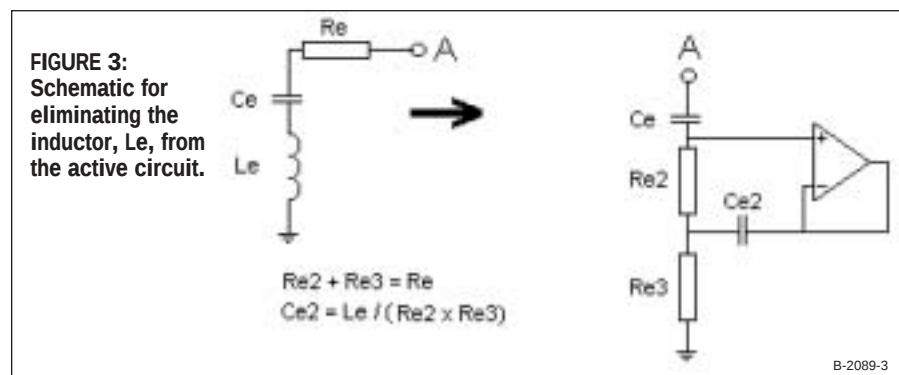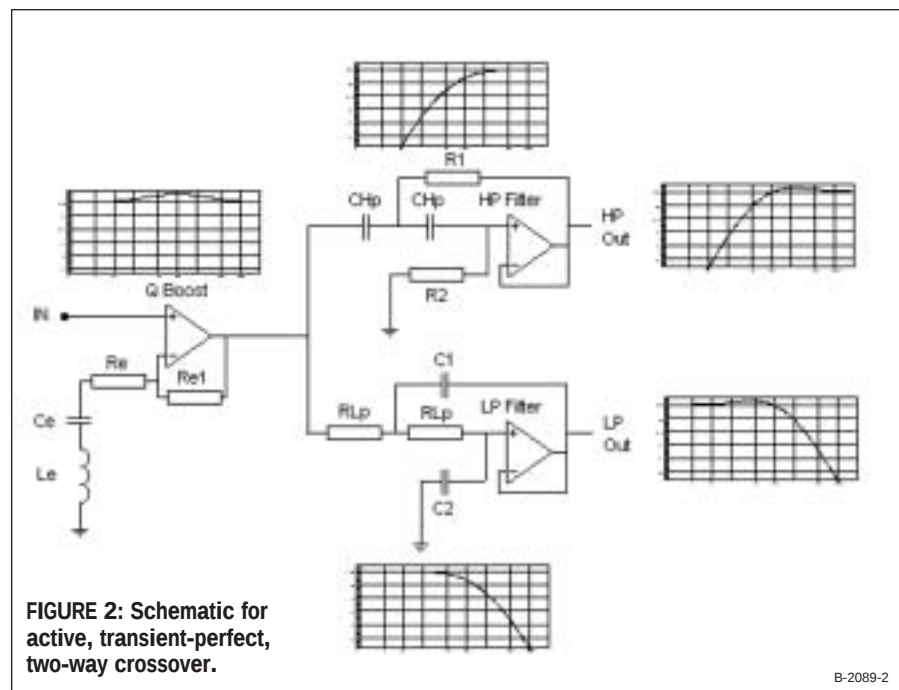$C1 = 0.0222\mu F$
 $C2 = 0.0347\mu F$
 $C_e = 0.1080\mu F$
 $L_e = 234.5mH$
 $R_{e3} = 2.21k\Omega$
 $Ce2 = 0.048\mu F$



I then constructed the circuits shown in *Figs. 2* and *3* around the Burr-Brown OPA2134 dual audio operational amplifier using metal film resistors with standard values as close to the CAD-generated values as possible. Polypropylene capacitors were used, paralleled to obtain the necessary values. One 2134 was used for the active equalization and active inductor; the second 2134 was used for the high-pass and low-pass filters. The circuit was powered by a ± 12 power supply salvaged from a circa 1980 RACAL computer modem.

I made measurements of the frequency response at the output of the equalizer circuit and at the output of the high- and low-pass filters using the Audio Tester¹ with a sine-wave sweep. The measured results are shown in *Fig. 5* and are in excellent agreement with the CAD design. I also measured the response of the system to a 250Hz square wave as generated using the Audio Tester.

The measured response of the high-pass, low-pass, and the summed output is compared to the input signal in *Fig. 6*. *Figure 7* shows the summed output and the input when the frequency is raised to 800Hz. Both figures show that the crossover retains waveform integrity within the limits of the generating/measuring system.

This transient-perfect nature of this type of crossover also lends itself directly to three- (or more) way crossovers

REFERENCES

Audio Tester, Shareware by Ulrich W. Muller, <http://www.sumuller.de/audiotester/>.

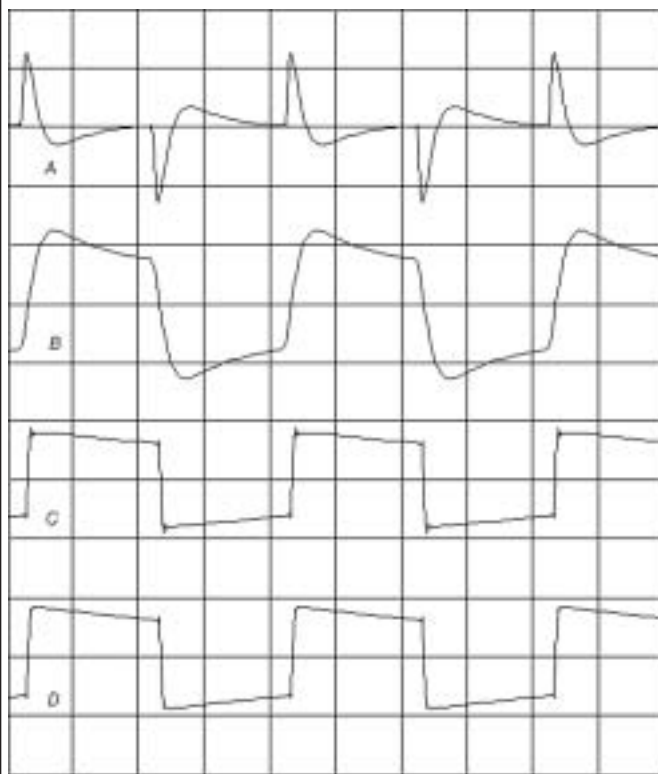


FIGURE 6: Measured 250Hz square wave response. A: high-pass output, B: low-pass output, C: summed output, D: input signal. Note: vertical scale varies for different sweeps.

B-2089-6

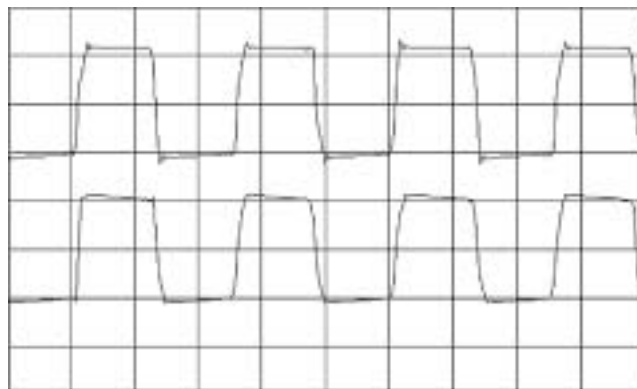


FIGURE 7: 800Hz square wave response. Upper trace: summed output, lower trace: input.

B-2089-7

with little additional effort. For example, the crossover can be cascaded without affecting the transient-perfect nature of the response. A second HP/LP/EQ block can be placed at the output of the HP or LP section

of a previous stage to produce a three-way transient-perfect crossover that also has flat summed amplitude and phase response. For additional information, refer to the May '01 issue of *audioXpress*. ♦

Sure we have middlemen.
FedEx & UPS, to name a couple.

www.AUDIOGON.com
HIGH END AUDIO MARKETPLACE

TURBOCHARGING YOUR REGA ARM



"Nothing less than total dynamite" **HI-FI WORLD MAGAZINE**

If you are the proud owner of any Rega arm why not utterly transform it into the league of super arms with the Origin live structural modification:- \$91. This modification will enable your Rega to perform at a level exceeding that of arms costing over \$1700. Rewiring with high grade litz cable is also offered at an additional \$85 and external rewiring is \$99. All these modifications are available in kit form if you wish to do the job yourself or you can send us your arm for us to do the work.

"I have to say the Rega modifications turn this humble arm into a real Giant killer. Gone is the rather grey, sterile sound of the cooking Rega. Instead, tonal colour is fresh, dynamics have great speed and impact, and the sound stage is huge." **HI FI WORLD SUPPLEMENT** (structural modification to an RB250)

WHAT HI-FI MAGAZINE gave this modification a 5 star rating.

For arm modifications we normally turn around your arm in 1 - 2 days

OTHER KITS & PRODUCTS FROM ORIGIN LIVE INCLUDE:-

- **TURNTABLES (Kits & Retail)**
"the best sounding deck here...sounds fantastic" **WHAT HI-FI MAGAZINE** group comparison test of 8 leading turntables
- **SILVER 250 TONEARM \$729**
Probably the best tonearm available at any price (except for the Silver Taper).
- **SILVER TAPER TONEARM \$1491**
- **DC MOTOR UPGRADE**
suitable to upgrade all turntables including Linn Lingo, Armageddon, Roksan, Thorens, Ariston, Rega, Systemdek etc \$319
Well reviewed as a massive upgrade for all turntables

FULL INFORMATION ON WEB SITE OR CONTACT:-

Origin live, 87 Chessel Crescent, Bitterne, Southampton SO19 4BT

Tel: 023 80442183 / 80578877 Fax: 023 80398905

E MAIL: originlive@originlive.com **WEB SITE:** <http://www.originlive.com>



6C33C-B Push-Pull Power Amplifier II

Some things are better the second time around . . . like this new, improved power amp from one of our tube enthusiasts in France.

By Daniel J.F. David

As you probably already know, hi-fi lovers are perfectionists. So it's no surprise that after publishing my article ("Triode

Power Amplifier 6C33C-B," GA 2/99), remarks from certain friends encouraged me to continue studying and improving this amplifier, especially increasing its

power, perfecting a lower-voltage phase inverter, and adding a new output transformer (*Photos 1-3*).

PREAMPLIFICATION

I kept the same preamplifier stage but used 12AT7 tubes (*Fig. 1*). With these the gain is 40, less than with the 12AX7, but with a larger input swing. The pre-amplifier and the phase inverter com-

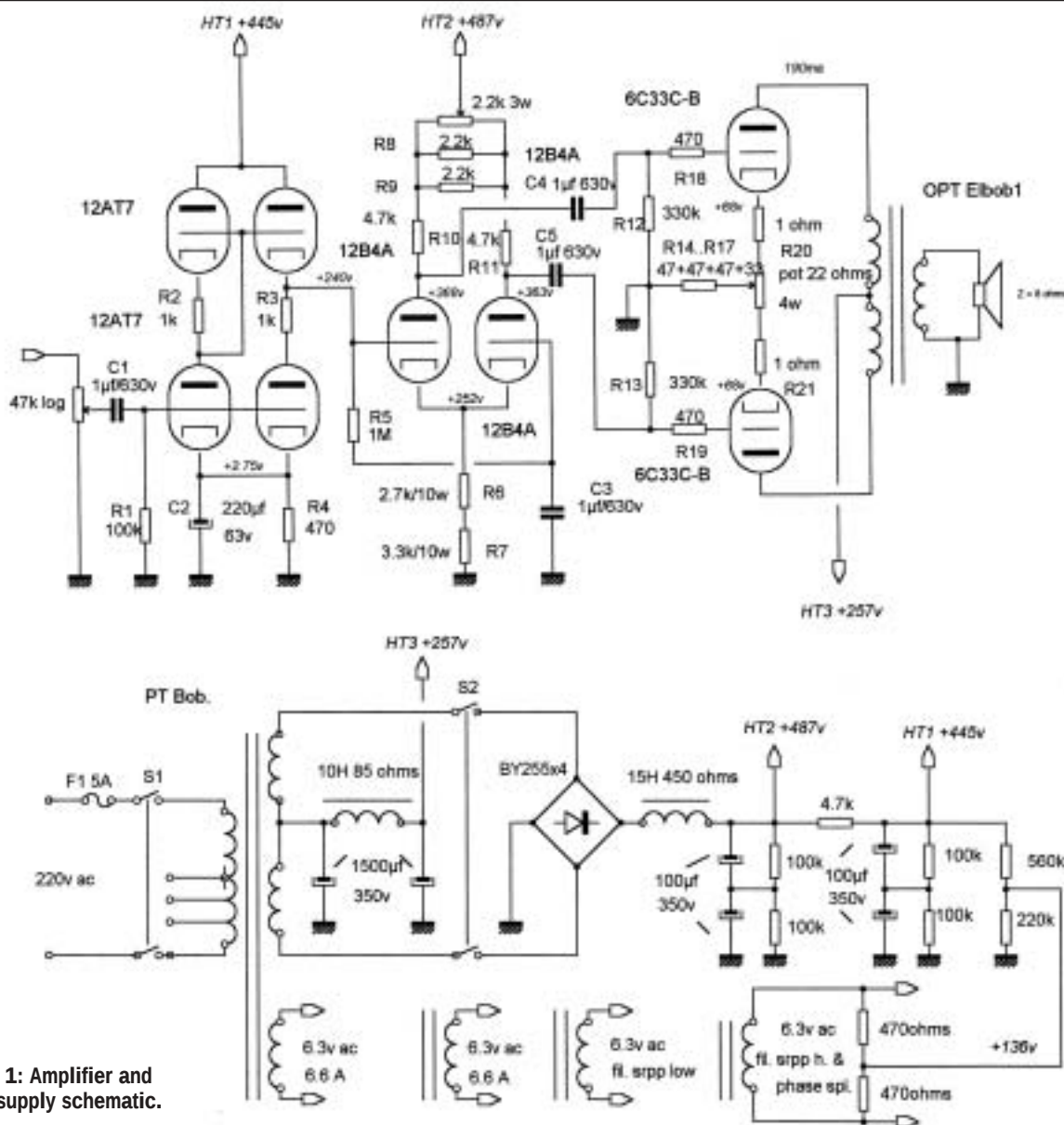


FIGURE 1: Amplifier and power-supply schematic.

G-2055-1

bined have a 108 gain, which is more than sufficient. The preamplifier is composed of a shunted-regulated push-pull (SRPP) and a directly coupled cathode charge stage.

I discovered this schematic a few years ago as described by José Gomez in an issue of the *L'Audiophile* magazine. After having experimented with it, he allied a bass output impedance, a graduated distortion spectrum composed of only odd harmonics (regularly graduated from low to high), and a high gain and output swing.

The V1 and V2 tubes function as a normal SRPP. If the V1 receives a positive alternance, its grid becomes less negative, the V1 plate voltage decreases (the internal resistance of the V1 decreases, as well), and the R2 terminal voltage increases. A more and more negative voltage is applied to the V2 grid (the internal resistance of the V2 increases) and at the same time the same increasingly negative voltage is applied to the V4 grid. The voltage of the V4 cathode decreases as well.

The input signal is applied to the V3 grid. The grid voltage of this tube is less and less negative (the internal resistance of the V3 decreases), and the plate voltage of the V3 decreases. You now have a constant voltage on R3, which is of a constant ohm value, equal to a constant current in the R3.

Theoretically, a constant-current source has infinite impedance. Therefore, the V4 has a cathode load with infinite impedance (in alternate). R3 in AC has a resistance, which is superior to its ohm value. In theory, the higher the triode load, the more linear the stage.

SCHMITT CATHODE-COUPLED PHASE INVERTER

I needed to use a high voltage with the cathode-coupled phase inverter in order to obtain a direct liaison with the preceding stage. Despite its qualities, I had to rethink this stage, turning to the Schmitt phase inverter. I used two 12B4As for a gain of 2.7 without distortion and 170V peak-to-peak (pp) output with a voltage of 487V, conserving a direct liaison with the preceding stage. All the resistors in this stage are 11W, non-inductive.

The balance of the phase inverter is

PHOTO 1:
The revised
6C33C-B
power amp.



Chelmer Valve Company Ltd

The Stables, Baddow Park, Great Baddow, Chelmsford
Essex, CM2 7SY, England.

email: sales@chelmervalue.com ** tel. 44 1245 241 300 fax. 44 1245 241 309 ** www.chelmervalue.com

for High Quality Audio Tubes

Everybody in the audio tube business knows that the justly famous brand names of yesteryear like Brimar, GEC, Mullard, RCA, Telefunken etc. etc. are scarce and often quite expensive.

Although we supply all major brands as available (and we have many in stock) our policy is to offer a range of tubes, all new and mostly of current manufacture, the best we can find from factories around the world, which we process to suit audio applications. The result – **CVC PREMIUM** Brand. Our special processing includes selection for **low noise, hum & microphony** on pre-amp tubes and controlled **burn-in** on power tubes to improve **stability** avoid tubes with weaknesses etc.

***** A selection of CVC PREMIUM Audio Tubes *****							
PRE-AMP TUBE		POWER TUBES		POWER TUBES cont.		RECTIFIERS cont.	
ECC81	5.90	EL34G	8.30	6L6/ 5881 WXT	9.00	5Y3GT	4.80
ECC82	5.90	EL34 (JJ)	8.50	6V6GT	5.50	5Z4GT	5.80
ECC83	5.90	EL34 (Large Dia)	11.00	6080	11.50	SOCKETS ETC.	
ECC85	6.60	EL84	5.50	6146B	11.00	B9A (Ch or PCB)	1.60
ECC88	5.70	EL509/519	13.00	6336A	48.00	Ditto, Gold Pl.	3.00
ECF82	5.50	E84L/7189	7.50	6550WA/WB	15.00	Octal (Ch or PCB)	1.80
ECL82	6.00	KT66	11.00	7581A	12.00	Ditto, Gold Pl.	4.20
ECL86	6.30	KT66R	22.50	807	10.70	UX4 (4-Pin)	3.60
EF86	6.00	KT77	13.20	811A	11.80	Ditto, Gold Pl.	5.50
E80F Gold Pin	11.00	KT88	13.50	812A	31.00	4 Pin Jumbo	10.00
E81CC Gold	8.00	KT88 (Special)	17.00	845 (New des)	33.50	Ditto, Gold Pl.	13.00
E82CC Gold	9.00	KT88 (GL Type)	30.00	RECTIFIERS		5 Pin (For 807)	3.30
E83CC Gold	8.50	PL509/519	9.90	EZ80	5.10	7 Pin (For 6C33C)	4.70
E88CC Gold	8.80	2A3 (4 pin)	15.50	EZ81	6.00	9 Pin (For EL509)	5.00
6EU7	7.00	2A3 (8 Pin)	17.50	GZ32	15.50	Screen can B9A	2.20
6SL7GT	8.90	211	23.00	GZ33	15.50	Ditto, Gold Pl.	4.30
6SN7GT	5.30	300B	45.00	GZ34	7.20	Top Con. (For 807)	1.70
6922	6.40	6C33C-B	25.00	GZ37	15.50	Ditto, (For EL509)	2.00
7025	7.00	6L6GC	7.60	5U4G	6.30	Retainer (For 5881)	2.20
		6L6WGC/5881	8.90	5V4GT	5.00		

***** And a few 'Other Brands', inc. rare types *****							
5R4GY Fivre/GE	8.50	6SL7GT STC	13.00	13E1 STC	100.00	6550C Svetlana	18.00
5R4WGY Chatham	10.50	6SN7GT Brimar	13.00	211/VT4C GE	120.00	6146B GE	18.50
5Y3WGT Sylv.	6.50	12AT7WA Mullard	6.00	300B JJ	56.00	A2900 GEC	15.00
6AS7GT Sylv.	12.00	12AU7 Mullard	12.50	300B Svetlana	80.00	E88CC Mullard	14.60
6AU6WC Sylv.	5.10	12AY7 GE / RCA	8.40	300B WE	195.00	F2a Siemens	145.00
6B4G Sylv.	27.00	12AZ7 West'h.	8.00	805 USA	52.00	KT66 GEC	69.00
6BW6 Brimar	5.40	12BH7A RCA	14.00	5842A GEC	15.00	KT88 JJ	17.40
6BX7GT GE / RCA	9.00	12BY7A GE	9.50	6080 Telef.	13.30	KT88 Svetlana	35.00
6CG7/6FQ7	8.50	12E1 STC	12.50	6550A GE	31.50	PX25 KR	128.00

ALL PRICES IN U. K. POUNDS £

Please note extras: carriage charge (£3.00 in U.K.) & in EEC VAT (17.50%). When ordering please state if matching required (add £1.00 per tube). Payment by credit card (VISA, AMEX etc.) or TRANSFER or CHEQUE (UK only). FAX email or POST your ORDER for immediate attention – We will send PROFORMA INVOICE if required. MILLIONS OF OTHER TUBES & SEMICONDUCTORS IN STOCK!

**** Valve Amplifiers sound better still with CVC PREMIUM Valves! ****

**

PRICE VALIDITY TO END APRIL 2002 – ASK ABOUT ANY TYPES NOT ON THIS LIST

done with a 2.2k 4W potentiometer. You may use a voltmeter or a scope, adding the two signals and setting the signal to minimum.

POWER STAGE

The power stage is identical to my previous amplifier. The 25W cathode resistors are set up on an aluminum radiator. Since thermal dissipation is always a problem, a larger ventilated radiator, occupying the entire base of the amplifier, is being studied.

The stage adjustments can be made with an audio-frequency (BF) generator at 40Hz. A distortiometer is connected to a load of 8Ω at the output of the amplifier. Set the 22Ω potentiometer for minimum distortion.

Or as a second solution, you can connect two voltmeters to the 1Ω resistors. Set the two voltages to the same value.

OUTPUT TRANSFORMER

I studied a new mains transformer, which determines the final result of the amplifier. It was built by Bobinelec, a very competent Alsacien (France) winding company. I tried several transformers before finding a definitive and efficient model. The output transformer bandpass goes from 10Hz to 40kHz without any attenuation, and its distor-

TABLE 1	
AMPLIFIER PARTS LIST	
(DOUBLE ALL PARTS FOR STEREO)	
AVAILABLE FROM CONRAD ELECTRONIC:	
RESISTORS	
R1, R22, R23, R24,	100k, 2W, MO
R25, R30, R31	1k, 2W, MO
R2, R3, R24	1MΩ, 2W, MO
R5	2.7k, 10W, ceramic
R6	3.3k, 10W, ceramic
R7	2.2k, 2W, MO
R8, R9	4.7k, 10W, ceramic
R10, R11	330k, 2W, MO
R12, R13	47Ω, 25W, wirewound,
R14-R16	no inductive
R17	33Ω, 25W, wirewound,
	no inductive
R4, R18, R19, R26, R27	470Ω, 2W, MO
R20, R21	1Ω, 2W, MO
R28	560k, 2W, MO
R29	220k, 2W, MO
POTENTIOMETERS	
P1	47k, pot ALPS, log
P2	2.2k, 3W, pot, linear
P3	22Ω, 4W, linear
CAPACITORS	
C1, C3, C4, C5	1μF/630V MKS
C2	220μF/63V
C5-C10	100μF/350V electrolytic

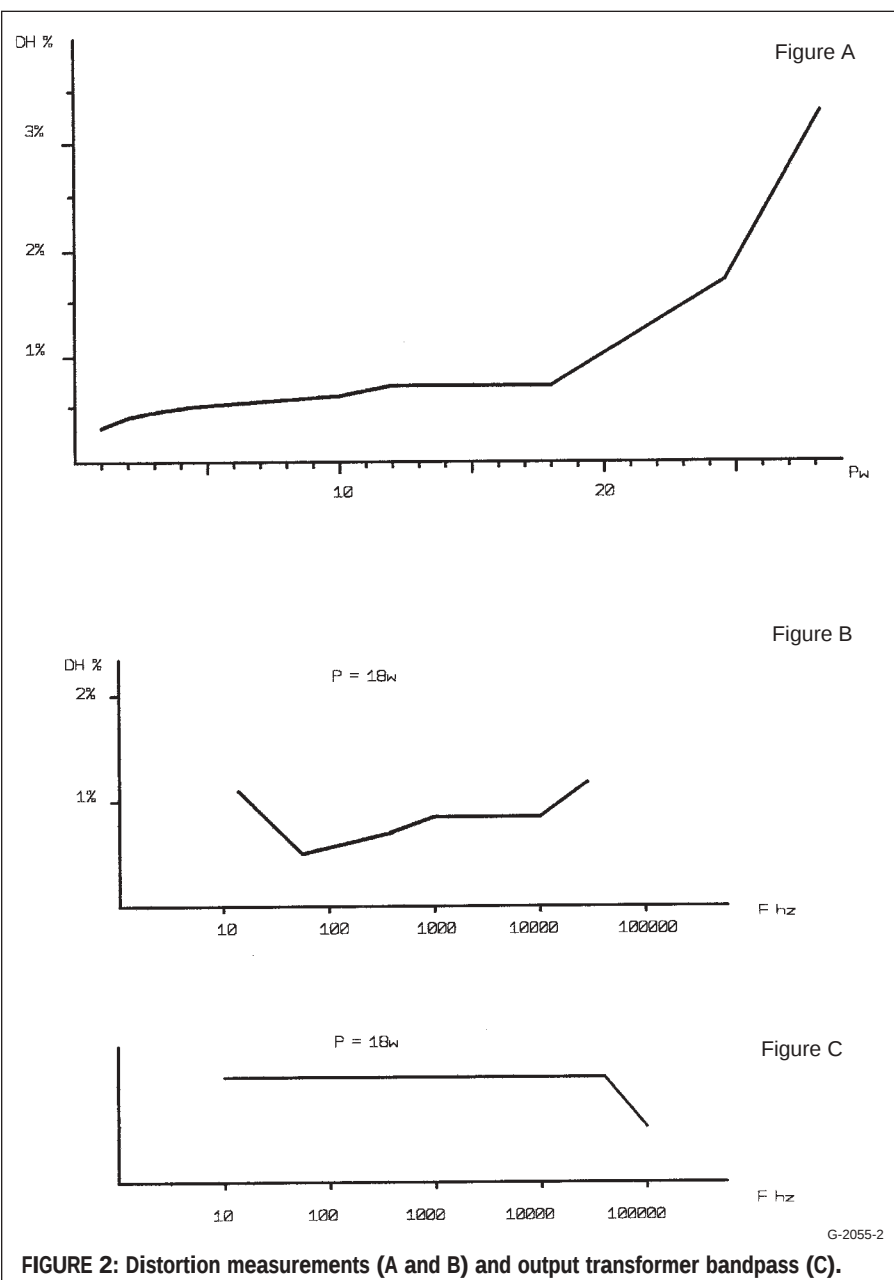


FIGURE 2: Distortion measurements (A and B) and output transformer bandpass (C).

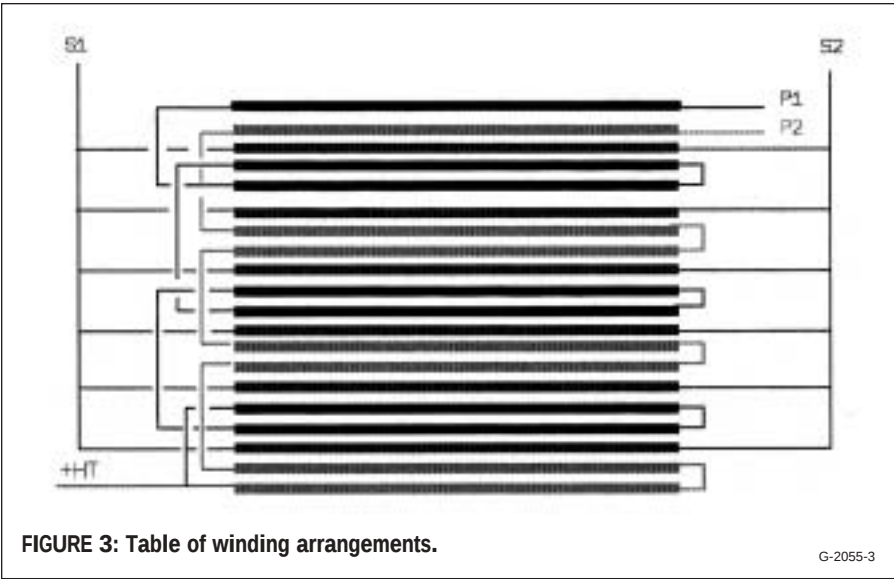


FIGURE 3: Table of winding arrangements.

tion rate goes from 10Hz to 40kHz, always below 1%, up to 20W (Fig. 2).

Finally, this transformer is easily reproduced at a competitive price. It is mounted on an EI magnetic circuit (105 × 126) of steel silicon sheets with oriented crystals. The theoretical primary inductance value of the transformer is 4.5H with a bandpass attenuation of 3dB to 10Hz with 1047 primary turns.

Due to winding constraints, 1092 primary turns are necessary to improve results of the lower frequencies. This was verified by electronic measuring.

The primary coil (Fig. 3) is sectioned into six parts and interlaced with six identical parallelized secondary coils. The leakage inductance is equally low and allows you to easily obtain high frequencies up to 40kHz. The transformation ratio automatically maintains the output power at 25W maximum in order to keep the total distortion rate below 1%.

POWER SUPPLY

The power-supply transformer was specially built by Bobinelec. It is composed of several primary coils, which allow us to accurately adjust the filament voltage on the 6C33C-B to 6.3V.

SOURCES

A.B.L.

Z.A. Lou Quiquihhan
30260 GAILHAIN
France
33-4-66-80-14-34
FAX 33-4-66-80-14-34
output transformer

ANTIQUE ELECTRONIC SUPPLY

6221 S. Maple Ave.
Tempe, AZ 85283
480-820-5411
FAX 480-820-4643
info@tubesandmore.com
tubesandmore.com
aluminum frame

BOBINELEC

9 rue A.Kastler "Ila Vigie" BP 20
67451 Otswald Cedex France
FAX (as dialed from the US) 33-3-88-67-32-27
Also: ACEA 6 rue François Verdier
31830 Plaisance du Touch France
FAX 33-5-61-86-61-89
power transformer

CHELMER VALVE COMPANY, LTD

The Stables Baddow Park
Great Baddow
Chelmsford Essex CM2 7SY
44-1245-241300
FAX 22-1245-241309
Sales@chelmervalue.com
www.chelmervalue.com
6C33C-B and sockets

AUDIO TRANSFORMERS

AMERICA'S PREMIER COIL WINDER

Engineering • Rewinding • Prototypes

McINTOSH - MARANTZ - HARMAN-KARDON
WESTERN ELECTRIC - TRIAD - ACROSOUND
FISHER - CHICAGO - STANCOR - DYNACO
LANGEVIN - PEERLESS - FENDER - MARSHALL
ELECTROSTATIC SPEAKER TRANSFORMERS

Williamson Amplifier Transformer Specialist
WE DESIGN AND BUILD TRANSFORMERS
FOR ANY POWER AMPLIFIER TUBE

PHONE: [414] 774-6625 FAX: [414] 774-4425

AUDIO TRANSFORMERS

185 NORTH 85th STREET

WAUWATOSA, WI 53226-4601

E-mail: AUTRAN@AOL.com

NO CATALOG


CUSTOM WORK

FREE SAMPLE

IF YOU BUY,
SELL, OR COLLECT

OLD RADIOS, YOU NEED...

ANTIQUE RADIO CLASSIFIED

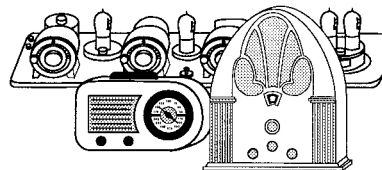

Antique Radio's Largest Monthly Magazine
100 Page Issues!

Classifieds - Ads for Parts & Services - Articles
Auction Prices - Meet & Flea Market Info. Also: Early TV, Art Deco,
Audio, Ham Equip., Books, Telegraph, 40's & 50's Radios & More...
Free 20-word ad each month for subscribers.

Subscriptions: \$19.95 for 6-month trial.
\$39.49 for 1 year (\$57.95 for 1st Class Mail).

Call or write for foreign rates.

Collector's Price Guide books by Bunis:

Antique Radios, 4th Ed. 8500 prices, 400 color photos\$18.95

Transistor Radios, 2nd Ed. 2900 prices, 375 color photos\$16.95

Payment required with order. Add \$3.00 per book order for shipping. In Mass. add 5% tax.



A.R.C., P.O. Box 802-A16, Carlisle, MA 01741

Phone: (978) 371-0512 — Fax: (978) 371-7129

Web: www.antiqueradio.com — E-mail: ARC@antiqueradio.com



The voltages are given only as an indication and can vary depending on the tubes used. At the start-up both switches are off. Turn on S1 for five minutes to pre-heat the tubes, then turn on S2 for the high voltage. The temperature of the tubes is stabilized after 20 minutes.

CONSTRUCTION

The amplifier is built on a P-H129 aluminum frame supplied by Antique Electronic Supply. The 6C33C-B supports are slightly elevated to help make thermal dissipation easier. The cathode resistors of the power stage are mounted on an aluminum radiator (Fig. 4).

As usual, the wiring should be done with care so as to avoid hum, oscillation, and other unpleasant problems. Electrical efficiency should prevail over esthetic efficiency, especially with this powerful amplifier. The filaments of the 6C33C-B use 6.6A each, so wire them away from the audio-frequency generation (BF signal) wires! Don't forget to twist these wires to lower the

magnetic field they can produce. As a usual precaution, use one ground per stage. These grounds should be wired together and connected to the frame at one point.

LISTENING RESULTS

With more power this unit represents one step further in quality. With better sound definition it achieves a softer, warmer, more melodious sound. The



PHOTO 2: Rear view.

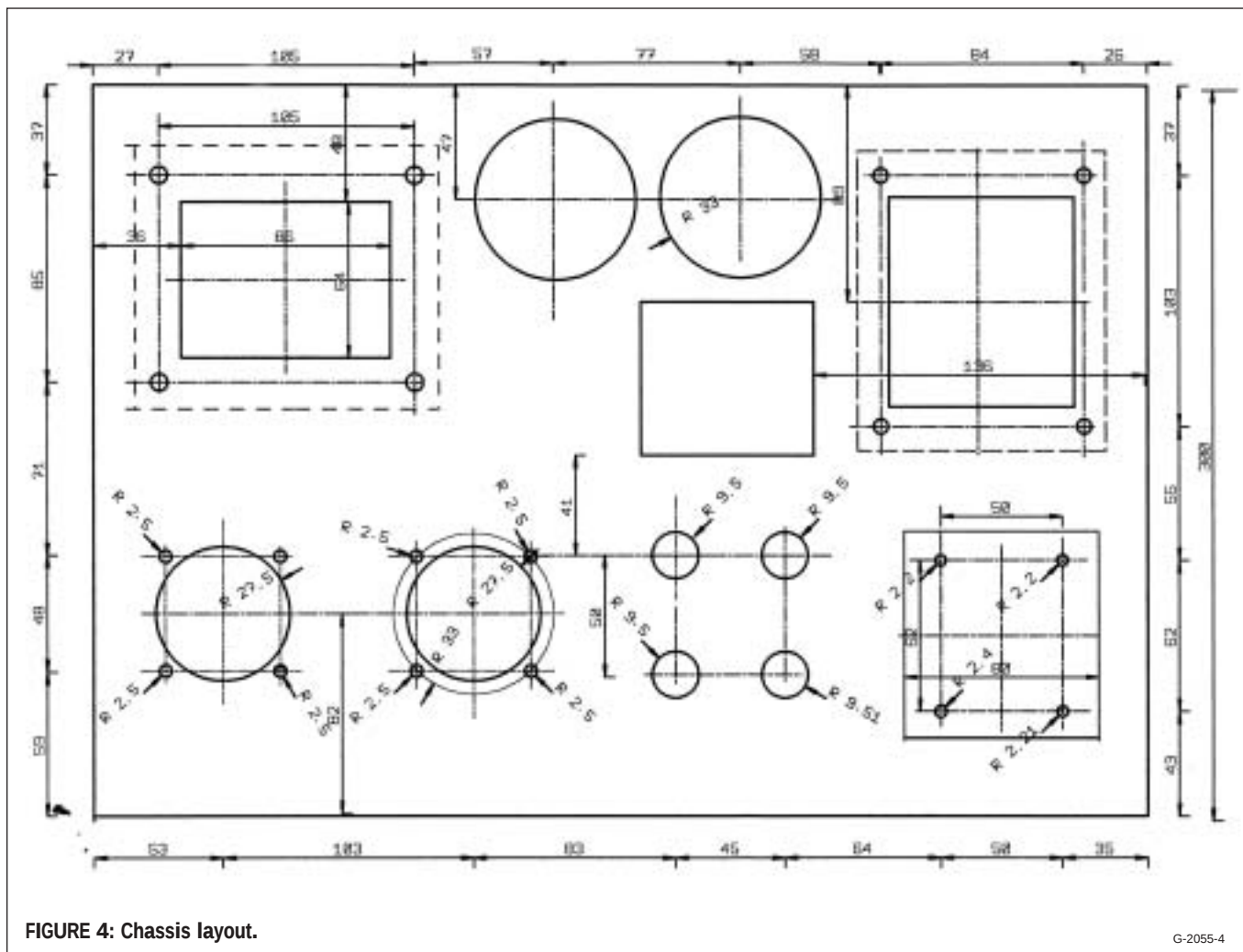


FIGURE 4: Chassis layout.

G-2055-4

transients are less powerful than with a split-load inverter; the bass tones are light and natural; the mediums are very definite; the high tones are more precise. Together this produces a very fine example of listening pleasure. I personally conducted my listening tests with

CDs from the *Revue de Son* magazine of various styles of music. I found the results to be excellent. ♦

Translated from French by Gretchen Marie Hromyak.

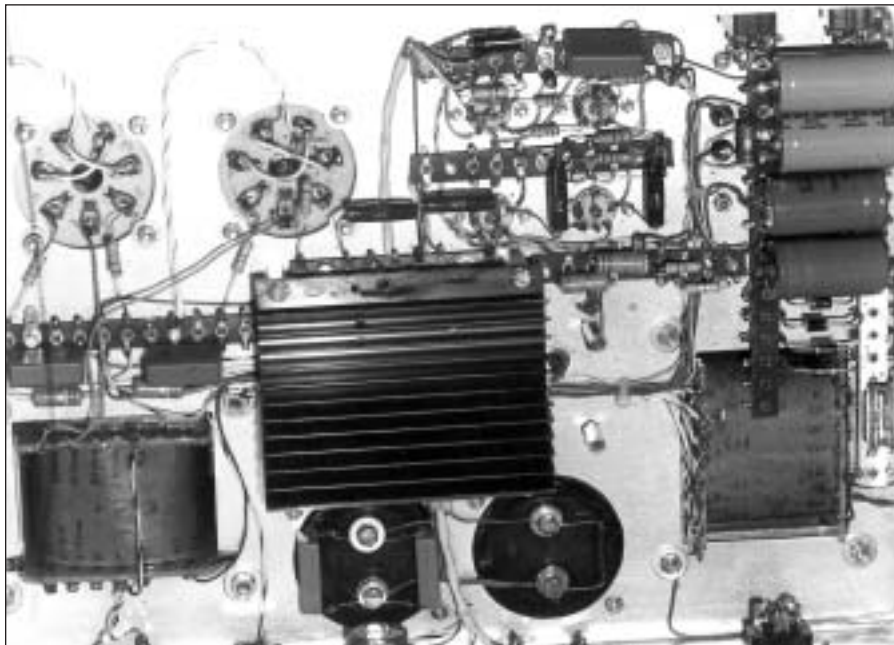


PHOTO 3: Bottom and internal view of amp.

Sound Product. Pure Sound.



Improve your audio experience with non-inductive

metal foil resistors by Alpha Electronics.

- Metal foil technology
- Available in *any* value
- Quality sound **for less**

Pure and simple...

Contact Sara at (763) 258-8550
Email: audiofoil@alpha-amer.com



Alpha Electronics Corp.
of America

Minneapolis, Minnesota
www.alpha-amer.com

COMPONENTS:


SOLEN HEPTA-LITZ AND STANDARD INDUCTORS AND CAPACITORS - THE CHOICE OF MANY HIGH-END SPEAKER MANUFACTURERS.

HARDWARE:

POWER RESISTORS, L-PADS, CABLE, ABSORBING AND DAMPING MATERIALS, GOLD SPEAKER TERMINALS, GOLD BANANA PLUGS AND BINDING POSTS, GRILL FASTENERS, PORT TUBES AND TRIM RINGS, PAN HEAD SCREWS, SPIKES AND TEE NUTS WITH ALLEN HEAD BOLTS AND PLENTY MORE...



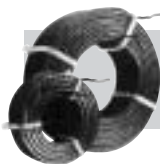Solen crossover components - used by the most discriminating loudspeaker manufacturers.



SOLEN HEPTA-LITZ INDUCTORS

Air Cored Inductors, Litz-Wire Perfect Lay Hexagonal Winding
Values from .10 mH to 30 mH
Wire Size from 1.3 mm (16AWG) to 2.6 mm (10 AWG) 7 Strands

SOLEN STANDARD INDUCTORS

Air Cored Inductors, Solid Wire Perfect Lay Hexagonal Winding
Values from .10 mH to 30mH
Wire Size from 0.8 mm (20AWG) to 2.6 mm (10 AWG)



SOLEN FAST CAPACITORS

Fast Capacitors, Metalized Polypropylene
Values from 0.10 μ F to 330 μ F
Voltage Rating: 630, 400, 250 VDC



CROSSOVER AND SPEAKER PARTS

Metalized Polyester Capacitors, 1.0 μ F to 47 μ F, 160 VDC, Non Polar Electrolytic Capacitor, 22 μ F to 330 μ F, 100 VDC, Power Resistors 10 W, 1.0 Ω to 82 Ω , 8 Ω L-Pads plus all the hardware and supplies to complete any speaker project.

ORDER THE FREE SOLEN CATALOG AND CD.
FORWARD YOUR REQUEST BY PHONE, FAX,
MAIL OR EMAIL - OR FILL IN THE ONLINE
REQUEST FORM AT SOLEN.CA.



SOLEN INC.

4470 Avenue Thibault
St-Hubert, QC J3Y 7T9
Canada

Tel: 450.656.2759

Fax: 450.443.4949

Email: solen@solen.ca

WEB: <http://www.solen.ca>

* Thagard's Power Supply Revisited

Norm Thagard's two-part series that appeared in our inaugural *aX* generated much reader response and appreciation of his sane, well-designed power supply. Here's a sampling. **By Tom Perazella**

Kudos on your article, "A Phono Pre-Preamplifier for the CD Era," in *audioXpress*, January and February 2001. I especially enjoyed the emphasis you placed on good, rather than expensive, power-supply design. The audio hobby is plagued with the notion that in order for something to be good, it must be prohibitively expensive. I sometimes think that there are people out there who try to cover up their lack of understanding by throwing money at a problem. That usually results in expensive failures rather than just failures.

I'd like to point out a few observations I've made over the years in designing my power supplies. When dealing with silicon rectifiers, or SCRs, Triacs, and other related devices, the surge current of the device is usually specified as the average current for a complete half cycle of conduction when the device is already carrying the maximum-rated current. In a capacitive power supply, as you mentioned, the current flows for only a short period of the cycle. In addition, the average current that each rectifier carries in a supply such as yours is far below its rating. Therefore, the peak current that the device can handle in this case should be in excess of the rated surge current.

CURRENT PROTECTION

Typical I^2T ratings for power dissipation also do not apply to rectifiers until the current is so high that the device transitions from a log response to a linear response. In a typical resistive device, if you double the current for half the time, you don't get the same dissipation, but twice the dissipation. That

is because as the current doubles, the voltage drop across the device doubles, leading to four times the power loss but for half the time. Since the drop across the diode junction responds in a log fashion to the current, the voltage drop does not double, and the dissipation is not four times during the shorter time period.

At a company where I formerly worked, some of their products were commercial studio electronic flash equipment. That equipment used rectifiers to isolate the large capacitor storage banks from each other. This was done to protect the switches that selected the number of capacitors to connect to the discharge path from being destroyed if banks were connected to each other when not at the same voltage. When working with large banks of ca-

pacitors, it does not take much voltage differential to produce sufficient currents to weld the sturdiest switch contacts together as the switch is actuated.

To protect those contacts, rectifiers rated at 6A were used between the capacitors and the selector switches. The main discharge current of the flash—well into the high hundreds of amps for a few milliseconds—were easily handled by these rectifiers with no problems. This does not mean that rectifiers cannot be destroyed by high currents. Rather, unless you are already at the maximum operating current of the rectifier, the surge ratings are conservative. In all cases, this assumes that the junction temperature is not exceeded in normal conditions by excessively high ambient temperatures or inadequate heatsinking.

Your advice to move the transformer away from the rest of the circuitry is dead on. Using a toroidal transformer can help minimize radiated energy, but for whatever remains, nothing beats distance. As the frequency of the radiat-

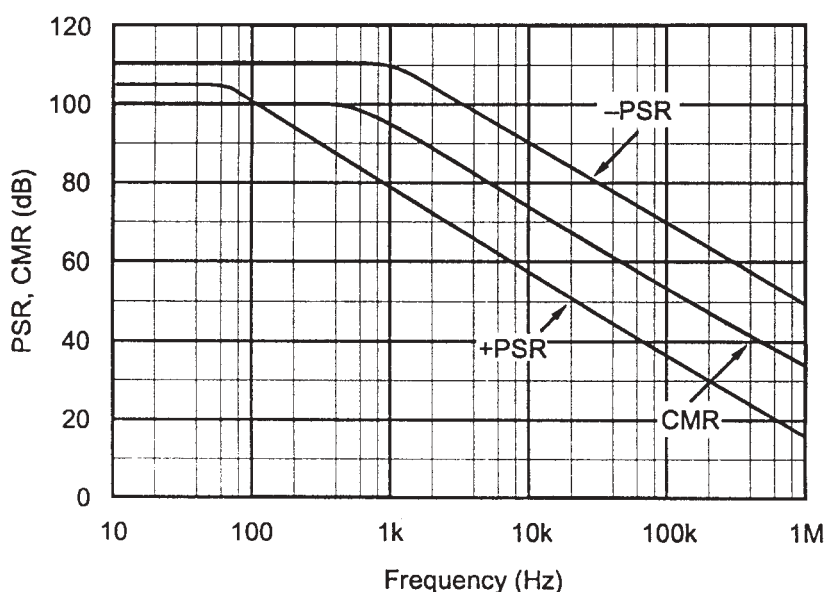


FIGURE 1: Power supply and common-mode rejection versus frequency.

A-1962-1

ed magnetic field goes down, it becomes progressively more difficult to use materials to attenuate the field. Look at the VLF communications in use by the military to contact submarines under the ocean.

PSRR

Evaluating the effect of ripple in the power supply is just an extension of the general power-supply rejection ratio (PSRR) of the circuit. PSRR has an important impact on the design of the power supply. I don't know whether you have measured that with your circuit, but I would bet it is similar to what you would find with many of today's high-quality integrated circuit op amps.

One of the critical factors to address when evaluating PSRR is the relationship of ratio to frequency. As the frequency of the power-supply fluctuations—be they ripple or induced noise—goes up, the rejection of that fluctuation by the circuit goes down. If you look at *Fig. 1* showing the PSRR curve of the OPA134 op amp—a typical example of a very good, modern design for audio—you will notice that the rejection ratio is above 100dB at DC for both sides of the supply. The negative side tops out at 110dB and the positive side reaches “only” 105dB. However, the positive side starts losing its ability to reject power-supply fluctuations at 80Hz and the negative at 1kHz.

It is very clear that reducing lower-frequency components of the fluctuation is not as important as reducing the higher-frequency components. The circuit is less able to reject the higher-frequency components, and it is therefore more important to attenuate those before they reach the circuit.

For example, the circuit can reduce the effect of a supply fluctuation by 105dB at 80Hz, but only 60dB at 10kHz. For the same perturbation of the output signal, the power supply must have a 10kHz fluctuation that is 45dB below any at the 80Hz level. The loss of rejection capability appears to be around 6dB per octave.

ELIMINATING NOISE

Your power-supply circuit using a resistor between the two capacitor sections seems to be a very good choice to roll off any high-frequency components that

may get through the transformer. Looking at even the first section of the filter, C101 or C102, you would think that those capacitors would eliminate any higher frequency noise that got through the transformer. In fact, that is probably true to a large degree.

However, depending on the capaci-

tors used, the series inductance of the cap could block some of the HF noise from reaching ground, passing it on. To compound that problem, most IC regulators also have a decreasing ability to reject ripple as the frequency increases. Looking at *Fig. 2*—the ripple rejection curve of the 78XX series of regulators—

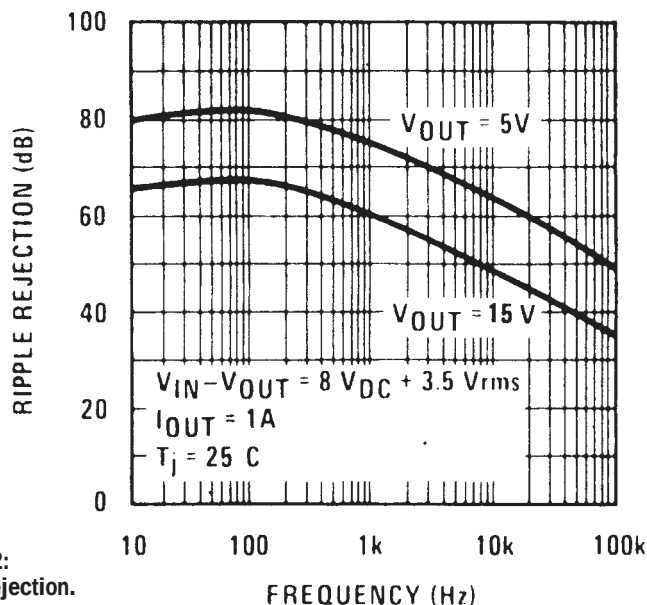


FIGURE 2: Ripple rejection.

A-1962-2

DH LABS

SILVER SONIC™
HIGH PERFORMANCE AUDIO CABLES

INTRODUCING The Air Matrix Interconnect and Q-10 Speaker Cable

www.silversonic.com



www.silversonic.com

DH Labs, Inc.

612 N. Orange Ave #A-2
(561) 745-6406

Jupiter, FL 33458

Toroids for Audio



Tube Output

Toroidal transformers for tube output applications. Plus related products.

Standard Series (push-pull)

Single-ended

Specialist Range

Special Designs

Power Transformers

Chokes

Chassis for Tube Amplifiers

PCB for 70W & 100W Amps

Book by Vanderveen

Electrostatic

Step-up toroidal transformers for Electrostatic loudspeaker applications.

Solid State Power

Low noise, low inrush
500 to 2000VA fully
encapsulated power
transformers.

Standard Power

A broad range of high
quality, approved,
toroidal transformers.
Designed for general
purpose applications.
From 15 to 1500VA.



PLITRON
MANUFACTURING INC

8-601 Magnetic Drive
Toronto, ON M3J 3J2
Canada

416-667-9914

FAX 667-8928

1-800-PLITRON

(1-800-754-8766)

www.plitron.com

you can see that the rejection peaks at about 68dB at around 100Hz, which is ideal for 60Hz ripple. Granted, capacitor-filtered supplies have higher frequency components to the ripple, but it's still a good start.

Your inclusion of the resistor between the two capacitors provides, in addition to ripple suppression at line frequencies, additional rolloff of higher frequency components that would not be effectively rejected by either the regulator or circuit. As far as the ripple is concerned in any capacitor input power supply, raising the secondary voltage and increasing the resistance into the first section will result in a more sinusoidal current flow, all things being equal. This resistance could be in the form of higher transformer secondary resistance or an external resistor. In fact, if you were to carry the concept to an extreme, an extremely high secondary voltage with a sufficiently high series resistor would effectively eliminate the average DC voltage that results on the capacitors from affecting the current waveshape. The charging current would closely approximate what you would see if the load were resistive.

There are obvious practical limitations to this concept, because if the load current were to decrease, the voltage division of the fixed resistor and effective circuit resistance would change, resulting in runaway voltages. In addition, efficiency decreases as the effective impedance of the feed increases in relationship to the circuit, although at the power consumption levels of supplies like this it is not a significant problem.

TWO PROBLEMS

There are two main problems that I have seen in supposedly high-end sup-

ply designs that fly in the face of logic. One is the concept that keeping the secondary voltage the same on a supply transformer feeding a low power consumption device, while vastly increasing its current capability, will greatly enhance the resultant sound quality. In fact, if the original transformer had sufficient current capability to keep the regulators from dropping out of regulation regardless of load and line fluctuations, there is no benefit to going to a higher secondary current capability at the same voltage level. Rather, you are better off having a higher secondary voltage at the required maximum current level expected. Then, you have a greater range of input voltages over which the supply can keep the regulators operating properly.

In addition, dissipation limits on the regulators can be a problem if the voltage and current capabilities are kept very stiff as the circuit current demands increase. When a higher secondary voltage transformer that has a higher secondary resistance is used, as the circuit demands increase, the input voltage to the regulator drops, limiting dissipation in the regulator, but shifting it to the transformer. This philosophy is obviously limited to relatively low power demands. The inefficiencies involved in this philosophy would be a problem in a multi-kilowatt amplifier application.

The second problem is the trend to try to speed up the response of the regulation circuit by using high-speed regulators with little or no output capacitance. On the surface this may look good. You might think that the lower capacitance plus fast regulators would reduce the time it took for the regulators to react to a change in output volt-

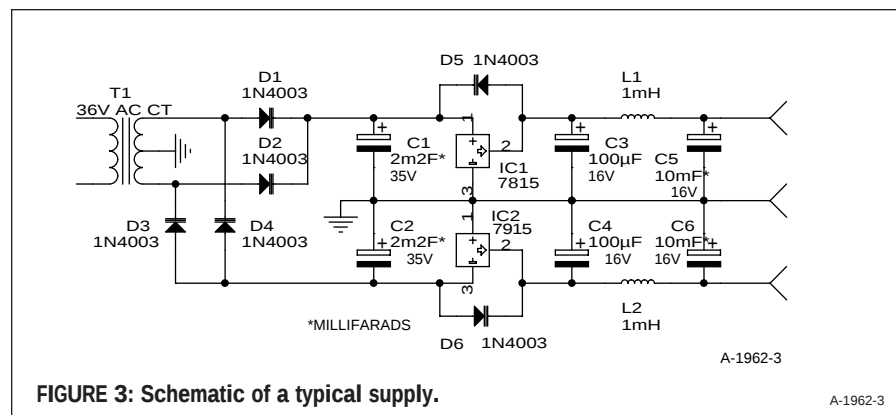


FIGURE 3: Schematic of a typical supply.

A-1962-3

age, resulting in smaller changes. However, speed does not necessarily relate to precision. In addition, even if the faster response resulted in smaller changes at the output of the regulation circuit, it does not necessarily lead to smaller changes in the output of the following circuitry.

Looking again at OPA134, assume the classical supply resulted in a fluctuation of 10mV at 120Hz. Due to the drop in PSRR with increasing frequency, if the higher speed regulators produced a voltage correction with a time constant relating to a frequency of 1kHz, the change in voltage would need to be less than 1mV to produce the same change in the output circuitry. In addition, at 1kHz, the resultant change would be far more objectionable. If the time constant equated to a frequency of 10kHz, to achieve the same level in output circuit fluctuation, the variation allowed by the regulator would need to be less than 0.1mV. With some devices, the PSRR can even go negative at very high frequencies; that is, the device can actually amplify the power-supply fluctuations.

SOLUTIONS

To solve some of these problems in the supplies I have built, I use an approach similar to yours, differing in only a few points. *Figure 3* is a schematic of a typical supply. First, I do not mount the regulators close to the output circuitry. Rather, I feed the rectified and filtered DC directly into the three terminal regulators. Small caps at the output of the regulators maintain stability.

Also note the protection diodes across both regulators, which do not take kindly to reverse voltages. In most cases, the load on the output of the regulators will assure that the output voltages always drop before the input voltages. However, if one of the input rectifiers or caps should fail, the regulator could also be destroyed. Ditto for an external voltage source inadvertently getting into the output circuit.

The other main difference is that I use two inductors and two additional capacitors before feeding the voltages to the rest of the circuitry. The combination of the inductors and capacitors provide a passive 12dB/octave rolloff of any high frequencies that manage to

sneak through the rest of the circuit. In addition, these inductors have a DC resistance of only 0.55Ω, causing a very negligible regulated voltage drop.

The very high output capacitance combined with the typical load currents involved lead to a very long time constant, and small changes that are easily compensated for by the regulators, as at those lower frequencies; the chokes are essentially a short circuit. Any fluctuations that may occur are definitely in the flat, high PSRR range of the output circuits. The output changes are very minimal and at frequencies totally below audibility. For the inductors, I use J. W. Miller part number 5258, available from Digi-Key for a unit cost of \$3.27.

Of course, to complete the process, I use local bypassing of the op amps directly at the power input leads. Typically I use 3.3μF tantalum caps in parallel with 100nF monolithic ceramic caps. It's also interesting to see how many audio-philosophes shun ceramic caps, when, in fact, they outperform all the so-called super foil caps in a bypass application. ♦

PASS DIY

Printed Circuit Boards

Key Components

Plans

Zen Variations

Pearl Phono

and more...

PO Box 12878
Reno, NV 89510

www.passdiy.com

Supplier
Of High
Quality
Speaker
Kits &
Components
For The Audio
Enthusiast

SELENIUM
LOUDSPEAKERS

vifa scan-speak

Cabasse

GOLDWOOD

B&C SPEAKERS

ACCUTON

VERSATRONICS INC.

FOCAL

AEON

Components & Accessories

RAVEN

LEAP

Crossover Design

Pioneer

115 S. Victory Blvd.
Burbank, CA 91502
Vox 818-846-9921
Fax 818-846-1009
www.speakercity.com

**SPEAKER
CITY U.S.A.**

McCawley

Orders Only! 800-595-9924
Mon-Sat 10am-6pm



High g_m Smart Power Tubes, Part 2

Our three-part look at high-transconductance vacuum tubes with low power handling capabilities continues.

By Stefano Perugini

The results summarized in Figs. 4, 6, and 7 of Part 1 reveal that the more interesting Western tubes (with high values in g_m and σ) are also rare and expensive, as any DIYer can easily verify. Fortunately the opening of ex-Soviet markets allows us to discover noteworthy vacuum devices. At the moment, these alternatives are still cheap and easily available and, with their excellent electrical characteristics, represent a good opportunity for the advanced audio experimenter.

This second part looks at three of these Russian high g_m vacuum tubes able to cover most low power hi-fi needs.

THE 6C45-IIIE

This vacuum tube (Photo 2) with its predecessor, the 6C15-IIIE, first appeared, in all probability, in the late '60s/early '70s. This valve is a perfect replacement for tubes such as 3A167M/CV5112, WE437A, and EC8020. Since the introduction in my website³, in 1997, code named by VT- Ω to avoid economic speculations (In Europe, for example, a 3A167M matched pair can approach \$250), this tube has gained an excellent reputation in the advanced DIY circles, and for very good reasons, because the application fields are wide and stimulating:

- **RF:** Wideband linear amplifiers from DC to 80MHz
- **High End Audio:** Monotube single-ended low power amplifiers, driver stage for 211/845 SE amplifiers in two-stage configurations, headphone amplifiers, line preamplifiers transformer loaded, small OTLs, A2 class driving, impedance matching
- **Pro Audio:** Vacuum tube amplifiers in low-impedance OTL balanced lines, high-current vacuum tube drivers


Description

The 6C45IIIE is a 9-pin miniature triode intended primarily for use in the high-frequency voltage amplification stage of wideband amplifiers.

Weight: 20g

Pin functions (Fig. 8)

1—cathode

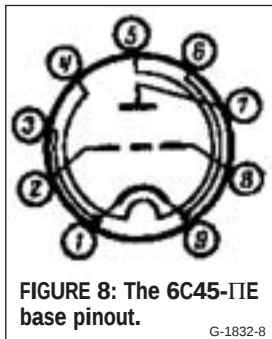

G-1832-8

PHOTO 2:
The 6C45-IIIE
triode.



- 2—grid
- 3—cathode
- 4—filament
- 5—filament
- 6—cathode
- 7—anode
- 8—grid
- 9—cathode

CHARACTERISTICS

(Figs. 9 and 10)

Heater voltage 6.3V
Plate voltage 150V
Cathode resistor for self-bias 30 Ω


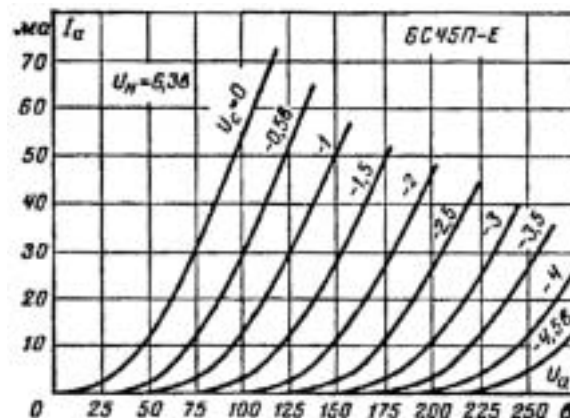


FIGURE 9: The 6C45-IIIE plate characteristics.

G-1832-9

FIGURE 10:
The 6C45-IIIE
transfer char-
acteristics.

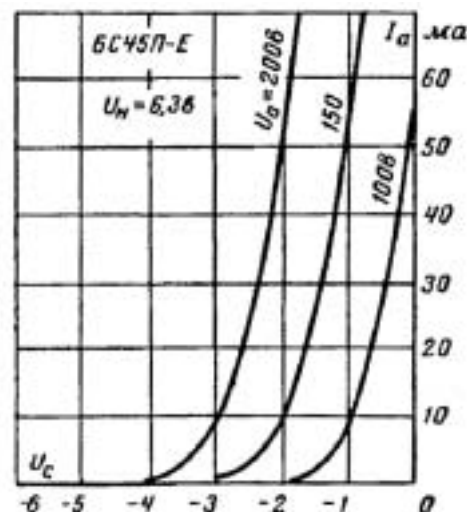


G-1832-10

General Characteristics

	Minimum	Nominal	Maximum
Heater current, mA	410	440	470
Plate current, mA	28	40	52

FIGURE 11:
The 6C45-ITE
dimensions.

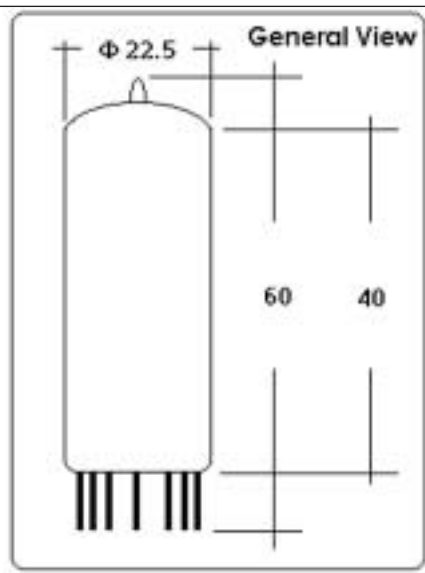

G-1832-11

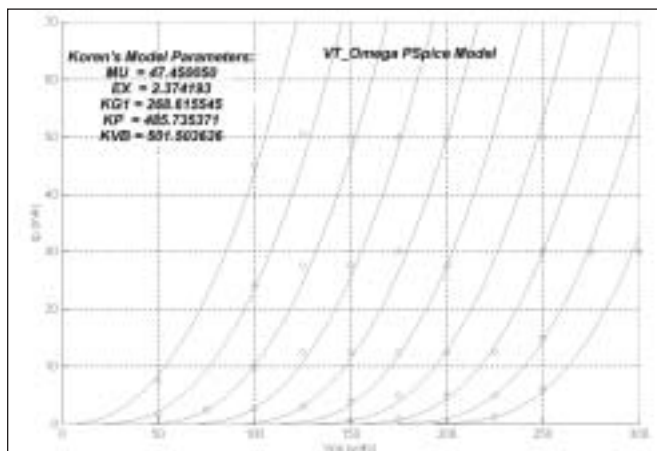


FIGURE 12: The plot of 6C45-ITE PSpice model.

G-1832-12

Slew rate, mA/V	34	45	56
Amplification factor	36	52	68
Input impedance			
at F = 60MHz, kΩ	—	3.5	—
Vibro-noise, mV (RMS)*	—	—	100
Lifetime guaranteed, hours	3000	—	—
Direct interelectrode capacitances:			
Input, pF	9.5	11.5	13.5
Output, pF	1.8	1.9	2.2
Heater-cathode, pF	—	6.8	9.5
Heater-grid	—	—	0.13

Center Design Points

Maximum heater voltage	6.6V
Minimum heater voltage	6.0V
Maximum plate voltage	150V
Maximum cathode-heater voltage**	100V
Maximum cathode current	52mA
Maximum plate dissipation	7.8W
Maximum grid resistance	150kΩ
Bulb temperature (common environment)	210C
Bulb temperature (T air = 85C)	230C

*measured with plate resistor = 0.5kΩ

**potential of heater is negative relative to cathode

Mechanical Data

Continuous vibration 500–600Hz with acceleration	Up to 6g
Single beats with acceleration	Up to 500g
Multiple beats with acceleration	Up to 75g
Temperature range	–60C to +85C
Humidity (with T = 40C)	Up to 98%

PSpice Model (Fig. 12)

.subckt 6C45-PE 1 2 3 ; plate grid cathode
+ params: mu=47.4501 ex=2.374193 kg1=268.615545
+kp=485.735371



DYNASONIC
οι ηχοποιητές

INTRODUCING THE NEXT GENERATION OF PLANAR TRANSDUCERS

PL-160 the first planar driver with esoteric-Binary Interlaced Coil- **BIC** diaphragm field exchangeable. A distinct performance driver with electroacoustic virtues, satisfying critical listeners and functionality motivating ambitious designers. All in a single, state of the art device.

FEATURES - PERFORMANCE - SPECIFICATIONS

- Ultrafast transient response, for stunning transparency
- Linear Phase response, for time coherent reproduction results in accurate imaging and sonic clarity
- True line source image behavior
- Controlled dispersion in horizontal and vertical plane
- Frequency response 1.6–40KHz
- Sensitivity 2.83vrms/1M 97db SPL
- Extremely light, ultrathin, Hi temperature, interchangeable diaphragms in Ohmic Values: 2x9 - 2x5,3 - 2x3,4"
- Constant resistive impedance throughout operating range for ideal amplifier load and easy crossover design
- Massive, Neodymium, High energy magnet system
- Magnetically shielded system
- Baffle mounting without screws
- Rear support for free standing upgrading applications
- Dimensions: W x H x Dmm: 84 x 164 x 100 Weight 1,5kg

THE NEW **BIC** DESIGN IDEAS THAT HELP YOU BUILT BETTER SPEAKERS


Double coil proprietary diaphragm configuration allows series connection for max transducer sensitivity or parallel connection for max power handling.

The two symmetrical interlaced coils, break the rules of acoustic reproduction in many fronts such as:

- Crossover at two different frequencies
- Feedback optimizer circuitry
- Magnetic damping circuitry
- DDL (Direct Digital Loudspeaker) circuitry
- Possible other inventive applications

Unit price: \$ 320 (includes delivery to your address)

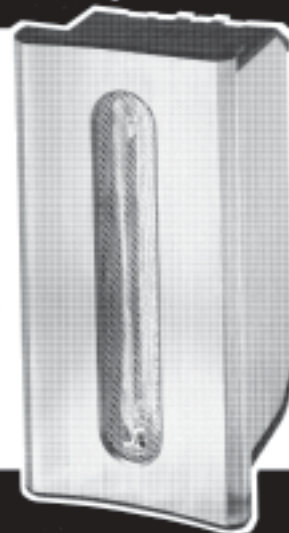*PL-160 is sold with 2 x 9 Ohms diaphragm.



For orders visit our web page www.dynasonic.gr E-mail: info@dynasonic.gr Or contact us directly at:
DYNASONIC LTD 59, Itrilis Septemvriou str., Athens 104 33, Greece, tel.: +30-1-88 30 311, fax: +30-1-82 29 483

```

+kvb=501.503636
+rgi=300
+ ccg=2.4p cgp=4p ccp=.7p
e1 7 0 value=
+{v(1,3)/kp*log(1+exp(kp*(1/mu+v(2,3)/sqrt(kvb+
+v(1,3)*v(1,3))))))}
re1 7 0 1g
g1 1 3 value= {(pwr(v(7),ex)+pws(v(7),ex))/kg1}
rcp 1 3 1g
c1 2 3 {ccg}
c2 1 2 {cgp}
c3 1 3 {ccp}
r1 2 5 {rgi}
d3 5 3 dx
.model dx d(is=1n rs=1
+cjo=10pf tt=1n)
.ends

```

THE 6H30

This double triode (*Photo 3*), although designed for high-current pulse mode operation, can be seen as an improved version of the E182CC-SQ vacuum tube and therefore perfect as a line preamplifier and driver for power tubes. The official presentation appeared as an advertisement in *Glass Audio* (3/99, 5/99, and 6/99) from Balanced Audio Technologies. Target applications include:

- **High End Audio:** Line preamplifiers (SRPPs, mu-followers balanced stages), headphone amps, Class AB2 low power OTLs, impedance matching
- **Pro Audio:** Low impedance, low gain OTL balanced lines, high current cathode followers

Description

Double triode for work in pulse modes in various radio devices

Shape—miniature glass bulb
Mass—20g Size—H = 72.5, D = 22.5
Pin functions (*Fig. 13*)

- 1—plate 1
- 2—grid 1
- 3—cathode 1
- 4—heater
- 5—heater
- 6—plate 2
- 7—grid 2
- 8—cathode 2
- 9—shield

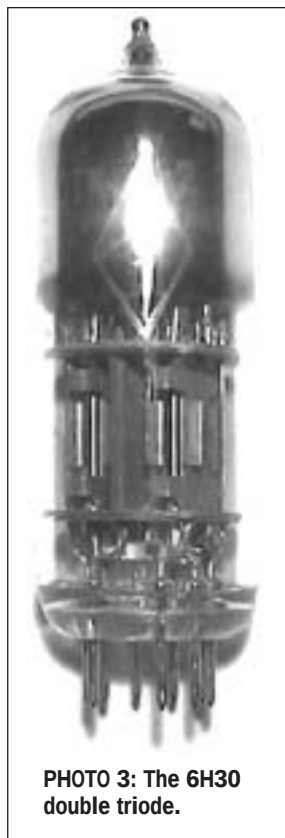


PHOTO 3: The 6H30 double triode.

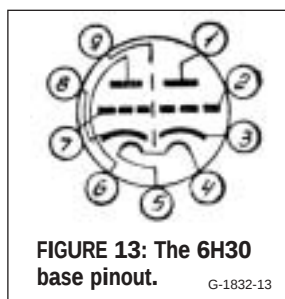


FIGURE 13: The 6H30 base pinout.

G-1832-13

General Characteristics

(*Figs. 14 and 15*)

(with heater voltage = 6.3V; plate voltage = 80V; self-bias resistor = 56Ω)

Heater current	825(+75-100)mA
Plate current for each triode	40(+10-10)mA
Pulse plate current for each triode	2-3A
Plate current with $U_g = -12V$	<30μA
Reverse grid current	<1μA
Slew rate	18(+5-5)mA/V
Amplification factor for each triode	15(+3-3)
Vibro-noise voltage with $R_p = 0.5k\Omega$	25-50mV
Direct interelectrode capacitances:	
Input(C_{gc})	6.3(+0.9-0.9)pF
Output(C_{cp})	2.4(+0.5-0.5)pF
Transfer(C_{gp})	6.0-7.1pF
Between anodes	<0.2pF
Heater-cathode	8.8(+2.7-1.8)pF
Lifetime	>10000hrs
Term of workability-pulse plate current	>1.7A

Center Design Points

Heater voltage	6.0-6.6V
Maximum plate voltage	250V
Maximum plate voltage for closed tube	1050V
Maximum grid voltage in pulse mode $t \leq 100\mu s$	-50V
Maximum heater-cathode voltage	400V
Maximum pulse current for each triode	6A
Maximum cathode current for each triode	100mA
Maximum plate dissipation for each triode	4W
Maximum grid dissipation for each triode	0.4W
Maximum grid resistance	300kΩ
Maximum bulb temperature	250°C

Mechanical Data

Continuous vibration 5-2000Hz with acceleration	20g
Multiple beats with acceleration	150g

PSpice Model (*Figs. 16-18*)

SUBCKT KTRIODE A G K
+ PARAMS: MU=37.58299 EX=1.132166 KG1=428.9745
KP=402.1368 KVB=321.0256
+ LG=0.2U VBIG=-0.2 EG=1.0389 KG=0.000769
KRG=3.685584 KVG=0.090943

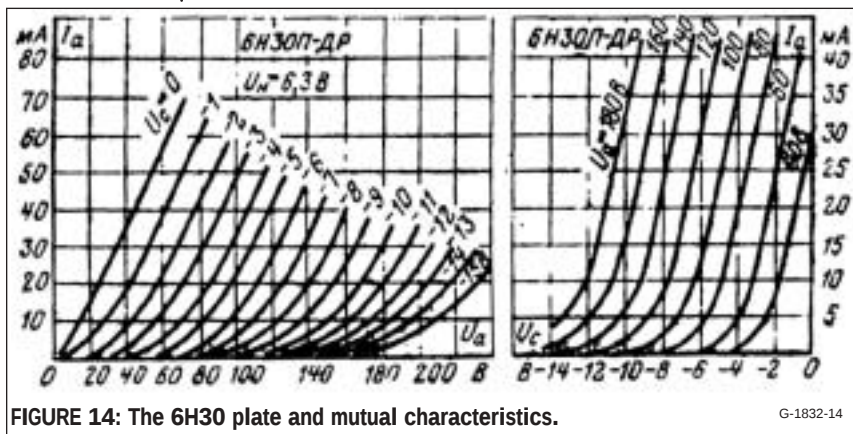


FIGURE 14: The 6H30 plate and mutual characteristics.

G-1832-14

+ CCG=2.4P CGP=3.9P CCP=0.7P CCH=5.6P

E1 7 0

VALUE={V(A,K)/KP*LOG(1+EXP(KP*(1/MU+V(G,K)/SQRT
KVB+V(A,K)*V(A,K))))}

RE1 7 0 1G

G1 A K VALUE = {(PWR(V(7), EX) + PWRS(V(7), EX)) /
KG1}

RCP A K 1G ;

C1 G K {CCG} ;

C2 G A {CGP} ;

C3 A K {CCP} ;

C4 K 0 {CCH} ;

E10 10 0 VALUE = {IF(V(A) - V(K) > 0, V(A) - V(K),
0)}

E11 11 0 VALUE = {IF(V(G) - V(K) > VBIG, V(G) -
V(K) - VBIG, 0)}

E12 12 0 VALUE = {(KG * (V(11) ** EG) *
0)}

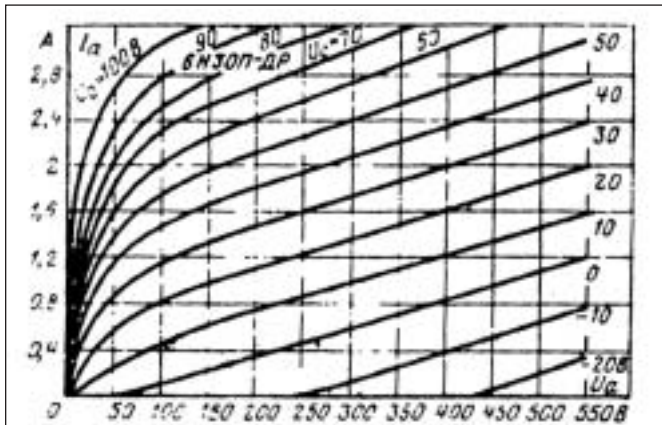


FIGURE 15: The 6H30 plate characteristics for positive grid driving.

G-1832-15

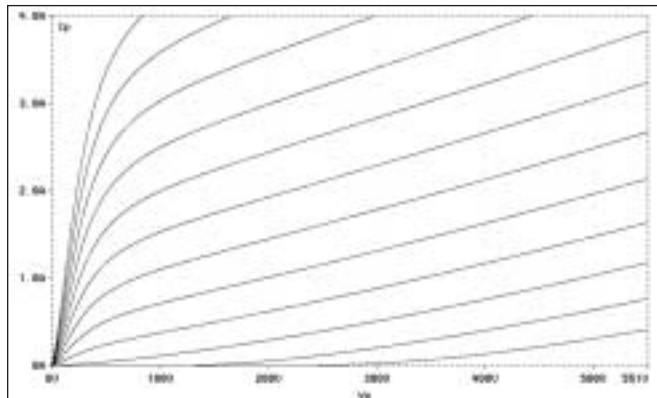


FIGURE 17: The plot of 6H30 PSpice model (plate characteristics for positive grid driving).

G-1832-17

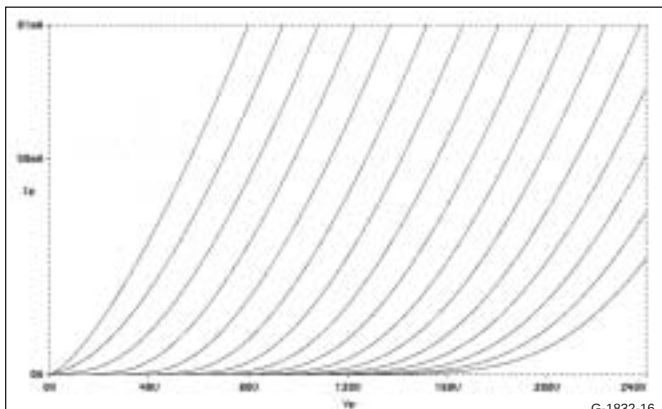


FIGURE 16: The plot of 6H30 PSpice model (plate characteristics).

G-1832-16

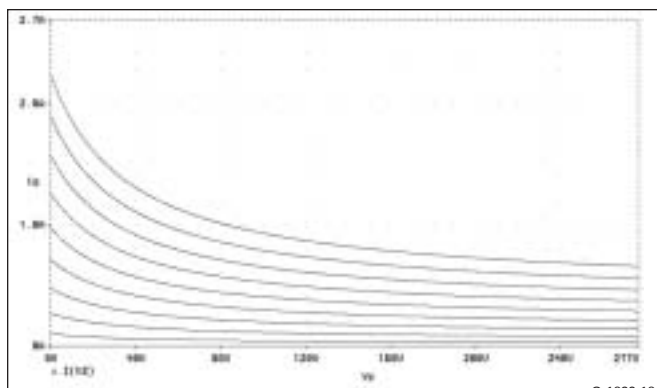


FIGURE 18: The plot of 6H30 PSpice model (grid currents).

G-1832-18


thetubestore.com

Your online source for name brand audio tubes

- Over 1000 types available online
- Perfect Pair matched power tubes
- Capacitors and sockets

Order online at **thetubestore.com**

or call toll free **1-877-570-0979**

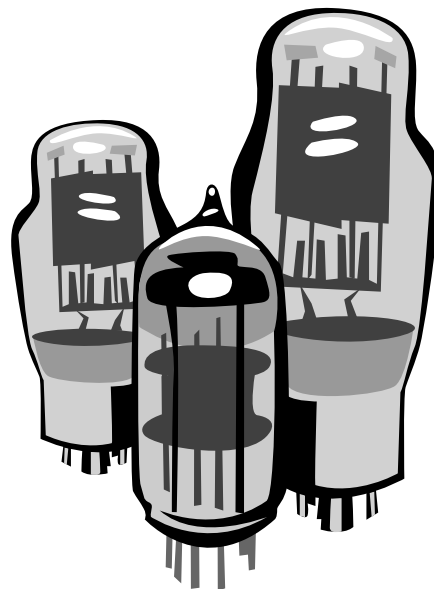

```

+ (((KRG - 1) / (KVG * V(10) + 1)) + 1)) + LG}
G2 G K VALUE = {IF(V(12) > LG, V(12), LG)}
.ENDS
*****
.SUBCKT 6N30P-DR A G K
X1 A G K KTRIODE
+ PARAMS: MU=14.82339 EX=1.386938 KG1=255.6717
KP=99.30537 KVB=1042.421
+ LG=0.2U VBIG=-0.1 EG=1.414474 KG=0.000769 KRG=5
KVG=0.027177
+ CCG=6.3P CGP=6.5P CCP=2.4P CCH=8P
.ENDS

```

THE 6C46

This subminiature tube (*Fig. 19*) born as a low-power series regulator is a sort of 6C33 bonsai. The more interesting characteristic is the low voltage/high current mode of operation. This excellent feature permits you to easily build a truly high-performance low-voltage line preamplifier. Further, the interesting plate dissipation ($P_d = 4.5W$) allows you to experiment with low-voltage low-power amplifiers.

Description

High reliability super-miniature glass triode with one anode and two separate grids and cathodes. Designed to be used in electronic voltage regulators. Lifetime ≥ 500 hrs. *Figure 20* shows the tube's plate characteristics.

Mass	< 7g
Heater voltage	6.3 (+0.7-0.6)V
Heater current	500 (+50-50)mA
Plate voltage	42V
Grid voltage	-1V
Slew rate	20 (+10-5)mA/V
Amplification factor	7 (+2-2)
Plate current	60 (+15-15)mA
Reverse grid current	0.4μA
Maximum plate voltage	250V
Maximum plate voltage for closed tube	330V
Minimum grid voltage	-75V
Maximum cathode current	100mA
Maximum plate dissipation	4.5W
Maximum heater-cathode voltage	150V
Maximum grid resistance	0.25MΩ


PSpice Model (*Fig. 21*)

```

.subckt vt6c46pe 1 2 3 ; plate grid cathode
+ params: mu=8.955 ex=1.5966 kg1=282.77 kp=31.47
kvb=796.640
+ rgi=2k ccg=6p cgp=7.5p ccp=1.76p
e1 7 0 value=
+{v(1,3)/kp*log(1+exp(kp*(1/mu+v(2,3)/sqrt(kvb+v(1

```

FIGURE 19: Sketch of 6C46 and base pinout.

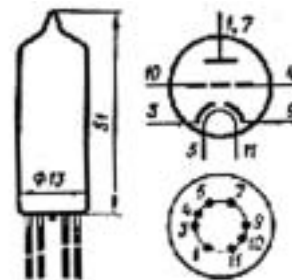

G-1832-19

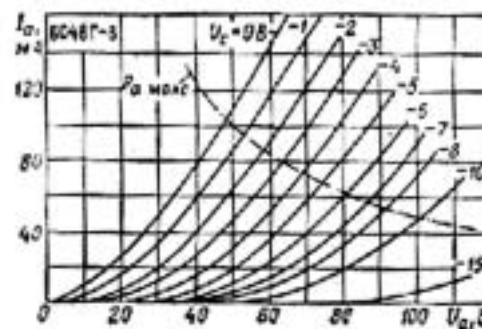


FIGURE 20: The 6C46 plate characteristics.

G-1832-20

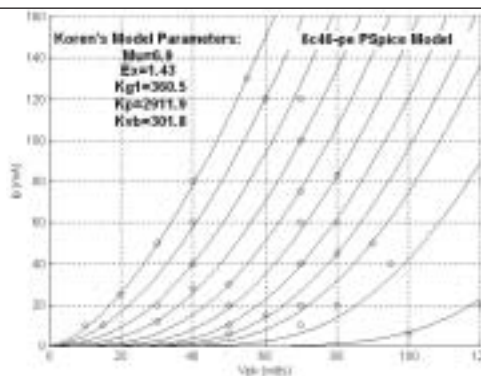


FIGURE 21: The plot of 6C46 PSpice model.

G-1832-21

```

,3)*v(1,3))))))}
re1 7 0 1g
g1 1 3 value= {(pwr(v(7),ex)+pwr(v(7),ex))/kg1}
rcp 1 3 1g
c1 2 3 {ccg}
c2 1 2 {cgp}
c3 1 3 {ccp}
r1 2 5 {rgi}
d3 5 3 dx
.model dx d(is=1n rs=1 cjo=10pf tt=1n)
.ends

```

CONCLUSION

The triodes 6C45, 6C46, and 6H30 are capable of covering all your low-power audio needs. In the third part of this article I'll present a few practical examples. For pricing and availability information, you can refer to the Russian distributor *STC Navigator*⁴.

ACKNOWLEDGMENT

I thank Pavel Skidan, who helped me in the search for technical documentation and in translating from Russian to English.

REFERENCES

3. <http://www.paeng-design.com>
4. <http://www.tubes.ru>

Going once. Going twice.
Going directly to your house.

www.AUDIOGON.com
HIGH END AUDIO MARKETPLACE

Product Review

Sony SACD Player Modification

Reviewed by Gary Galo

SACDmods.com Sony SCD-CE775 SACD Player Modification. SACDmods.com, 223 North 1st St., Cambridge, OH 43725, www.sacdmods.com. Prices (customer must supply the player for modification): \$325 for two-channel mod with new RCA connectors; \$355 for multi-channel mod with new RCA connectors.

SACDmods.com is a company specializing in modifications to Sony Super Audio CD players. The player I review here is the very popular SCD-CE775 (Photo 1), a recently-discontinued player that often sold on the street for less than \$200, a far cry from the five grand price tag of Sony's original SACD player, and their current flagship, the SCD-1. SACDmods also offers modifications to the Sony DVP-NS500V and SCD-C222ES players.

The SCD-CE775 is a five-disc changer offering the full 5.1 channel surround playback capability for multi-channel SACDs. A pair of conventional left and right outputs are also included for two-

channel stereo installations. The player comes with a full-featured remote. Photo 2 shows the rear of the unit.

BURR-BROWN DAC

Sony—a company known for products filled with their own proprietary chips—



PHOTO 1: Front view of the SCD-CE775 Super Audio CD Player. The stock and modified units are identical in appearance.



PHOTO 2: Rear view of the SCD-CE775. The stock PC-mount RCA jacks for the two-channel outputs are replaced with Cardas GRFA connectors by SACDmods.

ZALYTRON

**YOUR ONE STOP SPEAKER
AND SPEAKER COMPONENTS CENTER**

**Check our web site www.zalytron.com
for cutting edge technology in the
Speaker Industry. Need we say more?**

Call, Write, Fax or email for our latest catalog

Mailed FREE in the USA. Canada \$5 P&H, Worldwide \$10 P&H

ZALYTRON INDUSTRIES CORP.
469 JERICHO TURNPIKE, MINEOLA, N.Y. 11501
TEL. (516) 747-3515 • FAX (516) 294-1943
www.zalytron.com • email zalytron@juno.com

Our warehouse is open for pick-up 10 AM to 6 PM daily, Saturday 10 AM to 5 PM • UPS orders shipped same day • Minimum order \$50.00

actually uses Burr-Brown (now a division of Texas Instruments) DSD1702 D/A converters. The DSD1702 is a multi-format, delta-sigma converter supporting both PCM and DSD formats. In the PCM mode, the chip will accept sampling rates up to 200kHz, with datastreams up to 24-bit, though it does not support the DVD Audio standard.

Typical of D/A converters used in lower-cost CD players, the DSD1702 is a combination DAC and digital filter, and actually contains two digital filters. The PCM filter is an 8x-oversampling type, and the DSD filter offers three -3dB passband choices—50kHz, 60kHz, or 70kHz. The SCD-CE775 includes three DSD1702 chips, for the six output chan-

nels. Like most combination DAC/filter chips, the DSD1702 has a voltage output, with I/V conversion done internally.

Each channel of analog circuitry consists of half of an NJM2114 dual op-amp manufactured by JRC, and configured as a three-pole analog filter. The left and right stereo outputs are fed from the same op-amp as the front-left and front-right outputs for surround installations. A multi-channel/two-channel mode button ensures that these outputs function correctly in your particular installation. The NJM2114 offers several performance improvements over the 5532, including a 15V/ μ s slew rate and a 15MHz unity-gain bandwidth.

Electrolytic coupling capacitors are used on both the input and the output of each of the six channels. It is strange that Sony didn't opt for a low-offset and low input bias current FET-input chip for the analog stages. This would have allowed them to eliminate the electrolytic output coupling capacitor. Output coupling caps seem to be a bad habit with Sony and other Far East manufacturers. Even Sony's \$1700 SCD-C555ES and their top-of-the-line SCD-1 have capacitor-coupled outputs (these players do have separate D/A and digital filter chips, plus op-amps dedicated to I/V conversion).

The SCD-CE775 is not based on a DVD player. Consequently, it has a conventional power supply (*Photo 3*), rather than one of the noisy, sonically-menacing switching supplies found in all DVD players. This gives the player a head start, as far as modifications are concerned, because the modifier need not be concerned about trying to rid the player of the broadband, high-frequency noise inherent in switching supplies.

I know I will get flack for this statement, but I don't care: switching power supplies have no business in any piece of high-end audio equipment. There's only one reason to use them: they're small and cheap (OK, I guess that's two reasons). How many manufacturers of chips for digital audio have warned that low-noise supplies are important for best performance? Just read the data sheets, folks.

MODIFICATIONS

The modifications to the SCD-CE775 (*Photo 4*) consist of the following:


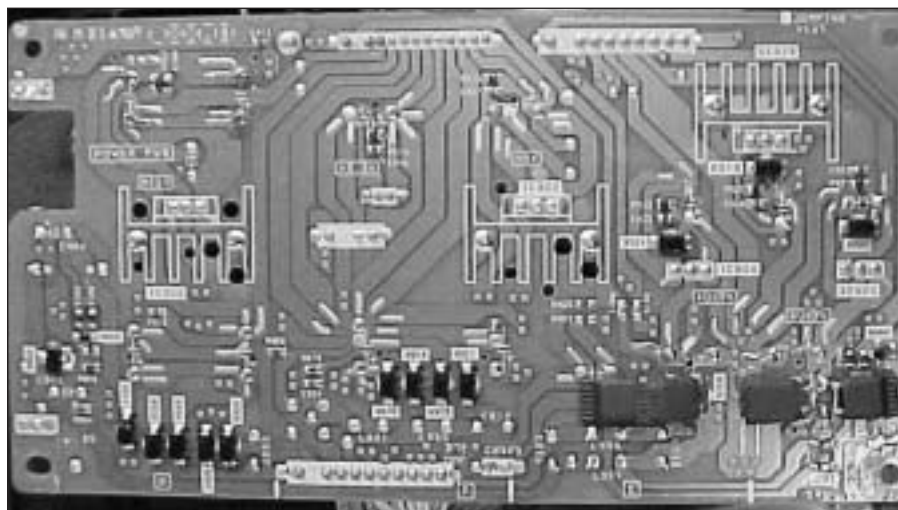


PHOTO 3: The modified power supply board. The Harris high-speed, soft-recovery rectifier diodes (FREDs) used in the power supply mod can be seen in the lower right, insulated with heat-shrink tubing (courtesy of SACDmods.com).

From the developers of IMP and Liberty Audiosuite... *-praxis-*

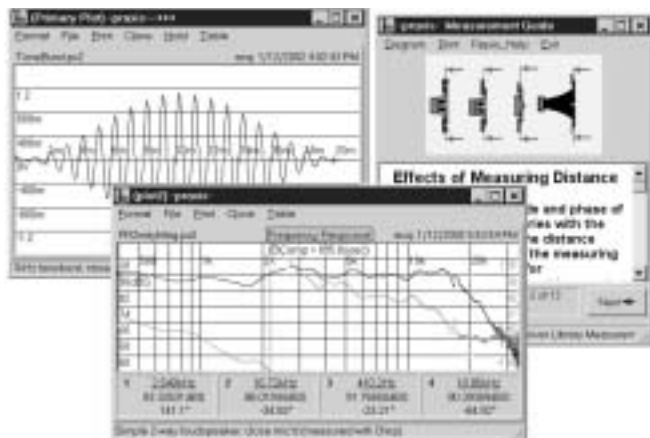Full Featured, customizable measurement system for loudspeakers, transducers, electronics, room acoustics, and vibrational systems.



Compatible with laptops and PCs and a wide variety of soundcards running under 32 bit Windows operating systems. Features built-in measurement guides for easy operation. Samples to 24-bit and 192kHz.

For more information please visit us at www.libinst.com

Liberty Instruments, Inc.
P.O. Box 1454, West Chester, OH 45071 USA
Phone/Fax 513-755-0252 carolst@one.net

- Harris high speed, soft recovery diodes (FREDs). These are installed on the supply board that powers the audio and clock circuits. This is a tricky procedure, because four surface-mount chip diodes are replaced with TO-220 cases, and the fit is very tight.
- Black Gate Capacitors. These are 47 μ F non-polar electrolytics, NX Hi-Q series, which replace the stock capacitors coupling the inputs and outputs of the analog op-amps.
- LC Audio LClock XO2. This clock board (*Photos 5 and 6*) is made in Denmark, and replaces the presumably jittery clock supplied by Sony. Further details on this clock are available on the LC Audio website, <http://www.lcaudio.dk/com/intlcl.htm>. As you will see, the clock is quite expensive, and accounts for most of the modification expense.
- Cardas GRFA RCA jacks. These replace the cheap PC-mount RCA jacks supplied with the stock player. The jacks are connected to the PC board with Vampire "Continuous-Cast" copper wire with Teflon® insulation.

SACDmods proprietor Matthew Anker sums up his modification philosophy this way: "Unlike a lot of the other companies that modify SACD players, I believe that simplicity is the best way to go. I will not bypass the Black Gates with film capacitors or change resistors to metal foil. These methods get you a harsh, metallic sound. The high frequencies would be emphasized to the

point that listening is no longer a pleasure; therefore, only a carefully selected blend of components is used in my mod. The carbon resistors in the player already are a very neutral sounding component, and match well with the Black Gate capacitors."

TEST TRACKS

SACDmods lent me a stock SCD-CE775,


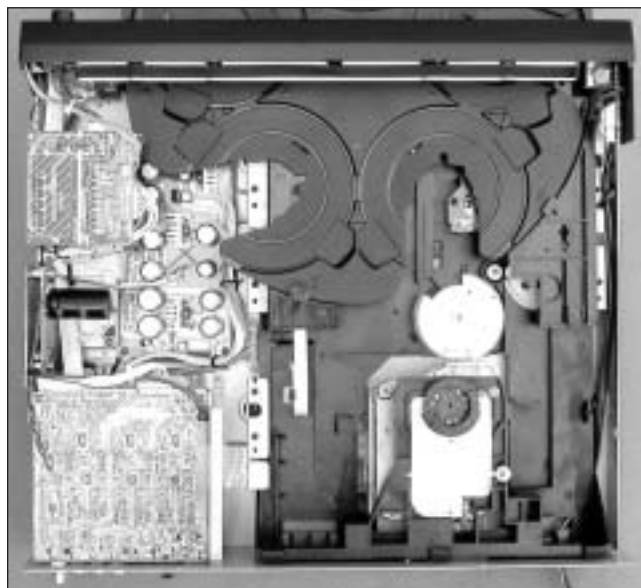


PHOTO 4: Inside the modified SCD-CE775. The analog board is in the lower left, and the new LClock XO2 board is just above the analog board. The power supply board is to the right of the clock board.

Amtrans Audio Series

Ultimate Attenuator for High-End Audio

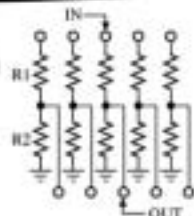- Attenuation-method:L-pad
- Resistor:Rikenohm RMG F-type(1%)
- Stereo:2channels
- Impedance:30k Ω



Compact-Type(23steps)
UATLS-30 36,000JPY

HighQuality-Type(25steps)
UATS-30 58,000JPY



Rikenohm

- Insulated Carbon Film Resistors
- High Quality Sound,High Reliability
- Anti-magnetic Cap&Wire
- OFC Gold-plated Wire
- E-24 Series

RMG 1/2 Watt F-type(1%) 180JPY
RMG 1 Watt F-type(1%) 240JPY
RMG 2 Watt F-type(1%) 310JPY



Seiden Switch



32-NEG-Series



56-SG-Series



43-NEG-Series

www.amtrans.co.jp

Amtrans

Amtrans Corporation

Bandai-bld.2F,2-10-14 Kanda-Awajicyo,Chiyoda-ku,Tokyo,101-0063 JAPAN
Phone:+81-03-5294-0301 Fax:+81-03-5294-0302 E-Mail:audio@amtrans.co.jp

ADIRE AUDIO

CHRISTMAS DAY



SALE

During the month of December, buy anything from our web store and receive a full 10% off your order. Any item and any quantity. To receive your discount, simply place your order through our web store and use a discount code of:

XMAS-02-SALE

**YOU WILL RECEIVE
10% OFF YOUR ENTIRE
ORDER! GOOD FOR
DECEMBER 2002 ONLY!**

Adire Audio carries a full range of kits, products, and services for the DIYer. Please contact us at:

WWW.ADIREAUDIO.COM

PH/FAX: 206-789-2919/800-437-2613

TELARC'S CLASSIC SOUNDSTREAM RECORDINGS RE-MASTERED

In 1978 Telarc, then a fledgling audiophile record label, made audio history with the issue of their first digitally-mastered, long-playing record, Frederick Fennell conducting the Cleveland Symphonic Winds in Gustav Holst's two *Suites for Military Band*, plus music by Bach and Handel. This album was quickly followed by Telarc's first digital orchestral recording, Robert Shaw and the Atlanta Symphony Orchestra performing Igor Stravinsky's 1919 *Firebird* suite, plus the Overture and "Polovetsian Dances" from Borodin's opera *Prince Igor* (Photo A). At the time these recordings were made, the classical recording industry was at an all-time low in terms of engineering, with most of the major labels capturing frustratingly unnatural sound due to over-use of multi-microphone techniques.

Telarc took several steps back, with Producer Robert Woods and Engineer Jack Renner opting for a purist approach. Borrowing the technique adopted by Robert Fine in his fabulous stereophonic recordings for Mercury in the late 1950s and early 1960s, Woods and Renner used only three spaced omnidirectional microphones (Schoeps Colette-Series SKM-52U). The results spoke for themselves—these recordings captured a symphony orchestra with remarkable realism, with natural imaging and depth, clarity and dynamics. Then, of course, there was that famous Telarc bass drum, taxing phono cartridges, power amps, and loudspeakers. (The drum head was facing the mikes. —Ed.)

Also noteworthy was the digital recording system used by Telarc, the Soundstream recorder designed by Dr. Thomas Stockham. Audiophiles were clearly divided on the merits of digital audio, and for years to come many would proclaim the virtues of analog sound. Indeed, many still do!

One thing was certain, however. Stockham's Soundstream recorder was well ahead of other digital recording systems in use at that time. To those of us who found Denon's digitally-mastered LPs of that period excruciatingly bad, the Soundstream recorder was a revelation, making a strong case for the potential of digital audio.

The Soundstream recorder was surprisingly advanced by late 1970s' standards. The sampling frequency was 50kHz, higher than what would be adopted a few years later for the Compact Disc. In addition, the system offered 16-bit performance at a time when anything over 14-bits was thought to be impractical.

The Soundstream system also used a Rockwell instrumentation recorder—modified, if my memory is correct—and arguably a better solution to the problem of digital audio storage than NTSC-encoding on videotape, which would become extremely popular in the early years of digital audio. Telarc's first digital recordings were made using a Studer Model 169 mixing console. By the time they recorded Stravinsky's *Le Sacre du Printemps* in 1980—with Lorin Maazel and the Cleveland Orchestra, another audiophile spectacular—they had switched to a Neotek console.

DSD CONVERSION

With the introduction of the Compact Disc, it was only natural that Telarc should transfer some of these pioneering recordings to the new consumer format. There were problems to be surmounted, however. Converting the 50kHz sampling rate of the Soundstream system to the 44.1kHz CD standard posed a nasty mathematical problem. You must remember that these transfers were done back in the 1980s, before the introduction of asynchronous sampling rate converters such as the Analog Devices AD1890-series and its successors. Surely, these CDs offered only an approximation of the original Soundstream masters.

Enter Sony's Direct Stream Digital recording, the mastering system for the Super Audio CD format. Within the past two years, Telarc has re-mastered some of their classic Soundstream recordings for issue in SACD format, using the best digital conversion technology. The conversion from the original Soundstream recordings to DSD has been done using a dCS 972 Sample Rate Converter with custom software. Fortunately, Telarc



PHOTO A: On the left, a Direct Stream Digital remastering of an audiophile classic, Robert Shaw's 1978 Soundstream recording of Stravinsky's *Firebird Suite*. On the right, the remaking of a Telarc chestnut, Tchaikovsky's *1812 Overture* with Erich Kunzel and the Cincinnati Pops Orchestra in an all-new DSD/SACD recording.

auricap

**World's finest capacitor,
Sonically transparent,
Superior technical
specifications.**

- Auricap is the best I have tried by a long, long way.
Kendrick Povey/VP Melbourne Audio Club
- An outstanding technical feat... They simply sound like no cap at all.
Jennifer Crock/Jenna Labs
- If you want absolute transparency, then you must give Auricaps a try.
Giorgia Pozzoli/TNTAudio.com

OEM & dealer inquiries invited.
Call (800) 565-4390

www.audience-av.com

has had the presence of mind to offer all of their SACDs in dual-layer format, so they will also play on conventional CD players. For the mastering of the CD layer, the DSD transfer is converted to CD format using Sony's Super Bit Mapping Direct system.

I compared the CD layers of the Shaw *Firebird* and Maazel *Le Sacre* to Telarc's previous CD releases and was amazed at the improvement in sound. The most noticeable difference was a dramatic improvement in space. The old CD transfers sounded dry and "up-front," lacking in hall ambience and a sense of the original recording venues, and somewhat hard in the treble region.

The new transfers sound like a different microphone pickup altogether (though they obviously are not). There is a tremendous improvement in hall sound, with correspondingly greater depth perspective and accuracy of placement within the soundstage. Overall, the recording venues sound considerably larger on the new transfers. A layer of edge and glare on the old CDs is largely removed by the new conversion process.

The SACD layers are better still. As Telarc points out in the booklets to the new issues, the SACD transfers offer listeners the ability to hear—for the first time—the sound that the recording team heard on the original Soundstream masters. In fact, these SACD transfers may sound even better than that, due to considerable advances in the digital-to-analog conversion process.

What is most impressive is how well these Soundstream recordings have held up over the past 24 years. They don't have the detail and resolution, or the warmth and absence of high-frequency artifacts of today's digital recording systems—especially SACD. Nor do they capture the harmonic richness of a symphony orchestra, or the sound of the original acoustic space, as well as current digital technology. But they still offer a satisfying—indeed impressive—audio experience, which I cannot say about any other digital recordings made during that period. The Telarc DSD re-masterings are a testament to the remarkable achievement of Thomas Stockham and the Telarc recording team.

so I could compare it to the modified player. For this review, I purchased Telarc's SACD remasterings of two of their classic Soundstream digital recordings—Stravinsky's *Firebird* suite conducted by Robert Shaw (SACD-60039) and *Le Sacre du Printemps* conducted by Lorin Maazel (SACD-60563). I offer a few thoughts on these early Telarc digital recordings in the sidebar accompanying this review.

SACDmods also lent me Telarc's SACD of Tchaikovsky's *1812 Overture* (Photo A), an all-new Direct Stream Digital remake of one of Telarc's most famous audiophile recordings (SACD-60541). I also tried Sony Classical's SACD re-masterings of Leonard Bernstein conducting his *Overture to Candide*, the symphonic dances from *West Side Story*, the symphonic suite from *On The Waterfront*, and the *Fancy Free* ballet. All Telarc issues are dual-layer, so they will play on a conventional CD player, as well. Sony Classical's SACD discs are single-layer, and will only play on SACD players.


LISTENING CRITIQUE

The stock Sony CE775 did not make a very strong case for the SACD format, and exhibited many of the characteristics of an inexpensive CD player. The sound is rather dry, slightly edgy in the treble, and lacking in a precise,

three-dimensional soundstage. If you compare the CD layers to the SACD layers on the Telarc recordings, the SACD layers are superior, but clearly well below the ultimate capabilities of

Our Samples Are Better Than

FREE!

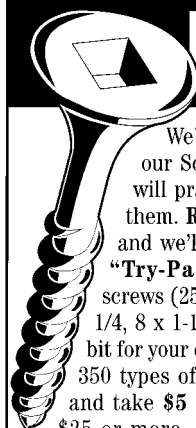

We're so sure you'll love our Square Drive Screws we will practically pay you to try them. **Return this ad with \$5** and we'll send you our famous "Try-Pack" Sampler of 100 screws (25 each of #8 x 5/8, 8 x 1-1/4, 8 x 1-1/2 and 8 x 2), a driver bit for your drill, our catalog listing 350 types of Square Drive screws, and take **\$5 off** your first order of \$25 or more, or **\$10 off** your first order of \$50 or more! (Limited time offer. Available in USA only.)

"We tried a box of 1-3/4" #8 prelubricated flat heads with nibs from McFeely's, which quickly became our favorite fastener." Speaker-Enclosure Screws, Robert J. Spear and Alexander F. Thornhill, *Speaker Builder*, 2/94

© 1996 McFeely's All Rights Reserved

McFEELY'S
SQUARE DRIVE SCREWS

PO Box 11169 • Lynchburg • VA • 24506
Call 1-800-443-7937 or Fax 1-800-847-7136

AURA
S O U N D



NSW1-205-8A
20mm "Cougar"
220-20kHz




NSW2-326-8A
33mm "Whisper"
250-16kHz




NS3-193-8-S43
3" Wide Range
80-15kHz

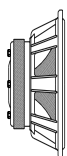- * **Shielded NRT Magnet Systems on all units, even the 18" Subwoofer!**
- * **Long Stroke Suspensions, 220Hz on a 20mm Dome!**
- * **Woofers Sizes: 10" & 12" Home and 10", 12", 15" and 18" Autosound/Home**
- * **Aurasound Drivers Open New Avenues in Speaker Design!**



MADISOUND SPEAKER COMPONENTS, INC.
8608 UNIVERSITY GREEN
P.O. BOX 44283
MADISON, WI 53744-4283 U.S.A.
TEL: 608-831-3433 FAX: 608-831-3771
e-mail: info@madisound.com
Web Page: http://www.madisound.com

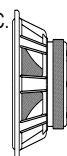

NS18-992-4A
18" Subwoofer (Autosound or Home Sub)

the format. I actually preferred the CD layers of the Telarc recordings played on my reference CD playback system to the SACD layers as reproduced by the stock Sony player.

The modifications performed by SACDmods changed the balance entirely. On the Telarc *1812* the modified player has almost none of the high-frequency spit and trash of the stock player. There is more detail and less congestion in passages for full orchestra. The sonic presentation is more open and airy, especially striking in the reproduction of the chorus near the beginning of the work (the addition of the chorus is a re-touching by the conductor). The low strings are much warmer on the modified player, and the high strings are silkier and more life-like. There is much greater retrieval of hall ambience, particularly around the players near the back of the orchestra.

On the 1980 Telarc *Le Sacre du Printemps* the woodwinds have much greater harmonic richness on the modified player, and the entire sonic presentation is far more spacious and nat-

ural. The 1978 *Firebird* has more effortless full-orchestral transients, and the famous Telarc bass-drum sound is deeper and fuller. On all three recordings the message is the same: the stock Sony CE775 doesn't reveal

enough of SACD's potential to justify the new format. The SACDmods remake most certainly does!

Sony Classical's *Bernstein Conducts Bernstein* SACD was not very impressive sonically. It is not categorically

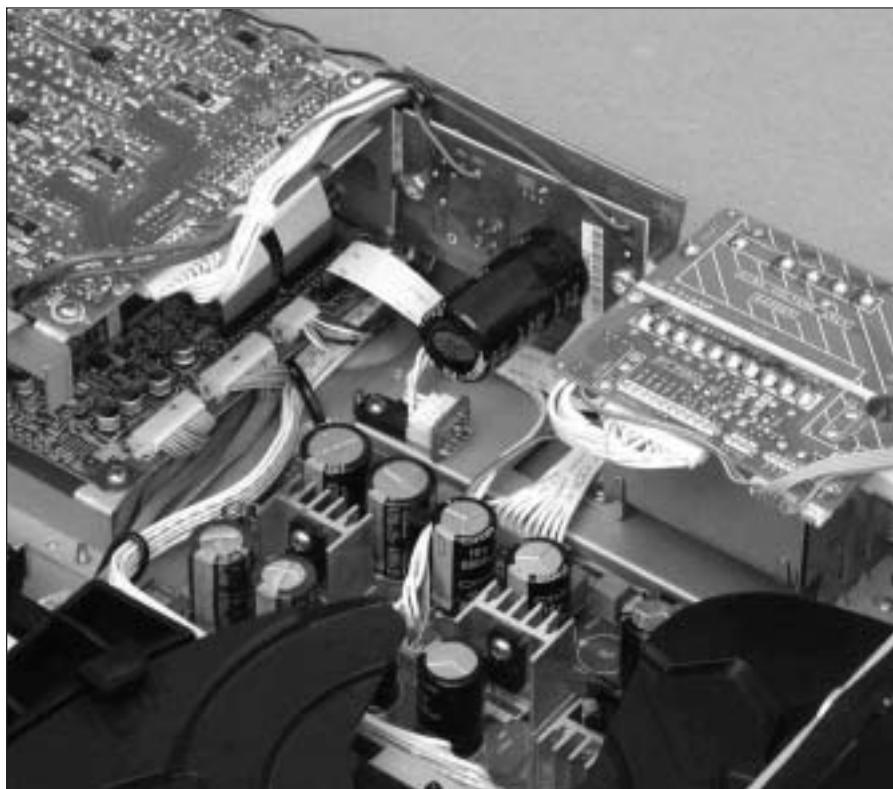


PHOTO 5: Close-up of the installed LC Audio LClock X02 board. Most of the circuitry is on the bottom side of the board, hidden by the aluminum mounting plate.



ELECTRA-PRINT
AUDIO CO.

S.E. OUTPUT TRANSFORMERS

- *Primaries to 10K
- *Power up to 100 watts
- *-1db 18hz to 40khz typical
- *Custom designs available

PUSH-PULL OUTPUTS

- *Built for triodes
- *Single output to load

INTERSTAGE TRANSFORMERS

- *Full bandwidth, up to 60ma
- *Single plate to P-P grids

LINE OUTPUTS

- *Full bandwidth, up to 60ma

POWER TRANSFORMERS

- *Custom built to your requirements
- *Power supply design advice

CHOKES/FILTER and AUDIO

- *Standard and custom HV filter chokes
- *High current filament chokes
- *High inductance audio plate chokes

specification and pricing catalog available
Visa, MC and Amex

ELECTRA-PRINT AUDIO CO.
4117 ROXANNE DR., LAS VEGAS, NV 89108
702-396-4909 FAX 702-396-4910
EMAIL electaudio@aol.com

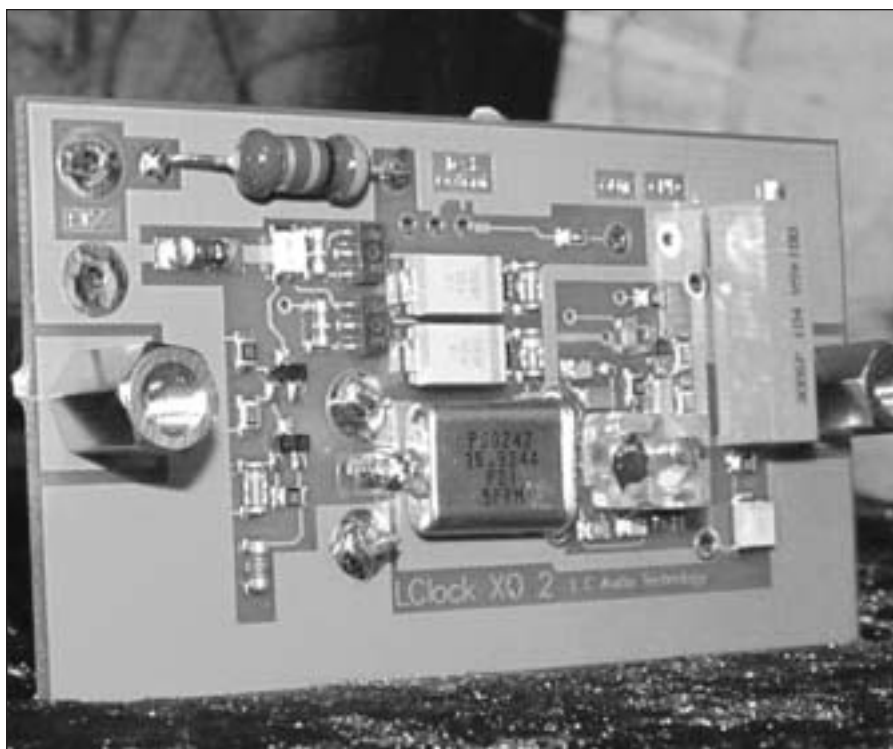


PHOTO 6: Component view of the LClock X02 board (courtesy of SACDmods.com).

better than its 20-bit CD counterpart (SMK 63085, part of the "Bernstein Century" series, re-mastered with Sony Super Bit Mapping). In fact, the SACD sounds as though it was made from an analog production copy, rather than the original session tapes. The CD version was produced by John McClure, one of the original session producers, and someone who obviously cared a great deal about doing justice to the original tapes. I did not find this Sony SACD particularly useful as reference material.

BATTLE OF THE FORMATS

There is considerable debate regarding which format is superior: SACD or 192kHz/24-bit DVD audio. I don't think that matter can be put to rest until identical recordings can be compared in both formats. I hope some of the best recordings from the analog era—classics from the Decca/London, RCA Victor Living Stereo, and Mercury catalogs—will be re-mastered in both formats so that meaningful comparisons can be made.

Another contender is the Vox/Turnabout recording of Rachmaninoff's *Symphonic Dances* (already available in a superb 96kHz/24-bit DVD from Classic Records, and one of my most valuable reference recordings). I would also expect outboard digital processors to become available for these formats, once a standard digital interface becomes available. We should hope, even though the datastreams are incompatible, that both formats can be accommodated by one transport and outboard D/A converter, with a common digital interface, with automatic detection of the source format.

In the meantime, the SACDmods.com re-make of the Sony SCD-CE775 SACD player is a very impressive performer, one that makes a convincing case for the new format, at an affordable price. If you own this or one of the other low-priced Sony SACD players, you should strongly consider having SACDmods rework your player. ❖

Manufacturer's response:

Since Mr. Galo reviewed the early version modified SCD-CE775 I submitted, I have added several tweaks to my modification packages.

- *Class A biasing of the front channel op-amp. This smoothes out the high frequencies by simply adding 2mA of bias current.*
- *Installation of two 1000µF Black Gate filtering capacitors on the ±7V supply to the op-amps and DAC. This lowers the noise floor considerably.*

Recently added as an option:

Installation of a 1 lb, 25VA toroidal power transformer for the audio board's power supply. This makes the CE775's power supply nearly identical to that of the C222ES. The transformer gives the bass more "punch" and completely separates the digital supply from the analog rendering a cleaner sound. This is a \$39.95 option that can be installed with a CE775 modification package.

Matthew Anker
www.SACDmods.com

Sure, we're an audio center.
Center of the universe, that is.

www.AUDIOGON.com
HIGH END AUDIO MARKETPLACE

Electronic Crossovers

Tube
Solid State
Powered
Passive Preamps
46 Step Attenuator
Power Amps
100% MOSFET



XM126 tube xover, available 2,3 and 4 way

*All available as kit also
Free Catalog:*

Marchand Electronics Inc.
PO Box 473
Webster, NY 14580
Phone (716) 872 0980
FAX (716) 872 1960
info@marchandelec.com
www.marchandelec.com



Precision Port™
Be Different - Sound Better

CLEANER SOUND
LESS DISTORTION
EASY INSTALLATION
GREATER SOUND PRESSURE LEVELS
DESIGNED AND MADE IN THE USA

Precision Sound Products, Inc.
725 Terra West Drive
Freeport, Illinois 61032
Phone: 815-599-0662 Fax: 309-279-0359
E-mail: nonoise@psp-inc.com
www.psp-inc.com

PATENT #5623132

Xpress Mail

LITTLE AMP

 I wish to thank Mr. David Wolze for his kind words ("Express Mail," April '02 *aX*, p. 65) regarding my article "A Great First Amplifier Project" (Dec. '01). I welcome his suggestions for upgrading with a different output transformer. I tried other trannies besides the #1608 Hammonds, but found them to be the best value for the price and also to be up to the task of supplying the proper load required by this "little amp." (Actually, the best upgrade for this project would be to replace the coupling caps with the Hovland MusiCaps available from Antique Electronic Supply.)

As a matter of fact, I even installed a pair of Hammond #1620s and tried the circuit with some 5881 tubes I had in stock. They sounded pretty good but will sound better after I change the B+ voltage, heater power supply, and the bias circuit. The "snubber" circuit Mr. Wolze mentioned may work in some cases, but I found that it often duplicates the circuits in some crossovers. And, yes, I agree that a circuit with a single 6Y6 with a UBT-3 output would probably work fine—sounding OK and certainly keeping the parts count down—but it could drive the cost of the project up, which was what I was trying to prevent for the benefit of first-time

builders who might not want to invest too much money in a project when they're not really sure of the outcome.

If someone really wants to build a single-ended amp with a low parts count, he could try using a 6L6, 6BQ5, 5881, or other similar type of tube in my single-ended project (Sept. '01, p. 20). You could do this with about 12 parts per channel and still have a sweet tube sound, by using a different power supply, adjusting the bias circuit, and the by-pass caps could be optional. As in all cases, the most expensive part in a single-ended amp is usually the output transformer.

The main purpose of the 12V6 push-pull amp was really to provide a good tube sound with a minimum of parts and an easy-to-construct project which is not very expensive for the first-time builder. Some other hobbyists who have built this amplifier say they really enjoy the sound it produces for such a small investment of their money and time. I truly hope others will enjoy it just as much!

Rick Spencer
Clovis, Calif.

CHOOSING TUBE CIRCUITS

 I have enjoyed several of Rick Spencer's articles in the past two years. However, I would appreciate it if

he could spend a little more space on the pros and cons of his circuit choices.

For his most recent article ("A Five-Channel Tube Home Theater Amp," June '02, p. 42), he used one separate cathode bias resistor for each 12V6 tube instead of a single one for both tubes. A shared cathode bias resistor is supposed to even out differences between tubes and provide better tube matching. He used a shared cathode bias resistor in a similar design in "A Great First Amplifier Project" (Dec. '01). Why the change? He also never mentioned whether tube matching is necessary for this type of circuit. Is it necessary?


I am new to tube amplifiers. Can he explain the sonic difference between a cathodyne phase splitter (Dynaco 70) versus the one used in his circuit? Both can achieve similar gain using two half tubes.

Bing Yang
bingyang99@hotmail.com

Rick Spencer responds:

I am glad you have enjoyed my articles in audioXpress. The pros and cons you mention in your letter can be narrowed down to the fact that all of the circuits used in my designs are very simple and, yet, are capable of

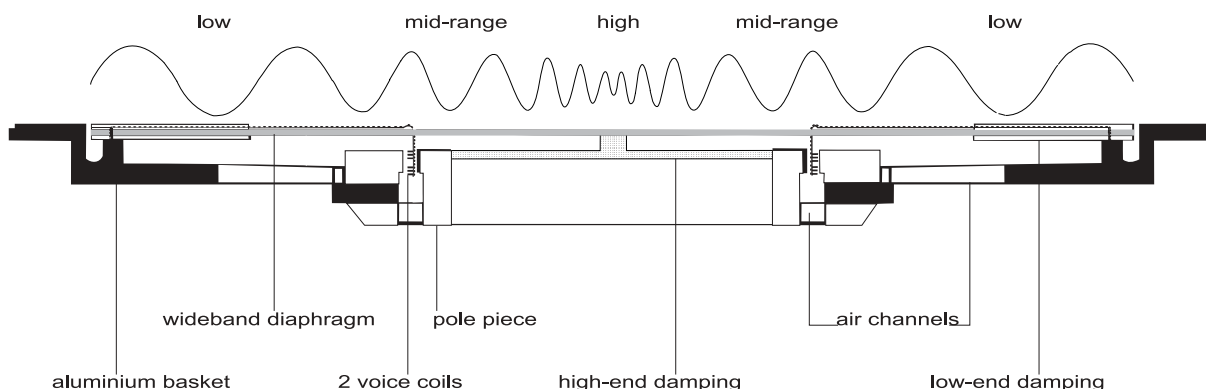MANGER Bending wave transducer "Natural accuracy"



E-Speakers.com

Los Angeles, California. 818 907-8942 / www.e-speakers.com

delivering a good sound when used properly. My single-ended 6550 amp used a super simple, low parts count circuit, and when teamed with the proper speakers and signal sources will almost bring tears to your eyes with its pure sound. The "little amp" (Dec. '01) also uses a straightforward simple circuit, has a low parts count, and will deliver a very good sound at a minimal cost.

I used this same circuit in the five-channel home theater amp project with only a slight change to the cathode bias arrangement. The engineers at RCA used this type of cathode resistor-capacitor setup in their design of a 6V6 amp back in 1959. I was curious to see whether I could obtain a smoother sound, better stability, and maximum power from each tube, so I used this type of arrangement and found what seems to be an overall improvement in sound quality. However, if you want to reduce your total parts count and keep things even more simple, then use the same type of circuit found in the 12V6 amp in Dec. '01.

As far as tube matching goes, you may request matching when you order your tubes from Antique Electronic Supply. Matched tubes will usually perform better, and I try to match mine on my tube testers. I also try to match resistor and capacitor values in critical parts of the circuit.

Regarding the Dynaco phase inverter circuits, when you consider the famous engineers that developed them you can only assume that they produced the results they were trying to achieve. I've repaired and upgraded (POOGEd) a couple of Dynaco amps, and I have always enjoyed their laid-back sound.

Rather than use a lot of space explaining the different types of inverters here, I suggest you try to obtain a copy of Glass Audio 1/90 from audioXpress and read the article by Daniel Norman concerning the inner workings of phase inverters ("Understanding Tube Phase Inverters," p. 12). I have never seen it explained better.

The most interesting inverter circuit I have seen is the Fisher 500-C. It featured a control labeled "phase inverter adjustment"(!). If you're curious about it you can find the diagram in issue #6, 1997 of Vacuum Tube Valley. And, since the design was used in a FISHER—well, what more can one say!

The phase inverter circuit I used in my 12V6 amps is really simple but will have slightly more distortion and phase shift than the ones submitted by Joseph Still in his Glass Audio 5/00 article ("A 20W \$260 Amplifier"). His style of inverter has reduced phase shift and only a small degree of imbal-

ance remains between its two outputs, which makes it very desirable for obtaining a smoother overall sound. If you have the room on your chassis then use his style of voltage amplifier and inverter. You can't go wrong with any of his designs. The choice is yours.

MC STEP-UP TRANSFORMER

K Peter Millett is to be commended on his excellent and very practical article on building a moving-coil (MC) input transformer unit (May '02, p. 58). There is no doubt that a properly designed passive unit is preferable to a specially designed active MC input stage, since it requires some unusual parameters of the input devices used to keep the noise level within acceptable limits. The main one is the rbe, which is the principal noise generator and must be as low as possible. Selected low-noise small-signal devices are not the prerequisites in this case, and, paradoxically, power transistors are more likely to be suitable! However, I'd like to expand on what he had to say with respect to the selection of the transformer (and I endorse his choice of the ones from Sowter, which are really microphone types).

My co-worker, the late Peter Baxandall, and I were involved with the design of a similar device for a British manufacturer of MC cartridges—the Mayware—sadly, no longer available, particularly because they carried a budget price and excellent value for money. The design brief was for a transformer interface that would accommodate a range of source Z cartridges, from 3 Ω (typical) to as high as 50 Ω . After ruling out the practicability of tapped transformers, we hit on the idea of a standard 1:40 designed specifically for a 3 Ω cartridge. This lifted the nominal 125 μ V output to 5mV and so, ideal for most moving magnet (MM) input stages.

After examining a range of representative MC cartridges, we then confirmed that all had one outstanding useful characteristic in common—that the source Z was substantially resistive at all frequencies. This may well contribute to the excellent and consistent performance, since MM types are a complex mix of reactance and resistance and normally require careful loading, standardized as we know at 50k Ω . Even so, you must still consider shunt capacitance of the input cable

JFETS

ULTRA LOW NOISE
LS843 - 3nV/Hz typ

TIGHT MATCHING
LS843 - 1 mV max

- ♦ N & P Channel
- ♦ Duals & Singles
- ♦ Custom Screening
- ♦ Die, SMT, Thru-Hole
- ♦ No Order Minimum
- ♦ COD's Accepted

Second Source for Domestic & Foreign JFETs & Bipolars

Full Service U.S. Manufacturer of Specialty Linear Products

LINEAR SYSTEMS

4042 Clipper Court
Fremont, CA 94538
510-490-9160/510-353-0261 (Fax)
E-mail: 3623671@MCIMAIL.COM
WWW.LINEARSYSTEMS.COM



KLEIN TECH SYSTEMS

"New Perspectives in Acoustic Engineering"

For Audio Engineers, Sound Engineers, and Serious Audiophiles

ACOUSTIC INTERFACE PADS


Improve Sound Quality and Safety

Composed of Space-Age Polymers

KTS Acoustic Interface Pads:

- ➔ Fastens Speaker Cabinets to Any Stand or Surface
- ➔ Isolates Distortion, Dampens and Absorbs Vibration
- ➔ Secures Objects for Stability and Safety
- ➔ Protects Tile, Wood, Linoleum, and Other Finishes
- ➔ Eliminates Destructive Spikes and Mounting Hardware
- ➔ Ideal for Center Channel Speakers, CD Players/Transports, Turntables, Amplifiers, Tape Players, CD Trays, and Chassis Vibration

Typical Application:

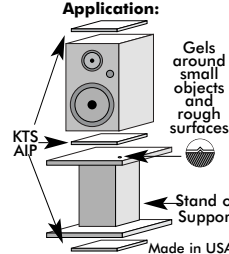

KTS adheres to a simple concept: **every** part of an audio chain contributes to the overall operation, acoustical performance and owner satisfaction. Why take chances? Get the most out of the system in which you've invested!

www.kleintechsys.com
561-969-2298 • Fax: 561-423-0388
email: support@kleintechsys.com

PTFE Insulated Twist-eye Terminal Strips



Made from the finest materials.

Lightly tinned 14 gauge OFHC Copper twist-eyes made and inserted by hand into 1/2" virgin PTFE stock.

Perfectly sized for larger audiophile grade components.

Complete with mounting holes and available with 1 to 6 terminals per strip.



www.grennanaudio.com

PMB 302, 8825 W. Olympic Blvd.
Beverly Hills, CA 90211

and its effect.

None of these factors are a problem with MC cartridges. Loading was also immaterial, as long as the reflected load was at least 3× the source Z; a little arithmetic shows that the 50kΩ reflects to a trifle over 30Ω. So no problem there. Now, what about a higher source Z cartridge, say 50Ω? Two factors to consider here: the signal is going to be much higher at the secondary, far higher than we need. The technique we adopted has, until now, remained a secret.

Certainly, it baffled at least one reviewer of the product as to how it seemed that the transformer had an adjustable step-up ratio. Some of the obscure theories were highly amusing, since as is so often the case, he lacked the engineering experience and training to work out what was a straightforward solution to the problem. We simply shunted the transformer secondary internally with a lower resistor, that by virtue of its attenuating action in series with the reflected source Z, brought the signal level down to what the input stage required. It also had the desirable effect of swamping the reactive compo-

nents of the transformer, now more dominant because of the higher source Z of the 50Ω cartridge.

In our case, an 18kΩ was the choice, and the reflected load now for a 3Ω cartridge becomes a trifle over 13Ω. I still have the prototype and a production model.

Reg Williamson
Kidsgrove Staffs, England

Peter Millett responds:

Thanks to Mr. Williamson for his compliments, and for an excellent way to simply make a "self-adjusting" MC step-up transformer.

If I understand correctly, the scheme used works basically by providing a relatively low impedance load for a higher impedance cartridge—in other words, the "3:1" rule for load:source impedance is intentionally violated. This works as an attenuator, because the source Z is nearly purely resistive—if it were not, the frequency response would be adversely affected. The result, then, is that output from a higher source impedance cartridge is attenuated more than that from a low source impedance cartridge.

GRANDMOS The SMART amplifier



2 Audiophile Masterpieces for the DIYer

TRIPHON The ULTIMATE crossover system



- ✓ Probably, the nearest approach to :
"A STRAIGHT WIRE WITH GAIN".
- ✓ High end 2 x 100 W_{RMS} / 8 ohms MOS-FET amplifier.
- ✓ SILVER plated PTFE / fiberglass printed circuit boards.
- ✓ SILVER plated connections.
- ✓ Military grade components.
- ✓ Only J-FET and MOS-FET audio transistors.
- ✓ NO CAPACITOR in the sound path *.
- ✓ Minimum wiring and easy construction.
- ✓ Outstanding performances.
- ✓ Absolute Transparency and Sound.
- ✓ Extremely reliable.
- ✓ Steady performances over years.

* : under certain conditions

To complete the GRANDMOS (or any good quality amplifier) we have designed the **TRIPHON system** :

- ✓ Musically neutral and transparent.
- ✓ 3-way electronic crossover.
- ✓ 6 or 12 dB/octave slope (true LINNKWITZ-RILEY filter).
- ✓ 4-channel Class A minimalist MOS-FET amplifier for MID and HIGH frequencies.
- ✓ Choice of cut-off frequency.
- ✓ PTFE / fiberglass printed circuit boards.
- ✓ Fully discrete component technology.
- ✓ SILVER plated connections.
- ✓ Minimal wiring.



by

Selectronic
INSTRUMENTS & ELECTRONICS

www.selectronic.fr

Phone : + 33 - 328 550 328 - Fax : +33 - 328 550 329
BP 513 59022 LILLE - FRANCE

>> Detailed information on www.selectronic.fr or by e-mail to : selectrocom@selectronic.fr <<

It seems as though you could also provide multiple load resistors (selected with a switch), or even a potentiometer, across the secondary. This would allow you to adjust to your liking.

CAR SUB CROSSOVERS

I've enjoyed reading "The Infinite Box: Constructing a Subwoofer" (April and May '02). In part 2 of the article, Mr. Wright discusses crossovers for subwoofers. It's been my experience in car audio that subwoofer crossovers have some special requirements worth mentioning. These should apply to home audio as well.

1. *Crossover Slope:* Assuming the subwoofer may be located some distance from the satellites, it's important that the listener cannot localize the sub. As Mr. Wright mentions, a low crossover frequency (80Hz) will help mask the sub's location. I'd like to add that a steep crossover slope is equally important here. A shallow slope (first or second order) allows some mid-bass energy to be reproduced by the sub, giving away its location.

The effect this produces in car systems is that the music is coming from in front of you, but the bass is coming from behind you. Depending on the crossover frequency and sub location, I would recommend a third- or fourth-order slope.

2. *Cutoff Frequency Control:* Just because you're using a fourth-order crossover slope for your sub doesn't mean the satellites need a complementary fourth-order crossover. In fact, it's common for satellites to be used in car audio without any crossover whatsoever.

But to provide a seamless blend between the main speakers and sub, the sub crossover should have a continuously variable cutoff frequency, which (along with a means for inverting the sub's polarity) will provide the means to achieve a high-quality blend with virtually any satellite configuration. This isn't an obvious result, but computer simulations with sealed and ported satellites—both with and without crossovers—confirm this conclusion.

Lundahl Transformers in the U.S.

K&K Audio is now selling the **premier European audio transformers** in the U.S.

High quality C-core transformers and chokes using silicon iron, mumetal, and amorphous cores.

- Power output transformers – SE or PP
- Interstage transformers – SE or PP
- Line output transformers – SE, PP, and parallel feed
- Input transformers – MC or line
- Audio chokes
- Power transformers
- Power supply chokes

High End Audio Kits using Lundahl Transformers

- MC Phono Step-up Unit
- Phono Preamplifier
- Line Stage Preamplifier
- Microphone Preamplifier


For more information on our products and services please contact us at:

www.kandkaudio.com

info@kandkaudio.com voice/fax 919 387-0911

Recone your own Speakers

\$39.95
plus shipping

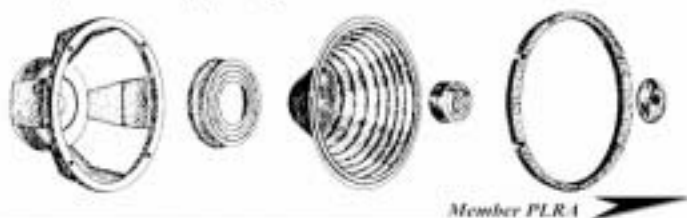

No More Secrets

This is a one hour comprehensive video on speaker reconing designed to make it easy for anyone to fully understand the procedure and even make custom woofers for your system.

This is the way it is done!



You may remember Bill Fitzmaurice as the writer for the audiopress article on Loudspeaker Reconing. The WVS Loudspeaker Reconing Video titled "Foundation of Understanding" has taught thousands how to recone and thanks to Bill, it is now available through this offer. You can have access to the exact same material and over 12,000 recone kits. Everything you need to recone or design your own using thousands of supplies available from WVS. Cones, Voice Coils, Spiders, Dustcaps, Foam and textile surrounds, Adhesives and specialty tools for the reconer. Bill has proven that reconing can be done at home with great success and so should you. Experiment and get customer support second to none in the industry.

WVS

1707 N Harrison St
Ft Wayne Indiana 46808

Phone: 260-424-5463 fax: 422-4133

Order on the web at:

www.recone.com

3. *Subsonic* Filter*: I'll lump this in with subwoofer crossover special requirements, too. A subsonic filter helps you stop torturing your woofer with infrasonic energy, especially with ported, TL, or IB designs.

The folks in car audio are already getting the message. Fourth-order continuously variable sub crossovers are readily available—even some entry-level car amps include this feature (e.g., US-Acoustics USX2050). After you've invested considerable time, money, and effort in your sub system, don't make your sub

crossover the weakest link!

Mark Rumreich
Indianapolis, Ind.

**More and more this term is regarded as an oxymoron. Mark Rumreich uses the proper term in his second sentence of that paragraph.—Ed.*

R. O. Wright responds:

I wish to thank Mr. Rumreich for his comments. They are most timely and go into a much more detailed explanation and appli-

cation of crossovers. G.R. Koonce and I had planned only a basic explanation of crossovers for the article.

DESIGNWARE

While cruising the web, I happened to stumble on a downloadable program that would be of great interest to *audioXpress* readers. It is a loudspeaker-modeling program named WinLsd. This is a very versatile program, which allows you to model sealed, vented, and band-pass designs. It contains a large driver database and has provisions for loading your own driver data. It automatically designs for the flattest response.

One extremely useful feature is the ability to change box tuning and/or box size simply by dragging your mouse. This allows you to see almost instantly how changes affect the speaker response.

A good example of the usefulness of this occurred when I recently modeled a utility speaker for which I wanted to use existing drivers on hand. The box with the flattest response was huge. In almost no time I was able to determine that I could knock off over a quarter of the volume and still have an acceptable response.

This program is available from <http://www.linearteam.dk/>, and is free. There is also now a "pro" version in its alpha state you can try that should be even more advanced. Hats off to the folks at Linear Team for providing such a useful and well-thought-out program at no charge. This is a true labor of love.

I have never used any other modeling program, so I cannot say how it compares to the "name brand" programs. It would make a good article if someone with experience were to make such a comparison.

Bob McHugh
Walker, Mich.

EDITORIAL RESPONSE

I just read your editorial for July '02 and wanted you to know that your child has grown into maturity quite nicely ("On Turning 32," p. 6). It made me realize that Madisound was born in 1972, and we have grown with you. It has been a good journey, and we appreciate all you have done for audio hobbyists over the years.

Larry Hitch
info@madisound.com

Over 2,000 Tube Types for All Applications

RECEIVING • SPECIAL PURPOSE • POWER • INDUSTRIAL • ANTIQUE

★ Highest Quality from the World's Most Popular Manufacturers ★

TYPE	TYPE	TYPE	TYPE
3A3C	6EJ7	12AZ7A	811A
5AR4	6GH8A	12BA6	812A
5R4GY	6GJ7	12BE6	813
5U4G	6HA5	12BH7A	2050/2050A
5Y3GT	6J5	15CW5	5749/5BA6W
6AJ8	6J7	17J2B	5814A
6AL5	6JZ8	30AE3	5881
6AQ5	6K7	33GY7A	5965
6AU6	6SA7	35W4	6146A/B
6AX5GT	6SG7	38HE7	6350
6BA6	6SJ7	50C5	6463
6BE6	6SK7	6267	
6BH6	6SN7GTB	6973	
6BL8	6SQ7	7025A	
6CA4	6U8A	7189A	
6CA7	6X4	7581A	
6CG3	6X5GT	KT88	
6CX8	6X8	2D21/EN91	
6CW5	12AT7	85A2/0G3	
6DL5	12AU6	108C1/0B2	
6DQ6B	12AU7	150C4/0A2	
6DR7	12AV6	572B	
6DX8	12AV7	805	
6EA8	12AX7A	807	
6EH7	12AY7	810	

VOLUME DISCOUNTS

Solid State
Replacements
as low as \$4.00

Write or call for
complete tube
range, price list
and accessories
catalog.



International ©



International Components Corporation

175 Marcus Blvd., Hauppauge, NY 11788 • N.Y. State 631-952-9595 • FAX 631-952-9597

Call TOLL FREE **800-645-9154**

www.icc107.com



CORRECTION

In our October issue we published a "Classic Circuitry" item featuring the Grommes Stereo Preamp, Model 209. We quoted A.A. Hart, who had sent us the diagram in 1985, and incidentally stated that Grommes has turned exclusively to making public address equipment after 1972.

Ironically enough, just at that moment, a rejuvenated and reorganized Grommes Precision was in the final stages of jumping back into the high-

quality audio business. They are very nearly ready to announce their first new tube product, a special limited reissue of their 260A 60W monoblock power amplifier. So we are pleased to correct our old 1985 news by announcing that Grommes Precision is "back." Even better news is that they are considering a later introduction of a kit version of the 260A. We will keep you posted on later developments. Meanwhile, you can look over their offerings at www.grommesprecision.com. ♦

STATEMENT OF OWNERSHIP, MANAGEMENT AND CIRCULATION

(Required by U.S.C. 3685.) Date of filing: Sept. 30, 2002. Title of Publication: AUDIOXPRESS. Publication Number: 0004-7546. Frequency of Issue: Monthly. Annual Subscription Price: \$34.95. Location of the headquarters or general business offices of the publisher: Audio Amateur Inc., PO Box 876, Peterborough, NH 03458-0876.

Publisher: Edward T. Dell, Jr., PO Box 876, Peterborough, NH 03458-0876. Assistant Publisher: Dennis Brisson, PO Box 876, Peterborough, NH 03458-0876. Owner: Audio Amateur Inc., PO Box 876, Peterborough, NH 03458-0876.

Stockholders owning or holding 1 percent or more of the total amount of stock: Edward T. Dell, Jr., PO Box 876, Peterborough, NH 03458-0876. Known bondholders, mortgages or other securities: None.

	Average # copies each issue during preceding 12 months	Single nearest to filing date
Total # copies printed	15,208	14,000
Mailed Subscriptions	8,216	7,567
Sales Through Dealers, Counter Sales and other		
Non-USPS distribution	5,609	5,333
Free Distribution (complimentary)	119	300
Total distribution	13,825	12,900
Copies not distributed	1,265	800
Total	15,208	14,000

I certify that the statements made by me above are correct and complete. Publication number 787-840. Edward T. Dell, Jr., Publisher.

One Groove

Five Signals

PERFECTLY ALIGNED

KAB introduces Groove Tuning™
A new concept that lets you mix the five signals of a mono groove for the best sound possible.

Learn More Online

KAB
Preserving The Sounds Of A Lifetime
www.kabusa.com

SONIC CRAFT

Bringing Loudspeakers and the Hobbyist into the 21st Century

A Proud North American Distributor of

ACCUTON

P.O. Box 9085, Wichita Falls, TX 76308, USA
Phone: (940) 689-9800; Fax: (940) 689-9618; E-mail: mail@soniccraft.com
See us at: www.soniccraft.com

2002 audioXpress Index

Subject

AC-POWER

"The AC Power Line and Audio Equipment, Part 3," Charles Hansen, February, p. 32

AMPLIFIERS

"A Beginner's Push-Pull or Single-Ended Amp," Larry Lisle, January, p. 24
"A PL504 PP Amplifier," Mark Taverniers, January, p. 42
"Zen Variations, Part 1: Zen-lightenment," Nelson Pass, March, p. 8
"Load-Invariant Power Amplifiers, Part 1," Douglas Self, March, p. 28
"A New Class-B Amplifier," Richard Modafferi, April, p. 6
"Load-Invariant Power Amplifiers, Part 2," Douglas Self, April, p. 40
"The ALL-FET Line Amp," Erno Borbely, May, p. 28
"A Practical Circlotron You Can Build," John Stewart, May, p. 34
"A Sensible McIntosh 225 Refurbish," T. D. Yeago, May, p. 52
"A Five-Channel Tube Home Theater Amp," Rick Spencer, June, p. 42
"The Zen Amp Variations, Part 2," Nelson Pass, July, p. 8
"A Marantz 8B Replica," Satoru Kobayashi, July, p. 14
"6B4G Stereo 90 Power Amp," Michael Burrows, August, p. 6
"The Zen Amp Variations, Part 3," Nelson Pass, August, p. 16
"A 6L6G Parallel SE Amp," Mark Weaver, September, p. 24
"A 100W/Channel AB Differential Input Amplifier, Part 1," Norman Thagard, November, p. 6
"Build a Low-Voltage Tube Hybrid Headphone/Line Amp," Pete Millett, November, p. 20
"A 100W/Channel AB Differential Input Amplifier, Part 2," Norman Thagard, December, p. 6
"Zen Variations Part 4: The Penultimate Zen," Nelson Pass, December, p. 16
"6C33C-B Push-Pull Power Amplifier II," Daniel J.F. David, December, p. 40

AUDIO AIDS

"Optimize Second-Order Filter Resistors," Doug Burkett, January, p. 60
"The Self-Balancing Phase Inverter," Michael Kornacker, March, p. 66
"Shishido 300B SE Amp Mod," Ignatius Chen, August, p. 68
"A Grounded Grid Line Stage," Ignatius Chen, October, p. 58
"A Log Control Using a Linear Pot," A. J. van Doorn, November, p. 69

BASS

"e-Bass: An Application of Phase Linear Sub-Bass Equalization," Graham Maynard, March, p. 38
"Bass and the Room," Martin Colloms, October, p. 4

BOOK REVIEWS

Electronic Circuit Action Series—Amplifier Circuits, Charles Hansen, March, p. 57

Audiocraft, Scott Frankland, April, p. 59
The Collector's Vacuum Tube Handbook, Larry Lisle, August, p. 64
Paul Wilbur Klipsch—The Life...The Legend, Richard Honeycutt, September, p. 72
Handbook for Sound Engineers, 3rd Ed., Richard Honeycutt, October, p. 56

CROSSOVERS

"A Passive, Low Level Crossover," Cornelius Morton, November, p. 16
"Design an Active Transient-Perfect Second-Order Crossover," John Kreskovsky, December, p. 36

DRIVER REPORT

"The Scan-Speak 18W/8531G00," Vance Dickason, January, p. 79

DRIVERS

"Dual-Driver Confusion Revisited," G. R. Koonce, August, p. 40

EDUCATION/INFO

"Harmony and Distortion, Part 1," Jean Hiraga, February, p. 26
"Harmony and Distortion, Part 2," Jean Hiraga, March, p. 48

ELECTRONIC TIPS & TECHNIQUES

"Choosing and Using Electronic Parts: A Survival Guide, Part 3," Charles Hansen, January, p. 28

LOUDSPEAKERS

"The Infinite Box Concept, Part 1," G. R. Koonce and R. O. Wright, Jr., January, p. 8
"Building the Adire KIT281 Speaker," Pete Millett, January, p. 34
"The Cadillac 16," Millard Johnson, January, p. 50
"The Ultra Fidelity Computer Sound System, Part 5," R. K. Stonjek, January, p. 54
"Panel Damping Studies: Reducing Loudspeaker Enclosure Vibrations," Jim Moriyasu, February, p. 12
"The Infinite Box Concept, Part 2," G. R. Koonce and R. O. Wright, Jr., February, p. 38
"Building a Highly Analytical Horn System," Louis W. Erath, March, p. 18
"The Infinite Box: Constructing a Subwoofer, Part 1," G. R. Koonce and R. O. Wright, Jr., April, p. 28
"A Trapezoidal Closed 3-Way," S. Batti, April, p. 48
"THOR: A D'Appolito Transmission Line," Joe D'Appolito, May, p. 8
"Listening Critique," Dennis Colin, May, p. 14
"The Infinite Box: Constructing a Subwoofer, Part 2," G. R. Koonce and R. O. Wright, Jr., May, p. 42
"The DR10a," Bill Fitzmaurice, June, p. 16
"A Flared Port Study," Jim Moriyasu, July, p. 28
"Measuring Passive Radiators," David Harris, June, p. 50
"Don't Toss It—Recone It," Bill Fitzmaurice, July, p. 34
"Diffraction Insights," Mithat Konar, July, p. 38
"It's Not Just a Speaker—It's Furniture," Bill

Fitzmaurice, August, p. 22
"Building the THORs," Edward T. Dell, Jr., September, p. 14
"Build Your Own Axisymmetric Tractrix Horn," Robert Roggeveen, September, p. 28
"Subwoofer Placement in Nonrectangular Rooms," Bohdan Raczynski, September, p. 40
"The DR12a Horn," Bill Fitzmaurice, October, p. 22
"The Extreme Subwoofer," Jim Moriyasu, October, p. 36
"A Drum-Head Midrange," Thomas C. Coerver, November, p. 34
"Damping Loudspeakers in Series," Dick Pierce, November, p. 38
"An Against the Wall Speaker," John Mattern, December, p. 24

POWER SUPPLIES

"A Safe Power Supply for Valves," Mike Pany-mo, April, p. 26
"Thagard's Power Supply Revisited," Tom Perazella, December, p. 46

PREAMPLIFIERS

"Big Mike and the Jimmy, Part 1," Paul J. Stamler, February, p. 6
"Big Mike and the Jimmy, Part 2," Paul J. Stamler, March, p. 22
"Big Mike and the Jimmy, Part 3," Paul J. Stamler, April, p. 16
"A Valve Preamplifier, Part 1," G. Haas, June, p. 8
"The Pearl Phono Stage," Wayne Colburn, June, p. 32
"A Valve Preamplifier, Part 2," G. Haas, July, p. 44
"A High-Performance Microphone Preamp," Ron Tipton, October, p. 10
"Updating Borbely's Line Amp," Glenn Wallberg, October, p. 32

PRODUCT REVIEWS

"Adire KIT281," Joseph D'Appolito, January, p. 61
"Listening Critique," Pete Millett, January, p. 63
"Boston Acoustics Home-Theater Loudspeaker System," Joseph D'Appolito, February, p. 46
"Listening Critique," Ken and Julie Ketler, February, p. 48
"RCM Akustik DL5A," Richard Honeycutt, February, p. 54
"The VacuTrace," Charles Hansen, February, p. 56
"The Origin Live Turntable Upgrade Kit," Edward T. Dell, Jr., March, p. 54
"Perpetual Technologies P-1A/P-3A," Gary Galo, April, p. 52
"GW Labs DSP," Gary Galo, May, p. 63
"FM Tuners: NAD and Parasound," Charles Hansen, June, p. 60
"Listening Critique," Nancy and Duncan MacArthur, June, p. 62
"Four ILP Amplifier Modules," Charles Hansen, July, p. 58
"Listening Critique," John and Sandra Schubel, July, p. 63
"Cara® Test Disk," Richard Honeycutt, August, p. 52

"EarMax Pro Tube Headphone Amplifier," Charles Hansen, September, p. 50
 "Listening Critique," Muse Kastanovich, September, p. 52
 "Titanic 10" Subwoofer Listening Critique," Julie and Ken Ketler, September, p. 56
 "Titanic 10" Test Report," Joseph D'Appolito, September, p. 57
 "The KAB Preamp," Gary Galo, October, p. 44
 "DH Labs Cables," Gary Galo, October, p. 54
 "S-5 Electronics K-12M," Charles Hansen, November, p. 47
 "Listening Critique," Duncan and Nancy MacArthur, November, p. 49
 "Vidsonix VCB-100," Kent English and Nelson Pass, November, p. 53
 "Sounds Cylindrical," Gary Galo, November, p. 56
 "Sony SACD Player Modification," Gary Galo, December, p. 55

SOFTWARE REVIEWS

"Wave Repair," Richard Mains, January, p. 66
 "Praxis from Liberty Instruments," Vance Dickason, July, p. 56
 "B2 Spice A/D v4," Tom Harman, August, p. 44
 "Cara® 2.0 Computer-Aided Room Acoustics Software," Richard Honeycutt, August, p. 48

TEST EQUIPMENT

"Universal Test Board for SMT Operational Amplifiers," Fernando Garcia, June, p. 26

TRANSFORMERS

"Moving-Coil Phono Cartridge Transformers," Pete Millett, May, p. 58

TUBES

"Followers: Cathode, Plate, and Others," Norman H. Crowhurst, September, p. 36
 "High g_m Smart Power Tubes, Part 1," Stefano Perugini, November, p. 42
 "Vacuum Tubes Born Again in Nanotube MEMS," R. Colin Johnson, November, p. 46
 "High g_m Smart Power Tubes, Part 2," Stefano Perugini, December, p. 50

MISCELLANEOUS

"FM Stereo Signal Generator," Charles Hansen, March, p. 32
 "A DVD Rescue," Darcy E. Staggs, July, p. 24
 "Relays for Loudspeaker Protection," Charles Hansen, August, p. 30
 "DASP-2002 Digital Audio Signal Processor," T. Giesberts, September, p. 4
 "Would You Take the Stereo?," Nancy MacArthur, September, p. 46
 "Creative Uses for 'A Universal Digital Out'," Ali Elam, October, p. 18
 "Octal to 7-Pin Tube Adapter," Charles Hansen, October, p. 42
 "Tuning in on the AM Band," Carlos E. Bauzá, November, p. 32

Author

BATTI, S.

"A Trapezoidal Closed 3-Way," April, p. 48

BAUZÁ, CARLOS E.

"Tuning in on the AM Band," November, p. 32

BORBELY, ERNO

"The ALL-FET Line Amp," May, p. 28

BURKETT, DOUG

"Optimize Second-Order Filter Resistors (Audio Aid)," January, p. 60

BURROWS, MICHAEL

"6B4G Stereo 90 Power Amp," August, p. 6

CHEN, IGNATIUS

"Shishido 300B SE Amp Mod (Audio Aid)," August, p. 68; "A Grounded Grid Line Stage (Glass Shard)," October, p. 58

COERVER, THOMAS C.

"A Drum-Head Midrange," November, p. 34

COLBURN, WAYNE

"The Pearl Phono Stage," June, p. 32

COLIN, DENNIS

"Listening Critique," May, p. 14

COLLOMS, MARTIN

"Bass and the Room," October, p. 4

CROWHURST, NORMAN H.

"Followers: Cathode, Plate, and Others," September, p. 36

D'APPOLITO, JOSEPH

"Adire KIT281 (Product Review)," January, p. 61; "Boston Acoustics Home-Theater Loudspeaker System (Product Review)," February, p. 46; "THOR: A D'Appolito Transmission Line," May, p. 8; "Titanic 10" Test Report," September, p. 57

DAVID, DANIEL J.F.

"6C33C-B Push-Pull Power Amplifier II," December, p. 40

DELL, EDWARD T., JR.

"The Origin Live Turntable Upgrade Kit (Product Review)," March, p. 54; "Building the THORs," September, p. 14

DICKASON, VANCE

"The Scan-Speak 18W/8531G00 (Driver Report)," January, p. 79; "Praxis from Liberty Instruments (Software Review)," July, p. 56

ELAM, ALI

"Creative Uses for 'A Universal Digital Out'," October, p. 18

ENGLISH, KENT

"Vidsonix VCB-100 (Product Review)," November, p. 53

ERATH, LOUIS W.

"Building a Highly Analytical Horn System," March, p. 18

FITZMAURICE, BILL

"The DR10a," June, p. 16; "Don't Toss It—Recone It," July, p. 34; "It's Not Just a Speaker—It's Furniture," August, p. 22; "The DR12a Horn," October, p. 22

FRANKLAND, SCOTT

Audiocraft (Book Review), April, p. 59

GALO, GARY

"Perpetual Technologies P-1A/P-3A (Product Review)," April, p. 52; "GW Labs DSP (Product Review)," May, p. 63; "The KAB Preamp (Product Review)," October, p. 44; "DH Labs Cables (to page 72)

The British specialists in tube amplifiers and pre-amplifier kits, loudspeaker kits and related publications

Visit our informative website:
www.worldaudiodesign.co.uk
 Enter our HD83 competition on-line



KIT88 integrated amplifier kit



300b PSE monobloc kit



Kel84 integrated amplifier kit



Series II modular pre-amplifier kit

World Audio design

World Audio Publishing Ltd.
 12a Spring Gardens.
 Newport Pagnell.
 Milton Keynes.
 MK16 0EE. England

tel/fax: 00 44 1908 218836
 e-mail: inquiries@worldaudiodesign.co.uk

Classifieds

VENDORS

Headphone amp, SUPER BUFFER, JFETs, MOSFETs
www.borbelyaudio.com

CONCRETE CABINET loudspeakers
www.faradaysound.co.uk
 Self-build instructions available

Principles of Power, tube audio books, kits, FAQ www.londonpower.com.

Repairs and upgrades for audio equipment. Let longtime aX contributor and VTV senior editor Eric Barbour make your system sound better.
 METASONIX, PMB 109, 881 11th St., Lakeport CA 95453, synth@metasonix.com, (707) 263-5343.

The LP track carries both stereo channels vs. alternating pits on the CD. The LP remains superior with "tight coupling for audio," \$15; using an "OTL amplifier circuit," \$35; driving efficient "Bass Horn" plans, \$50. Visa, MC. **STEEN AUDIO LAB**, PO Box 2185, Vancouver, BC V6B 3V7, CANADA.

tubes?
www.tubes.it

DIY HIFI
SUPPLY

www.diyhifisupply.com

Tubes: Valve Art, TJ Meshplate, Sovtek, Svetlana, China milspec NOS

Kits: Billie 300B, Ella KT88, Joplin 2A3, Basie pre, Origin Live turntable kit, DAC

Accessories: XO Clock, S&B transformers, SSC isolation

Parts: Audionote copper and silver caps, Goldpoint, DACT, Seiden, Bullet plugs, Ultra-refined silver wire, SCR, Kiwame, etc

www.diyhifisupply.com
sales@diyhifisupply.com

FINAL LABORATORY

battery-powered amplifiers • cotton dielectric cables
 OARUMA isolation bearings

Imported by Venus Hi-Fi
www.venushifi.com



All types of audio tubes. 300B 6DJ8 ECC81 ECC83 KT88 Mullard GEC Sylvania. Discount for large quantity. Billington UK. Tel (0)1403 784961. Fax (0)1403 783519. Email/website www.bel-tubes.co.uk

AD INDEX

ADVERTISER	PAGE
ACO Pacific Inc	29
Acousti-Soft	3
Adire Audio	58
All Electronics	23
Alpha Electronics Corp of America	45
Amtrans Corporation	57
Antique Radio Classified	43
Audience	58
Audio Amateur Corp.	
<i>audioXpress subscription</i>	71
Classifieds	70
Statement of Ownership	67
Website	71
Audio Advancements.....	21
Audio Consulting	35
Audio Electronic Supply.....	2
Audio Transformers	43
Audiogon.com	23,35,39,54,61
Cascade Audio Engineering	21
Chelmer Valve	41
Classified Audio-Video	7
Creative Sound Solutions	29
Danish Audio Connect	33
DH Labs Audio Cables	47
Dynasonic Ltd	51
E-Speakers	62

ADVERTISER	PAGE
EIFL	17
Electra Print Audio	60
Grennan Audio	64
Hammond Manufacturing	13
Harris Technologies.....	1
Hi Fi Do Inc	37
International Components	66
K&K Audio	65
KAB Electro-Acoustics.....	67
Kimber Kable/WBT-USA.....	CV2
Klein -Tech Systems.....	63
Langrex Supplies.....	19
Liberty Instruments	56
Linear Integrated Systems.....	63
Madisound Speakers.....	59
Marchand Electronics	61
Markertek Video Supply	35
McFeelys	59
Morel (IL)	31
Origin Live	39
Parts Connexion	11
Parts Express Int'l., Inc.	CV4
Pass Laboratories	49
Plitron Manufacturing.....	48
Precision Sound Products	61
Selectronics	64

ADVERTISER	PAGE
Solen, Inc.....	27,45
Sonic Craft.....	67
Sophia Electronics	15
Speaker City USA	49
Swans Speakers	25
Thetubestore.com	53
Tonian Labs	CV3
Usher Audio	9
WBT-USA/ Kimber Kable	CV2
World Audio Design.....	69
WVS	65
Zalytron Industries	55

CLASSIFIEDS

Billington Exports.....	70
Borbely Audio.....	70
DIY HiFi Supply	70
Faraday Sound	70
London Power	70
Metasonix	70
Steen Audio Lab	70
Venus HiFi	70
Vintage Hi-Fi	70

Yard Sale

FOR SALE

Altec 1569A (60W monoblock, 4—EL34), 2 for \$400; Teac 3340S 4-channel/4 track, \$290; Sherwood S8000 IV tube receiver, \$165. Packing/shipping extra. Rad Smith 734-769-2663.

2" x 5" horn piezo tweeters, 50W RMS, 3.5–25kHz response, 92dB SPL. Brand new, large quantity available, \$5 each plus shipping. For details e-mail Chris at HAL84CH@cs.com.

Heathkit AP-1615 preamp, Heathkit AD-1304 Active Audio Processor (dynamic range expander, dynamic hiss filter), Heathkit Audio Control Center AD-1307 (8 AC Sockets, 2 power meters, separate hookups for: 2 amplifiers, 2 sets of speakers, electrostatic headphones, 2 sets of normal headphones). Manuals included. \$100 plus shipping for all. cbest@santa-fe.net.

WANTED

Hobbyist seeking pre-recorded, 2-track reel-to-reel tapes—7.5 or 15 ips. Can be 1950s/1960s commercial product or old studio dubs. Andy Pennella, 203-329-7498 or ajpennella@att.net.

Yard Sale Guidelines

For information on how you can publish your free personal ad in *audioXpress*, visit our web site at www.audioXpress.com.

Classified Information

To find out how you can order an ad for the classified pages, see our web site at www.audioXpress.com.

Visit Our Website!

For More Audio Information,
Check Us Out.

audioXpress.com

BOOKS, BACK ISSUES,
MAGAZINES,
SOFTWARE DEMOS,
BARGAINS &
CLOSEOUTS

or E-mail us at
custserv@audioXpress.com

Audio Amateur, Inc.,
PO Box 876, Peterborough,
NH 03458-0876 USA
Phone: 603-924-9464 w Fax: 603-924-9467



If you've already renewed your subscription, thank you!

IT'S THE END OF 2002, IT'S TIME TO RENEW YOUR SUBSCRIPTION FOR 2003!

Sign up for another great year of projects, reviews, and some of the highest quality audio construction articles available anywhere.

Your renewal is only
**\$29.95 for 1 year or
\$53.95 for 2 years.**

CANADA ADD \$12 PER YEAR.
OVERSEAS RENEWALS: \$54.95,
1 YR; \$105, 2 YRS. REMIT IN
US\$ DRAWN ON A US BANK.

Or save even more and take a 3-year subscription for only
\$76.00! That's a 70% savings off the newsstand price!
OVERSEAS 3-YR RATE: \$147.00.

Call **1-888-924-9465** to renew or e-mail
custserv@audioXpress.com. **DO IT TODAY!**

We accept Mastercard, VISA, Discover, and American Express cards.

audioXpress, PO Box 876 Dept. X2, Peterborough, NH 03458-0876 USA
Phone: 603-924-9464 Fax: 603-924-9467
E-mail: custserv@audioXpress.com

RENEW ON-LINE AT www.audioXpress.com

(Product Review),” October, p. 54; “Sounds Cylindrical (Product Review),” November, p. 56; “Sony SACD Player Modification (Product Review),” December, p. 55

GARCIA, FERNANDO

“Universal Test Board for SMT Operational Amplifiers,” June, p. 26

GIESBERTS, T.

“DASP-2002 Digital Audio Signal Processor,” September, p. 4

HAAS, G.

“A Valve Preamplifier, Part 1,” June, p. 8; “A Valve Preamplifier, Part 2,” July, p. 44

HANSEN, CHARLES

“Choosing and Using Electronic Parts: A Survival Guide, Part 3,” January, p. 28; “The AC Power Line and Audio Equipment, Part 3,” February, p. 32; “The VacuTrace (Product Review),” February, p. 56; “FM Stereo Signal Generator,” March, p. 32; *Electronic Circuit Action Series—Amplifier Circuits* (Book Review), March, p. 57; “FM Tuners: NAD and Parasound (Product Review),” June, p. 60; “Four ILP Amplifier Modules (Product Review),” July, p. 58; “Relays for Loudspeaker Protection,” August, p. 30; “Ear-Max Pro Tube Headphone Amplifier (Product Review),” September, p. 50; “Octal to 7-Pin Tube Adapter,” October, p. 42; “S-5 Electronics K-12M (Product Review),” November, p. 47

HARMAN, TOM

“B2 Spice A/D v4 (Software Review),” August, p. 44

HARRIS, DAVID

“Measuring Passive Radiators,” June, p. 50

HIRAGA, JEAN

“Harmony and Distortion, Part 1,” February, p. 26; “Harmony and Distortion, Part 2,” March, p. 48

HONEYCUTT, RICHARD

“RCM Akustik DLSA (Product Review),” February, p. 54; “Cara® 2.0 Computer-Aided Room Acoustics Software (Software Review),” August, p. 48; “Cara® Test Disk (Product Review),” August, p. 52; *Paul Wilbur Klipsch—The Life...The Legend* (Book Review), September, p. 72; *Handbook for Sound Engineers, 3rd Ed.*, October, p. 56

JOHNSON, MILLARD

“The Cadillac 16,” January, p. 50

JOHNSON, R. COLIN

“Vacuum Tubes Born Again in Nanotube MEMS,” November, p. 46

KASTANOVICH, MUSE

“Listening Critique,” September, p. 52

KETLER, KEN AND JULIE

“Listening Critique,” February, p. 48; “Titanic 10” Subwoofer Listening Critique (Product Review),” September, p. 56

KOBAYASHI, SATORU

“A Marantz 8B Replica,” July, p. 14

KONAR, MITHAT

“Diffraction Insights,” July, p. 38

KOONCE, G. R.

“The Infinite Box Concept, Part 1,” January, p. 8; “The Infinite Box Concept, Part 2,” February, p. 38; “The Infinite Box: Constructing a Subwoofer, Part 1,” April, p. 28; “The Infinite Box: Constructing a Subwoofer, Part 2,” May, p. 42; “Dual-Driver Confusion Revisited,” August, p. 40

KORNACKER, MICHAEL

“The Self-Balancing Phase Inverter (Audio Aid),” March, p. 66

KRESKOVSKY, JOHN

“Design an Active Transient-Perfect Second-Order Crossover,” December, p. 36

LISLE, LARRY

“A Beginner’s Push-Pull or Single-Ended Amp,” January, p. 24; *The Collector’s Vacuum Tube Handbook* (Book Review), August, p. 64

MACARTHUR, NANCY

“Would You Take the Stereo?,” September, p. 46

MACARTHUR, NANCY AND DUNCAN

“Listening Critique,” June, p. 62; “Listening Critique,” November, p. 49

MAINS, RICHARD

“Wave Repair (Software Review),” January, p. 66

MATTERN, JOHN

“An Against the Wall Speaker,” December, p. 24

MAYNARD, GRAHAM

“e-Bass: An Application of Phase Linear Sub-Bass Equalization,” March, p. 38

MILLETT, PETE

“Building the Adire KIT281 Speaker,” January, p. 34; “Listening Critique,” January, p. 63; “Moving-Coil Phono Cartridge Transformers,” May, p. 58; “Build a Low-Voltage Tube Hybrid Headphone/Line Amp,” November, p. 20

MODAFFERI, RICHARD

“A New Class-B Amplifier,” April, p. 6

MORIYASU, JIM

“Panel Damping Studies: Reducing Loudspeaker Enclosure Vibrations,” February, p. 12; “A Flared Port Study,” July, p. 28; “The Extreme Subwoofer,” October, p. 36

MORTON, CORNELIUS

“A Passive, Low Level Crossover,” November, p. 16

PANYMO, MIKE

“A Safe Power Supply for Valves,” April, p. 26

PASS, NELSON

“Zen Variations, Part 1: Zen-lightenment,” March, p. 8; “The Zen Amp Variations, Part 2: The Penultimate Zen’s Current Source,” July, p. 8; “The Zen Amp Variations, Part 3,” August, p. 16; “Vidsonix VCB-100 (Product Review),” November, p. 53; “Zen Variations, Part 4: The Penultimate Zen,” December, p. 16

PERAZELLA, TOM

“Thagard’s Power Supply Revisited,” December, p. 46

PERUGINI, STEFANO

“High g_m Smart Power Tubes, Part 1,” November, p. 42; “High g_m Smart Power Tubes, Part 2,” December, p. 50

PIERCE, DICK

“Damping Loudspeakers in Series,” November, p. 38

RACZYNSKI, BOHDAN

“Subwoofer Placement in Nonrectangular Rooms,” September, p. 40.

ROGGEVEEN, ROBERT

“Build Your Own Axisymmetric Tractrix Horn,” September, p. 28

SCHUBEL, JOHN AND SANDRA

“Listening Critique,” July, p. 63

SELF, DOUGLAS

“Load-Invariant Power Amplifiers, Part 1,” March, p. 28; “Load-Invariant Power Amplifiers, Part 2,” April, p. 40

SPENCER, RICK

“A Five-Channel Tube Home Theater Amp,” June, p. 42

STAGGS, DARCY E.

“A DVD Rescue,” July, p. 24

STAMLER, PAUL J.

“Big Mike and the Jimmy, Part 1,” February, p. 6; “Big Mike and the Jimmy, Part 2,” March, p. 22; “Big Mike and the Jimmy, Part 3,” April, p. 16

STEWART, JOHN

“A Practical Circlotron You Can Build,” May, p. 34

STONJEK, R. K.

“The Ultra Fidelity Computer Sound System, Part 5,” January, p. 54

TAVERNIERS, MARK

“A PL504 PP Amplifier,” January, p. 42

THAGARD, NORMAN

“A 100W/Channel AB Differential Input Amplifier, Part 1,” November, p. 6; “A 100W/Channel AB Differential Input Amplifier, Part 2,” December, p. 6

TIPTON, RON

“A High-Performance Microphone Preamp,” October, p. 10

VAN DOORN, A. J.

“A Log Control Using a Linear Pot (Audio Aid),” November, p. 69

WALLBERG, GLENN

“Updating Borbely’s Line Amp,” October, p. 32

WEAVER, MARK

“A 6L6G Parallel SE Amp,” September, p. 24

WRIGHT, R. O., JR.

“The Infinite Box Concept, Part 1,” January, p. 8; “The Infinite Box Concept, Part 2,” February, p. 38; “The Infinite Box: Constructing a Subwoofer, Part 1,” April, p. 28; “The Infinite Box: Constructing a Subwoofer, Part 2,” May, p. 42

YEAGO, T. D.

“A Sensible McIntosh 225 Refurbish,” May, p. 52