

DISCOVER AN UNLIKELY TUBE POWER SUPPLY

audioXpress

THE AUDIO TECHNOLOGY AUTHORITY

MAY 2003

US \$7.00 Canada \$10.00

Continuing Audio Electronics, Glass Audio & Speaker Builder




A Tube Power Amp
You Can Easily Build

Improving
the Pass/Thagard A75


a TOWERING solution to
LOW FREQUENCIES

Simple
SATELLITES Studies

explore the BENEFITS
of TRANSFORMERS

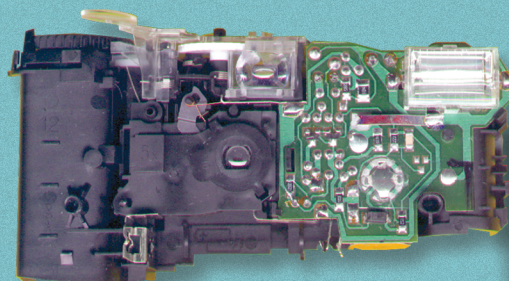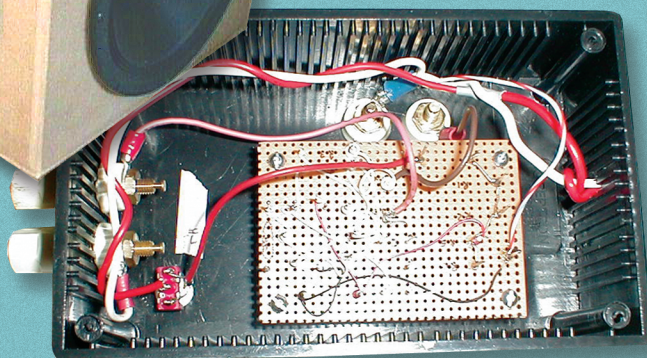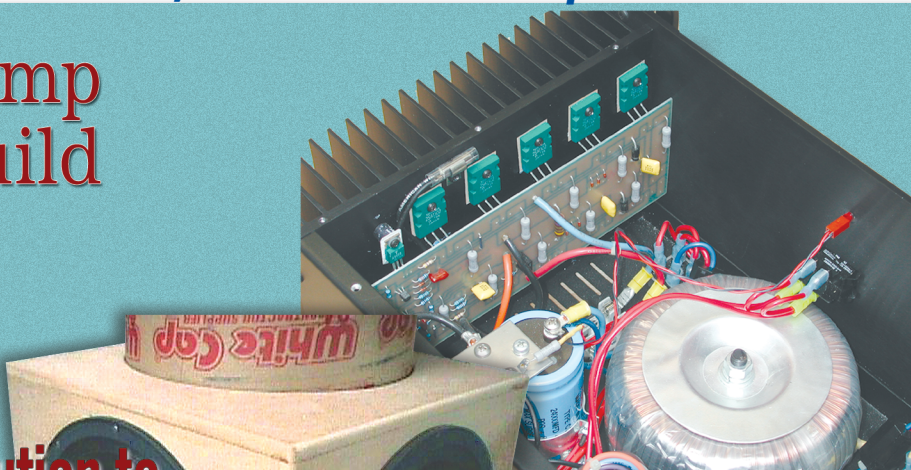


Accurately Measure
Very Low Resistance

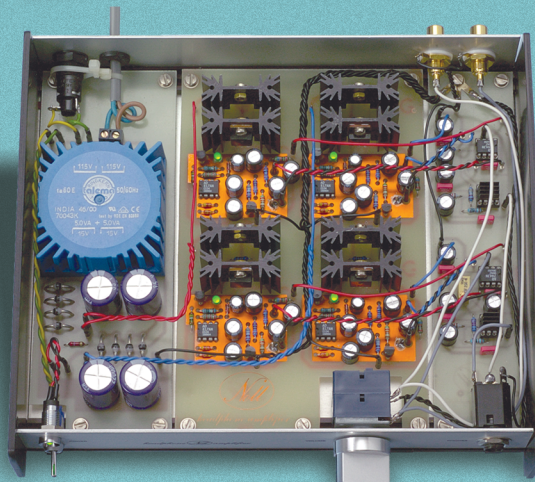

Plus: A First-Class Headphone Amp

www.audioXpress.com

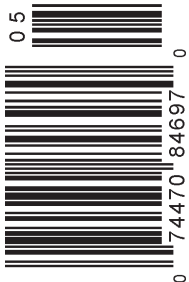

NEW !!

DH LABS

SILVER SONIC

HIGH PERFORMANCE AUDIO CABLES


The Ultimate RCA Connector

DH Labs "High Copper Alloy"

Virtually all of the RCA Connectors used by today's top cable manufacturers are made from brass. There are a number of different brass alloys, generally featuring a combination of copper (around 60%) and varying amounts of zinc, lead, and even tin. The presence of these other metals greatly reduces the manufacturing cost and conductivity of the resulting alloy.

The conductivity of brass alloys is only about 26% that of pure copper. This loss (almost 75%), directly affects the performance of a terminated cable.

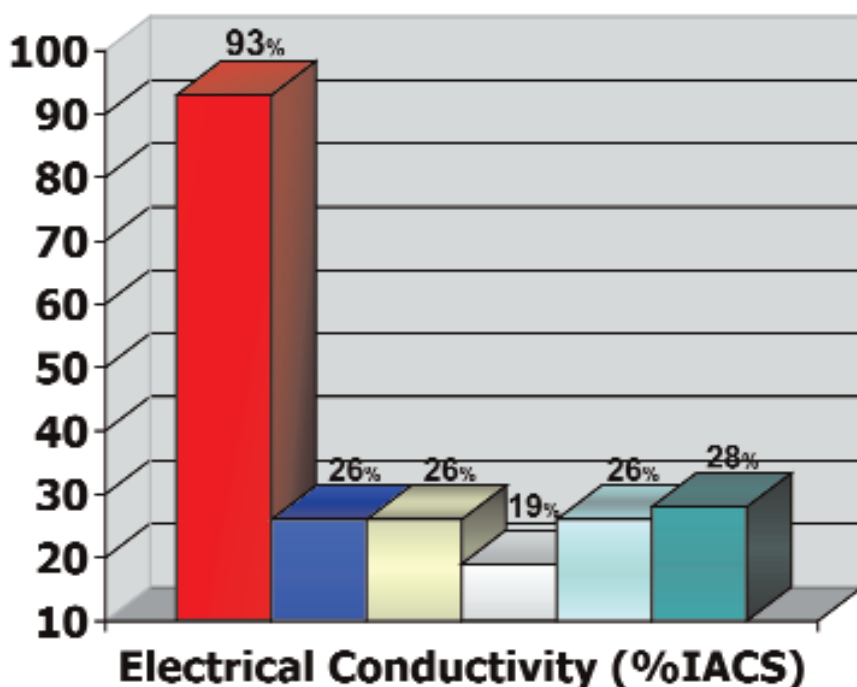Our exclusive "High Copper Alloy"™ material is sourced from the **U.S.A.** for purity, and composed of more than 99% pure copper. Simply stated, this is the finest connector anyone has ever made....



- **DH LABS HC ALLOY -**
Copper Content - 99.3%
- **WBT 101 TOP LINE -**
Copper Content - 68%*
- **VAMPIRE 807 -**
Copper Content - 63%**
- **VAMPIRE 800C -**
Copper Content - 88%**
- **CARDAS SRCA -**
Copper Content - 62%**
- **WBT 147 MID LINE -**
Copper Content - 52%*

*Taken from manufacturer's published data
**Determined by Certified Chemical Analysis

DH LABS

612 N. Orange Ave. #A-2
Jupiter, FL 33458

(561) 745-6406

www.silversonic.com

HC Alloy is a trademark of DH Labs, Inc.

DRIVERS:

- ATC
- AUDAX
- AUDIOTECHNOLOGY
- ETON
- FOSTEX
- ILLUSION AUDIO
- LPG
- MAX FIDELITY
- MOREL
- PEERLESS
- SCAN-SPEAK
- SEAS
- VIFA
- VISATON
- VOLT

COMPONENTS:

SOLEN HEPTA-LITZ AND STANDARD INDUCTORS AND CAPACITORS - THE CHOICE OF MANY HIGH-END SPEAKER MANUFACTURERS.

HARDWARE:

POWER RESISTORS, L-PADS, CABLE, ABSORBING AND DAMPING MATERIALS, GOLD SPEAKER TERMINALS, GOLD BANANA PLUGS AND BINDING POSTS, GRILL FASTENERS, PORT TUBES AND TRIM RINGS, PAN HEAD SCREWS, SPIKES AND TEE NUTS WITH ALLEN HEAD BOLTS AND PLENTY MORE...

CUSTOM
COMPUTER AIDED
CROSSOVER AND
CABINET DESIGN

HOW TO BOOKS

The Process of Design.



When designing a loudspeaker, the initial driver considerations and final driver choice can make or break a project. To ensure your success - you want the most complete information and specifications at your finger tips - the Solen catalog.

Order the **FREE** Solen catalog and CD - containing a wide selection of quality drivers - with complete manufacturer's spec sheets, as well as applications in detail on woofers, with predicted response in different sealed and vented enclosures. It is a valuable resource that will bring out the possibilities in your designs.

Order the **FREE** Solen CD Catalog.

Forward your request by phone, fax, mail or email - or fill in the online request form at solen.ca.



Name:	_____
Address:	_____ _____ _____
State/Prov:	_____
Zip/Postal Code:	_____
Country:	_____
Tel:	_____
Email:	_____



SOLEN INC.

4470 Avenue Thibault
St-Hubert, QC J3Y 7T9
Canada


Tel: 450.656.2759

Fax: 450.443.4949

Email: solen@solen.ca

Web: <http://www.solen.ca>

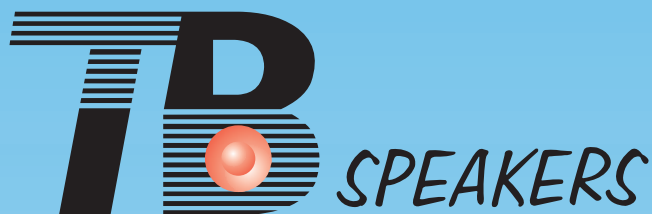Parts Express is a U.S. distributor of Tang Band drivers.



Tang Band Drivers Feature:

- ◆ Santoprene rubber surrounds maintain consistent, long-term performance
- ◆ Flat, heavily convoluted spiders allow a uniform motion in both the positive and negative stroke, reducing odd-order distortions.
- ◆ Venting under the spider reduces heat build up and power compression.
- ◆ Heavy-duty frames minimize resonance and result in a cosmetically attractive speaker.
- ◆ Magnetically shielded motor structures can be used in home theater & multimedia applications
- ◆ Underhung design in 3" models, resulting in low distortion, good bass response, and extended high-frequency reproduction.
- ◆ Extremely wide frequency response simplifies crossover design and enables use as full-range drivers.
- ◆ Ferrofluid enhanced tweeters exhibit superior mechanical damping at resonance, reducing harshness and improving heat extraction from the voice coil.




TB drivers are unique in incorporating many advanced features not found on most low-cost drivers. Their forte' is small, extended range drive units capable of covering very wide portions of the audio spectrum. In situations where a low-cost, high-performance driver is needed, Tang Band should be the first name to consider.

Check us out on the web for our full line of TB drivers as well as many other products, great daily deals, tech talk, and much more.



Part No. #264-820

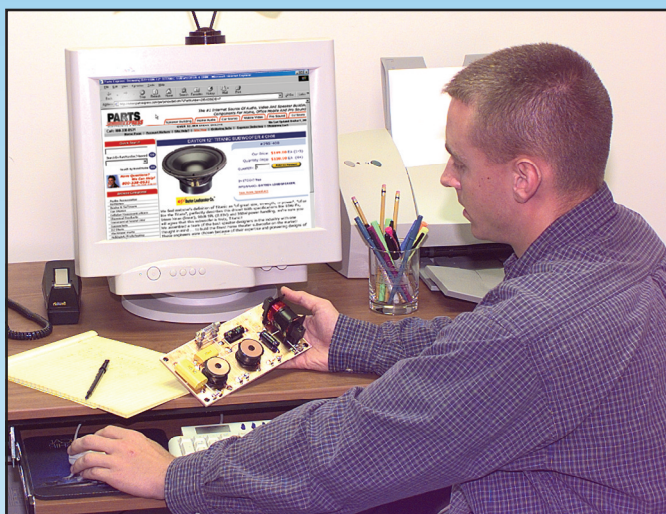

Part No. #264-818

www.partsexpress.com **1-800-338-0531**



**FREE CATALOG
GET YOURS ONLINE
TODAY!**

SOURCE CODE: AXM



The SPP Amplifier

Here's a long-forgotten, but still high-quality, power amp design that's easy to build, requiring no esoteric tubes or parts. **By Helmut Otte**

In the early '50s, Philips Europe began to equip some radios, TV sets, and hi-fi amplifiers with a so-called ironless power amplifier, a kind of SPP (series push-pull) with specially developed low-ohmic tubes and speakers of 200–800Ω, such as the famous 9710A and its derivatives. Depending on the kind of circuit used, the whole amplifier could become quite simple. Sophisticated design and the lack of an output transformer led to very good results—i.e., low distortion and wide bandwidth.

THE CIRCUITS

This kind of amplifier first appeared in a Philips high-end radio in 1955. This very asymmetrical circuit looks like the well-known SRPP with the upper pentode connected as a triode. The radio contained two of these amplifiers—one for the low frequencies and one for the high frequencies, feeding a total of four speakers (*Fig. 1*). It produced a fantastic sound.

About a year later, the low-ohmic EL86/6CW5 became available; it was better suited for the task, and the circuit changed to a more symmetrical one. The screen grids were supplied via resistors and coupled to their corresponding cathodes via capacitors. Output power was about 3–4W (*Fig. 2*).

The next step was to drive the grids of

both tubes separately, increasing the output power and—with the help of a bootstrap—the symmetry, too. A phase splitter delivers the out-of-phase voltages. Because the upper pentode works as a voltage follower, it needs a high input voltage. A bootstrap configuration via CB feeds the grid with the correct voltage (*Fig. 3*).

THE FINAL CIRCUIT

This section describes one of the SPP amplifiers I have built. I chose this circuit because no special parts are needed, and you can expect very good results. The circuit is simple and even a newcomer should be able to build it with success. The design is very flexible and suitable for all low-ohmic pentodes. There is no need for very high power-supply voltages (I dislike voltages of more than 350V).

To get as much power as possible the screen grids should be fed with voltages as high as the plate voltages from separate voltage sources, but this leads to a more complicated and expensive power supply. The tube manufacturer Valvo (a Philips division) developed a great idea to avoid this. In that circuit they replaced the screen grid resistors with chokes. The inductance of the chokes should be high—at least about 20H, the more the better. Normally these chokes will be mechanically large because there is a DC current—the screen grid current—flowing through them, and therefore they need a gap, enlarging the size to get a high inductance.

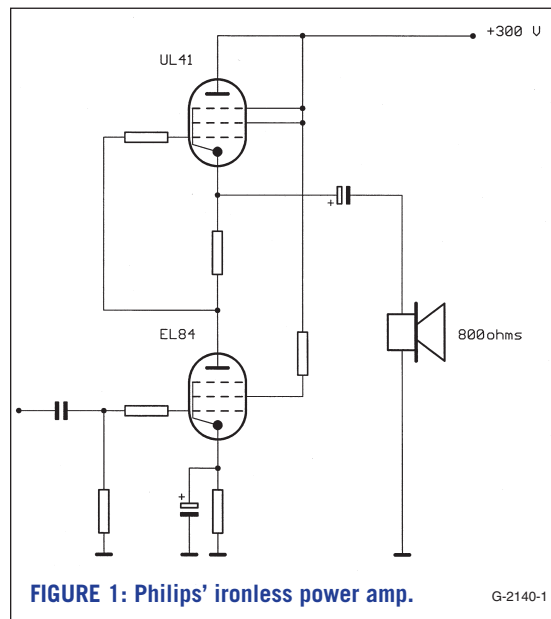


FIGURE 1: Philips' ironless power amp.

G-2140-1

The published elegant solution is to use a double choke and connect the windings in reverse so the magnetic effect of the DC currents is cancelled out. Now no gap is necessary, the choke dimensions may be smaller, and you have only one part. I used a simple small toroidal mains transformer with two identical high-voltage windings (i.e., 115V/115V) for this task. The quality is sufficient.

As mentioned previously, the upper pentode V3 acts as a voltage follower with a little less than unity gain and therefore needs a very high control voltage at the grid. A normal-connected phase splitter cannot deliver such a high voltage, but with the help of positive feedback (bootstrap) from the screen grid, the problem is solved by carrying high DC voltage and the output signal to the plate resistor R8 of the phase splitter tube. Without negative feedback significant distortion occurs long before full output power is reached. A NFB path from the output to the cathode of the first triode system via resistor R15 keeps distortion low. The value of R15 influences input sensitivity.

ABOUT THE AUTHOR

Born in 1948, Helmut Otte learned about electronics while working for the Philips Service Hamburg from 1964–1968. Afterwards, he studied electrotechnics, obtained a “Diplom-Ingenieur,” and since that time has worked at the University Of Applied Sciences Hamburg. His interests include listening to and making music (on bass guitar), as well as travelling and photography.

123


THREE LAYER PLATING

- Oxygen Free Copper plating - improves conductivity.
- Electroless Nickel plating - necessary to prevent the leeching of the copper through the gold layers.
- 24 k Gold plating - improves conductivity and prevents corrosion.



WATTGATE™

801-621-1501 • www.wattgate.com

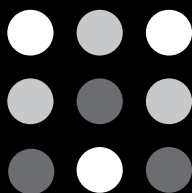

THE ART OF CONNECTION



WBT®
THE ART OF CONNECTION

- Small plugs are required for many HiFi gadgets. That's why we need small works of art such as the WBT-0147.
- Mini RCA plug WBT-0147 with patented collet chucking device, slotted centre pin, and Torx strain relief.

- And what about the soldering of the cable? The Mini WBT-0147 enables it in an unbelievably comfortable way.

WBT-0147...
A perfect solution.

801-621-1500 • www.wbtusa.com

With a value of 47k the input voltage for full power output is 1.6V. A higher value increases the input sensitivity, but distortion will also increase. Symmetry is adjusted with potentiometer P1 until you have about half of the supply voltage at the cathode of V3. A better way to adjust symmetry is watching the output voltage at full power with an oscilloscope until the signal doesn't clip only at one side.

The recommended load for an amplifier with these tubes is 800Ω. Nowadays speakers with this impedance are scarce. But you can use normal speak-




ers with impedances of 4–8Ω if you use an audio line matching transformer, which is available in very good qualities for only a fraction of the money you must spend for tube audio transformers. The low turn ratio and the low impedances yield a wide bandwidth and low losses. You can even build such a transformer yourself.

Output power of the amplifier with the values shown in Fig. 4 is nearly 8W before clipping. Depending on the amount of NFB, the output impedance is about 100Ω, causing a good damping factor for the speaker. Distortion at

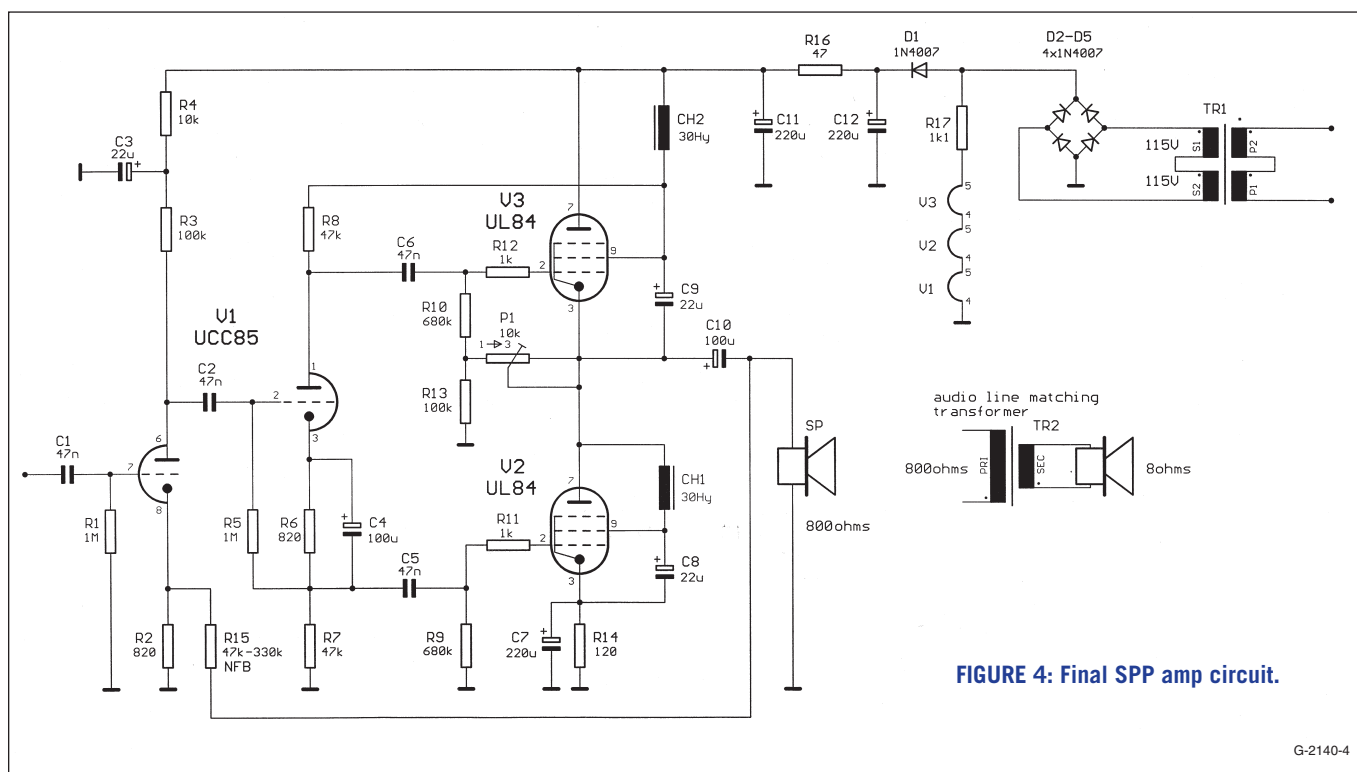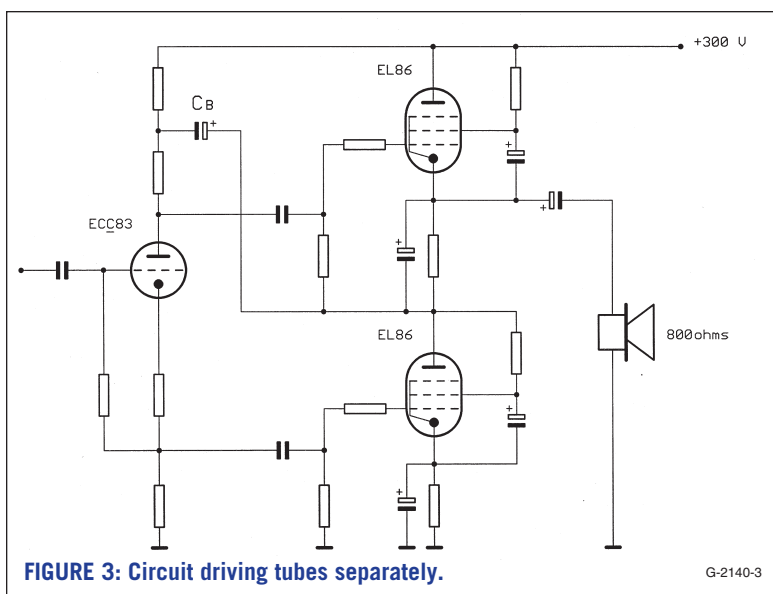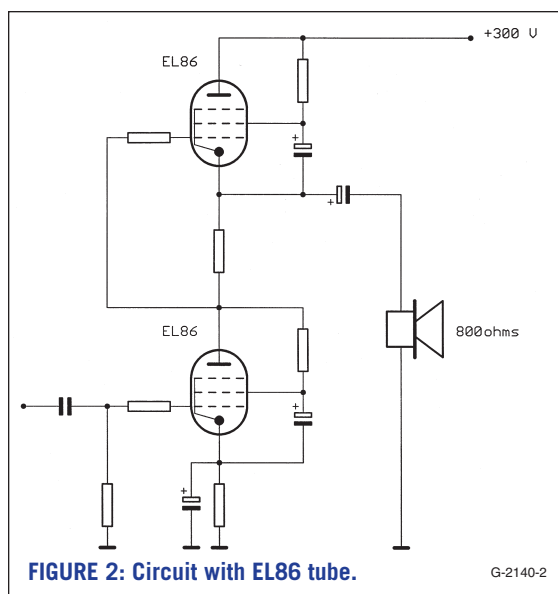7.5W is below 0.5%. Bandwidth exceeds 100kHz.

The power supply is very simple. Because I used series-heated tubes, there is no need for an extra heater winding on the mains transformer. The transformer itself is a simple 1:1 transformer with sufficient power to feed the circuit and the heaters.

The diode D1 decouples the heater string from the filter capacitors C11 and C12, and the heaters are supplied with the unfiltered voltage from the bridge rectifier. This voltage is 230V instead of 320V at C12. With D1 the volt-



We make parts for
our cables,
our OEMs,
and you...

Colorado
Welborne Labs
Full line parts dealer
971 E. Garden Dr
Littleton, CO 80126
Phone 303 470 6585

Illinois
Music Direct
Full line parts dealer
318 North Laflin St
Chicago, IL 60607
Phone 312 433 0200
www.musicdirect.com

California
Michael Percy Audio
11731 Stillwater Creek Rd
Nevada City, CA 95959
Phone 530 470 8650
www.percyaudio.com

Michigan
Audio Advisor
4717 Broadmoor, SE
Suite A
Kentwood, MI 49512
Phone 800 942 0220
www.audioadvisor.com

Washington
DIY Cable
153 Mountain Home Rd
Port Angeles, WA 98362
Phone 360 452 9373
www.diycable.com

Canada
Parts Connexion
2885 Sherwood Heights Dr
Oakville, Ontario L6J7H1
Phone 905 681 6902
www.partsconnexion.com

Singapore
Musiclink AV Distribution
66 Tannery Lane #03-10A
Sindo Building
Singapore 347805
Phone 65 8421142
turboc@pacifichet.sg

More information at
www.cardas.com



CARDAS



age drop at R17 is much lower and therefore power losses are lower.

MODIFICATION

You can easily modify the circuit—i.e., use tubes with a 6.3V heater such as 6CW5 for the output and 12AX7 for the driver stage. Only a slight change in the values of the cathode resistors R2, R6, and R14 will be necessary, and you need an additional heater winding on the mains transformer. Be careful with the value of R14, and don't exceed the maximum plate power of V2 and V3!

You could make another modification in the driver stage by using a long-tailed phase splitter, which should

TABLE 1
SOME SUITABLE TUBES

6.3V HEATER	SAME SYSTEM, DIFFERENT HEATER
EL81/6CJ6	PL81/21A6
EL86/6CW5	PL84/15CW5
	UL84/45B5
EL504	PL504/(28GB5)
EL508	PL508/17KW6
EL509/6KG6	PL509/40KG6
EL519	PL519
E130L	
E235L	

PARTS LIST

R1, R5	1M
R2, R6	820
R3, R13	100k
R4	10k
R7, R8	47k
R9, R10	680k
R11, R12	1k
R13	100k
R14	120
R15	47k-330k
R16	47 1W
R17	1k1 18W
P1	10k
C1, C2	47nF/400V
C5, C6	
C3, C8, C9	22μF/350V
C4	100μF/16V
C7	220μF/16V
C10	100μF/350V
C11, C12	220μF/350V
D1, D2, D3	1N4007
D4, D5	
V1	UCC85 Valvo, Telefunken, Siemens
V2, V3	UL84 Valvo, Telefunken, Siemens
CH1, CH2	Double-choke, see text
TR1	120VA, pri 2 × 115V, sec 2 × 115V
TR2	50VA, pri 800Ω, sec 4/8/16Ω
SP	Speaker 800Ω 9710A Philips or similar

work fine, too. You can increase output power using higher power tubes such as the 6KG6/EL509. Paralleling output tubes will also increase output power even further.

TUBES

For this amplifier concept I chose series-heated tubes for simplicity of the power supply. Most TV sweep pentodes are also a good choice, and there are many of them available for reasonable prices. One of the most powerful in current production by Svetlana, the EL509, will increase output power to about 30W with a load of 150–200Ω in this circuit. Another—perhaps the best but most expensive tube—is the E130L. And there are others. Table 1 shows a list with some recommended tubes. ♦

REFERENCES

VALVO-Handbuch Rundfunk-und Fernsehrohren 1957
VALVO-Handbuch Spezialrohren 1961
VALVO-Brief 6, Dezember 1959
VALVO-Brief 4, August 1961
Philips Service Circuit, Saturn 653/4E/3D
Philips Service Circuit, AG 9017
Svetlana (www.svetlana.com)
Winfried Knobloch, Röhrentechnik ganz modern, Pflaum Verlag München, ISBN 3-7905-0580-3

Products from Jensen Transformers

CATV GROUND ISOLATOR

Breaks CATV or Antenna "Ground Loops"

- Extremely high isolation eliminates 60Hz ground currents
- Low insertion loss maintains maximum signal to noise ratio



These transformer-based isolators prevent ground currents when connected between standard 75Ω CATV/antenna and TV/FM receiver. If not stopped, these currents often flow through other system equipment and interconnect cables, resulting in hum or buzz in sound systems or "hum bars" in video displays. Shipping wt: 1 lb.

For standard 75Ω CATV **PJ-VR1FF**\$51.95
For digital cable or cable modem **PJ-VRD1FF**\$59.95

Audio Ground Isolator

Stops Hum and Buzz in Unbalanced Interfaces

- Eliminates the inherent ground noise coupling mechanism

When used in unbalanced audio consumer interfaces, the dual channel isolator not only eliminates hum and buzz but also enhances audio quality by reducing "spectral contamination" due to ultrasonic and RF interference; the low frequency audio isolator provides unparalleled low frequency response while providing over 100dB of common mode isolation. Shipping wt: 1 lb. per unit.




Dual channel audio isolator **PJ-CL2RR**\$177.95
Low frequency audio isolator **PJ-SUB1RR**\$114.95

VIDEO ISOLATION TRANSFORMER

For 75Ω Systems

- Very high ground isolation: 120dB CMRR typ at 60Hz
- Low insertion loss: 0.55 dB typical

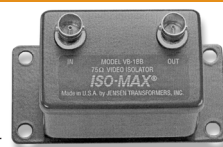When inserted into standard 75Ω video cabling, this transformer-based isolator eliminates video "hum bars," as well as the often associated audio hum or buzz in multimedia entertainment systems, by breaking the so-called "ground loop." Mounting holes allow easy horizontal or vertical mounting to standard rack rails. Shipping wt: 1 lb.



PJ-VB1BB\$104.95
BNC to RCA adapters for the Video Isolation Transformer (pair)\$5.00

MOVING COIL CARTRIDGE STEP-UP TRANSFORMERS

1:37 TURNS RATIO **PJ-JT34DX**\$104.95 Shipping wt: 1 lb.
1:10 TURNS RATIO **PJ-JT44DX**\$104.95 Shipping wt: 1 lb.

Call 1-888-924-9465

OR CHECK OUT JENSEN TRANSFORMERS PRODUCTS ON-LINE AT:
www.audioXpress.com/bksprods/equipindex.htm

Old Colony Sound Laboratory, PO Box 876
Dept. X3, Peterborough, NH 03458-0876 USA
Phone: 603-924-9464 Fax: 603-924-9467
E-mail: custserv@audioXpress.com



Over the Top

Music performance and craftsmanship that exceed your expectation in every way

Compass DANCER SERIES

Compass DANCER SERIES DESIGN HIGHLIGHTS:

- Carbon-paper woofer cone
- Silk-fabric soft dome tweeter; Ceramic type on some models
- Innovative magnet flux design with corrective cooper elements on all drivers, resulting in significantly reduced third and second harmonic distortions
- Cast aluminum driver frame
- Hand picked, matched-pair drivers on all models
- Phase coherent crossover designed by world renown master of speaker design, built with components of the highest quality and thoroughly tested with digital-based measuring equipment
- Massive, sonically dead front baffle which places drivers in a time-coherent physical arrangement
- Multi-chamber reinforced cabinet with solid wood side panels, handcrafted to the highest furniture grade



Behind the Scene

Dr. Joseph D'Appolito has been working as consultant for Usher Audio since early 2000. A world renown authority in audio and acoustics, Dr. D'Appolito holds BEE, SMEE, EE and Ph.D. degrees from RPI, MIT and the University of Massachusetts, and has published over 30 journal and conference papers. His most popular and influential brain child, however, has to be the MTM loudspeaker geometry, commonly known as the "D'Appolito Configuration," which is now used by dozens of manufacturers throughout Europe and North America.

Dr. D'Appolito designs crossover, specifies cabinet design, and tests prototype drivers for Usher Audio, all from his private lab in Boulder, Colorado. Although consulting to a couple of other companies, Dr. D'Appolito especially enjoys working with Usher Audio and always finds the tremendous value Usher Audio products represent a delightful surprise in today's High End audio world.

With an abundance of original concepts in loudspeaker design, backed by thirty years experience in manufacturing and matched with an eye for fashion and unparalleled attention to detail, is USHER the ideal original design manufacturer you've always been looking for? Find out the answer today by talking to an USHER representative.

USHER

USHER AUDIO TECHNOLOGY

67, Kai-Fong Street, Sec.1, Taipei 100, Taiwan

Tel: 886 2 23816299 Fax: 886 2 23711053

Web site: www.usheraudio.com E-mail: usher@ms11.hinet.net

A MOSFET Update of the Forte 1a Amplifier, Part 1

A simplified version of the Pass/Thagard A75 serves as an update for the Forte 1a amplifier. **By Joe Berry**

Since it first appeared back in 1992,^{1,2} the Pass/Thagard A75 amplifier has proven both a popular and a flexible project, with numerous and varied examples from around the world featured both here and on the Pass Labs website (www.passlabs.com). This article further demonstrates the versatility of the A75 by showing how you can adapt the design for use as an update to existing hardware. The hardware in this case is the Forte Model 1a, a 50W stereo Class A power amplifier whose original gain topology was also designed by Nelson Pass, but reflects an earlier design approach using a cascoded biFET voltage gain section feeding a Darlington BJT output stage.

This modification, which I've termed the Forte 1b, is guided by the requirement that it be fully reversible so that you can return the amplifier to stock condition if desired. In practice, this means that the basic update consists

simply of replacing the Forte 1a's heatsink-mounted PC board assemblies (Photo 1). To meet this constraint, I modified the A75 circuit for complete compatibility with the Forte 1a's existing physical layout, power supply, fusing, and thermal protection schemes.

It follows that the resulting amplifier is less powerful than the A75 and does without one or two of its refinements. However, the Forte 1b does preserve the A75's basic all-MOSFET approach, and still offers you a choice between local and global negative feedback, and between two-stage versus partial folded-cascode operation of the front end. Perhaps most importantly, the Forte 1b offers a different subjective experience from the 1a, and one that listeners may prefer.

POWER-SUPPLY CHANGES

The original A75 circuit (Fig. 1) operates from two split DC power supplies—an unregulated $\pm 40V$ for the output

stage and a regulated $\pm 50V$ for the “front end” or voltage gain section. Elevating the front end supply by 10V makes up for about 5V of output voltage swing lost through the HEXFET follower output stage, and another 5V lost through the cascoded second stage. This enables the A75 front end to swing the output to within a few volts of the unregulated supply rails, achieving a 75W output into 8 Ω .

By contrast, the FET/bipolar circuit of the Forte 1a (Fig. 2) works from a simple unregulated $\pm 36V$ DC power supply. The reduced voltage losses associated with the bipolar transistors in the Forte 1a allow the circuit to swing the output to within 4V or so of the supply rail without the need for a separate elevated front-end supply. Working from this power supply, the Forte 1a easily met its 50W (28.3V peak) 8 Ω continuous power rating.

Simply operating the unmodified A75 from such a supply would result in a maximum continuous 8 Ω output of some 35W, about 40% less than the Forte 1a's original power rating. This was a bit more loss than I could accept, so I removed the cascodes from the A75's second voltage-gain stage to reclaim about

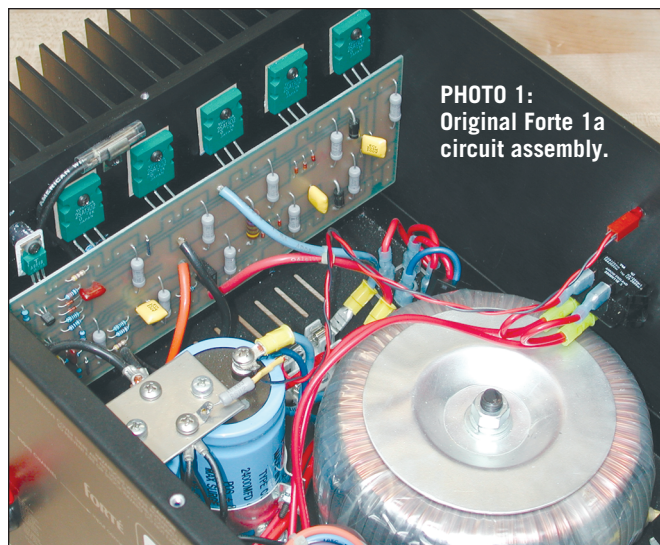


PHOTO 1:
Original Forte 1a
circuit assembly.

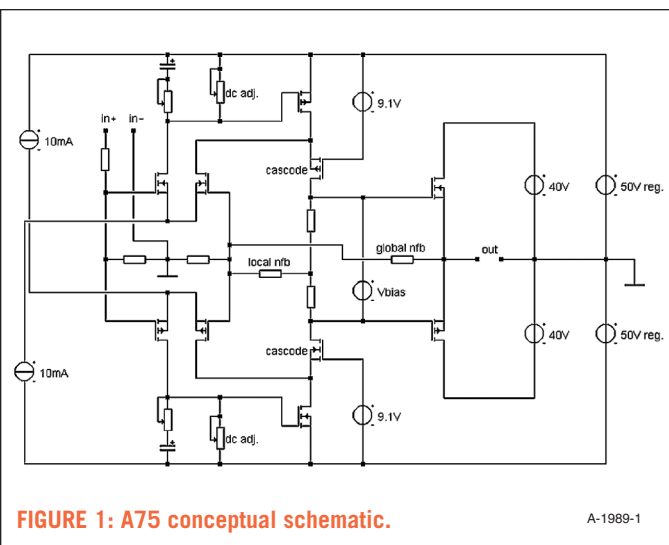



FIGURE 1: A75 conceptual schematic.

A-1989-1

HI-VI RESEARCH®
you can hear the difference

The new *compact* drivers

full range and midrange woofers

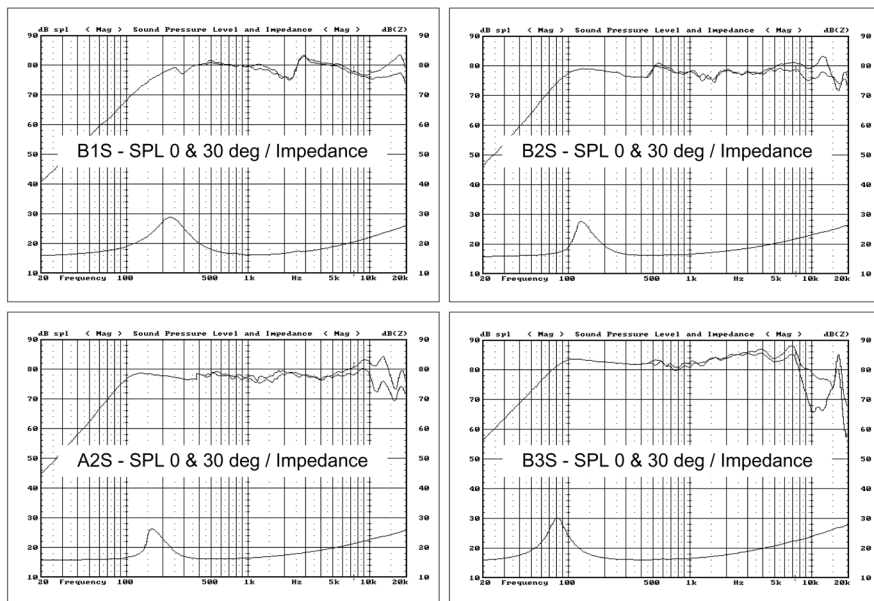

B1S



A2S



B2S



B3S

- ^ Aluminum-magnesium cone — an improvement over pure aluminum cone technology
- ^ 100% shielded magnet system - home theater/computer ready
- ^ Optimized T/S parameters for more flexible cabinet design



www.swanspeaker.com
www.dulcet.com

Distributed by
Parts Express
Tel: 1-800-338-0531
www.partsexpress.com

Hi-Vi RESEARCH(USA)

Swans Speaker Systems, Inc. 2550 Corporate Place, Suite C-103, Monterey Park, CA 91754 USA Tel: (323)-881-0606 Fax: (323)-881-0957 e-mail: jannie@swanspeaker.com

Hi-Vi RESEARCH(HongKong)

Hongo (Holdings) Ltd. Flat 1709, China Merchants Tower, Shun Tak Centre, 168-200 Connaught Road, Sheung Wan, Hong Kong Tel: (852)2587-8728 Fax: (852)2587-8768 e-mail: hongo@netvigator.com

Hi-Vi RESEARCH(China)

Hi-Vi RESEARCH ELECTRONIC CO.,LTD. FuXing Building, 21st / FL, East Tower, 163 HuangPu Ave, GuangZhou, Guangdong, China Tel: 86-20-34919808 Fax: 86-20-85201260 e-mail: yao@dulcet.com

©2002 Swans Speaker Systems, Inc. Hi-Vi RESEARCH and the Swan logo are registered trademark of Swans Speaker Systems, Inc. or its subsidiaries in the United State and other countries. All right reserved

5V of output swing. Thus modified, and working from the stock Forte 1a power supply, the new circuit just meets the Forte 1a's original 50W power rating.

CIRCUIT CHANGES

The conceptual schematic of Fig. 3 provides an overview of the Forte 1b circuit topology. The prototype circuit was prone to high-frequency oscillation unless the second stage was operated in its optional partial folded-cascode mode.

To allow for stable operation without the folded cascode, I added source degeneration resistors to each of the four

input stage MOSFETs. I treat these options (source resistors versus folded cascode) as mutually exclusive because the source resistors are needed only if you omit the partial folded-cascode option. Using both options together would reduce open-loop gain beyond the point needed for stability, and may audibly increase noise and distortion.

I also made a number of component-value changes to better match the circuit to the Forte 1a environment. For example, the heatsink was already drilled for ten plastic TO-3 power transistors, so I used physically similar TO-247 plastic HEXFETs in place of the

metal TO-3 devices originally specified for the A75. Likewise, I removed the option of balanced input from the circuit because there is no balanced input jack on the Forte 1a rear panel.

In addition, I adjusted the values in the feedback network to give the Forte 1b the same closed-loop gain of 20 (26dB) as the Forte 1a. Finally, because the A75's unbalanced input impedance value of 75k Ω seemed higher than necessary, I reduced it to 23k Ω for reduced high-frequency distortion. This new value is still high enough to present no problems for most preamplifiers.

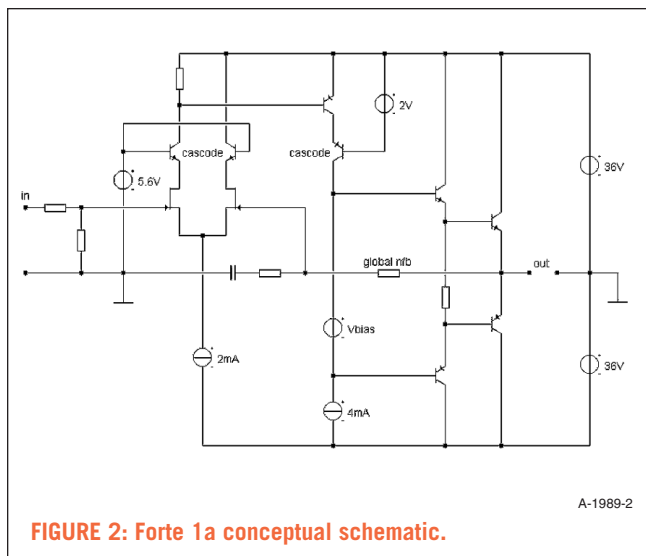


FIGURE 2: Forte 1a conceptual schematic.

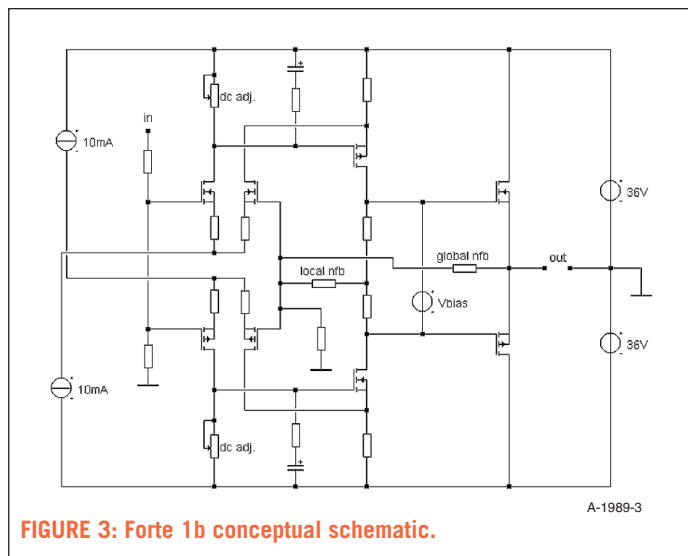


FIGURE 3: Forte 1b conceptual schematic.

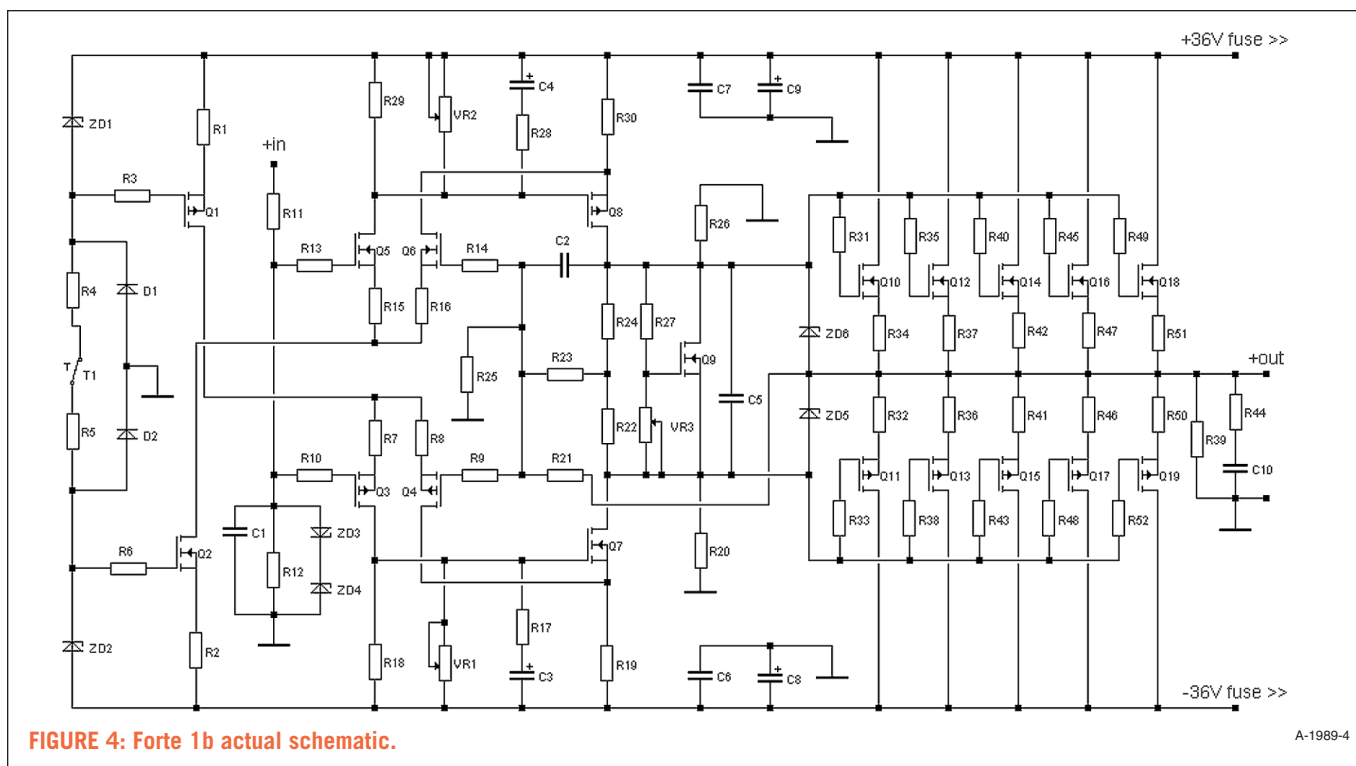


FIGURE 4: Forte 1b actual schematic.

THE CIRCUIT IN DETAIL

Figure 4 shows the actual schematic of the Forte 1b. Starting at the left, complementary MOSFETs Q1 and Q2 and associated components form the constant-current sources that bias the input stage. Current flowing through zener diode ZD1 sets up a constant 9.1V DC reference voltage at the gate of Q1, causing a constant current of about

$$(9.1 - 4)/R1 = 5.1/511 = 10\text{mA}$$

to flow in Q1. Likewise, Q2 and its associated components provide about 10mA of operating current for the N-channel half of the input stage. Gate resistors R3 and R6 suppress parasitic oscillations in these MOSFETs.

The series combination of ZD1, ZD2, R4, R5, and normally-closed thermal cutout T1 form a current path between the +36V and -36V rails. In normal operation, the current flowing through this path activates Q1 and Q2, and by extension, the circuit as a whole. If T1 or either of the two DC rail fuses (external to the circuit) opens, Q1 and Q2 both deactivate, shutting down the amplifier. In the event of a single DC rail fuse failure, clamping diodes D1 and D2 will ensure a hard shutdown of both Q1 and Q2 to prevent significant DC offset voltage from appearing at the amplifier output.

The complementary differential input stage consists of P-channel MOSFETs Q3 and Q4, N-channel MOSFETs Q5 and Q6, and associated components. Q3-Q4 and Q5-Q6 are matched pairs³ for improved current sharing and DC offset stability. The input signal is conditioned by a network consisting of R11, R12, C1, ZD3, and ZD4. R11 and C1 form a 4MHz low-pass filter, shunting RFI to ground at the input.

The series combination of R11-R12

sets the input impedance of the amplifier at about 23k Ω , high enough to prevent problems with most preamplifiers, but low enough to avoid excessive HF distortion and instability. Series zeners ZD3-ZD4 clamp the input to protect the input MOSFETs from excessive gate voltage.

The conditioned input signal is presented to the gates of Q3-Q5, while negative feedback from either the second stage or the output stage (or both) is presented to the gates of Q4-Q6. (Note that Q3-Q6 are also equipped with gate resistors to suppress parasitic oscilla-

tions.) If you install R23, feedback comes from the second stage, whereas if you use R21, feedback comes from the output stage. With both R21 and R23 installed, feedback from the second stage and output stage are combined, and the amplifier's closed-loop gain will drop by 6dB unless you change R21 and R23 from 22.1k Ω to 43.2k Ω each. As in the original A75, you can also use different values for R21 and R23 to mix the feedback in different proportions, if desired.

Optional source degeneration resistors R7-R8 and R15-R16 are installed



DRIVERS
SPEAKER KITS
ASSEMBLED SPEAKERS
AMPLIFIERS
DSP CONTROLLERS
CUSTOM SERVICES

Featured Product **B&C 8CX21**



Dual Concentric
Compression
Driver

High Resolution

High Sensitivity

Ideal for
Single
Ended Triode

www.emeraldphysics.com

ABOUT THE AUTHOR

Joe Berry is a long-time audio and radio enthusiast whose study of electronics began, as it did with many others, by reading the Alfred Morgan books in his grade-school library. Joe worked as an electronics service technician early in his career, but later moved into the field of technical education, where he has worked for 20 years, and in which he is now an independent design consultant. Joe holds a BA degree in Humanities from Emory University, where he also studied calculus, physics, and other subjects related to audio. E-mail: joeberry@mindspring.com.

Authorized Dealer



to ensure stability in the absence of the partial folded-cascode option. These resistors add local negative feedback to each input MOSFET to reduce open-

loop gain and increase input-stage bandwidth. Capacitor C2 forms a secondary feedback loop that enhances the stability of the closed-loop amplifier

and defines the high-frequency rolloff of the amplifier (-3dB) at just over 200kHz . In this design, 22pF seemed to offer the best compromise between

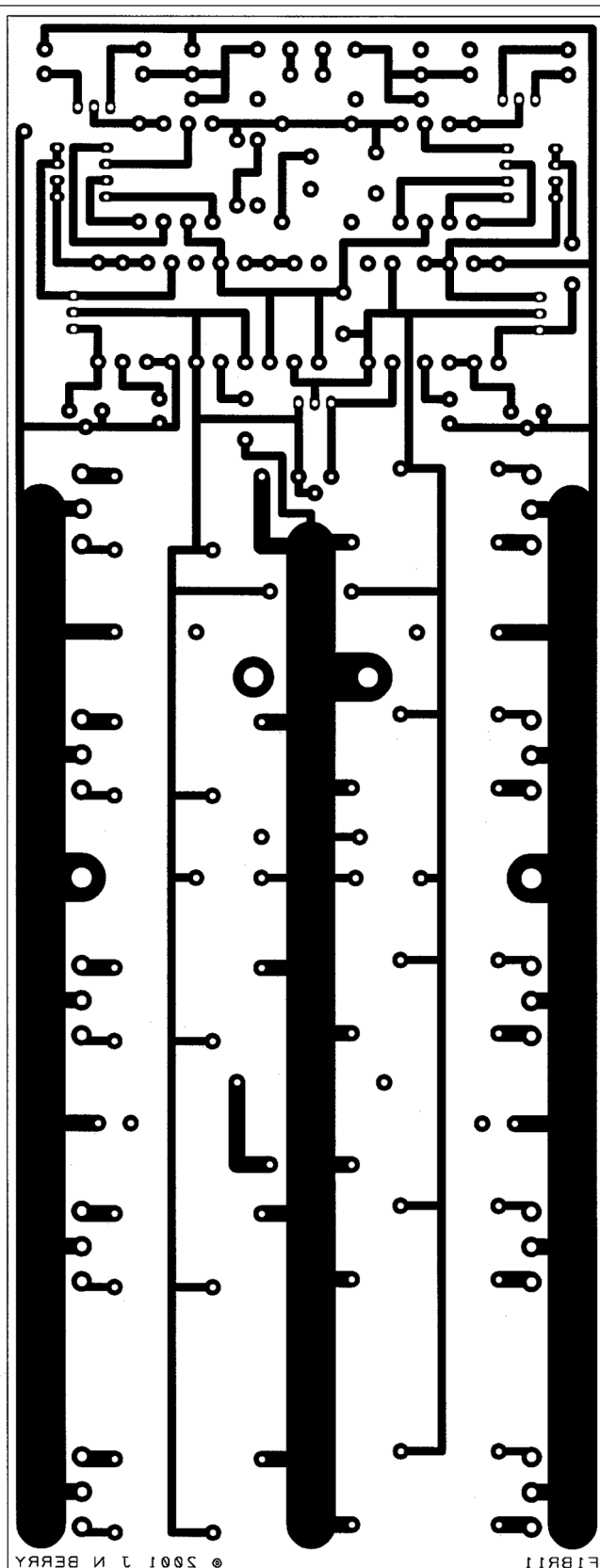
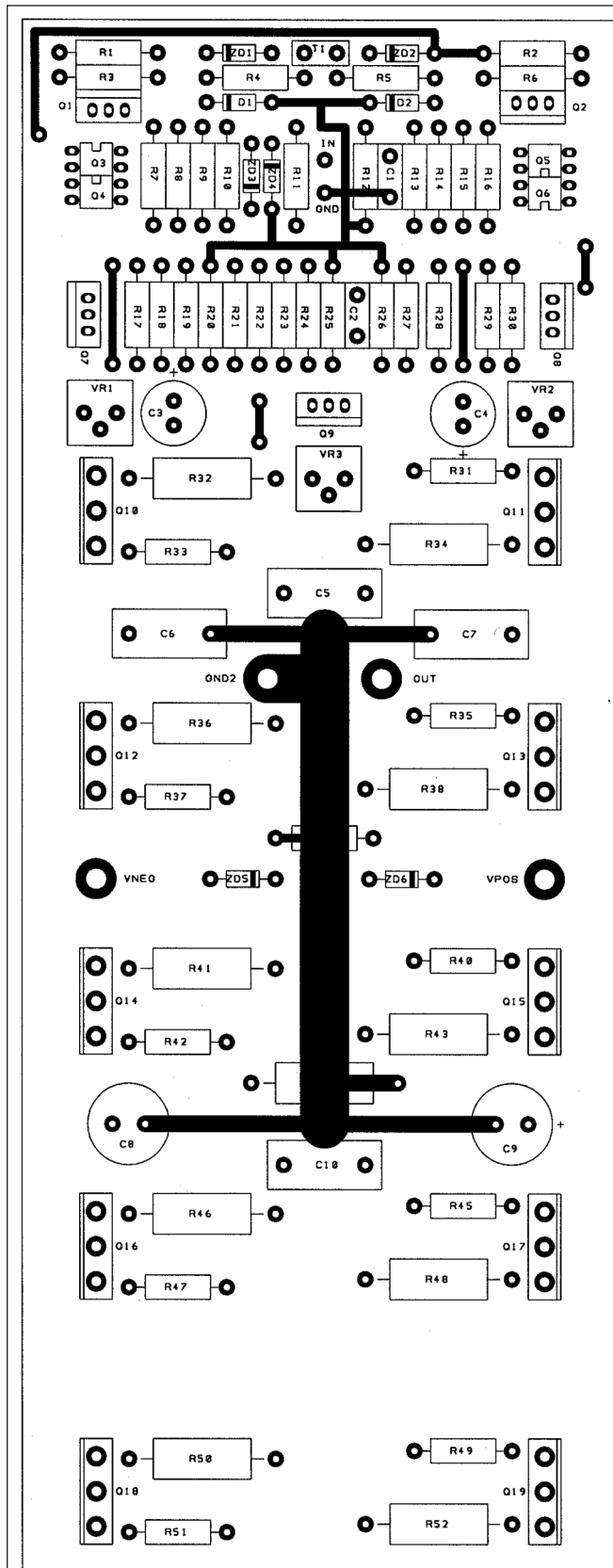


FIGURE 5A: Forte 1b PC board (top). Actual size is $3.65''\text{h} \times 9.5''\text{w}$.

FIGURE 5B: Forte 1b PC board (bottom).

damping and stability while avoiding the need for additional lag compensation. (The original A75 PC board includes provisions for lag compensation, but source degeneration obviates the need for this option here.)

OUTPUT STAGE

The output of the first stage drives second-stage complementary MOSFETs Q7 and Q8 and their associated components. DC bias voltage for Q7 and Q8 develops across R18 and R29 as a result of the DC current flowing in Q3 and Q5. Variable resistors VR1 and VR2 trim the values of R18 and R29 to adjust the bias for Q7 and Q8 and null the DC offset at the amplifier output.

VR1 and VR2 are ultimately set to give 1V across R19 and R30, the source resistors for Q7 and Q8. This reflects about 30mA of idle current in Q7 and Q8, plus an additional 5mA drawn through R19 and R30 by Q4 and Q6. The drains of Q7 and Q8 are loaded by resistors R20 and R26 to limit the open-loop gain of this stage and flatten its open-loop frequency response. R22 and R24, also in the Q7-Q8 drain circuit,

merely serve to produce a virtual ground takeoff point for the optional negative feedback connection via resistor R23.

At your discretion, you may set up the second stage to operate as a partial folded cascode by installing resistors R17 and R28 and capacitors C3 and C4. With these components removed, maximum signal voltage develops across R18 and R29, and Q7 and Q8 work mainly in common-source mode. With C3, R17, C4, and R28 installed, the signal voltage across R18 and R29 is attenuated, reducing the gain of the second stage by about 80%.

In this application, the nominal value of R17 and R28 is 221 Ω , just high enough to enable a 2:1 output current swing from Q7 and Q8. Lower values enhance the effect of the folded-cascode, but may also degrade the amplifier's power bandwidth as well as cause excessive hum at the output. Values below 100 Ω may cause self-oscillation in Q7 and Q8 and should be avoided. Also note that much higher values of R17 and R28 may produce feedback-loop instability unless you install R7-R8 and

R15-R16.

The output from the second stage drives complementary-symmetry MOSFET source-follower output stage Q10-Q19 and associated components. These MOSFETs are in matched sets⁴ with 221 Ω gate resistors and .47 Ω source resistors for improved AC and DC stability. ZD5 and ZD6 clamp the gate drive to the output stage to prevent damaging overvoltage that could occur if the amplifier output is shorted. These zeners also provide some protection against sustained overcurrent conditions, although in this application one or both of the channel's DC rail fuses will probably blow first.

The output stage is biased into Class A operation by adjustable voltage source Q9 and associated components. The bias voltage generated by Q9 has a mildly negative temperature coefficient that compensates for the tendency of the output stage bias to increase with temperature. VR3 provides the bias adjustment, and C5 bypasses Q9 at high frequencies.

A Zobel network consisting of C10 and R44 is included across the output



the authority on hi-fi DIY

Subscribe to **eConnexion**, a monthly email newsletter featuring the latest happenings at pcX - including great specials, clearance items & new product introductions.

Also our online catalog is expanding quickly.





PARTS CONNECTION

1-866-681-9602 www.partsconneXion.com

Tel: 905-681-9602 Fax: 905-631-5777 info@partsconneXion.com

Visa, MasterCard, American Express (+2%), Paypal (+2%), BidPay, Money Order/Bank Draft/Cashier's Check, Personal Check (after clearance)

2885 Sherwood Heights Drive, Unit #72, Oakville, Ontario, CANADA L6J 7H1

IMPORTANT NOTE: No "on-site/walk-in" business at this time... however, pick-up orders can be arranged by appointment only. Call for details.

MultiCap
InterCap
DynamicCap
QuicCap
BLUESHEN
AA
MR
CADDOCK
elkenohm
KIMBER KABLE
coeriz
DISCOVERY CABLE
EXPRESS
ONLINE
audioquest
W
W
W
W
W
SPECTRA DYNAMICS
CONNEX
Vampire
van der Hul
W
MATTEAT

terminals to ensure that the amplifier sees a resistive load at frequencies well above the audio band. R39 is in parallel with this network to provide a leakage path for any standing charge that may remain on the power-supply capacitors after you turn off the unit.

A global negative feedback connection will do essentially the same thing, but if you elect not to use global feedback, R39 prevents mysterious DC offset voltages from appearing at the unloaded output terminals after shutdown. While harmless enough in itself, this voltage could give rise to erroneous fault symptoms during bench testing.

Finally, I added decoupling capacitors C6–C9 during prototyping to prevent amplifier self-oscillation and to enhance stability when driving capacitive loads. The larger capacitors alone appeared to take care of both problems, but I added the smaller film caps to comply with the general recommenda-

tions of IR, Hitachi, and others for MOSFET amplifier power-supply rail decoupling.

NEW PC BOARD

Figures 5a and 5b are top and bottom views of the PC board developed for this project. The basic layout resembles that of the Forte 1a PC board, with the front-end components grouped together at one end and the output stage spread out over the remainder of the board. Ten TO-247 output MOSFETs mount directly to the heatsink in place of the Forte 1a's plastic TO-3 power transistors. Second-stage MOSFETs Q7 and Q8, which dissipate 1W each, mount to standoffs on the heatsink which formerly held the Forte 1a's TO-220 bipolar driver transistors.

The board layout shown here fits perfectly in the two Forte 1a samples I have modified. Still, key dimensions may have changed over the amplifier's

three-year production run, so I suggest that you first copy the PCB layout to scale (actual size 3.65" H × 9.5" W) and use it as a template to check your amplifiers for compatibility.

Copper traces on the top of the board provide separate ground connections for the front end and output stage. This conforms with the Forte 1a's original grounding scheme, which keeps the input and output stage grounds separate until they meet at the metal plate tied across the grounded terminals of the main power-supply filter capacitors.

The holes for the output and power-supply leads on the new PC board are sized to accept the original #12 stranded leads from the Forte 1a. You can recycle the original PC board wiring or supply new leads at your discretion. You should pre-cut new leads to the appropriate lengths and fit them with ring and push-on spade terminals matching those of the original. The input lead holes are likewise sized to accept the original Forte input cable, but should also be compatible with most replacement cables.

I found it best to install as many components as possible on the new PC boards before taking the amplifier apart. This includes all passive devices as well as input-stage MOSFETs Q1–Q6 and the output-stage bias MOSFET, Q9. It does not include the input, power, and output wiring (unless new wiring is used); the thermal cutout (unless a new unit is used); or MOSFETs Q7, Q8, and Q10–Q19. It's best to add these components as part of the assembly process, which I will cover next month in Part 2. ♦

TABLE 1
PARTS LIST FOR ONE CHANNEL

R1, R2	511Ω, ¼W metal film resistor
R3, R6, R9, R10, R13, R14, R17, R28, R31, R33, R35, R38, R40, R43, R45, R48, R49, R52	221Ω, ¼W metal film resistor
R4, R5	6.2kΩ, ¼W metal film resistor
R7, R8, R15, R16	39.2Ω, ¼W metal film resistor
R18, R29	1.5kΩ, ¼W metal film resistor
R19, R30	27.4Ω, ¼W metal film resistor
R20, R26, R39	10kΩ, ¼W metal film resistor
R12, R21, R23	22.1kΩ, ¼W metal film resistor (43.2k if R21 and R23 are both installed; see text)
R11, R22, R24, R25	1kΩ, ¼W metal film resistor
R27	2.65kΩ, ¼W metal film resistor
R32, R34, R36, R37, R41, R42, R46, R47, R50, R51	0.47Ω, 3W metal oxide resistor
R44	10Ω, 3W metal oxide resistor
VR1–VR3	5kΩ, ½W cermet trimmer potentiometer
C1, C2	22pF, 500V silver mica capacitor
C3, C4	220μF, 25V electrolytic capacitor
C5–C7, C10	100nF, 50 or 100V plastic film capacitor
C8, C9	220μF, 50V electrolytic capacitor
D1, D2	1A, 100PIV diode (1N4002)
ZD1–ZD6	9.1V, 1W zener diode (1N4739)
Q1, Q8	IRF9510 P-channel MOSFET
Q2, Q7, Q9	IRF510 N-channel MOSFET
Q3, Q4	IRFD9110 P-channel MOSFET (matched pair)
Q5, Q6	IRFD110 N-channel MOSFET (matched pair)
Q10, Q12, Q14, Q16, Q18	IRFP240 N-channel MOSFET (matched set)
Q11, Q13, Q15, Q17, Q19	IRFP9240 P-channel MOSFET (matched set)
T1	Thermal cutout, normally closed, 85°C
Miscellaneous (per channel)	TO-220 thermally conductive insulating pads (2 qty) • TO-247 thermally conductive insulating pads (10 qty) • Conical/Belleville washers for #6 screws (e.g., McMaster-Carr Part # 90127A007) (10 qty) • Nylon shoulder washers for TO-220 (e.g., Digi-Key Part # 3049K-ND) (2 qty) • 3AG, 3A fast-blow fuses for testing (2 qty) Keystone CL-60 inrush current suppressors (2 qty), three-lug terminal strip, ferrite clamps (2 qty), 14-gauge power cord (1 qty)
Optional (per amplifier; see text)	

REFERENCES

1. Thagard, Norman, and Pass, Nelson, "Build the A75 Power Amplifier (Part 1)," *TAA* 4/92, p. 9.
2. Thagard, Norman, and Pass, Nelson, "Build the A75 Power Amplifier (Part 2)," *TAA* 1/93, p. 20.
3. *Ibid.*, pp. 23–25.
4. Pass, Nelson, "Bride of Son of Zen: The Next Generation," *AE* 5/97, pp. 7–8.

Buy low. Sell hi-fi.

www.AUDIOGON.com
HIGH END AUDIO MARKETPLACE

Transformers & Enclosures

In Stock...



"Classic" Tube Output:

Single Ended (up to 75 watts),
Push-Pull and Potted (up to 280 watts)





Torodial Power:

13 sizes (15 - 1500 VA)
6 VAC - 240 VAC




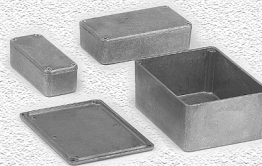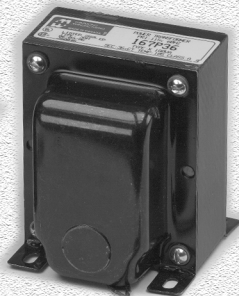Filament & Low Voltage Power Transformers: Open & Enclosed



Enclosures:

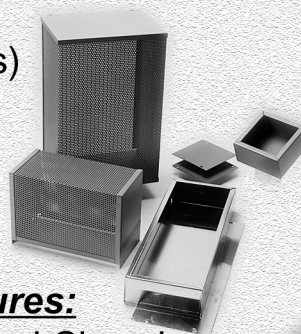Aluminum & Steel Chassis,
Diecast Aluminum, Plastic
and Rack Mount



"Classic"

High Voltage Transformers:
Plate, Plate/Filament Combo
& Filter Chokes (Open & Enclosed)



Contact us for free catalogs & a list of stocking distributors



HAMMOND MANUFACTURING™

256 Sonwil Dr. - Cheektowaga, NY 14225 USA
Phone: (716) 651-0086 Fax: (716) 651-0726

394 Edinburgh Rd., N. - Guelph, Ontario N1H 1E5 Canada
Phone: (519) 822-2960 Fax: (519) 822-0715

www.hammondmfg.com



Budget Milliohmmeter Bridge

Build this device for those times when you need to measure voice-coil or other low resistance values. **By Charles Hansen**

When measuring the actual voice-coil resistance of a loudspeaker driver, most digital multimeters (DMM) do not have the accuracy or resolution for the job. Their test leads add a significant amount of series resistance that introduces additional error.

This project is designed to measure low values of resistance to 1% accuracy or better. I designed the original version of this bridge to measure generator and transformer winding resistances in situations or locations where it was impractical to use an AC line powered precision HP 4261A LCR meter. Parts cost is about \$45.

HOW IT WORKS

The schematic diagram for the milliohmmeter bridge is shown in *Fig. 1*, and the parts list is in *Table 1*. The circuit is based on the familiar Wheatstone bridge. Power comes from a small 12V 1.3Ah sealed lead-acid battery that I bought surplus NOS (*Photo 1*). You could also use a *well-filtered* 12V DC supply.

R1 and R2 form two legs of the bridge. I chose their value to limit the test current to less than 60mA. The unknown resistance connects to binding posts J1 and J2. A known variable resistance then connects to J3 and J4. When the known resistance equals the unknown resistance, the bridge is nulled (balanced) and the voltage between J1 and J3 is zero.

The original Wheatstone bridges used a very sensitive center-zero analog meter movement called a galvanometer to indicate when the bridge was nulled. You could connect your DMM from J1

to J3 to indicate the null point, but you would run into the same accuracy and resolution problems that limit your ability to measure low resistance in the first place.

In order to obtain a very accurate null indication, I used an LT1017 dual precision comparator and two indicator LEDs. If the known resistance is too high, the output of U1a goes low, lighting the "HI" LED1. If the known resistance is too low, the output of U1b goes low, lighting the "LO" LED1. These LEDs tell you the direction you must change the adjustable known resistance in order to achieve null.

R3 and R4 introduce a small amount of hysteresis into each comparator circuit. At

the exact null point, both LEDs are turned off. For an 8Ω unknown resistance, this null point is accurate to within 0.001Ω of the value of known resistance. Thus, the finer the adjustment of the known resistance, the finer the measurement tolerance of the unknown resistance. CR1 provides reverse polarity protection, while C1 and C2 filter any noise pickup from the comparator circuit.

DECADE BOX

My original application used a precision decade box accurate to 0.5% for the "known" resistor. Another alternative is



PHOTO 1: Top view of unit with battery.

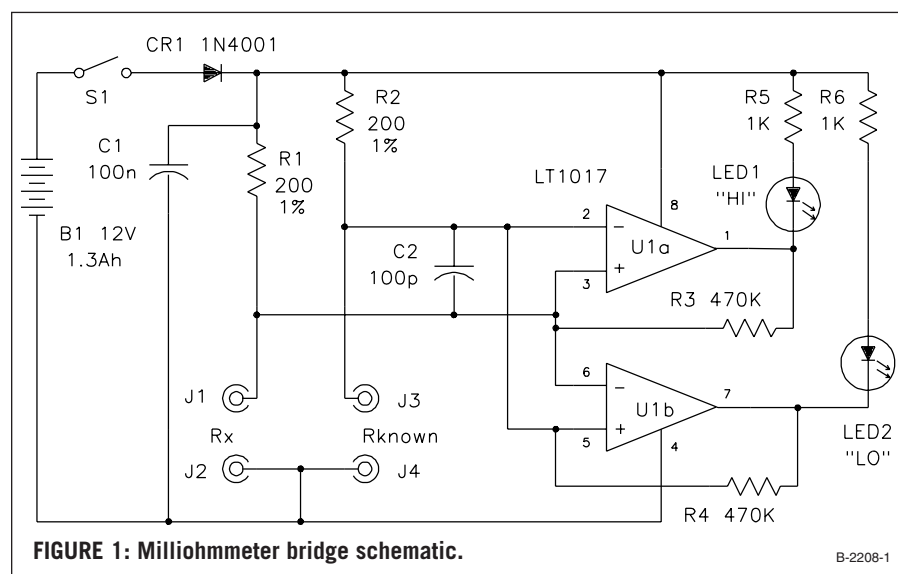


FIGURE 1: Milliohmmeter bridge schematic.

B-2208-1

a precision multi-turn dial-counter potentiometer. Low resistance versions of these devices are hard to find and cost upwards of \$100.

You can make your own 0.1Ω-step decade box with the precision 3W 1% resistors and switches listed in the parts list. The schematic is shown in

Fig. 2. You can use the same ABS enclosure I used for the bridge circuitry.

The decade box uses inexpensive switches with nickel contacts. The total resistance of the internal connecting wire (22-gage), the switch contacts, and the binding posts add up to almost 0.1Ω. For this reason, the "0.1Ω" point

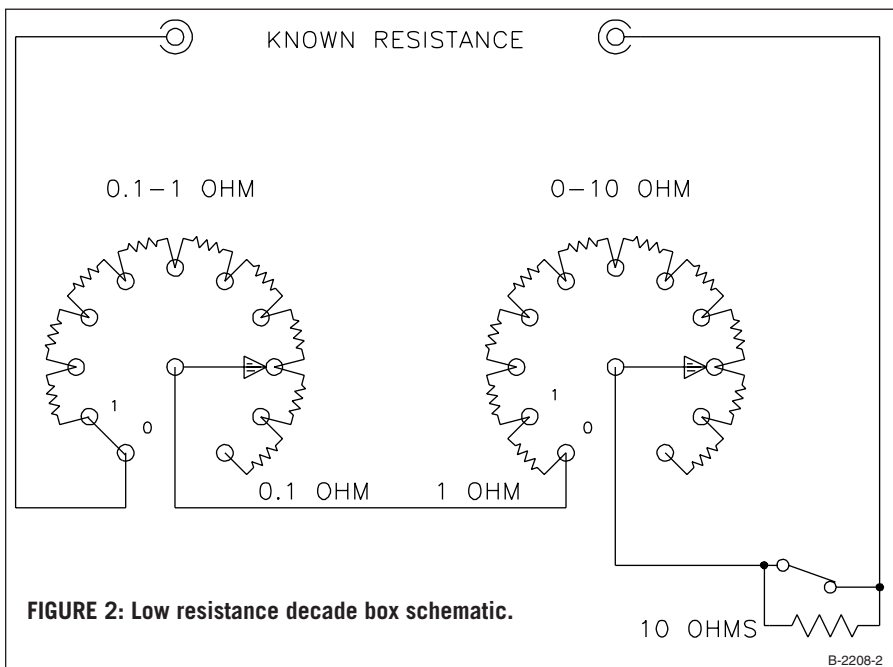


FIGURE 2: Low resistance decade box schematic.

ADIRE AUDIO

MAELSTROM



The ultimate high efficiency bass driver for home and PA.

Maelstrom is our high efficiency, high displacement subwoofer driver. With a true 3 liters of fully linear displacement capability, and a low Fs, Maelstrom can generate tremendous amounts of deep bass output. Coupled with a 96 dB sensitivity, Maelstrom takes very little power to utilize it's full potential.

ON SALE THROUGH APRIL FOR \$225! ORDER THROUGH OUR WEB STORE AND USE A SALE CODE OF MAEL-AX TO GET \$74 OFF THE RETAIL PRICE!


Fs: 20 Hz	SPL: 96 dB
Qms: 19.11	Xmax: 26mm pp
Qes: 0.29	Sd: 1180 cm
Qts: 0.28	Pmax: 1000W
Vas: 460L	PRICE: \$225 (SALE)

Adire Audio carries a full range of kits, products, and services for the DIYer. Please contact us at:

WWW.ADIREAUDIO.COM
PHONE: 425-778-WOOF (9663)


Design speaker boxes with BassBox Pro

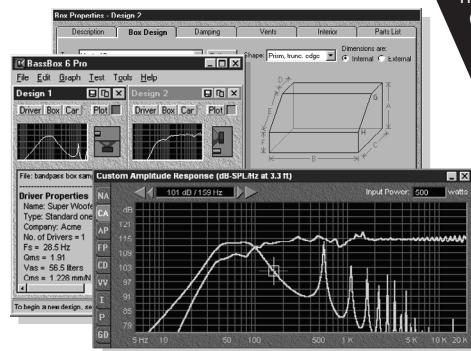Design speaker boxes for any space: car, truck, van, home hi-fi, home theater, pro sound, studio, stage, PA and musical instruments. Import acoustic measurements. For example, the response of a car can be imported to simulate the in-car response.



Sophisticated Driver Modeling and Advanced Box Design

- Multiple drivers with isobaric, push-pull and bessel options. • 3 dual voice coil wiring options. • "Expert Mode" dynamically analyzes driver parameters. • Design closed, vented, bandpass and passive radiator boxes. • "Suggest" feature provides fast box design. • All box types account for leakage losses and internal absorption. • Advanced vent calculation. • Bandpass boxes can be single or double-tuned with 2 or 3 chambers. • 22 box shapes (shown below). • Open up to 10 designs at one time. • Analyze small-signal performance with: Normalized Amplitude Response, Impedance, Phase and Group Delay graphs. • Analyze large-signal performance with: Custom Amplitude Response, Max Acoustic Power, Max Electric Input Power, Cone Displacement and Vent Air Velocity graphs. • Includes a helpful "Design Wizard" for beginners.

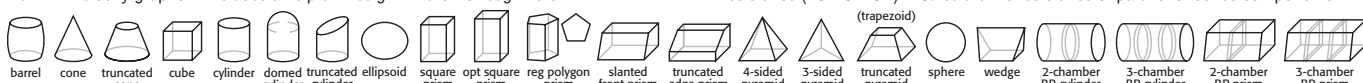

Need help with your speaker designs? BassBox Pro & Xover Pro can help!



Harris Tech Pro software for Microsoft® Windows can help you quickly create professional speaker designs. Our software is easy to use with features like "Welcome" windows, context-sensitive "balloon" help, extensive online manuals with tutorials and beautifully illustrated printed manuals. We include the world's largest driver database with the parameters for many thousands of drivers.

For more information please visit our internet website at:
www.ht-audio.com


Tel: 269-641-5924
Fax: 269-641-5738
sales@ht-audio.com

Harris Technologies, Inc.
P.O. Box 622
Edwardsburg, MI
49112-0622
U.S.A.

\$129
plus S&H

Design crossovers with Xover Pro

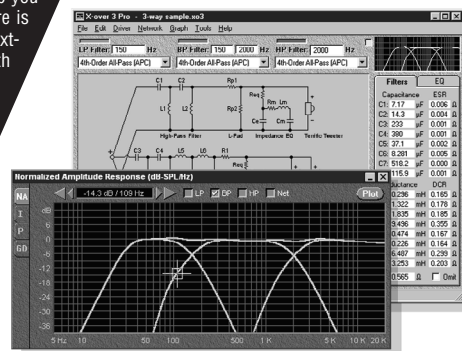Design 2-way and 3-way passive crossover networks, high-pass, band-pass or low-pass filters, impedance equalization, L-pads and series or parallel notch filters. Its Thiele-Small model provides professional results without complex testing.



\$99
plus S&H

Passive Crossover Filters and Scalable Driver Modeling

- 1st, 2nd, 3rd and 4th-order "ladder" filter topologies. • Parallel crossover topology. • 2-way crossovers offer Bessel, Butterworth, Chebyshev, Gaussian, Legendre, Linear-Phase and Linkwitz-Riley filters. • 3-way crossovers offer All-Pass Crossover (APC) and Constant-Power Crossover (CPC) filters. Xover Pro's capabilities scale to fit the amount of driver data. • A crossover, filter or L-pad can be designed with just the nominal impedance of each driver. • With full Thiele-Small parameters, impedance equalization can be designed and the performance graphed. • Graphs include: Normalized Amplitude Response, Impedance, Phase & Group Delay. • Graphs can include the full speaker response including the box. • Estimate component resistance (ESR & DCR). • Calculate the resistance of parallel or series components.

on the first rotary switch uses a jumper rather than an actual 0.1Ω resistor. If you can borrow an accurate lab quality milliohmmeter, you can make a calibration label for your decade box and improve the accuracy of your measurements even further.

The design in *Fig. 2* is adjustable from 0.1Ω to 21Ω , which will cover all the voice coils you should encounter. The "12" position on the two rotary switches is not connected, allowing an open circuit position. If you like, you can add another resistor to the series string on each deck to extend the range by another 1.1Ω . You can also easily redesign the circuit to measure higher resistances by changing the values of R1 and R2, and the range of the decade box used to balance the bridge.

CIRCUIT BOARD LAYOUT AND CONSTRUCTION

I used a plastic enclosure for the bridge circuitry, with most of the parts on a small wire-wrapped perfboard connected with standard T49 wire-wrap pins and a wire-wrap DIP socket for U1 (*Photo 2*). Four $4-40 \times \frac{3}{4}$ " spacers support the PC board with the components facing the top of the enclosure. This allowed me to let the two lead-supported LEDs show through two $\frac{3}{16}$ " holes drilled in the top of the enclosure.

The unknown (Rx) resistor terminal posts J1 and J2 are just above the LEDs in *Photo 1*. J3 and J4 are on the right side of the enclosure. The power switch is on the lower right side of the top. The 12V battery is connected to the bridge enclosure with a two-pole flat trailer-towing connector that I purchased at Pep Boys.

There is nothing critical about the internal wiring, except the four inputs to U1 should have the shortest length possible, and C1 and C2 should be located as close to U1 as possible.

USING THE MILLIOHMMETER BRIDGE

One of the problems with accurate mil-

liohm measurements is the length of the leads between the test meter and the unknown resistance. The HP 4261A uses 4-wire Kelvin leads to compensate for the drop in the leads carrying the test current to the unknown resistance.

You can provide another form of compensation by making two equal-length sets of test leads. One set connects from the Rx input jacks to the unknown resistance, the other from the known resistance jacks to the decade box. In this way the drop in each set of leads should be equal at null. Alternatively, you can measure the effect of the speaker cables you want to use by connecting them between the driver and the bridge unit, and using the shortest possible leads between the decade resistor and the bridge unit.

I was able to measure a precision 0.01% test resistor of exactly 6.98Ω to 6.978Ω using this simple test tool. You can obtain this extra decade of accuracy by shunting the low resistance decade box with a higher resistance and computing the parallel resistance of the two "known" resistors. ♦

SOURCES

Digi-Key Corp.
701 Brooks Ave. South
Thief River Falls, MN 56701-0677
1-800-344-4539
www.digikey.com

Mouser Electronics
958 N. Main
Mansfield, TX 76063-4827
1-800-346-6873
www.mouser.com

Parts Express
725 Pleasant Valley Dr.
Springboro, OH 45066-1158
www.partsexpress.com

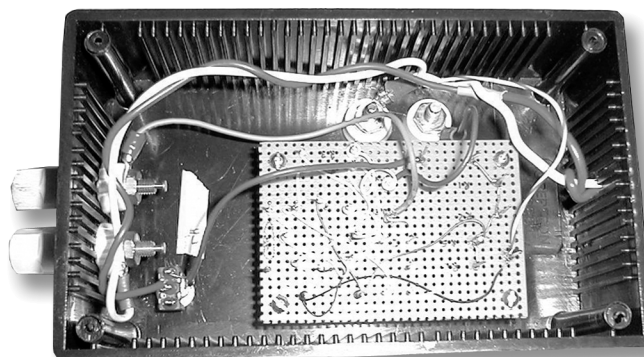


PHOTO 2:
Interior view.

TABLE 1
PARTS LIST

SYMBOL	VALUE	DESCRIPTION	VENDOR/PART NO.
B1	12V 1.3Ah	Panasonic LC-R121R3PU (or Parts Express)	(surplus) Parts Express 149-135
C1	100nF 100V	Ceramic Z5U	Mouser 140-100Q9-104Z
C2	100pF 50V	Ceramic NP0	Mouser 140-50S5-101J
CR1	1N4001	1A 50V	Mouser 583-1N4001
LED1, LED2	MV8013	Red T-1 3/4 LED	Mouser 512-MV8103
J1-J4		Binding post, white	Mouser 164-4206
P1		2-pole flat trailer connector 0.250 × 0.032 female lug	Pep Boys 47965 Mouser 644-DNF18-250C
R1, R2	200Ω 3W 1%	Wire wound	Mouser 71-RS2B-200
R3, R4	470k 5% 1/4W	Carbon film	Mouser 291-470K
R5, R6	1K 5% 1/4W	Carbon film	Mouser 291-1K
S1, Sdb	SPST	Mini toggle	Mouser 108-MS550K
U1		LT1017 dual comparator	DK LT1017CN8-ND
		8-pin wire wrap DIP socket	Mouser 575-293308
		5.9 × 3.5 × 2.2 ABS enclosure	Mouser 400-1562
Rdb (9)	0.1Ω 3W 1%	Wire wound	Mouser 71-RS2B-0.1
Rdb (10)	1.0Ω 3W 1%	Wire wound	Mouser 71-RS2B-1.0
Rdb	10Ω 3W 1%	Wire wound	Mouser 71-RS2B-10
Jdb (4)		Binding post, white	Mouser 164-4206
Sdb (2)	1P 12 POS	Rotary sw	Mouser 10YX112

ADDITIONAL MATERIALS:

Perfboard, nylon spacers, hook-up wire, solder, hardware, and so on.

Chat, browse, bid, buy, sell
or simply click 'til it hurts.

www.AUDIOGON.com
HIGH END AUDIO MARKETPLACE

Look!!

Click <http://www.eifl.co.jp>
or send e-mail to info@eifl.co.jp
for more products information



■ Cartridge

Model	Price (US\$)	Postage (Air Economy)	
Denon DL-102 (MONO)	150	Area I \$ 18	China, Korea Hong Kong Taiwan
Denon DL-103 (STEREO)	200	Area II \$ 22	Singapore Malaysia Indonesia
Denon DL-103R (STEREO)	250	Area III \$ 27	North America Oceania Europe
Denon DL-103 PRO (STEREO)	350	Area IV \$ 34	Africa South America
Shelter Model 501 II (CROWN JEWEL REFERENCE)	750	These Area I ~ IV are for all products except book.	
Shelter Model 901 (CROWN JEWEL SE)	1,400		

■ Japanese Audio Book

Postage \$ 15

Title	Price (US \$)
Attractive Tube Amps Vol. 1&2 (Isamu Asano)	30 each
The Joy of Vintage Tube Amps 1&2 (Tadaatsu Atarashi)	30 each NEW
Direct & Indirect Tube Amps (Kiyokazu Matsunami)	40 NEW
SE Amps by Transmitting Tubes (Kouichi Shishido)	50
The Remembrance of Sound Post (Susumu Sakuma)	30
Classic Valve (Hisashi Ohtsuka)	40
MJ Selected 300B Amps (MJ)	30
Top-Sounding Vintage Power Tubes (Stereo Sound)	30
Output Trans of The World (Stereo Sound)	30
20TH CENTURY OF AUDIO (Stereo Sound)	30
Vintage Speaker Units (Stereo Sound)	30 NEW
Tube Amp Craft Guide (MJ)	30

■ MC STEP UP TRANS

Model	Specifications			Price (US\$)	Postage**
	Pri.Imp(Ω)	Sec.Imp(kΩ)	Response		
Shelter Model 411	3~15	47	20Hz~50kHz	980	Area I \$ 25
Jensen JE-34K-DX	3	47	20Hz~20kHz	550	Area II \$ 30
Peerless 4722	38	50	20Hz~20kHz	300	Area III \$ 40
					Area IV \$ 50

** Air Economy

■ STAX

Model	Price(US\$)
OMEGA II System(SR-007+SRM-007t)	Ask
SRS-5050 System W MK II	
SRS-4040 Signature System II	
SRS-3030 Classic System II	
SRS-2020 Basic System II	
SR-001 MK2(S-001 MK II +SRM-001)	

■ Speaker

Model	Specifications					Price* (US\$)	Postage** (US\$)			
	D (cm)	Ω	Response	db	w		I	II	III	IV
Fostex FE208 Σ	20	8	45Hz~20kHz	96.5	100	296	62	74	120	156
Fostex FE168 Σ	16	8	60Hz~20kHz	94	80	236	42	50	73	98

* Price is for a pair ** Air Economy

■ TANGO TRANS (ISO) (40models are available now)

Model	Specifications				Price (US\$)	Postage** (US\$)			
	W	Pri.Imp(kΩ)	Freq Response	Application		I	II	III	IV
XE-20S (SE OPT)	20	2.5, 3.5, 5	20Hz~90kHz	300B,50,2A3	396	47	56	84	113
U-808 (SE OPT)	25	2, 2.5, 3.5, 5	20Hz~65kHz	6L6,50,2A3	242	42	50	73	98
XE-60-5 (PP OPT)	60	5	4Hz~80kHz	300B,KT-88,EL34	620	62	74	115	156
FX-40-5 (PP OPT)	40	5	4Hz~80kHz	2A3,EL34,6L6	320	47	56	84	113
FC-30-3.5S (SE OPT) [XE-60-3.5S]	30	3.5	20Hz~100kHz	300B,50,PX-25	620	62	74	115	156
FC-30-10S (SE OPT) [XE-60-10SNF]	30	10	30Hz~50kHz	211,845	620	62	74	115	156
X-10SF [X-10S]	40	10W/SG Tap	20Hz~55kHz	211,845	1160	90	110	180	251
NC-14 (Interstage)	—	[1+1 : 1+1] 5	25Hz~40kHz	[30mA] 6V6 (T)	264	30	40	50	70
NC-16 (Interstage)	—	[1+1 : 2+2] 7	25Hz~20kHz	[15mA] 6SN7	264	30	40	50	70
NC-20F (NC-20) (Interstage)	—	[1 : 1] 5	18Hz~80kHz	[30mA] 6V6 (T)	640	42	50	73	98
NP-126 (Pre Out)	—	20,10	20Hz~30kHz	[10mA] 6SN7	264	30	40	50	70

Price is for a Pair

■ TAMURA TRANS (All models are available)

** Air Economy

F-7002 (Permalloy)	10	3.5	15Hz~50kHz	300B,50	836	60	70	110	145
F-7003 (Permalloy)	10	5	15Hz~50kHz	300B,50	836	60	70	110	145
F-2013	40	10	20Hz~50kHz	211,242	786	70	84	133	181
F-5002 (Amorphous)	8	3	10Hz~100kHz	300B,2A3	1276	65	80	120	160

Price is for a Pair

** Air Economy

E-I-F-L
EIFL Corporation

1-8, Fujimi 2-chome, Sayama City, Saitama Pref. 350-1306 JAPAN.

Phone:+81-(0)42-956-1178 FAX:+81-(0)42-950-1667

E-mail:info@eifl.co.jp

Wire Transfer:MIZUHO BANK, SWIFT No.MHBKJPJT a/c # 294-9100866



Card Charge 6%

The Legend of EL PIPE-O

This woofer transmission-line project takes achieving low frequencies to new heights. **By Kent English and Nelson Pass**

Most woofers just don't quite do the lowest octave. You read the specs that say "usable response: 20Hz–20kHz," and you know that the 20Hz part of it is wildly optimistic. Achieving very low frequencies at reasonable power levels is not an easy job; the acoustic impedance experienced by a speaker cone declines as the inverse of the square of the frequency. As a practical matter, woofers and their enclosures need to be very large to reproduce the lowest octave properly. Even when you compensate with frequency equalization and more amplifier power, the performance suffers as you reach the excursion and power-handling limitations of a small cone in a small box.

Let's face it. Size does matter.

This is the saga of El Pipe-O, an adventure in over-the-edge woofer construction. The name El Pipe-O came from its striking resemblance to a legendary smoking appliance belonging to one of Pass' roommates in college that was the object of worship by a small cult.

El Pipe-O consists of very large woofers mated to large cylindrical transmission lines. The goal is to get good powerful response down to 20Hz at levels where the room starts to rattle before the loudspeaker.

BASS REFLEX ENCLOSURES

Suspended by elastic material, woofer cones have a natural fundamental resonant frequency at which the motion increases dramatically, and below which the response drops off at a sharp rate. Many woofer enclosures attempt to set up some sort of counter-resonance that is used to damp out this uncontrolled

motion and turn it into getting a little more bass out of the speaker. The two most popular approaches are the bass-reflex enclosure and the transmission line.

The bass-reflex enclosure has the woofer mounted in a box that has a specific internal volume and an opening to the outside. Any box with an opening has its own acoustic resonance, known as Helmholtz resonance, which you experience when you blow into the opening of a beer bottle. Varying the volume of the box or the size of the opening (called the port) adjusts the frequency of resonance, and you can tune it to the same frequency as the resonance of the woofer.

When the box's resonance is the same as the woofer's resonance, you

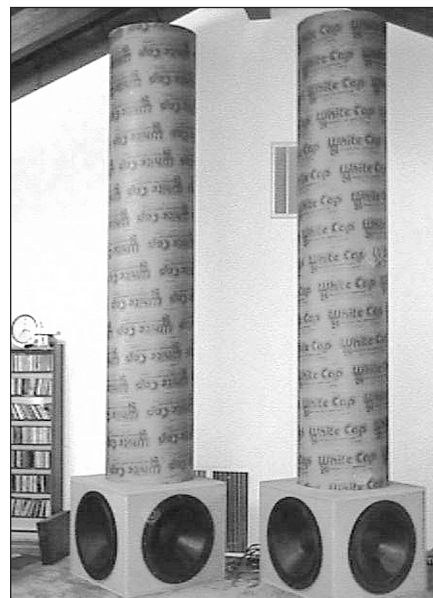



PHOTO 1: Sonotube speakers standing tall.

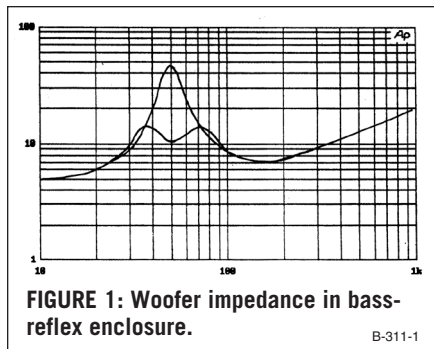get an interesting effect: The woofer experiences acoustic loading, which damps out its uncontrolled motion, and the port delivers extra acoustic output to the outside world. The performance

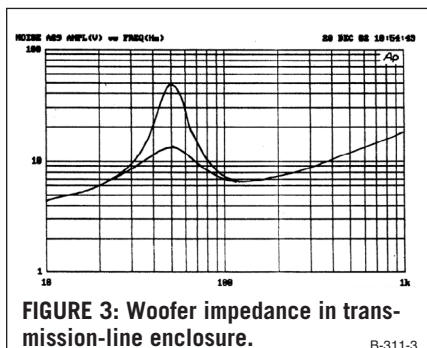


PHOTO 2: Closeup of speaker.

improves because the cone moves less and the output is boosted at the lowest



frequencies. You can see this in the impedance curves of *Fig. 1*. The impedance of the woofer reflects the motion of the cone, and here you see a compar-





ison between the woofer's impedance in free air versus its impedance in a tuned bass-reflex enclosure.

PIPE DREAMS

A transmission line offers a different approach to achieving a similar effect. In any tube-shaped object, closed at one end, a resonance develops at the frequency where the wavelength is four times the length of the tube. This effect is exploited in numerous musical instruments, particularly the pipe organ.

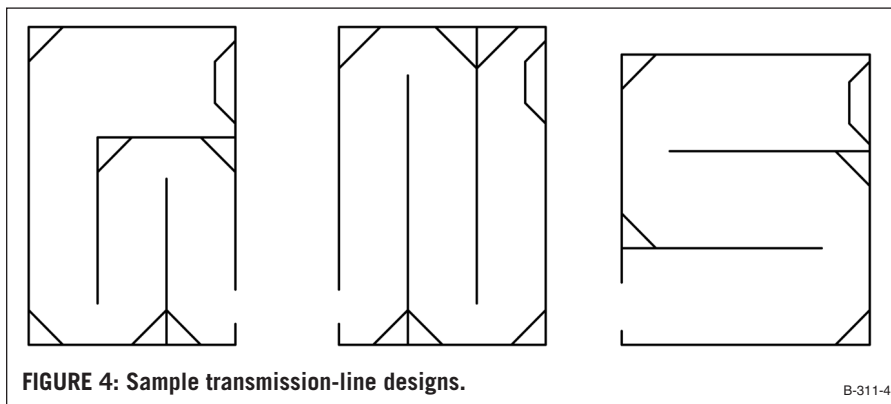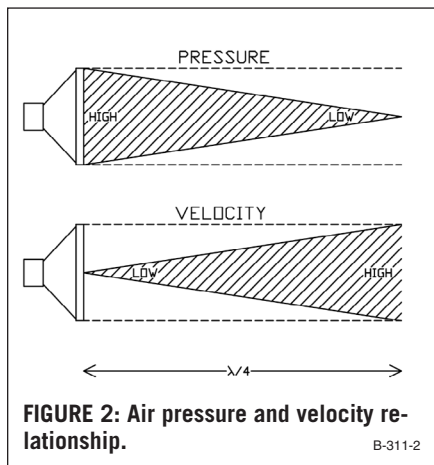The wavelength of a frequency is the speed the wave travels divided by the frequency. For sound going through



GRANDMOS

The SMART amplifier



2 Audiophile Masterpieces for the DIYer

TRIPHON

The ULTIMATE crossover system



- ✓ Probably, the nearest approach to :
"A STRAIGHT WIRE WITH GAIN".
- ✓ High end 2 x 100 W_{RMS} / 8 ohms MOS-FET amplifier.
- ✓ SILVER plated PTFE / fiberglass printed circuit boards.
- ✓ SILVER plated connections.
- ✓ Military grade components.
- ✓ Only J-FET and MOS-FET audio transistors.
- ✓ NO CAPACITOR in the sound path *.
- ✓ Minimum wiring and easy construction.
- ✓ Outstanding performances.
- ✓ Absolute Transparency and Sound.
- ✓ Extremely reliable.
- ✓ Steady performances over years.

* : under certain conditions

To complete the GRANDMOS (or any good quality amplifier) we have designed the **TRIPHON system** :

- ✓ Musically neutral and transparent.
- ✓ 3-way electronic crossover.
- ✓ 6 or 12 dB/octave slope (true LINNKWITZ-RILEY filter).
- ✓ 4-channel Class A minimalist MOS-FET amplifier for MID and HIGH frequencies.
- ✓ Choice of cut-off frequency.
- ✓ PTFE / fiberglass printed circuit boards.
- ✓ Fully discrete component technology.
- ✓ SILVER plated connections.
- ✓ Minimal wiring.

by
Selectronic
L'UNIVERS ELECTRONIQUE

www.selectronic.fr

Phone : + 33 - 328 550 328 - Fax : +33 - 328 550 329
BP 513 59022 LILLE - FRANCE

>> Detailed information on www.selectronic.fr or by e-mail to : selectrocom@selectronic.fr <<

The Soniccraft SC12NRT

The SC12NRT is the newest driver in our line of Soniccraft woofers. The new SC12NRT uses the powerful **Aurasound NRT motor**. The **shielded** motor provides **peak excursion over 1 inch**. And you can place this powerful woofer right next to your picture tube.



Flange Ø
12 1/4"

Cutout Ø
11 1/8"

Specifications:

Fs	23.7 Hz
Nominal Impedance	4.0 Ω
Power	300 watts
Sensitivity	88.5 dB
Re	3.7 Ω
Vas	97.686 ltrs
Qms	9.627
Qes	0.517
Qts	0.491
Sd	0.0457 sqM
BL	12.075 TM
Cms	329.38 μM/N
Mms	136.92 gram
Le@1kHz	1.277 mH
Underhung voice coil geometry	
Neodymium NRT magnet system	
Polypropylene cone, inverted dust cap	
X-max 15mm peak	
Cast Frame with vented spider	
Extra Long Stroke foam surround	
Gold plated binding posts	
Conex fiber spider	
Large vented magnet system	

Recommended Enclosures:

- 3 cubic feet vented, F3 25Hz (3" vent by 12" long)
- 2.7 cubic feet sealed, F3 35Hz

Consider using this driver in our 3ft³ enclosure with our KG5230 300 watt amplifier.

Woofer Price \$230.00 Each

Madisound Speaker Components, Inc.
8608 University Green #10
P.O. Box 44283
Madison, WI 53744 USA
T: 608-831-3433; F: 608-831-3771
email: info@madisound.com

air, that speed is approximately 1100' per second. At 20Hz, the wavelength is about 55', which is where a 14' tube will resonate.

With a loudspeaker mounted at one end of the tube, essentially closing off that end, the mass and elasticity of the air in the tube will cause a favored frequency where the tube is one-quarter the wavelength. In Fig. 2 you see that at this frequency the pressure and air motion are 90° out of phase with each other, so that high pressure develops at the closed end where motion is not favored, and high air motion occurs at the open end, where it can flow easily to the outside and no wall favors the buildup of air pressure.

This resonance is similar to that of the bass-reflex enclosure, and it has a similar effect. Figure 3 shows the impedance of a woofer in free air and in a transmission line tube tuned to the res-

onant frequency. Like the bass-reflex, the transmission line damps out the

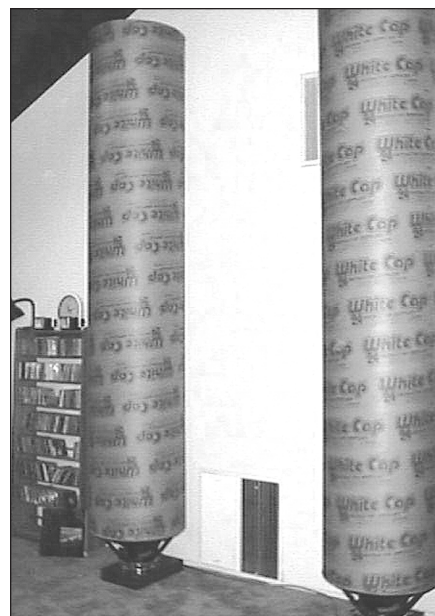


PHOTO 3: Reconfigured woofers.

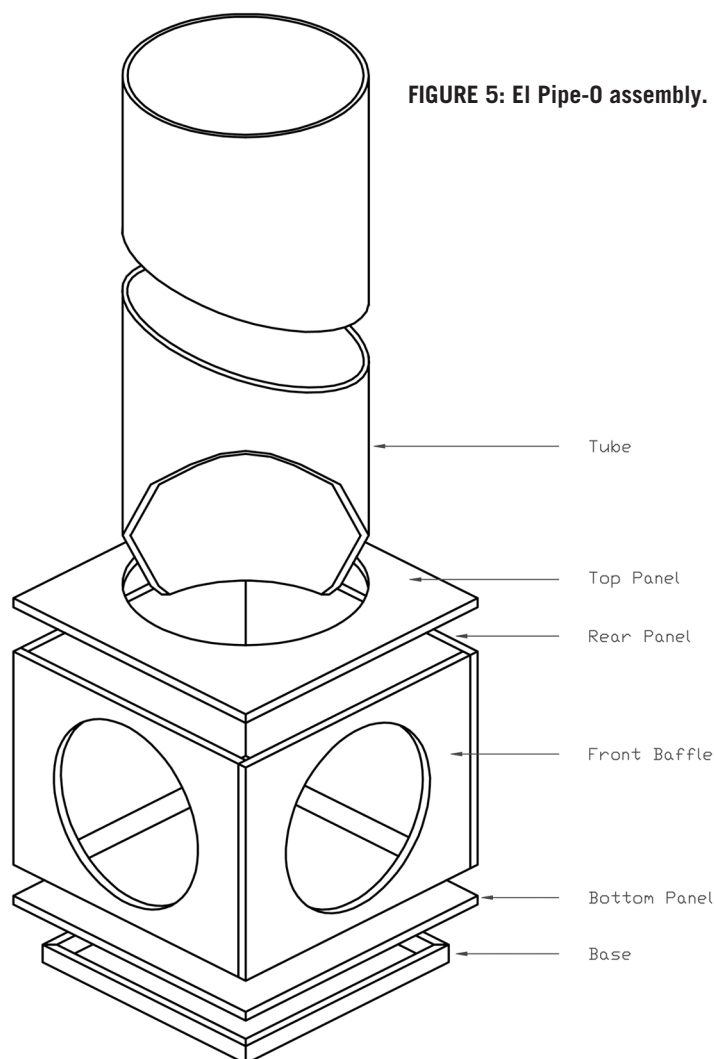


FIGURE 5: EI Pipe-0 assembly.

B-311-5

resonant motion of the cone, but with a lower "Q," or sharpness, so that you tend to get a single bump instead of the double bump of *Fig. 1*. Also like the bass-reflex, the output from the opening delivers more acoustic energy to the room, extending the response and power at the lowest frequencies.

We favor a well-done transmission line over a bass-reflex enclosure. The bass is tighter and less boomy. It also tends to extend deeper. Part of this effect comes from the actual lowering of the resonant frequency of the woofer due to the additional air mass it must push in the pipe.

You can adjust the "Q" or sharpness of both the bass-reflex and transmission line enclosures by stuffing them with wool, Dacron, or fiberglass. The more fibrous material you put in them, the more damped the effect. Resistive material of this sort also tends to increase the apparent volume of the enclosure for a bass-reflex and the length of the enclosure for a transmission line. Choice of the density of this material is often left to the discretion of the constructor, with the instructions, "Stuff to taste."

As with horns, the best transmission line is a straight one, with no bends. Bends compromise the effect, but often not so much that they still aren't useful. Quite a few transmission lines have been designed which have bends in them in order to fit them into a reasonable space. *Figure 4* shows a couple of examples. They work well, exhibiting only minor compromise.

Our favorite configuration is one in which the rear wave exits at the rear near the floor. In this case, the floor adds some acoustic loading for greater output, and the opening, pointed away from the listener, is at some distance from the front of the woofer. This approach minimizes interaction between the woofer's front and rear wave at higher frequencies and also effectively adds a little length to the line.

However, El Pipe-O is going to be a straight vertical tube, with the woofer(s) at the bottom and the open end of the pipe at the top. It is not going to fit in an 8' high listening room.

ENTER THE SONOTUBE

Of course, we can build our transmis-

sion line any way we like out of wood, or those gigantic plastic storm drain type pipes, or even those monstrous concrete sewer pipes. Perhaps somewhere along the Alaskan pipeline is one happy audiophile, but we are going to do it the easy way—with Sonotubes.

Sonotubes are heavy-duty cardboard-type tubing used to cast concrete into pillars. They are available in a number of diameters and lengths, and are generally found in metropolitan areas. We usually buy them at White Cap stores, and we have played with 8", 14", and 24" diameters. We get them in 12' lengths, and the store will usually cut them to a desired length. If not, they are easy to cut with a saber saw. Oh yeah, and they are pretty cheap.

Because they are cylindrical, the tubes are very strong, like eggs, for pressure which is equal around the circumference of the tube, which is what they will experience in a transmission line. Also, the fiber material in the walls is dense and fairly dead acoustically, making them a good choice. For this project we bought a pair of 12' long, 24" diameter Sonotubes.

TURBOCHARGING YOUR REGA ARM



"Nothing less than total dynamite" **HI-FI WORLD MAGAZINE**

If you are the proud owner of any Rega arm why not utterly transform it into the league of super arms with the Origin live structural modification:- \$91. This modification will enable your Rega to perform at a level exceeding that of arms costing over \$1700. Rewiring with high grade litz cable is also offered at an additional \$85 and external rewiring is \$99. All these modifications are available in kit form if you wish to do the job yourself or you can send us your arm for us to do the work.

"I have to say the Rega modifications turn this humble arm into a real Giant killer. Gone is the rather grey, sterile sound of the cooking Rega. Instead, tonal colour is fresh, dynamics have great speed and impact, and the sound stage is huge." **HI FI WORLD SUPPLEMENT** (structural modification to an RB250)

WHAT HI-FI MAGAZINE gave this modification a 5 star rating.

For arm modifications we normally turn around your arm in 1 - 2 days

OTHER KITS & PRODUCTS FROM ORIGIN LIVE INCLUDE:-

- **TURNABLES** (Kits & Retail)
"the best sounding deck here...sounds fantastic" **WHAT HI-FI MAGAZINE** group comparison test of 8 leading turntables
- **SIIVER 250 TONEARM \$729**
Probably the best tonearm available at any price (except for the Silver Taper).
- **SILVER TAPER TONEARM \$1491**
- **DC MOTOR UPGRADE**
suitable to upgrade all turntables including Linn Lingo, Armageddon, Roksan, Thorens, Ariston, Rega, Systemdek etc \$319
Well reviewed as a massive upgrade for all turntables

FULL INFORMATION ON WEB SITE OR CONTACT:-

Origin live, 87 Chessel Crescent, Bitterne, Southampton SO19 4BT

Tel: 023 80442183 / 80578877 Fax: 023 80398905

E MAIL: originlive@originlive.com

WEB SITE: <http://www.originlive.com>

THE WOOFERS

If you read the MCM catalog (www.mcmelectronics.com), then you've undoubtedly seen them. Part# 55-1835, 21" low frequency pro woofer. Eight ohms, 96dB at 1W, 25Hz resonance, 200W RMS, 800W peak. Price: \$395.

Pass couldn't help himself and bought four of them. They sat around for a couple of years in boxes until we decided to make El Pipe-O. In fact, El Pipe-O was the excuse to use them up. They look to be copies of a large Focal woofer, but the manufacturing quality is not quite as high. If you buy these, we recommend that you test them right away for voice coil mis-alignment. You can do this by pumping a low-frequency signal into them while listening for scraping.

CONSTRUCTION

We decided to use two woofers per side to maximize the cone surface area and power handling of each speaker. We used MDF for the boxes so that the woofers were mounted on adjacent sides and the sonotubes were inserted from the top and supported on the floor of the box, with the sonotubes truncated at an angle that provided a good opening between the tube and the box.

Figures 5-10 provide details of the construction and dimensions of the boxes and cuts. The usual speaker construction techniques are appropriate, including the use of bracing and sealing materials.

Because of the size and weight of the speakers, final construction needs to be at the spot where they are to be used. We mounted the tubes and glued them in place at the box opening and on the box floor, and used silicone sealant around the juncture of box and tube. We also wired the woofers in parallel, to form 4Ω loads on each channel, and filled the box loosely with Dacron prior to mounting the woofers using lag bolts and string caulk.



Finally, we filled the tubes themselves with 20 lb of Dacron each. *Photos 1 and 2* show the finished speakers.

PERFORMANCE

Figure 11 shows the near-field response curve of the drivers without equalization or crossover filters, driven at 1W (2.83V). Figure 12 shows the response curve of El Pipe-O at 1m away, where

room effects can start to be observed. Both curves are calibrated so that zero equals a 100dB level.

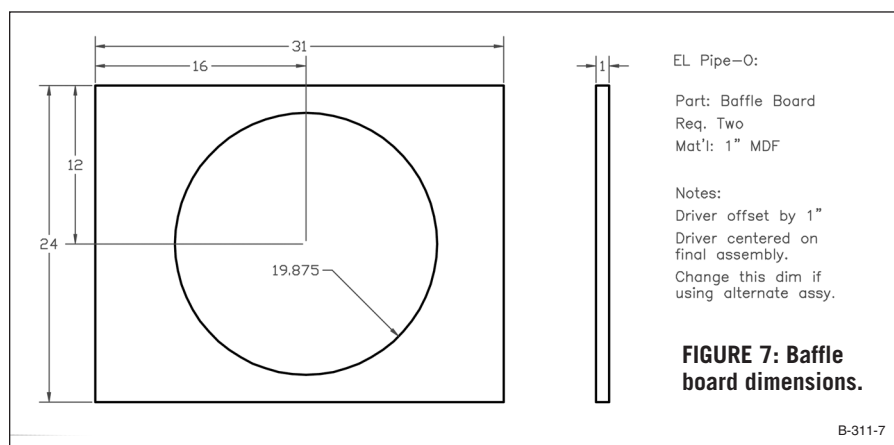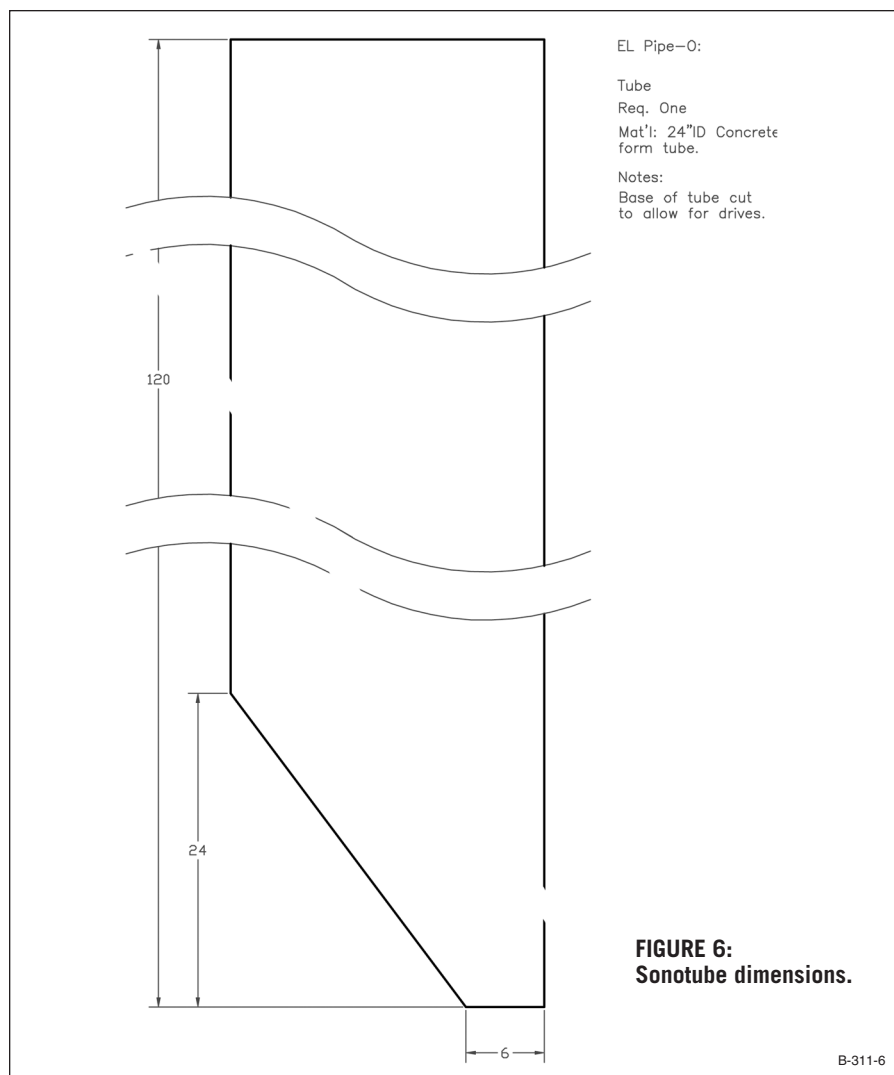Like many big woofers, the response curve extends out to higher frequencies irregularly and with questionable transient response. Also evident from the curves is the need for some equalization to make the woofer truly flat down to 20Hz. No problem . . . we will simply



Sure we have middlemen.
FedEx & UPS, to name a couple.

www.AUDIOGON.com
HIGH END AUDIO MARKETPLACE

make a crossover filter that accomplishes both requirements.

Using a Pass XVR1, we set up, measured, and listened to a wide variety of possible crossover filters—varying frequency, slope, and Q. Ultimately we settled on a two-pole, 22Hz low-pass filter as the best-sounding compromise. *Figure 13* shows the near-field response with no filter, one-pole low-pass (6dB/octave) at 22Hz, and the two-pole low-pass (12dB/octave) that we ended up using. *Figure 14* shows the response at 1m. Note that active filtering does not alter the sensitivity of the loud-

speaker, which ranges from about 85 to 103dB/W.

Pass's listening room measures 30' × 30', with a 14' ceiling at the center. The height of El Pipe-O at 12' means that we were unable to play with corner placement, so we placed the speakers a few feet apart just behind where speakers would ordinarily be, allowing about 2' space between the pipe openings and the ceiling.

The final result (bottom curve) measures about ±3dB in the room from about 13Hz to 75Hz, and it goes away rapidly enough at higher frequencies to


avoid being obnoxious. We evaluated the performance in systems using the Fostex 204 "full range" speaker, the TAD1101 with a Raven R2 on the top, and (over time) a fairly wide sampling of conventional speakers, none of which had a particularly strong bottom end.

A very important consideration is the quality of transition from subwoofer to an ordinary woofer; the phase and amplitude of the mixed response must be smooth or it can sound pretty awful. If these aren't right, the bass can become very boomy from peaks or suffer frequency drop-outs that destroy the attack.

Fortunately, El Pipe-O "plays well with others," as long as there is not too much distance between the big woofers and the higher-frequency drivers. We found that placing the main speakers directly in front of the transmission lines worked best.

ACTIVE CROSSOVER

Figure 15 shows an active op-amp-type circuit that delivers the crossover filter characteristic we used, which is a two-pole low-pass at 22Hz. The tolerances are not at all critical, and just about

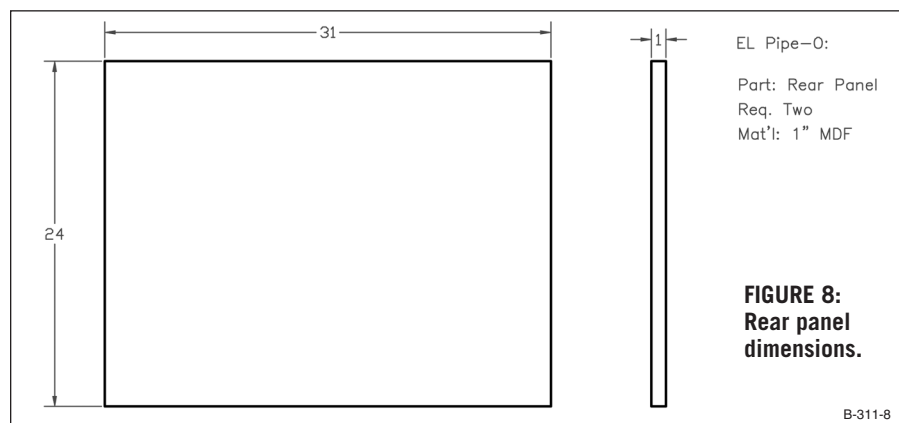

Hi-Fi Do Inc.

BUY & SELL

**OVER A
MILLION
HITS/WEEK**

USED AMPLIFIERS, SPEAKERS, BOOKS, ACCESSORIES etc.

www.hifido.co.jp

OSAKA(Overseas Dept.): 4-6-10 NIPPONBASHI NANIWA-KU OSAKA JAPAN



TOKYO:TOKUHARA BLD 5-5-7 SOTOKANDA CHIYODA-KU TOKYO JAPAN

NAGOYA:3-11-30 OOSU NAKA-KU NAGOYA JAPAN

PHONE 816-4396-7611 FAX 816-4396-7621







PHOTO 4: Closeup of single woofer on granite block.

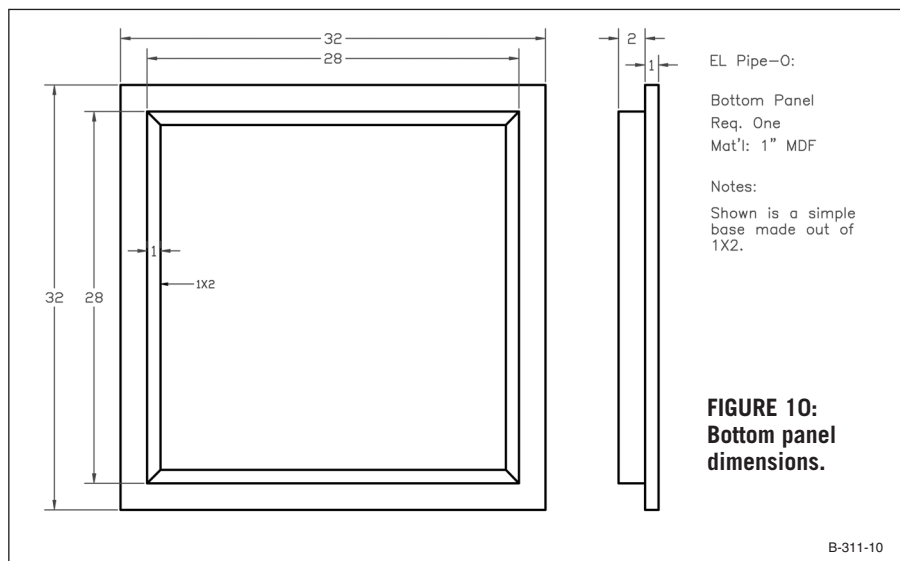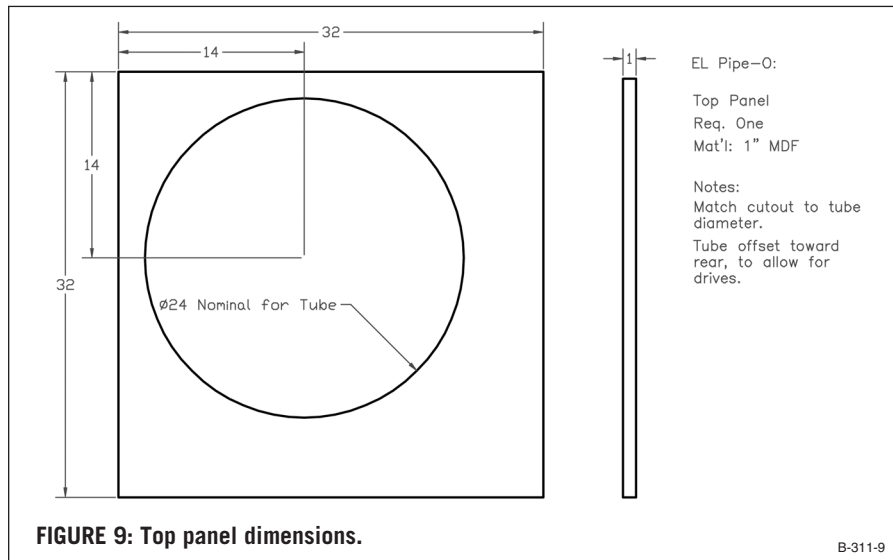

any ordinary high-quality gain circuit will do.

PASSIVE ACTIVE CROSSOVER

Figure 16 shows a "passive" circuit designed to be placed at the output of the amplifier driving the main speakers which filters and attenuates that signal for feeding to the amplifier(s) driving El Pipe-O. As with the active filter, the tolerances and such are not particularly critical, but note that this circuit is not designed to be driven by an amplifier with balanced outputs, where both output connections are "live." It assumes the amplifier (–) connection is at ground, and also assumes that the

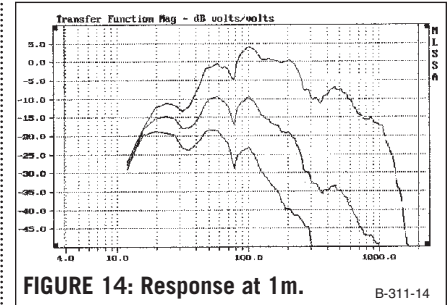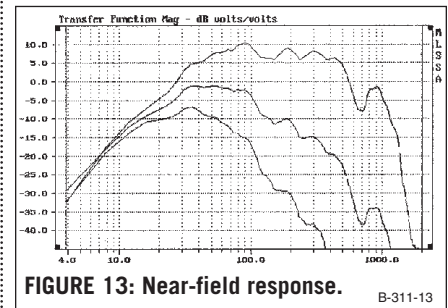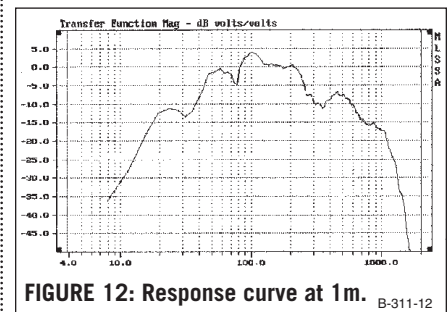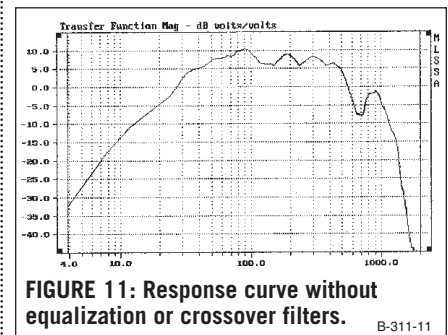

ground of the driving amplifier and the ground of the bass amplifier are at similar potentials (which they usually are). If you wish to build just one El Pipe-O for both channels, you can give each of the two woofers its own crossover and amplifier, or you can mix inputs at the input of the crossover, giving each channel its own input resistor with twice the resistance value shown in Fig. 16.

THE SOUND

Well, of course this is the best part. First,

you need to go through your record collection looking for material that goes down this low. A lot of nice-sounding music doesn't go below 40Hz or so, and if you listen to this material, you don't really get the impression that anything particularly special is happening.

This is good, because we didn't want the speaker to offer up a freak show of special effects where it's not wanted; we want neutral and seamless performance in the upper bass. No, we wanted the freak show to be down around 20Hz.


Movie soundtracks are a good source of this sort of thing: *Jurassic Park* or *Dracula*. Pink Floyd's *Dark Side of the Moon*. You know what kind of records we're talking about.

Funny things happen when your speakers are flat to 13Hz. You need to be careful about your tonearm, your windows, your neighbors, and your bowels. After we got the system running, we spent a hour or so going around the room bolting down or otherwise re-arranging knick-knacks, shelving, furniture, and windows that began rattling. After that, we called up our friends and had a little party. And another.

THE PARTY INCIDENT

The first listening sessions were run with 100W amplifiers. Of course, the El Pipe-O calls for monster amplifiers, so we acquired Pass X1000s, which can do about 4,000W peak (per channel) into 4Ω. The occasion of firing these up called for another party, during which we drank a lot of Cabernet and then decided to test the power-handling claims of the woofer manufacturer.


These claims were fairly accurate at

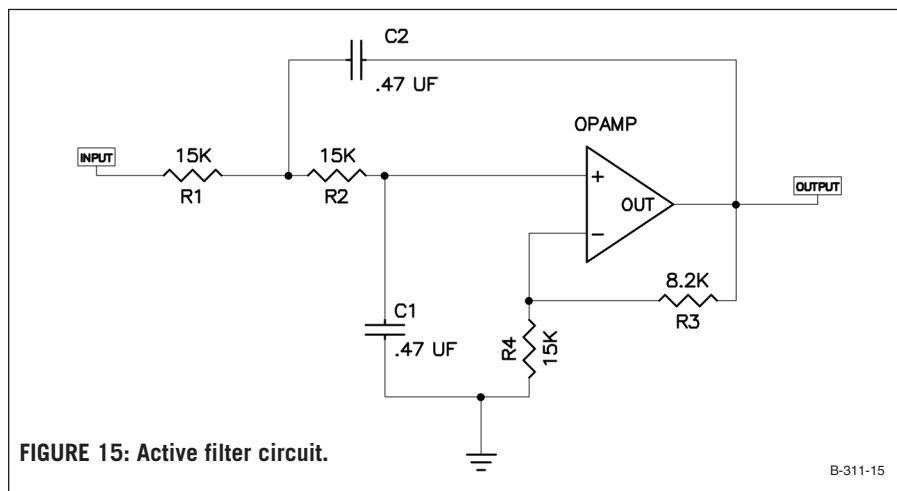

The Ultimate Acoustic Analysis System.

*For real-time testing of
Audio System performance!*

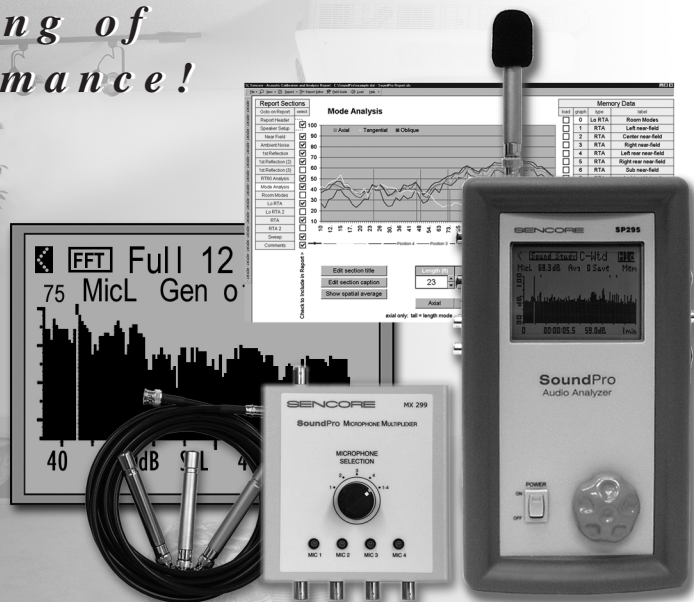- 1/12th Octave Real-Time Analyzer (RTA)
 - Energy-Time Graph (ETG) with octave & 1/2 octave band filters
 - Sound Pressure Level Meter
- Speaker Distortion Meter (THD+N)
 - Signal to Noise Ratio
 - Speaker Polarity Test
- Integrated Audio Signal Generator
- Handheld, Portable, Battery Operated
- Serial Data Download and Report Software



Powerful • Portable • Affordable

SENCORE

1-800-736-2673 • sencore.com • e-mail sales@sencore.com

Subscribe To The **SENCORE** News at www.sencore.com

The British specialists in tube amplifiers and pre-amplifier kits, loudspeaker kits and related publications

Visit our informative website:
www.worldaudiodesign.co.uk
 Enter our HD83 competition on-line



KIT88 integrated amplifier kit



300b PSE monobloc kit



Kel84 integrated amplifier kit



Series II modular pre-amplifier kit

World Audio design

World Audio Publishing Ltd.
 12a Spring Gardens.
 Newport Pagnell.
 Milton Keynes.
 MK16 0EE. England

tel/fax: 00 44 1908 218836
 e-mail: inquiries@worldaudiodesign.co.uk

800W peak each, and at the end of this event we were down to two woofers.

RECONSTRUCTION

Rather than spend another \$800 on woofers, we decided to try single woofers on each side, so we took apart the tubes and reconfigured them as 10' tubes with a woofer at the bottom. We made a nice cylindrical coupler out of MDF to mate the woofer to the tube (Fig. 17) and set them on the woofer's magnet on blocks of granite (Photos 3 and 4). On top of the coupler, we placed some of the kind of plastic grid used in elevator lights to keep the Dacron from

falling onto the woofer cones. The tubes were stuffed the same, and we used the same crossover filter.

Figure 18 shows the near-field output of the single woofer without the filters, which actually turned out a bit flatter than the twin driver models. The results of moving out into the room at 2m are shown in Fig. 19, and applying the filter in Fig. 20. Noting the differences between the twin- and single-woofer versions, you see that the single woofer gives flatter response at frequencies above 20Hz, but falls off more quickly below 20Hz. Nevertheless, it manages a respectable $\pm 2\text{dB}$ from 20 to 80Hz.

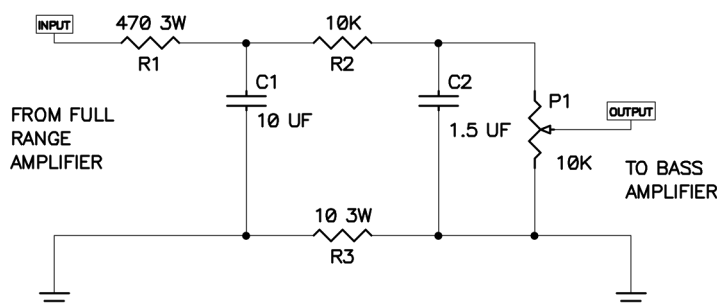


FIGURE 16: Passive filter circuit.

B-311-16

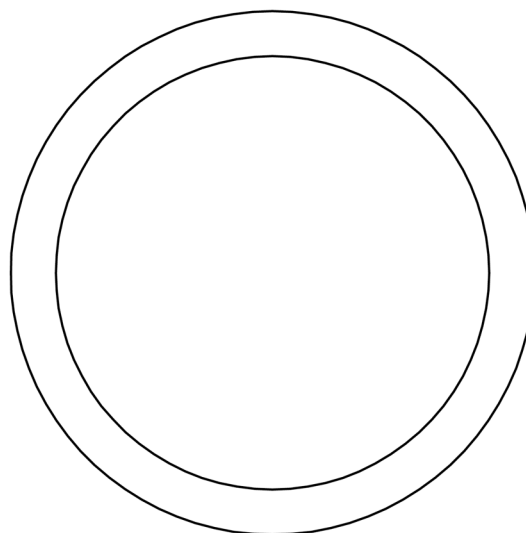


FIGURE 17: Cylindrical coupler.

B-311-17

The reconstructed version sounded about as good as the original, and probably gives a smoother transition to other speakers. It doesn't have quite the same power handling and doesn't go quite as low, but in our

opinion, it ended up being a slightly more elegant result.

CONCLUSION

Except for the sheer scale of the endeavor, this was a remarkably easy project. Sonotubes make great transmission lines, and the vertical floor to ceiling approach is simple and effective.

They might be tall, but the footprint is small, and maybe your spouse will let you keep them if you finish them properly. If you have an 8' ceiling, you can make two out of a 12' piece of 8" diameter, and find yourself decent 8" woofers resonant at about 40Hz. Then you can start having parties, too. ♦

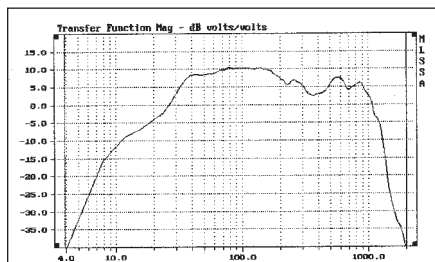


FIGURE 18: Single woofer near-field output.

B-311-18

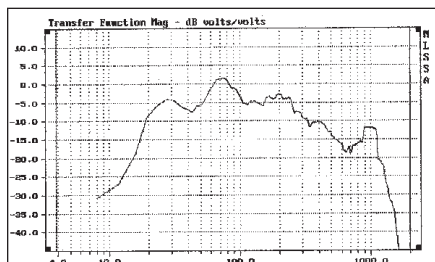


FIGURE 19: Response at 2m.

B-311-19

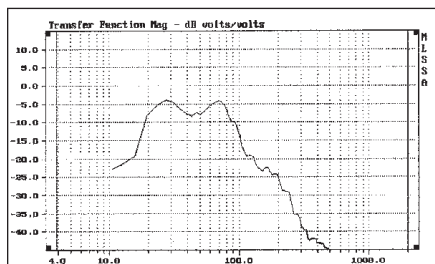


FIGURE 20: Response with filter.

B-311-20

Supplier
Of High
Quality
Speaker
Kits &
Components
For The Audio
Enthusiast



SELENIUM
LOUDSPEAKERS

vifa scan-speak

Cabasse

GOLDWOOD

B&C SPEAKERS



ACCUTON



VERSA-TRONICS INC.



LEAP

AEON

Components & Accessories

RAVEN

Crossover Design

Pioneer

115 S. Victory Blvd.
Burbank, CA 91502
Vox 818-846-9921
Fax 818-846-1009
www.speakercity.com



McCauley

**SPEAKER
CITY U.S.A.**

Orders Only! 800-595-9924
Mon-Sat 10am-6pm

ZALYTRON

**YOUR ONE STOP SPEAKER
AND SPEAKER COMPONENTS CENTER**

**Check our web site www.zalytron.com
for cutting edge technology in the
Speaker Industry. Need we say more?**

Call, Write, Fax or email for our latest catalog

Mailed FREE in the USA. Canada \$5 P&H, Worldwide \$10 P&H

ZALYTRON INDUSTRIES CORP.
469 JERICHO TURNPIKE, MINEOLA, N.Y. 11501
TEL. (516) 747-3515 • FAX (516) 294-1943
www.zalytron.com • email zalytron@juno.com

Our warehouse is open for pick-up 10 AM to 6 PM daily, Saturday 10 AM to 5 PM • UPS orders shipped same day • Minimum order \$50.00

Simple Satellites, Part 1

This pair of audio veterans presents their findings, as they set out to design a “simple” satellite system. **By G. R. Koonce and R. O. Wright, Jr.**

Since developing the infinite box (IB) subwoofer¹, we thought it useful to develop some simple companion satellites, requiring no crossover construction by the reader. Our goal was small satellites with a component cost limit of about \$50 each; however, the costs of some selected drivers have since increased.

You could use two such satellites for a two-channel stereo system, or several for a 5.1-, 6.1-, or 7.1-channel multichannel system. The subwoofer covers the range 25 to over 100Hz. All we needed was a satellite that covered from about 100Hz to 20kHz!

Ideally, the satellites would be built with shielded drivers to allow use near a TV or monitor. Such a satellite might not fit the exact specifications for multichannel speakers, but could be used for that purpose. By the conclusion of this work, we had modified two of our satellite types so they were no longer simple or cheap, but their sonic performance warrants documenting the modifications. *Photo 1* shows the five small satellite types developed in this work.

BACKGROUND (BY R. O. WRIGHT, JR.)

The genesis of this article dates to the early 1980s, when I attended the Consumer Electronics Show in Chicago and saw a full-range speaker (approximately 100Hz to 20kHz is considered full-range by most commercial OEMs) manufactured by one of Japan's leading electrical firms for the car in-

dustry. It was an unusual flat planar design, and later I discovered that it never made it into final production.

With the turn of the century, I began another technical odyssey, which in its final form would bring me full circle and inspire us to document the Infinite Box (IB) design concept. Since the late 1970s, I had used Owens-Corning's 700 Series sound damping material in speaker enclosures, but I had never seen it in any merchandised speakers—only in the prosound speakers, and not much of it there. This led me to ship GRK a package of the sound damping material to experiment with. GRK found it to be a most interesting material, so much so, that we generated a research article on IB box design, which appeared in *audioXpress*².

When we analyzed the data for the IB box design, we found the box size was somewhat independent of the speaker parameters. This led to an article¹ on a

simple, compact, and inexpensive subwoofer that would generate sound below 100Hz.

SATELLITE DRIVER(S)

To meet the criteria of a simple basic IB satellite design, we adopted a full-range speaker concept. This was the impetus for me to resume my search for a full-range driver. Those of you intrigued by the concept of a single full-range speaker and who have access to the Internet should try the “Single Speaker Website” (melhuish.org/audio/index.htm). This is an extensive website dealing with full-range speakers.

The full-range speaker design configuration has many technical advantages:

- component simplicity
- no problems with a crossover design and the component assembly
- only one box design

These are only a few of the major physical and technical advantages this type of design offers. My original search for a full-range driver began in the middle to late 1980s and yielded only very expensive esoteric drivers

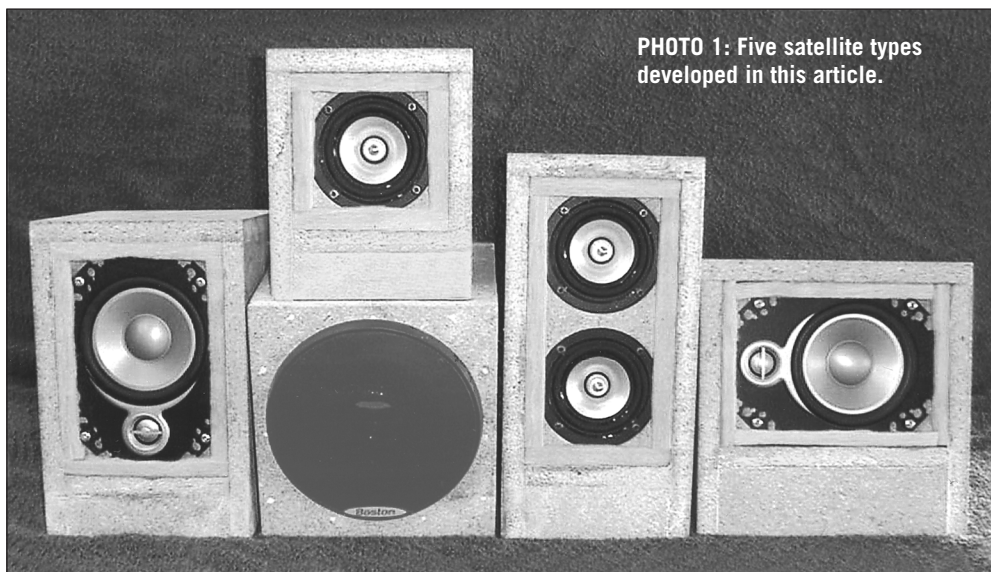


PHOTO 1: Five satellite types developed in this article.

that were not very practical for a normal design or pocketbook.

The modern-day search turned out to be an involved worldwide search spanning many months and did yield success. Over a period of months, GRK received a number of drivers to test to see whether they would meet our requirements (about 100Hz to 20kHz). In the end we chose only the best to turn into projects for this article.

DEFINITION OF SPEAKER

For the purposes of this article, we define a speaker as being composed of two components: the driver(s) and the enclosure/box, which is the mounting for the drivers. When combined, these two components form a complete speaker.

DRIVER CLASSIFICATION AND AUDIO CHARACTERISTICS

Basic moving-coil diaphragm drivers are designed in two general types. The first is a plain driver having a cone, or cone modified with a whizzer, a basket, and a motor mechanism. A whizzer is a small freestanding cone mounted to the existing voice-coil former and is used to extend the frequency range of the driver. Tweeters are a variation or special design of the basic driver. In a tweeter the diaphragm and the voice coil are made together. This produces a small, light assembly that can operate efficiently in the high-frequency range.

The second type is a compound driver, which consists of two or more plain drivers made as a single homogeneous unit with a built-in crossover. In smaller sizes, these drivers are mainly made for the automotive market and are classified as coaxial drivers or plate drivers, depending on their design. The drivers tested for this article were all two-way, and our discussion and definitions center only on these, although there are three-way and sometimes four-way compound drivers available.

The automotive coaxial drivers have the tweeter mounted in front of the low-frequency driver on the same axis. The plate drivers have a tweeter and the low-frequency driver mounted in a side-by-side configuration using one single mounting frame or plate.

In testing these, we noted some gen-

eral patterns about their frequency response. Most truly full-range plain drivers had small cones, 3" to 4" or less. The frequency response of these ranged from excellent to only acceptable, depending on the design. The larger full-range drivers used whizzers to extend their frequency range. The ones we tested always had very rough high-frequency phase and magnitude responses.

The compound drivers tested generally gave a reasonably smooth bass response and sometimes a smooth midrange response. Many of the car coaxes had midrange anomalies due to a poor transition from woofer to tweeter using the very simple crossover. The high frequencies seemed to be a little exaggerated (often referred to as "hot" on the top end), which is to be expected in a car driver.

Cars have a great deal of sound damping material built into the passenger compartment, which absorbs the high frequencies. They are almost always listened to in an off-axis configuration, and making the high frequencies a little exaggerated will even-out the total listener response. Even in home applications it

is not uncommon to listen to speakers in an off-axis mode.

Most of the coaxial drivers had rough high-frequency responses. The power cepstrum plots for the car coaxes also showed them full of echoes due to the tweeter structure mounted out in front of the woofer. Thus they might not sound as clean as other configurations. The only plate driver tested was the best of all the compound drivers. It gave a passable response in its original form.

MULTICHANNEL SYSTEMS

The two de facto standards in the multichannel systems are the present-day two-channel stereo, whose standards are well known, and the surround sound format by Dolby Laboratories, Inc. Dolby has three different standards in today's marketplace—5.1-, 6.1-, and 7.1-channel. We were able to obtain basic information on the three systems from the data on the 5.1-channel system³, but the complete technical specifications were unavailable at the time of writing. All three are defined by using specification numbers as a key to the format.

In the 5.1-channel specification the

SEARCH & BUY ONLINE
www.mouser.com

209,000+
**ELECTRONIC
COMPONENTS**

Semiconductors, Optoelectronics, Lamps & Holders, LED's, Displays, Wire & Cable, Connectors, Assemblies, Sockets, Terminals, Terminal Blocks, Capacitors, Resistors, Potentiometers, Crystals, Oscillators, Inductors, Transformers, Circuit Protection, Fuses & Holders, Resettable Fuses, Breakers, Thermistors, Varistors, Industrial Automation, Switches, Relays, Speakers, Piezo Devices, Microphones, Fans, Heatsinks, Knobs, Hardware, Cabinets, Racks, Enclosures, Batteries, Battery Chargers, Battery Holders & Snaps, Power Supplies, DC-DC Converters, UPS Systems, AC Adapters, Panel Meters, Test Equipment, Tools & Equipment, Supplies & Chemicals, Prototyping Supplies . . .

MOUSER 
ELECTRONICS

"5" denotes five discrete independent channels: a front center, front left, front right, surround left, and surround right speakers. The surround channels drive the two side speakers. In addition, a low-frequency effects (LFE) channel denoted by the ".1" drives one or more subwoofers. The bass from the other channels, which may have bass-limited speakers, can normally be redirected to the LFE channel.

It is recommended that the center speaker be full-range while limiting the surround channels' bandwidth to 100Hz to 7kHz. Most applications won't permit a full-range center speaker, so bass management is provided, limiting the center channel to above 100Hz when needed.

Generally, commercial equipment limits the bandwidth fed to all channels. The LFE will get only low-frequency information (120Hz maximum) and the other channels only the higher frequencies. Lower-priced equipment may use a fixed frequency to separate the channels; however, much equipment offers a selectable frequency of 80, 100, or

120Hz. This information indicates that satellites that cover 100Hz up are applicable to a 5.1-channel system.

CROSSEOVERS

Crossovers come in a vast variety of delineations and formats. Our market research showed that most available audio system crossovers (in contrast to mostly passive types built into speaker enclosures) are second- and third-order, with fourth-order being the top end of the range. The active crossovers were far more prevalent than the passive types in audio system designs. The automotive industry has pioneered the second-, third-, and fourth-order compact integrated low-frequency crossover amplifiers, which you could use for this application.

After considering our technical needs for finite control of volume to equalize the speaker SPLs and distinct separation of the bass from the treble so as not to over-drive the satellite speakers, we chose an AC powered active fourth-order (24dB per octave) crossover discussed later in this article.

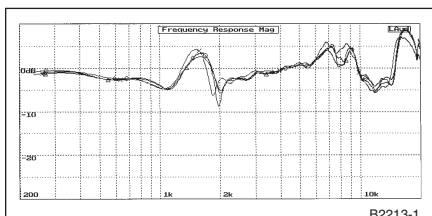


FIGURE 1: Measured responses of four Infinity 462.5CFP compound drivers.

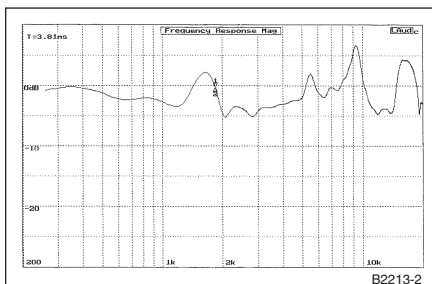


FIGURE 2: Response of Infinity 462.5CFP at 20° off-axis toward woofer.

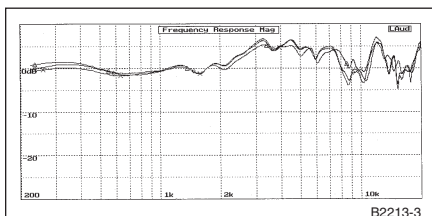


FIGURE 3: Effects of grille structure on Boston Acoustics FX5 coax.

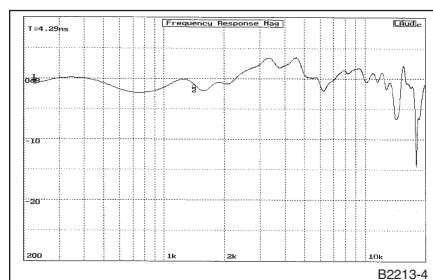


FIGURE 4: Response of FX5 at 20° off-axis toward crossover capacitor.

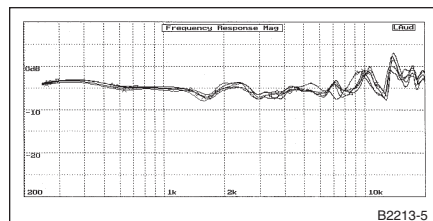


FIGURE 5: Measured responses of five TBspeakers W3-871s drivers.

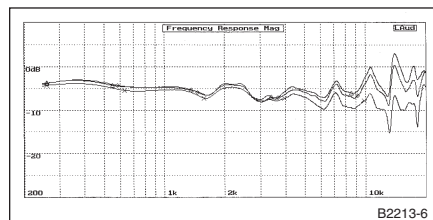


FIGURE 6: Measured directivity of TBspeakers W3-871s drivers.

BOXES

We preferred to keep the satellites small while using the IB approach to continue learning about this technique. These boxes were not assured of performance down to 100Hz via the IB design rules²; that would have made the boxes too big. We simply built them at a minimum practical size, and we would take what frequency response they offered.

It is doubtful that the IB approach offers a big advantage for systems doing 100Hz up. Thus you might try the selected drivers in other box types. You could build closed boxes from the designs shown by omitting the damping layers and making the back solid. It would be good to retain the damping panel, which forms a perimeter stiffener for the box walls. You could partially fill the boxes with your favorite damping material. Unless you can definitely keep all low-frequency content out of the satellite, we do not recommend a vented box with these small drivers.

DIFFRACTION SPREADING LOSS

The concept of diffraction spreading loss (DSL) is covered in references 2, 4, and 5. It basically refers to the fact that a driver will produce a different on-axis response in a small freestanding box than it does mounted in a wall. This can result in subwoofer/satellite systems that sound weak just above the subwoofer's upper limit.

With very small satellites this "weakness" can extend up to almost 1kHz. The result is a system that has the bass and highs, but sounds "hollow" because the midrange is partially missing. Many subwoofer/satellite systems, unfortunately, produce such sound.

The cure for small enclosures is DSL compensation (discussed towards the end of the article). For enclosures out in the room on stands, compensation for the full theoretical 6dB DSL is recommended. Our experience with large floor-standing enclosures with low

**TABLE 1
CATALOG INFORMATION ON
INFINITY 462.5CFP DRIVER**

Impedance: 4Ω
Power handling: 60W RMS, 180W peak
Frequency response: 75Hz–21kHz
Sensitivity: 90dB/2.83V/m (Equivalent to about 87dB/W/m)
Shielded: No

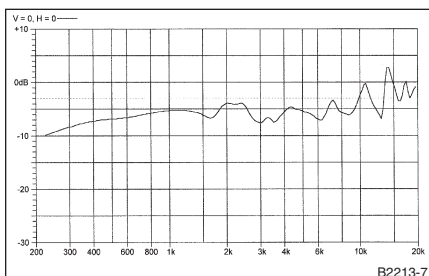


FIGURE 7: Effect of 6dB DSL on single W3-871s driver in 5 1/2" wide box.

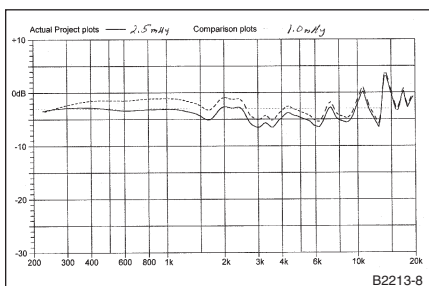


FIGURE 8: Response of dual W3-871s drivers giving 6dB DSL compensation.

mounted woofers is that 3–4dB DSL compensation can provide a well-balanced sound. We hoped to learn the proper DSL compensation for small floor-standing satellites.

SELECTED DRIVERS

One driver of choice is the Infinity Kappa 462.5CFP 4 × 6" plate compound driver (Table 1). Figure 1 shows the measured responses for four of these units. The response is not too smooth or flat, but note the droop from about 200Hz to 1kHz. This would offer some DSL compensation for a small box. The best axis for listening with this unit is about 20° off the tweeter centerline toward the woofer (Fig. 2).

We developed two enclosures using this compound driver that attempt to place the listener on the desired axis. The first approach (boxes #1 and #2) has the woofer and tweeter mounted side-by-side. This configuration, as developed in reference 6, places the listener on the proper axis by using mirror-imaged pairs with the tweeter al-

**TABLE 2
CATALOG INFORMATION ON
BOSTON ACOUSTICS FX5 DRIVER**

Impedance: 4Ω
Power handling: recommended amplifier is 12 to 100W
Frequency response: 60Hz–20kHz
Sensitivity: 90dB/W/m
Shielded: No

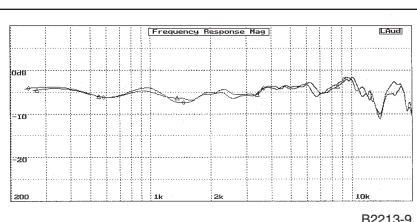


FIGURE 9: On-axis responses for two W3-881s drivers.

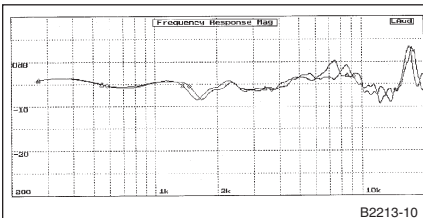


FIGURE 10: On-axis responses for two W3-879s drivers.

ways outboard. With the boxes facing straight out, the normal configuration for stereo listening places the listener on the desired axis.

Getting the desired listening angle with the conventional tweeter-above-woofer layout would require an unrealistic tipping of the front panel. Thus we placed the woofer above the tweeter for

auricap



**World's finest capacitor,
Sonically transparent,
Superior technical
specifications.**

- Auricap is the best I have tried by a long, long way.
Kendrick Pavey/VP Melbourne Audio Club
- Auricaps are great parts, and represent a significant step forward in capacitor technology and audio-musical performance... Better and cheaper. What more can you ask for?
Jennifer White-Wolf Crock, Sr. Technical Editor - Positive Feedback Magazine
- If you want absolute transparency, then you must give Auricaps a try.
Giorgio Pozzoli/TNTAudio.com

**OEM & dealer inquiries invited.
Call (800) 565-4390
www.audience-av.com**

Precision Acoustic Measurements Require Precision Microphones



PS9200KIT™ \$1650 USD

**A complete IEC and ANSI traceable Type 1 Measurement
Microphone System 2 Hz to 40 kHz, 15 dBA to 160 dB SPL**
*1/2 inch capsule *4012 Preamp *PS9200 2 Channel PS
*AC adaptor *WS1 windscreen *SC1 die cut storage case.
Options: 511E Calibrator; 1 & 1/4 inch mics; and Gain for
DRA's MLSSA and other board level products.

ACO Pacific, Inc.
2604 Read Ave. Belmont, CA 94002 USA
Tel: (650) 595-8588 FAX: (650) 591-2891
e-mail acopac@acopacific.com

ACoustics Begins With ACO™

the other set of enclosures (boxes #3 and #4). This approach has worked well in the past.

A CAR COAX

The best car coax in our testing was the Boston Acoustics FX5 unit (Table 2). Figure 3 shows the on-axis response for one FX5 unit with and without the grille structure supplied with the driver. Typical of the car coaxes, the tweeter level is too high relative to the woofer. Less typical is the fact that the grille and its mounting frame do not make a major response change.

The better-designed car coaxes had grille structures causing little adverse effect. On the FX5, the structure used to mount the tweeter gives a directivity that varies with which direction you move off-axis. The best angle for listening was about 20° off-axis toward the side where the tweeter’s crossover capacitor is mounted (Fig. 4).

A reason for building with the FX5 unit was the simplicity of the enclosure. You just mount the FX5 on the front of a box and use the supplied grille and frame. The enclosure has a vertical front panel to get the desired listening axis, and the driver is mounted inverted with the crossover capacitor at the top (boxes #5 and #6). We wished to see whether such a simple satellite would be acceptable. Readers can try the same approach with other car coaxes they may have on hand.

A 3" FULL-RANGE DRIVER

The final driver selected was the TBspeakers W3-871s shielded nominal 3" driver available from NUERA Acoustic Technologies (Table 3). TBspeakers is the name used in North America for drivers made by Tang Band Speakers. Since completion of this work, we have identified Creative Sound Solutions and RAW Acoustics as alternate sources for this driver. This was the only single-cone, full-range driver that we

originally located useful down to near 100Hz.

Good consistency is shown in the measured responses for five units (Fig. 5). This driver holds up well to 20° off-axis (Fig. 6). You need to listen to this driver nearly on-axis.

The small enclosures (boxes #7 and #8) developed for this driver indicated a

potential DSL problem. The modeled on-axis response (Fig. 7) for this driver in a 5½" wide box out in the room is suppressed all the way up to about 1kHz. Thus we developed a second enclosure (boxes #9 and #10) using two vertically aligned drivers per box. The top driver is used full-range, while the bottom driver is used only for DSL compensation. This

TABLE 4
BASIC DIMENSIONS OF ALL SATELLITES

BOXES	DRIVER(S)	FRONT HEIGHT	WIDTH	SIDE DEPTH	TIP ANGLE	APPROX. DEAD AIR VOLUME
#1&2	462.5CFP	8.4	8.3	6.0	19	66.7
#3&4	462.5CFP	9.55	6.3	6.0	10	66.7
#5&6	FX5 coax	7.35	7.0	7.3*	0	93.9
#7&8	W3-871s	7.0	5.63	6.4	10	43.2
#9&10	(2)W3-871s	11.4	5.63	6.4	12	82.4

Notes:
Linear dimensions in inches.
Front height is along front of box, not height when tipped.
Side depth is along side of box, not depth when tipped.
Tip angle is degrees front panel is tipped back.
Dead air volume is box volume between front panel and start of the damping layers in cubic inches.
*Depth for boxes #5 and #6 includes driver and grille sticking out in front of the box.

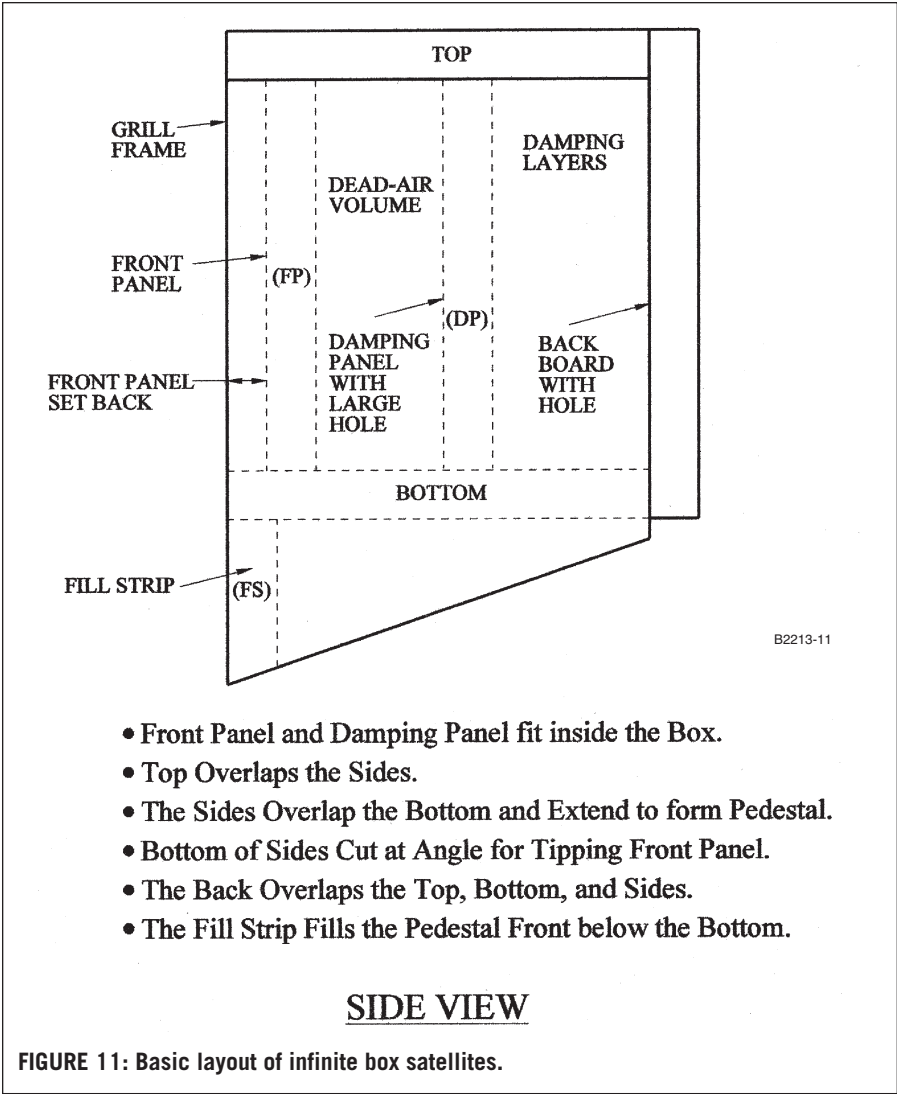


TABLE 3 CATALOG INFORMATION ON TBSPEAKERS W3-871S DRIVERS
Impedance: 8Ω
Power handling: 15W rated, 30W maximum
Frequency response: 110Hz–20kHz
Sensitivity: 87dB/W/m
Shielded: Yes

violates our goal of no reader-built crossover, but it is simply a single coil.

The modeled on-axis response (*Fig. 8*) for the two-driver system with coils of 1.0 and 2.5mH shows the coil inductance is not critical. We thought the DSL compensation thus offered was worth the trouble of a second driver and single coil, because it stayed within our cost range.

A potential problem with these 3" full-range drivers was their ability to play loudly enough. They are rated at 15W input with a power sensitivity of 87dB/W/m (*Table 3*). Its main advantage is being fully shielded.

With the single-driver satellite you have a system with no crossover above 100Hz. The dual-driver satellite has two of the same driver type producing the midrange slowly fading to a single driv-

er for the high frequency portion. We designed both enclosure types using this driver to place the seated listener near on-axis with the driver producing the high frequencies.


ALTERNATE DRIVERS

Since completing the satellite construction, we discovered that Parts Express now offers some of the drivers sold by TBspeakers. They do not offer the W3-871s unit that we used, but do offer some other promising nominal 3" units. We tested two of these types as possible alternatives. Factory response plots and other test results are available on the Parts Express website.

Figure 9 shows the measured response of two samples of the TBspeakers W3-881s shielded driver (Parts Express #264-812). This unit does not look

as good to us as the W3-871s, but is surely a usable alternate. This driver will mount in the same hole as the W3-871s with a bit of filing and relocating the mounting screw holes. We performed no listening tests with this driver type.

Figure 10 shows the measured response of two samples of the TBspeakers W3-879s shielded driver (Parts Ex-

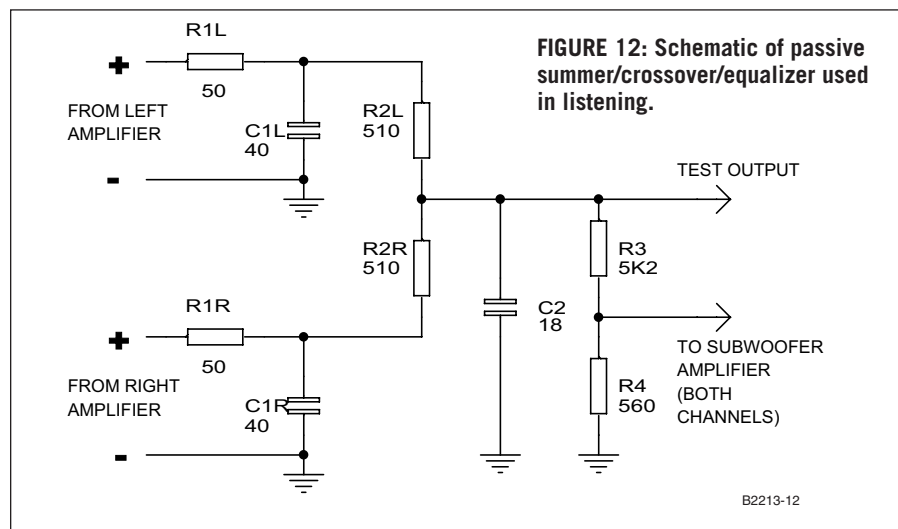

Sound Product. Pure Sound.

Improve your audio experience with non-inductive **metal foil resistors** by Alpha Electronics.

- Metal foil technology
- Available in *any* value
- Quality sound **for less**

Pure and simple...

Contact Sara at **(763) 258-8550**
Email: audiofoil@alpha-amer.com

AE Alpha Electronics Corp. of America
Minneapolis, Minnesota
www.alpha-amer.com



JENA KITS!





18 & 22 gauge Ultra-Wire
for your projects



Maringo 320 I.E.C.
Deep Immersion CRYO

All I.E.C. and NEMA terminations available.

CRYO-Hubbell Duplex

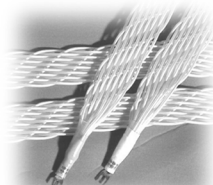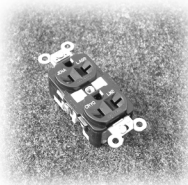


Speak-Easy Cables

Our expensive ultra high-end products have earned us a "Formula 1" status. Surprising to some, we also offer very affordable and DIY products stepped in the same design philosophy.

Our authentic liquid nitrogen cryogenic immersion techniques are definitive state of the art.

Our DIY components offer the utmost performance at popular prices, all immersion CRYO treated.

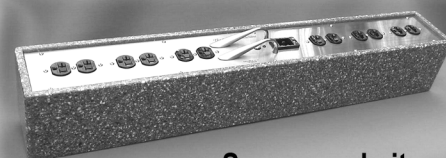DIY interconnect and speaker cable kits
RCA and XLR cable and panel components
AC power parts - wide assortment



See our website

JENA LABS
www.jenalabs.com

press #264-810). These curves show a much larger dip in the 9 to 16kHz range than shown in the factory curve, and we doubt these units would sound as good as the W3-871s units. This driver mounts in the same hole as the W3-871s. Again, we did no listening tests with this driver type.

BASIC CONSTRUCTION

Table 4 shows basic dimensions of all the satellites as constructed from $\frac{5}{8}$ " particleboard. For all boxes, except those for the car coax, the front panel is recessed to provide a frame for the grille cloth (Fig. 11). A vertical damping panel with its center cut out is mounted near mid-depth. This panel forms a perimeter stiffener on the box walls while retaining the forward side of the Owens-Corning #705 damping-material layers. The back board slightly compresses the damping layers and contains a hole about 120% of the driver cone area.

Owens-Corning offers a family of materials called the 700 Series Insulation. This series has rigid and semi-rigid fiberglass-based materials of a variety of densities, which are available in a variety of thicknesses and come unfaced or faced with various plastic materials. All these IBs use a nominal 2" thickness of the #705 material, which we refer to as OC #705 damping material and has a density of about 5–6 lb per cubic foot. You could use one layer of nominal 2" material, or two layers of nominal 1" material as we did. If the material you have is "faced," peel it off.

At this time we do not know of a direct equivalent to the OC #705 damping

material. For these satellites, operating from 100Hz up, you should feel free to experiment with other high-density fiberglass-based tangled-fibrous materials that you find available locally.

To minimize box size, we simply screwed the back on to the top, bottom, and sides of the box. Since particleboard has little holding power for screws driven into the edge, we glued $\frac{1}{4}$ " dowels into the box pieces to take the screws. Building a removable back that will cap the rear of the box and fit accurately is a problem. We cut the back about $\frac{1}{8}$ " oversize in both dimensions so that after installation we could rout it to size with a flush-cutting bit. This makes extra work, but yields a small box that looks good.

Our plan for finishing the boxes was to apply stick-on vinyl, then staple on the front grille cloth, and finally put a thin frame around the grille edges. See details on finishing boxes using this construction in reference 7. You should feel free to use your favorite finishing method.

We built the boxes for the FX5 car coax drivers with the front panel capping the front of the box. This fit the same way as the back board: made oversize and then cut flush with a router. These boxes use the grilles and frames that come shipped with the drivers.

Most of the boxes required that the front panel be tipped at an angle. We accomplished this by extending the box sides past the bottom board and cutting them at the desired angle, thus tipping the entire box. All these boxes are rectangular internally.

For use on stands, you can cut this bottom "pedestal" such that the box stands vertical with perhaps another board added at the pedestal bottom. Note that even vertical-standing boxes need a short pedestal to accommodate the driver wire. With an IB you can't easily run the wire out the back of the box. The bottom pedestals of boxes #9 and #10, for the dual 3" drivers, were extra high to mount the single crossover coil in this location.

Keep the following in mind when building small satellite boxes:

- 1) When you place a small driver in a front panel that is $\frac{5}{8}$ " thick, you will "strangle" it by restricting the flow of air to the rear of the cone. The front panel must be relieved by router or by hand in the areas between the driver struts connecting the frame's front rim to the magnet structure. This is especially true of drivers intended for automotive application where they would normally mount in a thin metal panel.
- 2) You must accurately cut the various pieces to construct small boxes; you will not be able to hide $\frac{1}{16}$ " errors. The designs shown minimize cutting error problems.
- 3) In some cases you must flush-mount the driver to assure the proper response.
- 4) Some front panel treatment is necessary to limit high-frequency edge diffraction problems at the grille frame.

LISTENING TESTS (BY G. R. KOONCE)

I performed all listening tests in my

Notes:

- 1.0 Both amplifiers do not invert the signal.
- 2.0 The summer/crossover/equalizer drives both subwoofer channels and sets level
- 3.0 Satellites are driven in reverse polarity to subwoofer.
- 4.0 The summer/crossover/equalizer was developed for the subwoofer, see reference 1

See Note 3.0

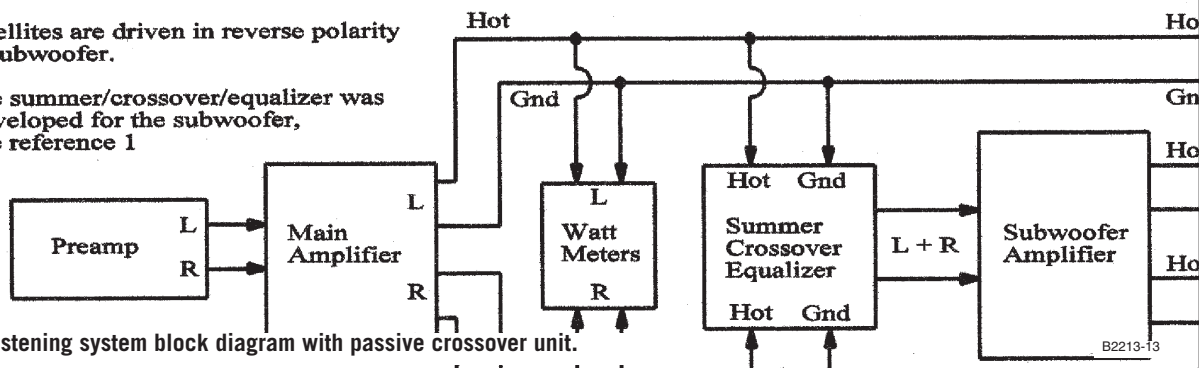


FIGURE 13: Listening system block diagram with passive crossover unit.

garage using the 12" IB subwoofer developed in reference 1, for a two-channel stereo system with the subwoofer in the center and the satellites to each side. All speakers were on the floor and away from all walls. I used standard music CDs and SACDs, but no movie soundtracks or other special recordings.

PASSIVE SUBWOOFER CROSSOVER

The first listening tests included the passive summer/crossover/equalizer previously developed for the subwoofer (Fig. 12). This approach feeds the full bandwidth signals to the satellites (Fig. 13). These signals are then summed and filtered to provide a second-order low-pass and then fed to the subwoofer amplifier.

This approach requires that the main amplifier driving the satellites have both speaker returns tied to amplifier ground (see reference 1 for other requirements). The advantage of this approach is its simplicity. The disadvantage is that the satellites see the bass frequencies, which limits their ability to play loudly.

I tried all five-satellite pairs with this configuration. Warble tone sweeps verified that all satellites required connection with reverse polarity to integrate properly with the subwoofer. Both amplifiers I used in this testing do not invert the signal.

It was quickly evident that this approach severely limited the playing level, as the tiny cones in all the satellites were dancing around badly. The boxes with the Infinity plate drivers (#1-#4) could play at a reasonable level, as could the FX5 car coaxes (#5 and #6). The boxes using the 3" full-range speakers (#7-#10) were limited pretty much to background playing levels via this approach.

The conclusions about each satellite type with this configuration are the same as for later testing using actual crossovers. The basic conclusion is that this simple approach is useful only for playing background level music with small satellite boxes.

SECOND-ORDER CROSSOVER PROBLEMS

The plan next called for testing the satellites with second-order crossovers, first active and then passive units. All did not go well. Reconfigured with two active second-order monaural cross-

overs, the system was working as intended. Suddenly all sorts of bad sounds emerged from the speakers requiring immediate system shutdown. Fortunately, no speakers were harmed.

The basic system using only the main amplifier was determined to play

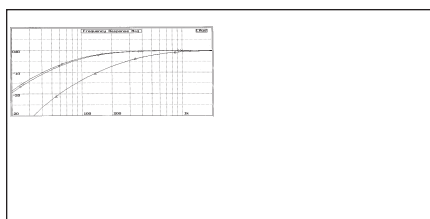


FIGURE 14: Response of FMOD high-pass crossovers.

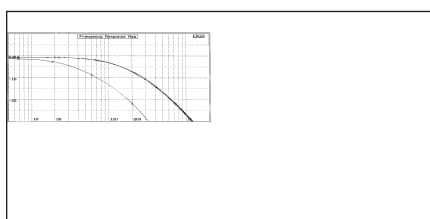


FIGURE 15: Response of FMOD low-pass crossovers.



... for the love of music ...

Atlantis • Audio Note • Benz-Micro
Billy Bags • Blue Circle • Cain & Cain
Cambridge Audio • Chord
Consonance • Echo Busters
Final Laboratory • Grado
Jean-Marie Reynaud • JENA Labs
Kuzma • Living Voice • Loth-X
Manley Labs • Music Hall • nOrh
Shanling • Shun Mook • VansEvers
Vecteur • WAVAC • Zoethecus

Bloomington, Indiana
812-320-4004
www.venushifi.com

SPEAKERWORKS

SPECIALISTS IN SPEAKER REPAIR AND REPLACEMENT GRILLES

FACTORY AUTHORIZED FOR:
ADS, Advent, Altec, B•I•C
Venturi, EPI, E-V, Cerwin-Vega,
Infinity, JBL Pro & Consumer

WE SELL Grille Cloth, Dust Caps,
Adhesives, Cones and Spiders.

REPLACEMENT GRILLES for
Altec, B•I•C, Cerwin-Vega, JBL
& Marantz, Plus CUSTOM Work

**REFOAM KITS FOR MOST
SPEAKERS - only \$25 (JBL
slightly higher). Repair Kit For
Two Speakers Includes Shims,
Dust Caps & Two Adhesives**

WE BUY BLOWN SPEAKERS: ALTEC, E-V & JBL



1-800-526-8879



NO CATALOG AVAILABLE

CALL US FOR HARD TO FIND DISCONTINUED PARTS
4732 South Mingo / Tulsa, Oklahoma / 74146

just fine, and the subwoofer amplifier and electronic crossovers tested on the bench could not be made to act up. However, I was reluctant to try these crossovers again and decided to use the fourth-order crossover, which proved to be so "right" that I never returned to the second-order types.

Unfortunately, these active crossovers were needed to supply gain controls for listening with the passive second-order crossovers. I had purchased (from Parts Express) some of the small Harrison FMOD passive crossover units, which come as pairs for the left and right channels and plug into the amplifier input, and then the normal input wire

plugs into them. They are available as second-order high-pass (HP) or low-pass (LP) units at a variety of frequencies. Because I was not going to be able to listen to these units, I decided to test them to see whether they did as claimed when "plugged into any amplifier."

I had purchased a pair of LP (Parts Express #266-254) and HP (Parts Express #266-274) units at 100Hz, so I could test the individual units as second-order crossovers or cascade the pair (plug one into the other) and test them as fourth-order crossovers. I had been told that these units could be "stacked" this way.

I tested the FMOD crossovers using Liberty Instrument's Audiosuite. Thus they were driven by a low impedance source and loaded by about 50k Ω , typical of the input impedance range for amplifiers. Figure 14 shows performance of the HP units.

Individually, the units produce the anticipated response. The two units cascaded do not produce a fourth-order response and the level is about 13dB down at 100Hz. It is clear the HP units should not be used cascaded.

The LP units also show a reasonable response (Fig. 15) used alone into about 50k Ω . Note there is some low-frequency loss, slightly less than a dB. Again, cascading two of the units to attempt a fourth-order crossover does not work, as the response shows more low-frequency loss and is down about 13dB at 100Hz. Clearly, you should not directly cascade the FMOD units in an attempt to make a fourth-order crossover. Such

cascading would be practical if you placed a buffer amplifier between the FMOD crossover units.

I then tested the individual crossover units with an additional 10k Ω load; the total load now being about 8.3k Ω . The HP test result (Fig. 16) shows the -3dB point has moved to about 162Hz and the response is down 5.7dB at 100Hz. The LP response (Fig. 17) shows a low-frequency loss of about 2.8dB and is only down by an additional 1.85dB at 100Hz. Clearly, you should use the FMOD units only when the input impedance of the amplifier they drive is about 50k Ω or above.

One problem with these passive crossovers is their expense. If you plan to try several frequencies, the cost could exceed that of buying a variable-frequency electronic crossover. However, they are handy for testing or where space is limited.

FOURTH-ORDER CROSSOVER

I next configured the system with an active fourth-order crossover (Fig. 18), an Applied Research and Technology Model #310 unit (available from Parts Express). This crossover can be used as either a single channel three-way or a stereo two-way crossover with adjustable crossover frequencies. It has gain controls for all outputs along with the ability to mute any individual output. This unit has balanced XLR jacks along with single-ended 1/4" mono phone jacks for all inputs and outputs.

I used the single-ended inputs/outputs with the Radio Shack phone plug to RCA phono jack adapters (#274-320 or #274-884). Be a bit careful with these adapters, because I found the shell contact for the ground was undersized, so I had to squeeze the phono plug shells with pliers to assure a solid ground connection.

This crossover worked well and con-

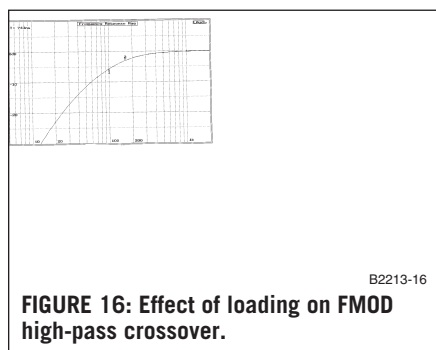


FIGURE 16: Effect of loading on FMOD high-pass crossover.

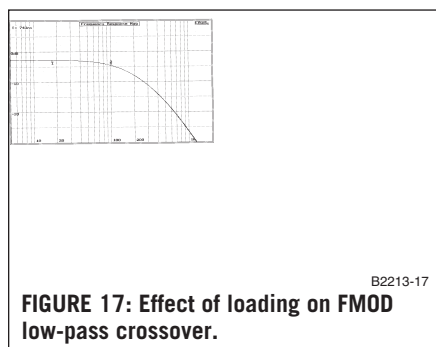


FIGURE 17: Effect of loading on FMOD low-pass crossover.

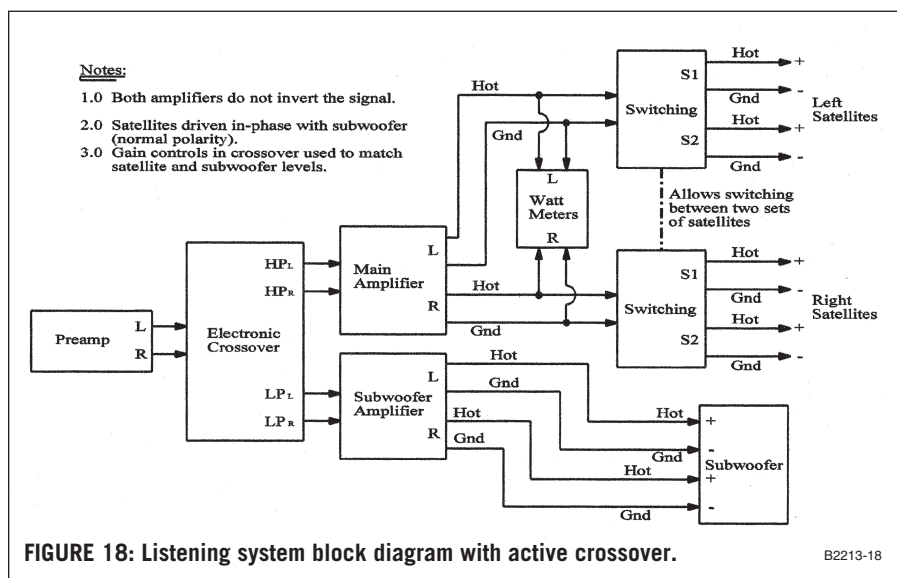


FIGURE 18: Listening system block diagram with active crossover.

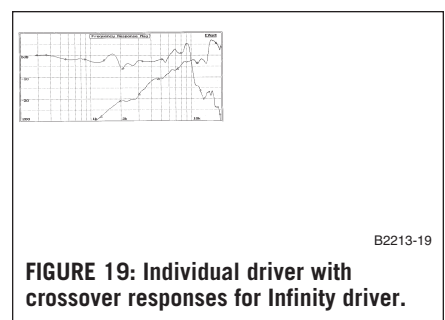


FIGURE 19: Individual driver with crossover responses for Infinity driver.

vinced me that a fourth-order crossover is the way to go when using small satellites in a two-channel system. A higher-order crossover would probably also be fine, but the fourth-order offers outputs that are in-phase at the crossover point. With a multichannel system, the receiver/amplifier should provide the needed crossover functions if you make sure to set it so all the satellites are fed a restricted frequency range. One of the labeled frequency points on the ART #310 crossover's scale was 110Hz, so we used it throughout the testing. In all cases using this crossover, the satellites were driven with the same polarity as the subwoofer.

Note in Fig. 18 that the wattmeters monitor only the power to the satellites. Also, the system has switching between two pairs of satellites without changing the input to the subwoofer. This allowed direct comparison of two satellite pairs while playing music. With this crossover, the satellites could play at a much higher level, because they were not receiving low-frequency signals.

After many years of working with speakers, I was a bit shocked to hear drums pounding away while I lifted the satellite grille cloth to see the cones barely moving. Loud music was possible with less than 10W into the satellites.

INFINITY PLATE COMPOUND DRIVERS

By the conclusion of this work we had modified the Infinity compound drivers used in boxes #1–#4. The listening results in this section pertain to using the drivers as purchased; results with the optional modifications are covered later.

Boxes #1 and #2 use these compound drivers in a side-by-side configuration, while boxes #3 and #4 use them in a woofer-over-tweeter configuration. In comparisons, boxes #3 and #4 won on

all points. The side-by-side configuration had shown a very wide sweet spot in past incarnations, but here seemed no better than boxes #3 and #4. From here on, discussion pertains only to boxes #3 and #4.

These boxes produce a very high presence sound, but are not “in-your-face,” because the image is from the plane of the boxes rearward. They will play very loudly, and in general the sound is better than I had expected from looking at the driver test responses. The highs do not sound as clean as I would like, but are not “hard.” I had hoped for better performance from these compound drivers.

This is an acceptable satellite, but should be used on the floor and not on stands. The tonal balance would probably improve with the boxes nearer the rear wall, but imaging might suffer.


The best listening was with the boxes facing straight out and not angled toward the listener. This is a good satellite choice if you play loud music. These drivers played at 20W average input and loved it. The drivers are not shielded, and the satellites are nominal 4Ω systems.

BOSTON ACOUSTICS FX5 CAR COAXES

Boxes #5 and #6 use these drivers. These satellites are clearly too “hot” in the high end and sounded a bit strident. The boxes sounded best angled outward slightly. By playing with this angle you can control the sound a major amount.


These satellites have very high presence with a bit of “in-your-face” sound. They are not good candidates for use on stands, but probably sound best near the floor/rear-wall interface.

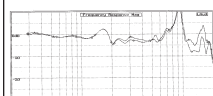These drivers have the highest sensitivity of all the ones we tested and will play loudly. On the floor, away from the rear wall, they do have that “hollow” sound due to DSL, and they do not



B2213-20

FIGURE 20: Response of bare woofer for Infinity driver.

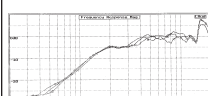

B2213-21

FIGURE 21: Response of bare tweeter for Infinity driver.

οι ηχοποιήτες

DYNASONIC

Planar transducers combining

➤ exceptional sound performance
and ➤ design challenges offered by **BIC**

info: The Binary Interlaced Coil technology, is based on a proprietary diaphragm (Patent pending) of two symmetrical coils of aluminium, printed one into each other on a very thin 12μ high temperature polyimide film, aligned within the dense field of a Neodymium magnetic structure.

This double coil configuration, firstly gives the flexibility of use either in series connection for maximum sensitivity or in parallel for increased power capability.

Secondly the **BIC** technology with its symmetry can inspire and motivate designers to a variety of applications:

- Direct Digital Loudspeaker
- Crossing over at two frequencies
- Push - Pull Circuitry
- Feedback Optimizing Circuitry
- Other inventive output circuitry such as

2 terminal network	4 terminal network
* Single coil operation	* two winding transformer
* double coil series	* two winding autotransformer
	* two winding P. Pull

PL-160

PL-97*

*available after 05-31-2003

DYNASONIC LTD, 59, tritis Septemvriou str., Athens 104 33, Greece, www.dynasonic.gr, E-mail: info@dynasonic.gr tel.: 0030-210-88 30 311, fax: 0030-210-82 29 483

The audio engineer's hands-on X-over design & speaker voicing tool.

ATTENTION!
Audio professionals, hobbyists, installers and University students/professors.

The Virtual CROSSOVER BOX™

by **Vidsonix** Audio 4 Industry

MODEL VCB-100

Shipping Wt:
7 lbs.
K-VCB100
\$249.95

Now includes our exclusive Crossover Design Pocket Slide Tool!

Call 1-888-924-9465 today or order on-line at www.audioXpress.com!

Old Colony Sound Laboratory
PO Box 876, Dept. LIS2
Peterborough, NH 03458-0876 USA
888-924-9465 Fax: 603-924-9467
E-mail: custserv@audioXpress.com

We also design and manufacture home theater, marine, and professional loudspeakers and accessories. Individual drivers, including all Thiele-Small parameters, are also available on our website.

Vidsonix Design Works
28415 Industry Dr. #510, Valencia, CA 91355
(661) 775-2760
www.VIDSONIX.com
©2003 VIDSONIX. All Rights Reserved

sound as good as boxes #3 and #4. Their main merits are the very simple construction and low cost. These drivers are not shielded, and the satellites are nominal 4Ω systems.

TBSPEAKERS 3" FULL-RANGE DRIVERS

We first tried the single-driver boxes #7 and #8. The satellites were toed in so that the drivers aimed directly at the listener. These boxes have a very pleasant musical sound, but something was missing. The highs were there, and it was clear you were not listening to a metal-dome tweeter, but to a mellow soft-dome tweeter.

I liked the basic sound, despite the "hollow" effects of small boxes due to DSL. If used on the floor against the back wall or in a bookcase, they might be fine. However, even on the floor out in the room they are not acceptable.

Playing level was not really a problem. Background listening was only a fraction of a watt into each satellite, and about 5W per satellite was reasonably loud. There should be no problem in this regard for a multichannel system. The imaging and clarity were good.

Switching to the dual-driver boxes #9 and #10—again aimed at the listener—was a shock. From systems that were weak in the 100Hz to, say, 500Hz range, you now had systems that were strong in that range. To my ears they were too strong when on the floor, sounding ab-

solutely bass heavy. It made voices slightly husky. I needed to keep reminding myself that 3" drivers were producing that sound.

As with the single-driver boxes, a few watts to each satellite was sufficient for listening. Switching between single- and dual-driver boxes on orchestral music was very interesting. The dual-driver boxes revealed all sorts of music that was being lost with the single-driver boxes. I thought the dual-driver boxes would sound better off the floor (more later).

I experimented with coils from 1.3 to 2.5mH and liked the design value of 2.5mH best. This is not a good satellite choice for boxes that will be on the floor and against the back wall, such as in a bookcase. It is an ideal choice for boxes on stands out in the room. Clarity and imaging were very good, but the strong output in the 100–500Hz range yields what I call "Cambridge" sound, and some may be bothered by a lack of high presence. On the floor, these satellites are just great for listening to classical music at background level.

I thought that perhaps the 6dB DSL compensation for boxes #9 and #10 was excessive. Reducing the DSL compensation to about 3dB could be accomplished by simply inserting a 3dB L-pad between the coil and the bottom driver. Theory says this is a bad idea. If you pad a driver, you raise its Q and destroy the electrical damping. Also, you now

have the two tiny woofers sharing the same air volume while playing at different levels and having different Qs.




Would the use of an IB and the fact that the drivers were not used to handle the bass overcome these problems? It was simple enough to try, so I listened with such a pad included. Theory wins this one, as the sound was terrible. The DSL compensation was reduced, but the sound of musical transients was horrible and produced some very strange-sounding drums.

As an alternative, I raised boxes #9 and #10 up off the floor on 13" tall open boxes of about the same footprint. This gave the best sound, even though this aimed the listening axis a bit too high. There is little doubt that these are the best satellites that we developed (with unmodified drivers), if you plan to put the speakers on stands out in the room.

Build boxes with vertical front panels and use stands that place the top driver at about ear level. With the boxes 13" off the floor, the presence was better, yielding a better overall sound.

SUMMARY FOR 3" FULL-RANGE DRIVER BOXES

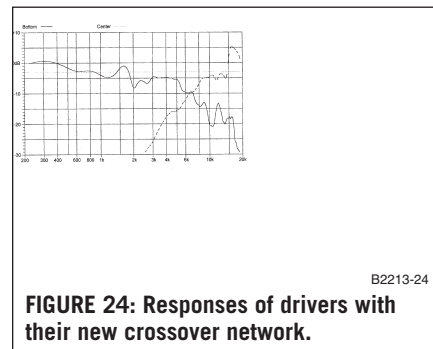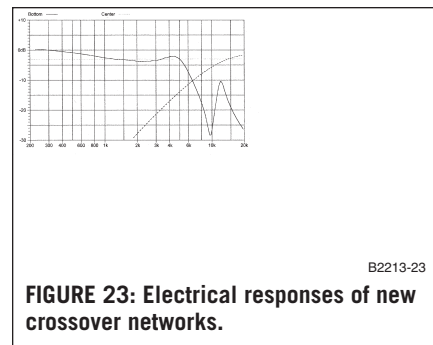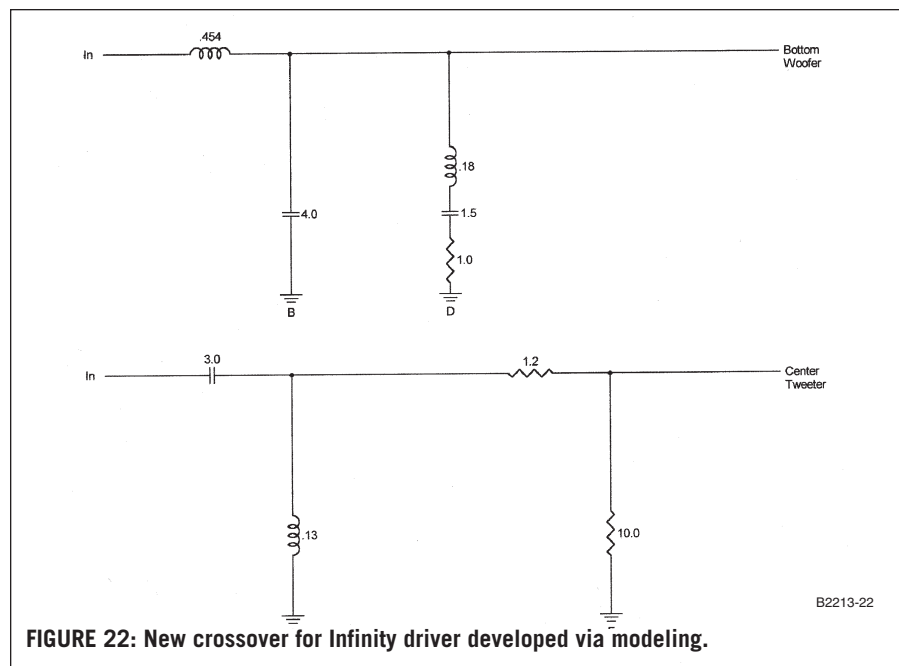Even when on the floor, the single-driver satellite boxes #7 and #8 suffer from a "hollow" sound due to DSL. They may be fine when near the back wall, as in a bookcase, but they would be terrible on stands out in a room. If you play your



music extremely loudly, these are not acceptable candidates—they are shielded drivers, and the satellites are nominal 8Ω systems.

The dual-driver satellite boxes #9 and #10 are the best satellites we developed—before modifying the Infinity drivers. I thought that on the floor, they were a bit overcompensated for DSL. These small boxes would be ideal out in the room on stands. They can really play no louder than the single-driver boxes, even though they sound louder due to the filled-in 100–500Hz range. Thus they are not the best choice for playing loud music.

Used alone, without subwoofer, they would make good computer speakers because of the limited power requirement with the listener so close. Again, the drivers are shielded, but these satellites are nominal 4Ω systems.

INFINITY DRIVER MODIFICATIONS (BY G. R. KOONCE)

ROW and I both shun writing construction articles that require you to modify the driver. Here is a voluntary major modification that we developed after completing the basic satellite work. When done, your satellites will no longer be simple or cheap. They will, however, be good-sounding, small satellites that are worth the cost and effort.

I was not happy with the sound of the




Infinity plate driver in either box type. I had expected more from this driver based on it being a real two-way compound driver and its reputation. These are high-technology drivers with the woofer and tweeter using a ceramic-coated aluminum cone and dome.

The test results had not been encouraging, leading you to expect a “bright” sound, probably by design because of the intended automotive application. I did expect clean highs with a ¾” dome tweeter, but believed I did not get them. I thought that some simple modifications such as changing the crossover capacitors to film units and adding a little padding on the tweeter could improve the sound.

I started by examining the factory crossover (CO) network, composed of a second-order low-pass (LP) on the woofer and a first-order high-pass (HP) on the tweeter, both using non-polar electrolytic capacitors. Both drivers are nominal 4Ω with the tweeter driven with reverse polarity. The LP coil value was unmarked, but assuming a Butterworth LP for 4Ω, the 5.6μF capacitor would mean CO about 5kHz. The 3.3μF capacitor in the HP meant CO at about 12kHz. But the response (Fig. 1) sure did not show a gaping hole from 5 to 12kHz, so something was strange.

SOME STRANGE TEST RESULTS

I disconnected the tweeter from the woofer so I could drive them independently and tested one unit. The individual responses of the drivers with their CO (Fig. 19) tell the story. The woofer does not go away at 5kHz, but is the major contributor up to 10kHz. While not shown, the LP network interacts with the woofer impedance to produce additional electrical peaking. Those highs I did not enjoy were coming from the woofer and not the dome tweeter. The tweeter makes a low contribution

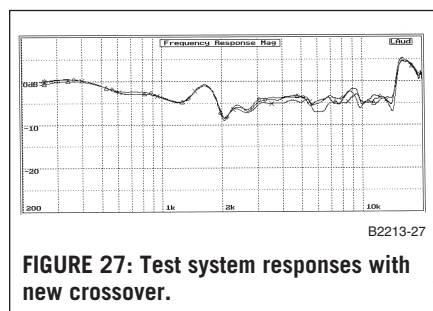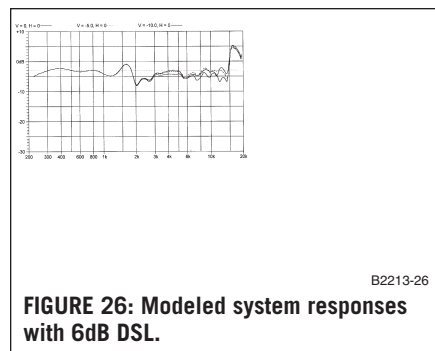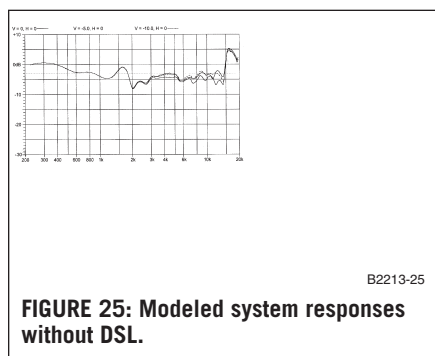

PTFE Insulated Twist-eye Terminal Strips



Made from the finest materials.

Lightly tinned 14 gauge OFHC Copper twist-eyes made and inserted by hand into ½” virgin PTFE stock.

Perfectly sized for larger audiophile grade components.


Complete with mounting holes and available with 1 to 6 terminals per strip.



www.grennanaudio.com

PMB 302, 8825 W. Olympic Blvd.
Beverly Hills, CA 90211

Our Samples Are Better Than FREE!

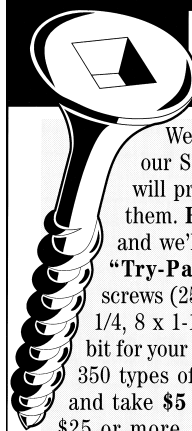

We're so sure you'll love our Square Drive Screws we will practically pay you to try them. **Return this ad with \$5** and we'll send you our famous “Try-Pack” Sampler of 100 screws (25 each of #8 x 5/8, 8 x 1-1/4, 8 x 1-1/2 and 8 x 2), a driver bit for your drill, our catalog listing 350 types of Square Drive screws, and take **\$5 off** your first order of \$25 or more, or **\$10 off** your first order of \$50 or more! (Limited time offer. Available in USA only.)

“We tried a box of 1-3/4” #8 prelubricated flat heads with nibs from McFeely's, which quickly became our favorite fastener.” Speaker-Enclosure Screws, Robert J. Spear and Alexander F. Thornhill, *Speaker Builder*, 2/94

© 1996 McFeely's All Rights Reserved

McFEELY'S
SQUARE DRIVE SCREWS

PO Box 11169 • Lynchburg • VA • 24506
Call 1-800-443-7937 or Fax 1-800-847-7136

from 10kHz to about 16kHz, then has a major peak to 20kHz.

Figure 20 shows the response of just the bare woofer on-axis and 10° off-axis. The woofer has a terrible peak in the 9kHz range that Infinity had included in the woofer passband. Such peaks are common with metal cone drivers and require some attention in the CO design.

Figure 21 shows the bare tweeter response from on-axis to off-axis 20°. Other than the nasty peak above, say, 16kHz, this is a nice-looking response for a ¾" tweeter. Examination of the driver responses indicated that CO around 6kHz would be good with a second-order HP protecting the tweeter.

Based on the measured driver response and impedance curves, we developed a new CO using modeling techniques (Fig. 22). The woofer and tweeter are both driven with positive polarity. The LP consists of a second-order network optimized to increase the down slope from 200Hz to 1kHz for DSL compensation. The series R-L-C network shunted across the woofer terminals cures the peak around 9kHz. The tweeter HP is a second-order network followed by a 3dB pad.

Figure 23 shows the electrical responses of these networks loaded by their driver. The effect of the shunt network on curing the 9kHz peak is clearly evident. The acoustic response of each driver with its CO network (Fig. 24) shows the down slope for DSL compensation and CO at about 6.5kHz. We did not attempt to cure the woofer anomaly around 1.5kHz to 2kHz or the tweeter peak above 16kHz.

The modeled system response without DSL (Fig. 25) shows the droop from low frequency and then a basically flat response up to 16kHz. The response is stable from on-axis with the tweeter to 10° down from the tweeter axis toward the woofer. This is the response range used for listening with boxes #1–#4. Figure 26 shows the same plots including

6dB of DSL, demonstrating that the system has a full 6dB DSL compensation.

TESTING THE NEW CROSSOVER

We breadboarded the new CO and used it to test one Infinity driver. Note that the 0.180mH coil in the shunt network comes from the original factory CO. It has enough resistance so that you could omit the 1Ω resistor shown in the modeling schematic to save one more component. The test results (Fig. 27) for the same angles as were used in the modeling (Fig. 25) are in good agreement. Note that DSL does not appear in the type testing used here.

We modified the Infinity drivers for boxes #1 and #2 to remove the factory CO and brought out individual wires for the woofer and tweeter. After listening tests, we assembled the new COs under the box pedestal. We also tried the new CO in breadboard form and then installed it in boxes #3 and #4, which pose a problem, because the pedestal is very small.

Using small coils and putting the shunt network inside the box mounted on the driver allowed us to fit the CO under the pedestal. It is unlikely with the coils available today that you could fit the CO under the box unless you increased the pedestal height. Table 5 lists the additional components needed to modify a pair of #1 and #2 or #3 and #4 boxes.

HOW DO THEY SOUND?

The original boxes sounded light just above the subwoofer range and had excessive highs that were not as clean as I had expected, but now I had very fine-sounding satellites. With this CO modification both box types are great satellites that can play loudly. You could use either type on stands built with a flat bottom rather than the tipped front

panel. Adjust the stand height so a seated listener's ears are at tweeter height for boxes #1 and #2 and a bit above tweeter height for boxes #3 and #4. You could place boxes #3 and #4 on tall stands and build them upside down, i.e., invert the front panel to put the tweeter at the top.

At most times boxes #1 and #2 and boxes #3 and #4 sound very similar. Boxes #3 and #4 have very specific imaging—almost analytical. Boxes #1 and #2 now show the very wide sweet spot I had learned to expect with the side-by-side configuration. Their image is not quite as specific as boxes #3 and #4, but they offer a wider soundstage. On some music I preferred boxes #3 and #4, and on other music I preferred boxes #1 and #2, so I could never select a clear winner. Other listeners offered similar opinions.

Infinity has recently raised the price of the Kappa 462.5CFP plate drivers. This, plus the cost of parts for the new CO, make these rather expensive satellites. Also, you need to assemble a reasonably complex CO network.

REFERENCES

1. Koonce, G. R., and Wright, Jr., R. O., "The Infinite Box: Constructing a Subwoofer," April 2002 aX, p. 28, and May 2002, p. 42.
2. Koonce, G. R., and Wright, Jr., R. O., "The Infinite Box Concept," January 2002 aX, p. 8, and February 2002, p. 38.
3. "5.1-Channel Production Guidelines," Issue 1, S00/12957, Dolby Laboratories, Inc., www.dolby.com.
4. Gonzalez, Ralph, "Balancing Small Speakers," SB 3/87, p. 44.
5. D'Appolito, Joseph, *Testing Loudspeakers*, ISBN: 1-882580-17-6, 1998, p. 58. Old Colony Sound Lab, PO Box 87, Peterborough, NH 03458-0876, 603-924-9464, Fax 603-924-9467, custserv@audioXpress.com.
6. Koonce, G. R., "Side Saddle: A New Two-Way," SB 3/97, p. 10.
7. Koonce, G. R., "A Pair of Computer Speaker System Designs," March 2001 aX, p. 8, and April 2001, p. 30.

CREDITS

I would like to thank the many people and companies that supplied technical assistance in the performance of this work. Listing is alphabetical by company: Boston Acoustics; Eminence Speaker Corporation LLC, Tom James; Infinity Systems (Harman-Kardon), Andy Wehmeyer; Madisound, Bryan Kane; Near Audio (Bogen Communications, Inc.), Bill Kielyka; NUERA Acoustic Technology (Tang Band Speakers, Taipei City ROC), Billy Lau; Parts Express, Karl Keyes and Darren Kzuma; RAW Acoustics, Al Wooley (formerly with NUERA Acoustic Technology). I would like to thank Mark Rumreich for his most valuable research work in finding active fourth-order automotive subwoofer amplifiers/crossovers for this article.

TABLE 5
MATERIAL TO MODIFY A PAIR OF
BOXES #1–#4

QTY.	COMPONENTS FOR NEW CROSSOVER
2	0.45mH coils for the woofer
2	4.0μF film capacitors for the woofer
2	0.18mH coils taken from original factory crossovers
2	1.5μF film capacitors for the shunt network
2	3.0μF film capacitors for the tweeter
2	0.13mH coils for the tweeter
Misc.	Extra wire to bring out tweeter directly

Going once. Going twice.
Going directly to your house.

www.AUDIOGON.com
HIGH END AUDIO MARKETPLACE

Modifying the Infinity drivers to remove the original CO parts and attach wires to the tweeter terminals exposes them to possible damage. Note that the woofer terminal closest to the wide input terminal is the plus woofer terminal. On the tweeter a red dot marks the plus terminal. While these are not simple satellites to build, they are good-

sounding small boxes that show more of what I had expected from the Infinity Kappa drivers.

Part 2 of this article covers construction details for the five enclosure types, discusses diffraction spreading loss compensation, and summarizes the overall work. ♦

SOURCES

Boston Acoustics, Inc.

300 Jubilee Drive
Peabody, MA 01960
978-538-5000
www.bostonacoustics.com

Creative Sound Solutions

32-32691 Garibaldi
Abbotsford, BC, Canada V2T-5T7
604-504-3954
www.creativesound.ca

Eminence Speaker Corporation LLC

PO Box 360
838 Mulberry Pike
Eminence, KY 40019
502-645-5622
www.eminence-speaker.com

Infinity Systems, Inc.

250 Crossways Park Drive
Woodbury, NY 11797
800-553-3332
www.infinitysystems.com

Madisound Speaker Components

PO Box 44283
Madison WI 53744
800-831-3433
www.madisound.com

MCM Electronics

650 Congress Park Drive
Centerville OH, 45459
937-434-0031
www.mcmelectronics.com

Near Audio (Bogen Communications, Inc.)

14 Main St.
Brunswick ME 04011
207-798-5606
www.nearspeakers.com

NUERA Acoustic Technology

6538 Albery Place
Burnaby BC, Canada, V5E-4G2
604-517-6683, Mr. Billy Lau
www.nuera-acoustic.ca

Owens Corning—For information on obtaining the #705 damping material, call the Customer Service Center: 800-328-7617

Parts Express

725 Pleasant Valley Dr.
Springboro, OH 45066-1158
800-338-0531
www.partsexpress.com

Radio Shack Corporation

300 West 3rd St., Suite 1200
Fort Worth, TX 76102-2912
www.radioshack.com

RAW Acoustics

16756-85 Ave.
Surrey, BC Canada, V4N-4W3
604-576-8951
www.rawacoustics.ca

AMPLIFIER SOURCES

Following is a list of some of the companies who can supply continuously variable frequency car amplifiers with 24dB per octave filter slope. These will all require a nominal 12V (13.8V actually) power supply at approximately a 20A rating for home use. You can purchase the power supplies from either Parts Express or MCM Electronics.

Alpine Electronics of America, Inc.

19145 Gramercy Place
Torrance, CA 90501
800-421-2284
www.alpine1.com
Alpine MRP-M200, 150W × 1 into 4Ω, eq., subsonic filter, polarity switch.

USA Acoustics

2424 Blanding Ave.
Alameda, CA 94501
510-864-7005
www.usacoustics.com
USACOUSTICS USX2050, 160W × 1 into 4Ω and USACOUSTICS USX2050, 280W × 1 into 4Ω.

JL Audio, Inc.

10369 North Commerce Pkwy.
Miramar, FL 33025
954-443-1100
www.jlaudio.com
JL AUDIO 250/1, 250W × 1 into 4Ω, eq., subsonic filter, class D.

For others who prefer to purchase a more conventional subwoofer amplifier with a built-in crossover, these crossovers are second- and third-order only, often referred to as "plate amplifiers." Here are several sources for these amplifiers:

Adire Audio

1111 Elliott Ave. West
Seattle, WA 98119
206-789-2919
www.adireaudio.com
Adire HS200, 200W into 8Ω, eq., subsonic filter, polarity sw., and Adire HS500, 490W into 8Ω, eq., subsonic filter, polarity switch.

Parts Express

725 Pleasant Valley Dr.
Springboro, OH 45066-1158
800-338-0531
www.partsexpress.com
250W subwoofer amplifiers, part numbers 300-792, -793, -794, -796.


Marchand Electronics, Inc.

PO Box 473
Webster, NY 14580
716-872-0980
www.marchandelec.com
XM Series not including the XM46.

The only fourth-order passive crossover is available from:

Marchand Electronics, Inc.

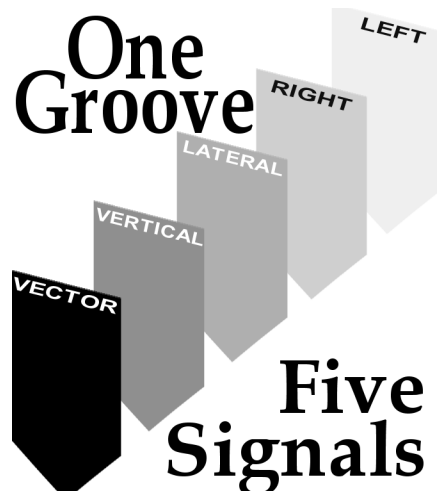PO Box 473
Webster, NY 14580
716-872-0980
www.marchandelec.com
XM46.



One Groove Five Signals PERFECTLY ALIGNED

KAB introduces Groove Tuning™
A new concept that lets you mix the five signals of a mono groove for the best sound possible.

Learn More Online

KAB
Preserving The Sounds
Of A Lifetime
www.kabusa.com

Electronic Crossovers

Tube

Solid State

Line Level Passive
Crossovers

Custom Solutions

We can customize our crossovers to your specific needs. We can add notch filters, baffle step compensation, etc....

All available as kit

Free Catalog:

Marchand Electronics Inc.

PO Box 473

Webster, NY 14580

Phone (585) 872 0980

FAX (585) 872 1960

info@marchandelec.com

www.marchandelec.com



Disposable Camera = Tube Power

One man's junk is another man's treasure. Discover how you can recycle the cast-off camera into your next tube project. **By Graham Dicker**

After building tube projects for many years, I find that one of the most annoying tasks is building the power supply for the project. The filament voltages never provide a problem, but the H.T. voltage supply always becomes a task. One of the easier methods I have used over the years is to use a reverse-connected power transformer and a rectifier to provide a few hundred volts H.T. An example of this method is shown in *Fig. 1*, which is the method I use in a future issue of *aX* in my sound card preamp power supply project.

Recently, however, I have discovered that disposable film cameras are being sold by the millions, with some being recycled and others ending up in the landfill. If you ask them nicely, most film processors will give the old shells away for free. Inside of these shells lies a nice DC to DC inverter ideal to use for small preamp or portable projects.

Photo 1 shows three of the most common cameras in the marketplace; most

are made in Taiwan or China and marketed by a variety of companies. You can purchase them in quantities of ten for around \$2.99 USD new with film, or \$4 USD for single quantities. The ones you need for recycling are those with the built-in flash.

I pried apart with a screwdriver the two plastic clamshells, to reveal the inner workings of the camera (*Photo 2*). Inside were all the plastic mechanics, including the viewfinder and camera lenses, which you may choose to keep for optic projects. You can also see the printed circuit board with the DC to DC converter, which you can easily remove.

Photo 3 shows some examples. The different type numbers are shown in the same order as the original cameras

TABLE 1
CAMERA INVERTER TEST RESULTS

LOAD (k)	VOLTAGE (V)	CURRENT (mA)	POWER (mW)
1000	300	0.30	90.00
330	255	0.77	197.05
220	253	1.15	290.95
100	235	2.35	552.25
47	203	4.32	876.79
22	165	7.50	1237.50

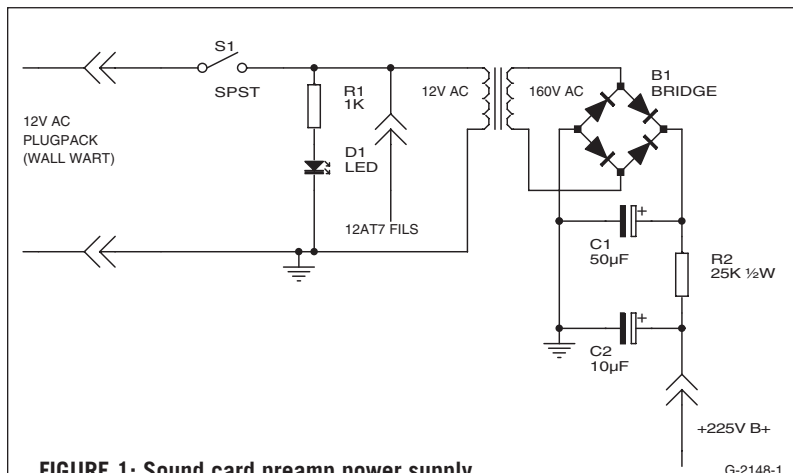


FIGURE 1: Sound card preamp power supply.



PHOTO 1: Some popular disposable cameras.

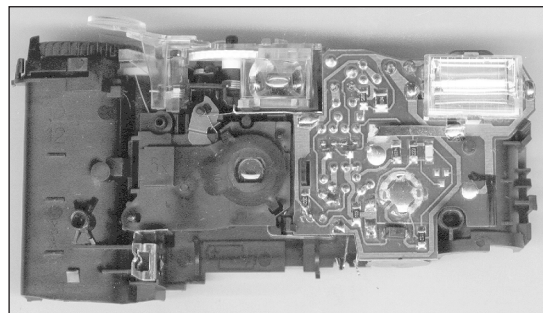


PHOTO 2: Inside the camera.

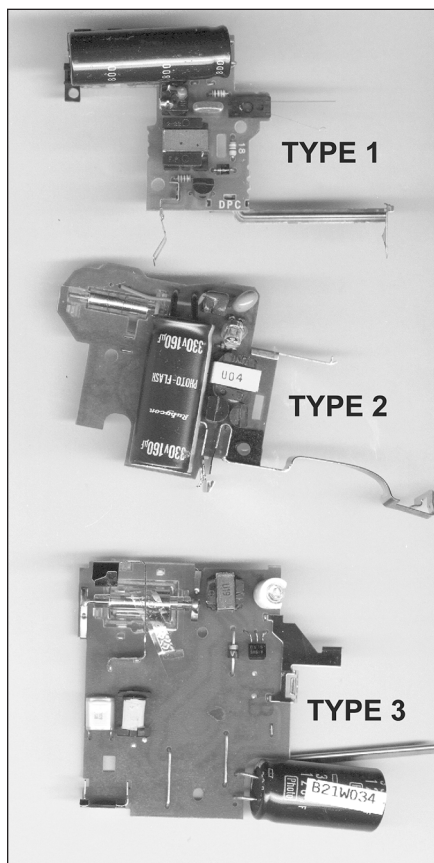


PHOTO 3: Converters from the cameras in Photo 1.

in *Photo 1*. The basic performance of each converter I tested was so similar that I tend to conclude that it doesn't matter which one you use.

The schematic diagram of one of the converters is shown in *Fig. 2*. A 1.5V single-cell battery is used to power the inverter. The inverter transformer consists of a small ferrite core with around seven turns bifilar wound for the primary and the feedback winding. The circuit is a self-sustaining feedback circuit that runs at approximately 6kHz. The secondary winding consists of around 175 turns providing about 220V AC, which is half-wave-rectified by a single 1N4004 diode. This is filtered by a 160µF 300VW electrolytic capacitor.

When the DC voltage approaches approximately 270V, the relaxation oscillator formed by the neon (and its stray capacitance) along with the 220k series resistor lets the neon flash to indicate charging of the filter capacitor. This voltage is applied across the flash tube, which is triggered by the secondary voltage of the trigger transformer. A large current pulse is provided by charging the .1µF capacitor through the

www.audiokits.com

build better audio

All-FET Millennium Class A Amplifier
All-FET Ribbon 20/40W Amplifier
All-FET Balanced Line Amp
Class A Headphone Amplifier
Accessories/Parts
All-FET DAC

Distributing select designs of
Borbely Audio in North America.

We accept MasterCard, Visa, Discover and American Express.

Completed kits available. Contact info@audiokits.com.

audiokits.com
Audiophile Euphoria™

LANGREX SUPPLIES LTD

DISTRIBUTORS OF ELECTRONIC VALVES, TUBES & SEMICONDUCTORS AND I.C.S.

1 MAYO ROAD, CROYDON, SURREY, ENGLAND CR0 2QP

24 HOUR EXPRESS MAIL ORDER SERVICE ON STOCK ITEMS

E-MAIL: LANGREX@AOL.COM

PHONE

44-208-684-1166

FAX

44-208-684-3056

A SELECTION OF OUR STOCKS OF NEW ORIGINAL VALVES/TUBES MANY OTHER BRANDS AVAILABLE

STANDARD TYPES			AMERICAN TYPES			SPECIAL QUALITY TYPES		
ECC81	RFT	3.00	5R4GY	RCA	7.50	A2900/CV6091	G.E.C.	17.50
ECC82	RFT	6.00	5U4GB	SYLVANIA	15.00	E82CC	SIEMENS	7.50
ECC83	RFT	8.00	5Y3WGT	SYLVANIA	5.00	E83CC	TESLA	7.50
ECC83	EI	4.00	6BX7GT	GE	7.50	E88CC G. PIN	TESLA	8.50
ECC85	RFT	5.00	6FQ7	EI	5.00	E188CC	MULLARD	20.00
ECC88	BRIMAR	6.00	6L6GC	SYLVANIA	20.00	ECC81/6201	G.E.	5.00
ECC88	MULLARD	10.00	6L6WGB	SYLVANIA	15.00	ECC81/CV4024	MULLARD	6.00
ECL82	MULLARD	5.00	6SL7GT	USA	7.50	ECC81/M8162	MULLARD	7.50
ECL86	TUNGSRAM	10.00	6SN7GT	USA	7.50	ECC81/6201 G. PIN	MULLARD	10.00
EF86	USSR	5.00	6V6GT	BRIMAR	7.50	ECC82/CV4003	MULLARD	15.00
EF86	MULLARD	15.00	12AX7WA	SYLVANIA	7.50	ECC82/M8136	MULLARD	17.50
EL34	EI	6.00	12BH7	BRIMAR	12.00	ECC83/CV4004	MULLARD	40.00
EL37	MULLARD	30.00	12BY7A	G.E.	7.00			
EL84	USSR	3.00	211/VT4C	G.E.	85.00			
EL509	MULLARD	10.00	807	HYTRON	7.50			
EL519	EI	7.50	5687WB	ECG	6.00			
EZ80	MULLARD	5.00	6072A	G.E.	10.00			
EZ81	MULLARD	10.00	6080	RCA	10.00			
GZ32	MULLARD	25.00	6146B	G.E.	15.00			
GZ33/37	MULLARD	20.00	6922	E.C.G.	6.00			
PL509	MULLARD	10.00	6973	RCA	15.00			
UCH81	MULLARD	3.00	7308	SYLVANIA	5.00			
UCL82	MULLARD	2.00	SV6550C	SVETLANA	20.00			

MANY OTHER BRANDS AVAILABLE

These are a selection from our stock of over 6,000 types. Please call or FAX for an immediate quotation on any types not listed. We are one of the largest distributors of valves in the UK. Same day dispatch. Visa/Mastercard acceptable. Air Post/ Packing (Please Enquire). Obsolete types are our speciality.

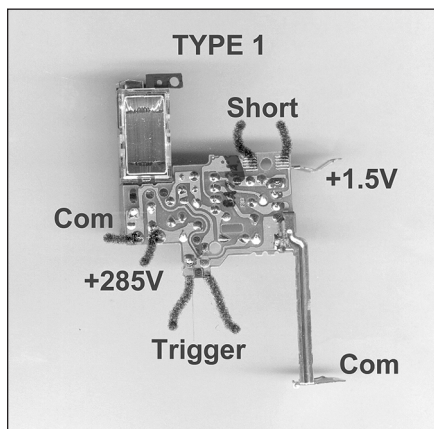


PHOTO 4: Modification to type 1 inverter.

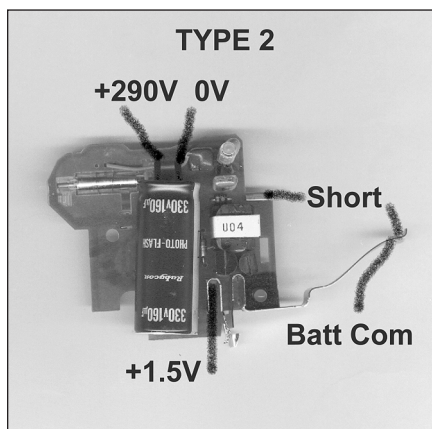


PHOTO 5: Type 2 inverter mod.

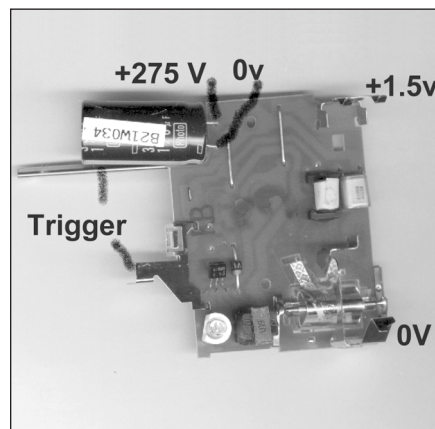


PHOTO 6: Type 3 inverter mod.

series 10k resistor, with the capacitor in series with the trigger transformer primary. When the trigger switch is closed, the capacitor discharges through the transformer primary, pro-

ducing a high-voltage trigger pulse for the strobe tube.

Table 1 shows the test results of loading the output of the DC to DC converter with different resistors. You can obtain a range of load currents with useful output voltages and use these for tube amplifier projects. Loads above 7mA cause excessive heating of the ferrite core and/or the oscillator transistor.

The test figures also show a dramatic drop in output voltage above the 1W

output level. Load currents from 1 to 4mA are, however, most useful to power up to four average triode sections with the usual 100k plate loads. The falloff in output voltage with load current is better shown in the graph of Fig. 3. The most useful output is in the 0-4mA and 200-300V region.

Photo 4 shows where I was able to tap off the DC voltage from a type 1 inverter, in this case around 285V. You can ignore the trigger contacts and

Sure, we're an audio center.
Center of the universe, that is.

www.AUDIOGON.com
HIGH END AUDIO MARKETPLACE



audioXpress 2002 on CD-ROM

Now you can have the 2002 series of *audioXpress* for your computer. The complete volume for 2002 has been transformed to electronic format for your convenience. The table of contents for each issue have been gathered into a single file which contains links to the articles, departments, etc. within each issue. A great reference tool for the audio enthusiast. Shipping Wt: 1 lb.

CDAX2 *audioXpress* subscriber priceonly \$14.95*
All others\$34.95*

*Shipping add \$6.00 in US & Canada;
\$7.00 other surface; \$11.25 other air.

To order your own CD of the
2002 series of *audioXpress*
call toll-free
1-888-924-9465
or e-mail
custserv@audioXpress.com.

audioXpress, PO Box 876 Dept. X2
Peterborough, NH 03458-0876 USA
Phone: 603-924-9464 Fax: 603-924-9467
E-mail: custserv@audioXpress.com

ORDER ON-LINE AT www.audioXpress.com

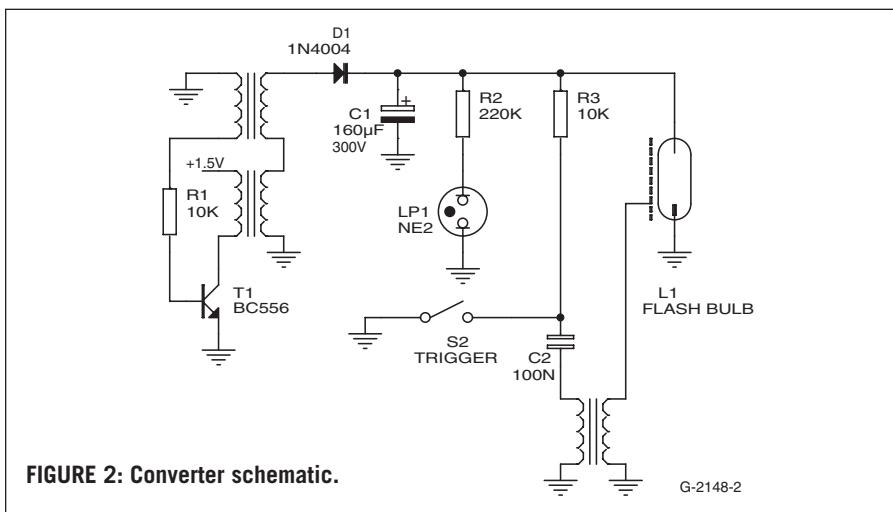


FIGURE 2: Converter schematic.

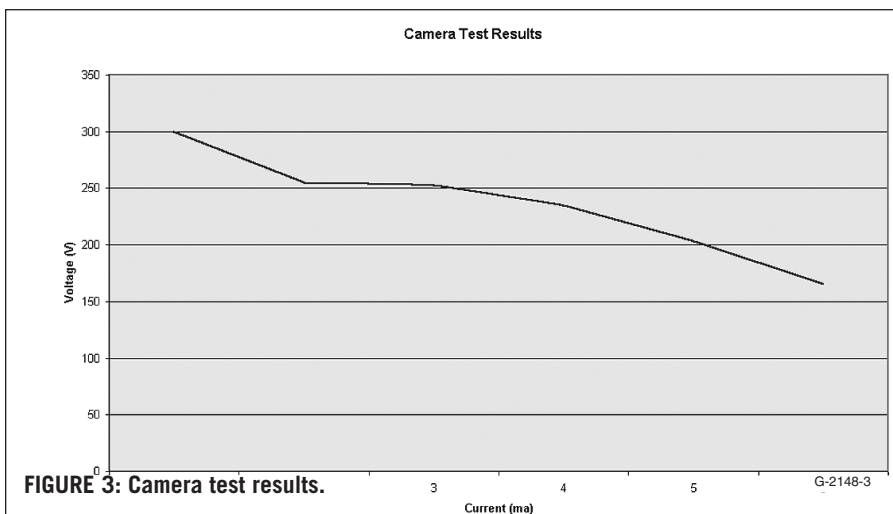


FIGURE 3: Camera test results.

apply a 1.5V DC supply to the contacts as shown. You also need to short out the two pads indicated to keep the oscillator working all of the time. *Photos 5 and 6* show where to hook up inverter types 2 and 3 in a similar manner.

All three inverters showed little ripple in the DC output and little radiated noise. If you wish, you can easily enclose the inverters in a metal tin for shielding. *Figure 4* shows a simple power-supply circuit to provide 1.5V for the inverter. I have one of these built into a jiffy box along with a 12V center-tapped transformer for filaments, which I use for prototyping valve circuits. ♦

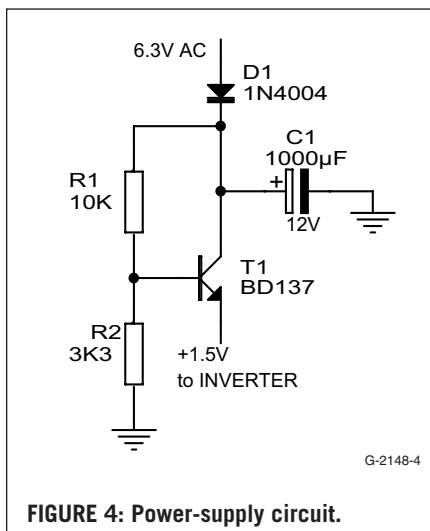


FIGURE 4: Power-supply circuit.

Toroids for Audio



Tube Output

Toroidal transformers for tube output applications. Plus related products.

Standard Series (push-pull)

Single-ended

Specialist Range

Special Designs

Power Transformers

Chokes

Chassis for Tube Amplifiers

PCB for 70W & 100W Amps

Book by Vanderveen

Electrostatic

Step-up toroidal transformers for Electrostatic loudspeaker applications.

Solid State Power

Low noise, low inrush
500 to 2000VA fully encapsulated power transformers.

Standard Power

A broad range of high quality, approved, toroidal transformers. Designed for general purpose applications. From 15 to 1500VA.



PLITRON
MANUFACTURING INC

8-601 Magnetic Drive

Toronto, ON M3J 3J2

Canada

416-667-9914

FAX 667-8928

1-800-PLITRON

(1-800-754-8766)

www.plitron.com

Visit Our Website
www.audioXpress.com

Audio Uses of Transformers

The author calls on readers to contribute information and pool resources to retrieve wisdom otherwise partially lost. **By Peter Buddee**

As a long-time reader of *Audio Amateur* publications, I find it difficult to start writing without first answering the classic question: How did I become an audio addict in the first place?

In my case, it is very easy to pinpoint in time and space. As a teenager in the summer of '64, I accompanied my father to an industrial exhibition in a small Swedish town. In the exhibit booth of the most popular Swedish home electronics producer, I saw enthroned an open-reel tape recorder with its spools rotating at a higher speed than I had ever imagined possible, giving an almost hypnotic visual effect. At the side of the tape recorder there was a pair of headphones. So, what does a young teenager interested in music and electronics do in a situation like this? Right, he puts on the headphones!

Since this was my first exposure to true high-quality sound reproduction, I simply wasn't prepared for the result. Up until this moment, I had heard only medium-fi music reproduction, but now I was receiving the sound quality of an open-reel prerecorded tape at 7½ ips . . . plus the effect of stereo reproduction (also new to me), combined with the spooky "throwing you in the middle of the orchestra" effect given by the headphones.

There is only one expression able to register the impact this event had on me: "Wow!"

ACKNOWLEDGMENT

To Per Lundahl at Lundahl Transformers in Sweden, for his patience in answering all possible (and some quite impossible!) questions during this process. I think his major reaction now is surprise. With his company's background mainly in pro audio, he now seems to understand that the technology used in his products could prove eminently useful in audiophile applications.

Although I do not recollect the music I heard that day, the impact of the sound quality has set my priorities ever since. My favorite pastime became music listening—live or canned. But if reproduced, it needed to be of the "best possible" sound quality.

I began tinkering with replay equipment, trying to improve sound quality whenever possible. I became a classic *Audio Amateur* reader. Also, I joined a network of audiophiles that fed and sustained my interest. Some of the members of this group became designers and manufacturers of audio equipment, as well as recording engineers. Over the years, the number of active members would vary, but there was always a core group, keen on honoring continuity.

This group eventually accumulated quite some insight into audio-related matters. Also, it has access to a continuous timeline, stretching over decades, seeing the trends coming and going.

THE REAL ISSUE

There is one audio chain component that has remained—over the years—relatively unchanged in people's minds. If I said, "This component has always been seen as a necessary evil, to be used only when necessary," what would your first guess be? The right answer is (at least in this case!), "the audio transformer."

It has become clearer in recent years that the dominant perception of audio transformers does not contain the whole truth. As usual (!), the truth proves to be more complex than traditional understanding, giving good reasons to look a bit deeper into the matter.

Accepting (as always) the need to use a properly designed component in a

properly designed circuit, this group has, over the last couple of years, compiled a list of possible uses for audio transformers. The more we thought about this issue, the more obvious it became to us that there seemed to be a lot of prejudice getting in the way of really good solutions. If you observe the recording industry, or the broadcast companies, you face a very different attitude towards transformers. The group found application after application coming to the surface, where a transformer potentially could provide a very satisfying solution.

Very early results of testing some new ideas (being primarily forgotten old ideas!) seemed to very much support our view. We also found that we had an interesting supplier of audio transformers, with strong goals, living in central Sweden close to the Baltic Sea. Oddly enough, it wasn't until rather late in the process we discovered each other, so that we could tap into the more detailed knowledge base available in this organization.

Overall, my wish is to challenge all readers, requesting input from each reader who has experience with any of the applications described here. I am quite convinced there is much more to tell than a single person could possibly manage to find by himself in a lifetime!

Enough background material for each application could result in one or more articles supporting the very best solutions for each application.

THE APPLICATIONS LIST

So, at last, here's our list. It tries to follow "the general direction" of the signal path, and so it would be correct to start with:

1. The Moving-Coil Step-up Transformer—a common place to observe a transformer. There could be many reasons why the transformer seems to be a common solution to bring the

output of a moving-coil cartridge to the correct level for connecting to the 47k Ω phono input. To the best of my knowledge, I haven't seen any attempt in many years to analyze this solution compared to the "active MC input amplifier." Input, anyone?

2. Line-Level Preamp Input Transformers—rather unusual today, it does provide galvanic isolation between signal ground in the preamp and any device feeding it, at the same time providing an elegant way to go from balanced to single-end, or vice versa.

3. Preamp Output Transformer—galvanic isolation, impedance, and level matching are easily available for this configuration.

4. Line-Level "Problem Solver" Transformer—basically a "one-to-one" unit, you could insert between, say, a preamp and a power amp (in the cable) to ensure no DC interactions between the two. This application is a classic pro audio solution to ground problems.

5. Power Amp Input Transformer—again, galvanic isolation, general matching and balanced to single end conversion are available here.

6. Power Amp Interstage Transformer—general matching, but also eliminating the coupling capacitor in the signal path before the output tube grids. Given a transformer with good enough symmetry, this would allow the transformer to be used as a phase splitter before push-pull output tubes.

7. Power Amp Output Transformers—the classic use for transformers in audiophile equipment. Most often used in tubed circuits, there are some exceptions in which solid-state solutions actually have output transformers. I would love to see what thinking is available today, for both of these applications!

8. The Plate (Anode) Choke—not being a true transformer, it has a lot in common with its brother. The most important feature here is the inductive load it presents the active device, giving the tube a more linear way of working. This is according to the textbooks, but what does experience say?

By the way, the fact that the (normal) transformer also provides this inductive load to the drive circuit is only rarely mentioned when discussing

transformer applications. Is everybody aware of this fact?

Talking about chokes, there are several more applications including this device:

9. The Grid Choke

10. Power Supply Filter Choke

Having made this list to look more and more like a list of inductive components, there is one more item to go; at least it is a true transformer:

11. Mains (Power) Transformer—not actually in the signal path, it would still be able to contribute to the sound quality of the circuit it supplies. What do we know about the way the mains transformer influences sound reproduction?

Reading through this text, I would like to call it "NOS ideas"! Indeed, it all seems to be much about retrieving partially lost knowledge, and the phrase, "New Old Stock," could perhaps be viewed as appropriate.

Now, anybody who has anything to share with the rest of us, please do so! ♦

Lundahl Transformers in the U.S.

K&K Audio is now selling the **premier European audio transformers** in the U.S.

High quality C-core transformers and chokes using silicon iron, mumetal, and amorphous cores.

- Power output transformers – SE or PP
- Interstage transformers – SE or PP
- Line output transformers – SE, PP, and parallel feed
- Input transformers – MC or line
- Audio chokes
- Power transformers
- Power supply chokes

High End Audio Kits using Lundahl Transformers

- MC Phono Step-up Unit
- Phono Preamp
- Line Stage Preamp
- Microphone Preamp

For more information on our products and services please contact us at:

www.kandkaudio.com

info@kandkaudio.com voice/fax 919 387-0911

ALL ELECTRONICS

C O R P O R A T I O N

12 Vdc 1.25 amp Power Supply

DVE # DSA-0151-12
2.1mm I.D. coax power plug.
Center positive. UL, CSA.

CAT # PS-1215

\$7²⁵
each



10 for \$6.95 each • 100 for \$6.50 each

Neo-Cylinder Magnet

Shiny, nickel plated neodymium cylinder. 0.25" diameter x 0.2" long.

CAT # MAG-76

2 for \$1⁰⁰

50 for 35¢ each
100 for 25¢ each



SHOP OUR ONLINE STORE
www.allelectronics.com

LEDs (Light Emitting Diodes)

SUPER BRIGHT RED 6,000 mcd T-1 3/4

CAT# LED-94 75¢ each

100 for \$50.00 • 1,000 for \$350.00

BLUE - water-clear 1,500 mcd T-1 3/4

CAT# LED-74 \$1.75 each

100 for \$115.00 • 1,000 for \$950.00

WHITE - water-clear 3,000 mcd T-1 3/4

CAT# LED-75 \$2.00 each

100 for \$165.00 • 1,000 for \$1300.00




10 Compartment Plastic Storage box

Transparent hinged plastic box with 10 compartments. Great for parts storage or display of small items. Outside dimensions 7" x 3.4" x 1.25". Friction-lock lid with dual clasps. Each box individually wrapped in a cardboard sleeve. CAT # SB-10

Case of 36 for \$30.60
(85¢ each)

\$1⁰⁰
each

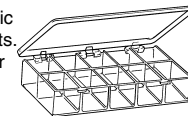

ORDER TOLL FREE
1-800-826-5432

CHARGE ORDERS to Visa, Mastercard,
American Express or Discover

TERMS: NO MINIMUM ORDER. Shipping and handling for the 48 continental U.S.A. \$6.00 per order. All others including AK, HI, PR or Canada must pay full shipping. All orders delivered in CALIFORNIA must include local state sales tax. Quantities Limited. NO COD. Prices subject to change without notice.

CALL, WRITE
FAX or E-MAIL
for our **FREE**

**96 Page
CATALOG**
Outside the U.S.A.
send \$3.00 postage.

MAIL ORDERS TO:
**ALL ELECTRONICS
CORPORATION**
P.O. Box 567
Van Nuys, CA 91408
FAX (818)781-2653

e-mail allcorp@allcorp.com

Showcase

A Headphone Amp

By Klaus Noll


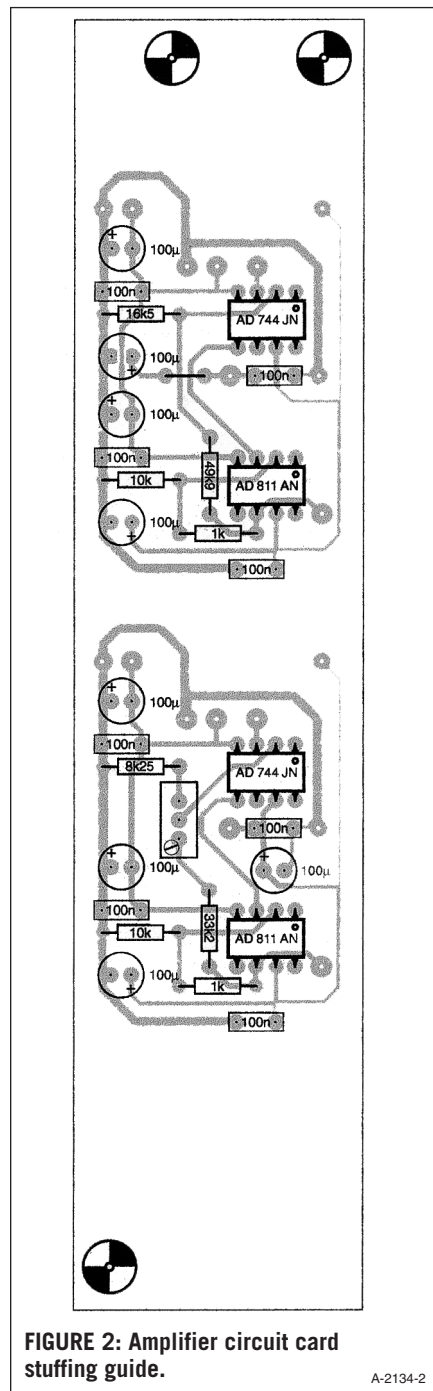




PHOTO 1:
Headphone amp.

This project, a small headphone amplifier (Photo 1), was sparked by Gary Galo and his remark about the values of the Pooge 5 line amp stage (AD744/AD811) in conjunction with the Jung/

Didden regulators (described in TAA 1-4/95 and reviewed in AE 4/00) in his kit review of PHONES-01 in *Audio Electronics* 2/00.

I had been toying with the idea of

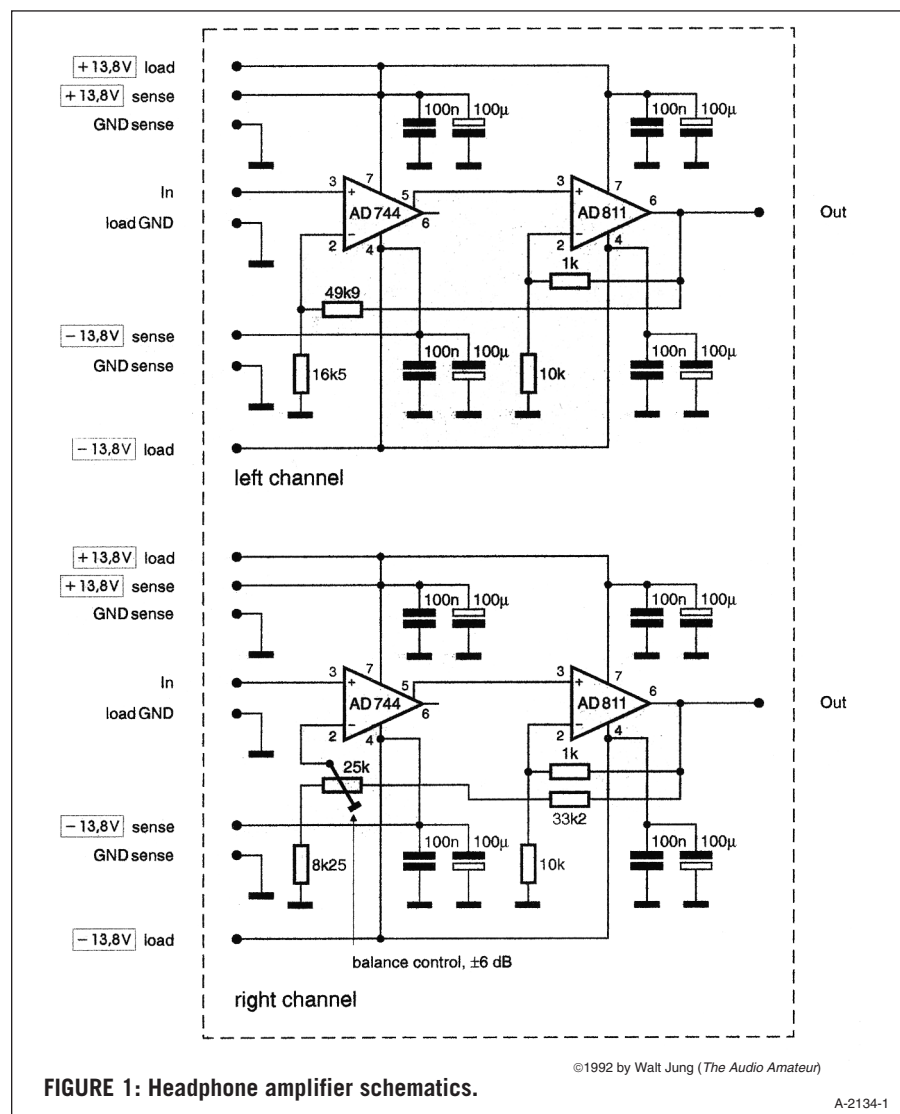

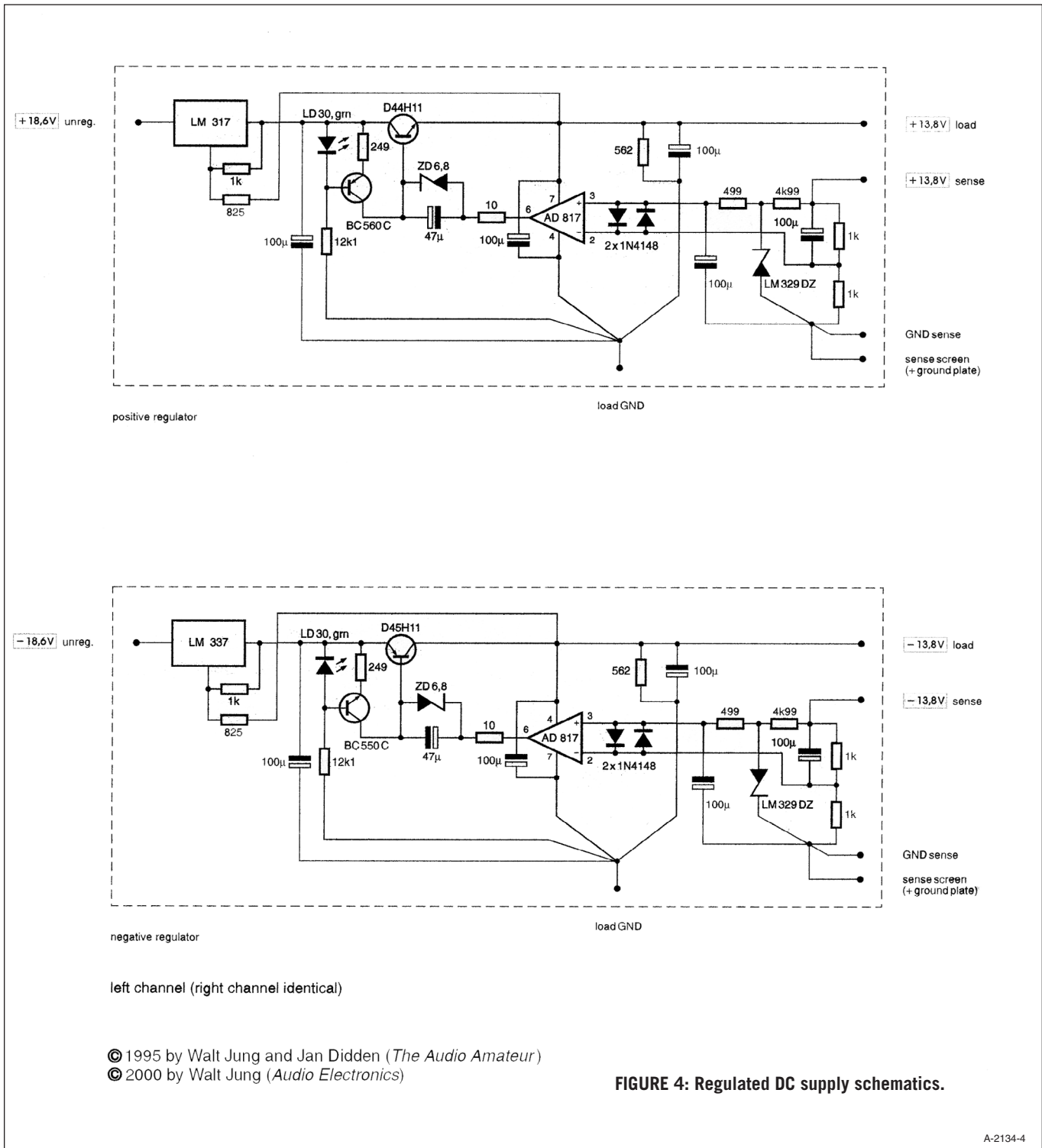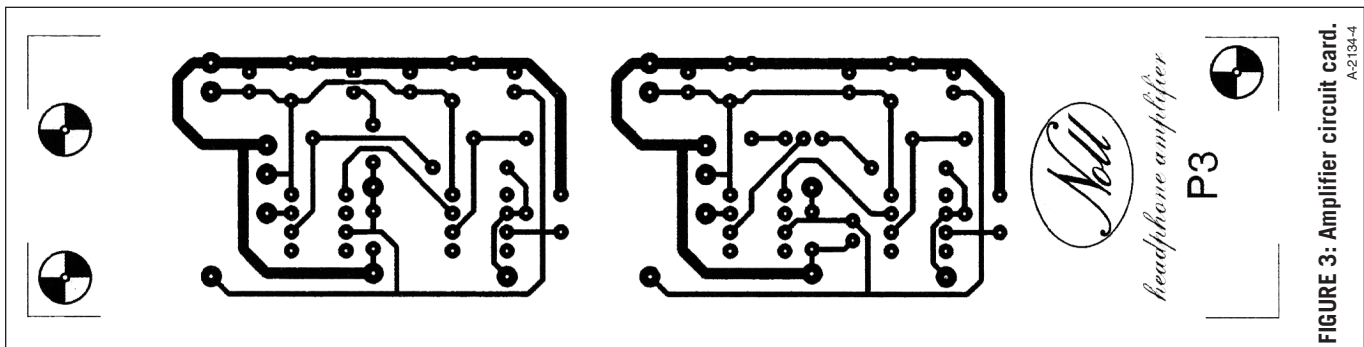

working with the regulators for a while, but was deterred by the apparent complexity of the issue. The work-over in AE 4/00, I think, proves me right.

The purpose of the project was to design a piece of equipment which was first class in every respect. I incorporat-

ed all the suggestions Walt Jung had laid down in his review; i.e., special rectifier diodes (only type available: BYV 28-100), preregulators, and so on. I opted for the AD817, even at the risk of sacrificing a bit of performance, for two reasons: I found the header arrange-

ment of the SMD AD825 too fiddly for my geriatric eyes, and, anyway, the AD825 wasn't available from any of the four retailers I contacted (Analog Devices ICs are very difficult for the amateur to acquire).

Figures 1-3 show the amp schematic

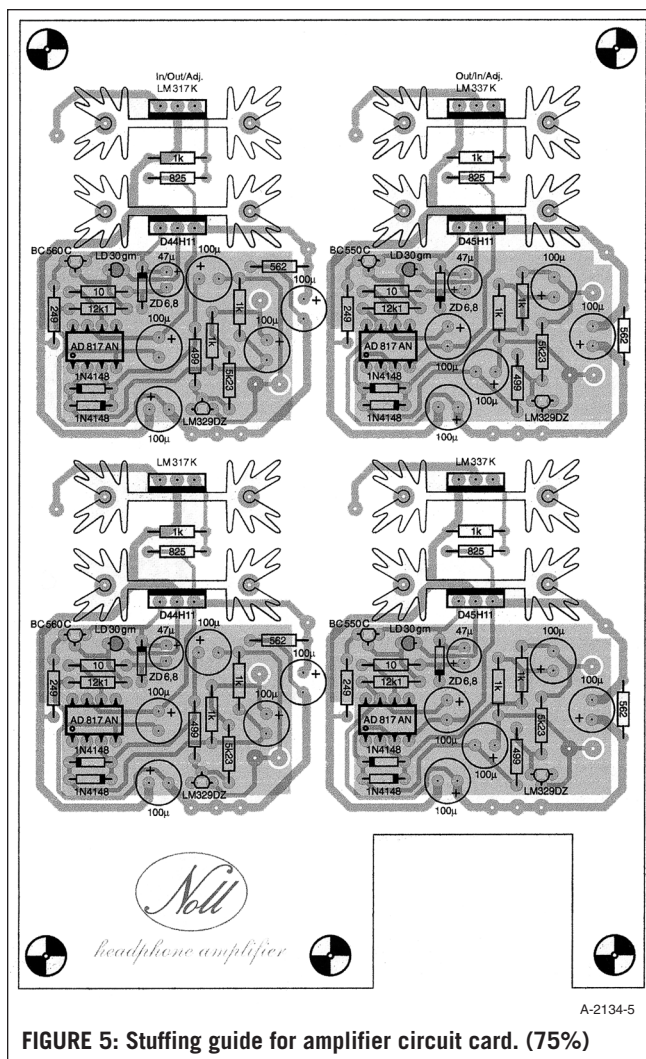


FIGURE 5: Stuffing guide for amplifier circuit card. (75%)

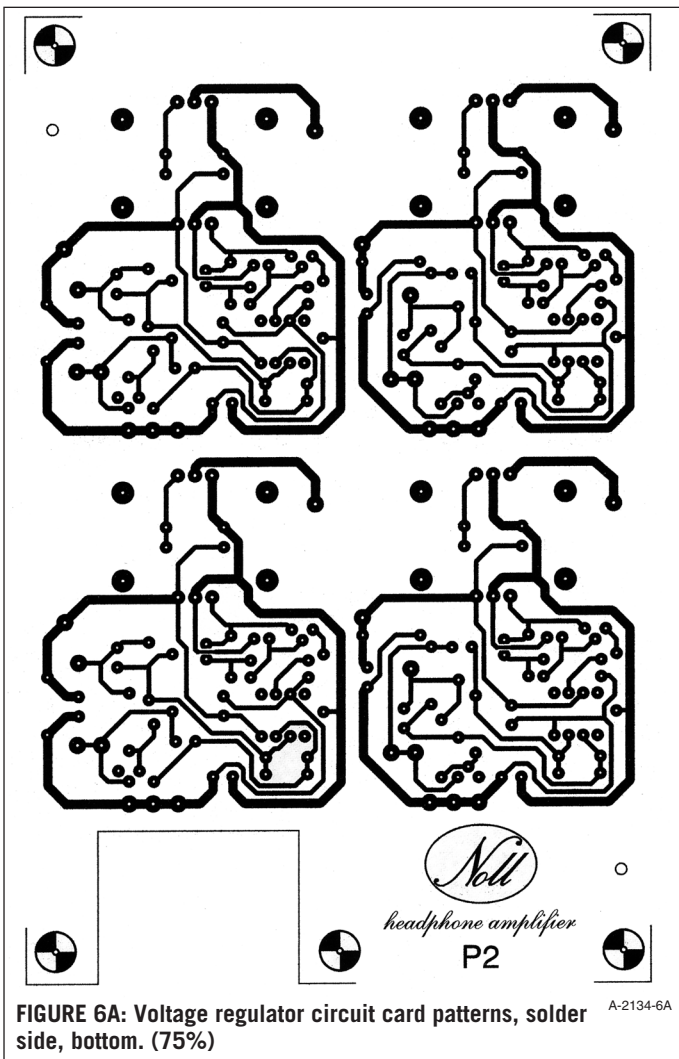


FIGURE 6A: Voltage regulator circuit card patterns, solder side, bottom. (75%)

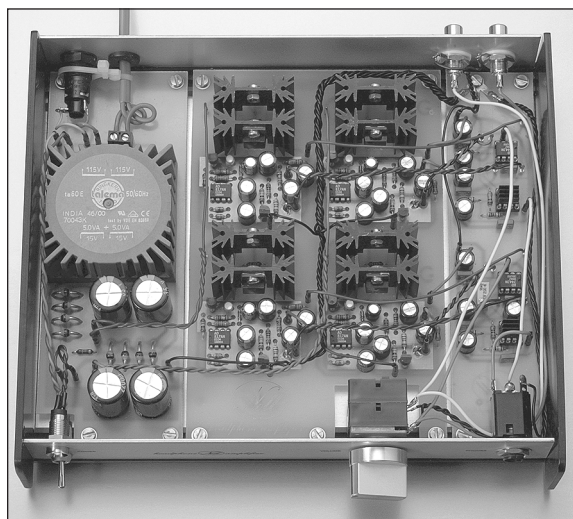


PHOTO 2: Inside the amp.


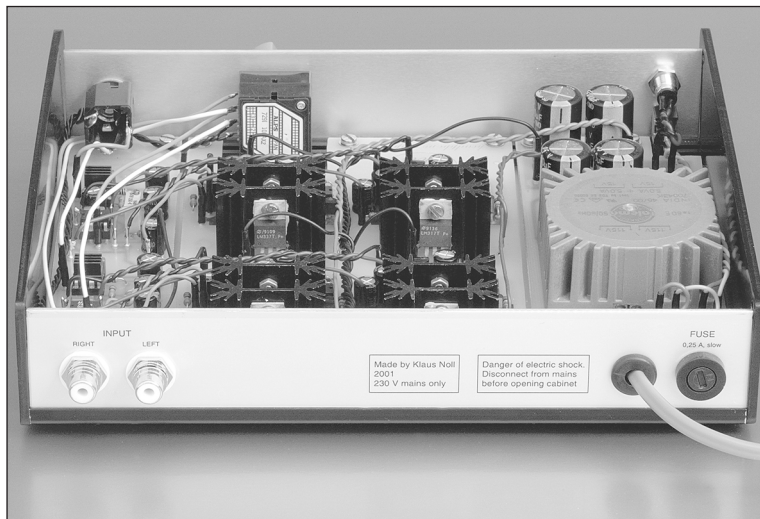
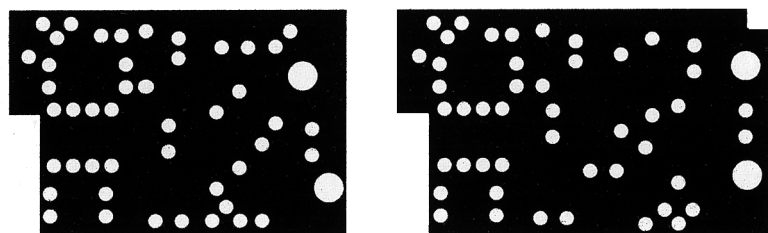


PHOTO 3: Rear view.

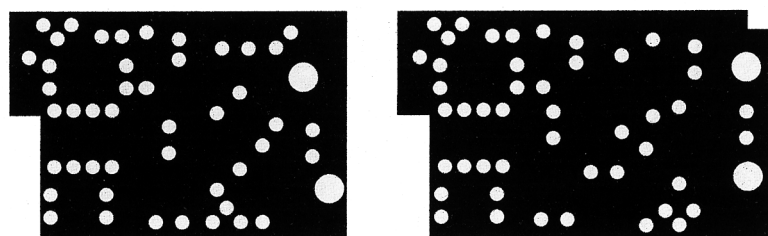

headphone amplifier

FIGURE 6B: Voltage regulator circuit card pattern top foil.

A-2134-6B

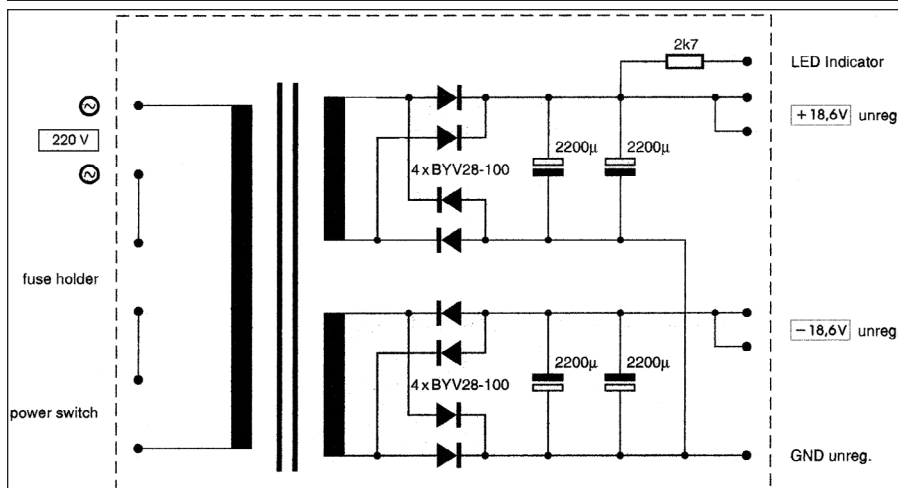


FIGURE 7: Raw DC supply.

A-2134-7

and board layouts. The voltage regulator schematic and board layouts are in *Figs. 4-6*. And the DC supply information is shown in *Figs. 7-9*.

I designed a PCB for the regulator/prereg section, based on Jan Didden's original trace pattern, with space for two positive and two negative regulators/preregs, which provide $\pm 14V$ for the two amplifiers. You can see this board (*Photo 2*) in the middle of the cabinet (which, by the way, is the MC-10 from Sescom, who were extremely helpful and friendly in getting the cases sent to Europe). All four regulators worked faultlessly right from the beginning. The eight heatsinks are probably hopelessly oversized, but I liked the looks of them (silly to put them in a closed cabinet). The AD811s carry little heatsinks, stuck on with heat-conductive sticky foil normally used for fixing heatsinks on CPUs.

The signal is fed straight to the volume pot from a separate line stage in my preamp, bypassing its volume control and then through the 744/811 amp to the phones jack (*Photo 3*). Amplification is four times and can be varied by $\pm 6dB$ in the right channel to enable the adjustment of balance if necessary.



I use a Beyer Dynamics DT 880 pair of headphones (600 Ω nominal impedance) which are rather ancient. (You may want to buy some modern phones.)

What about the sound? Gary Galo was right to maintain that this was probably the best headphone amp available. The sound is simply overwhelming and light-years away from what usually emanates from the outlets of commercial equipment, prestigious CD players, and tape machines. The amp, on the other hand, mercilessly reveals recording faults such as momentary clipping (even on noble records) or misbalancings in the soundstage.

Mr. Galo was a bit off the track as far as the costs of such an amp are concerned. I certainly didn't spend thousands of dollars on the project, but managed to complete it for under \$300. ♦

SOURCE

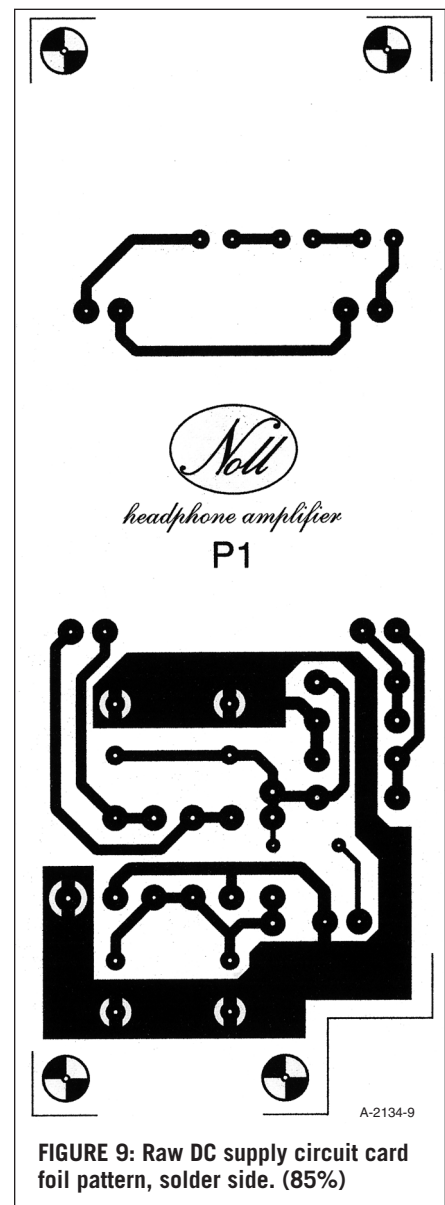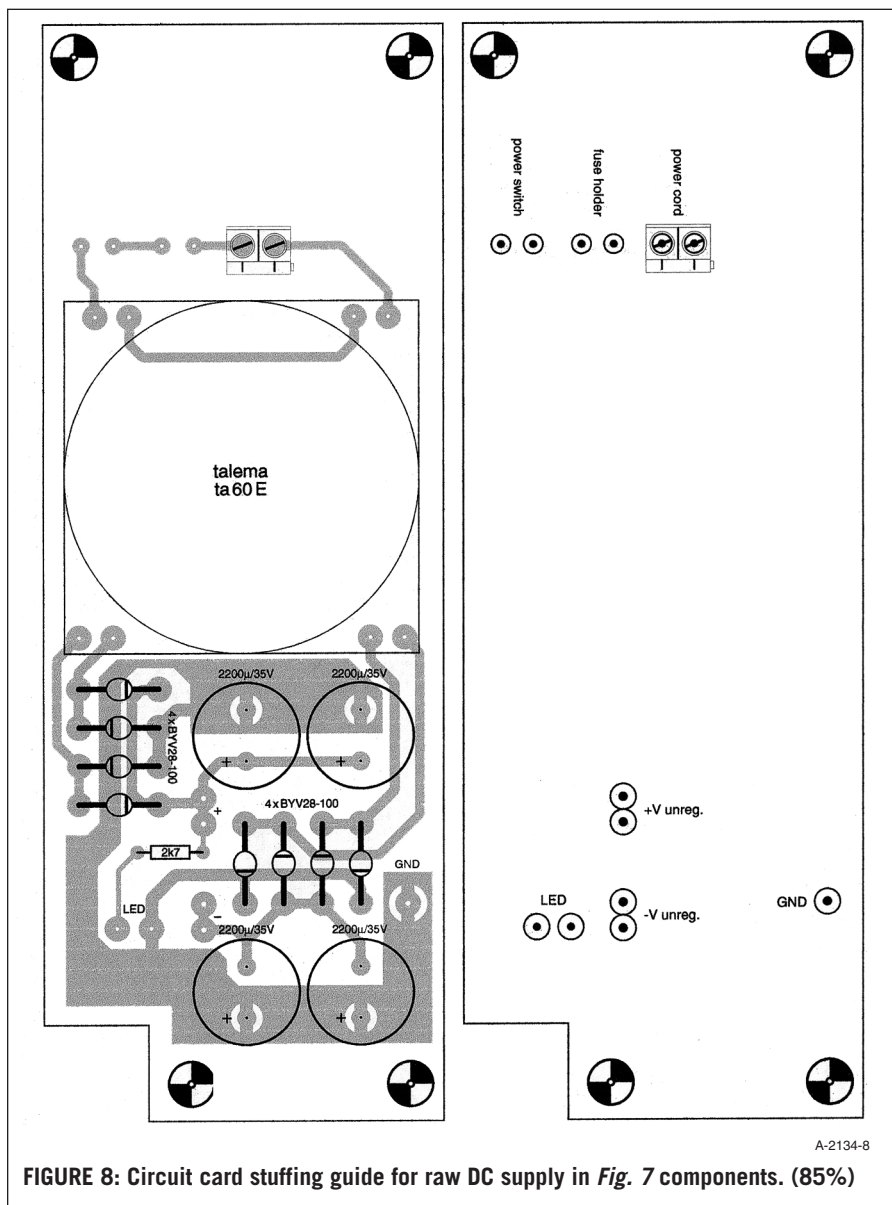Sescom
517 Main Street
PO Box 839
Wellsville, KS 66092
785-883-3009
FAX 785-883-4422




thetubestore.com

Your online source for name brand audio tubes

- Over 1000 types available online
- Perfect Pair matched power tubes
- Capacitors and sockets

Order online at **thetubestore.com**

or call toll free **1-877-570-0979**

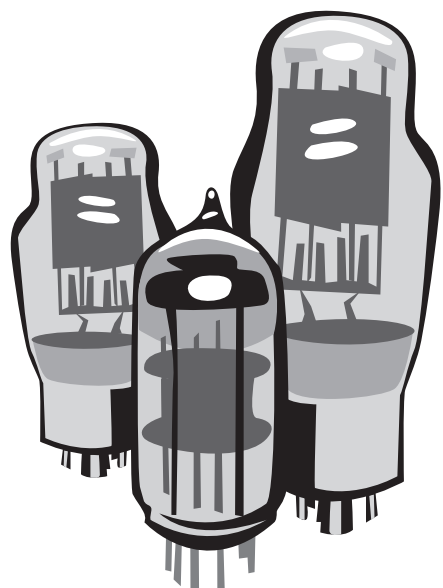

Xpress Mail

POSSIBILITIES

 "Damping Loudspeakers in Series" by Dick Pierce (aX, Nov. '02, p. 38) should convince anyone that series connection of (assumed identical) speakers has no effect on damping. But in the interest of encouraging people to look for the simplest solution to a problem, I'd like to point out the simplest analysis of series damping, namely, symmetry.

Consider two identical speakers (or any electrical impedances including reactance and/or nonlinearity) in series, with any voltage V_1 applied to the series pair. By simple symmetry, the voltage across each element must be $V_{1/2}$, for *all conditions*. Thus, with two identical speakers in series, each speaker always sees $V_{1/2}$. Therefore, if V_1 is constant, so is the voltage across each speaker, regardless of frequency or current drawn. *The speaker can't tell this symmetry-derived constancy from a voltage source $V_{1/2}$ driving it individually.* Thus all parameters, such as current vs. frequency, are the same (except for half the drive) as if the speaker were solely connected to a constant-voltage source. Hence, *damping also is unaffected.*

The argument that one speaker's resistance decreases the other's damping is flawed: if, say, a 4Ω speaker were connected in series with a 4Ω resistor, certainly the electrical damping would be halved (twice the Q_{ES}). But the second speaker is *not a resistor!* Rather, its voltage/current ratio and phase (impedance) varies with frequency (and anything else, such as nonlinearity of mechanics) in exactly the same way as the other speaker. *This preserves the symmetry, therefore the constancy of individual speaker voltages.*

As an aside, the electrical dual would be two identical speakers in parallel, driven from a constant-current source. The current would split equally.

But what about the real world of non-identical speakers (say in series)? No longer symmetrical, damping *will* be affected. For example, suppose (exagger-

ated for clarity) one speaker of a sealed-box pair has a resonant impedance peak at 40Hz, the other at 50Hz (acoustic interactions ignored). Then at 40Hz, the first speaker presents a higher impedance to the second than the latter's own. (Also, the impedance phases are different.) Vice versa at 50Hz. Thus, the voltage across each speaker will rise ($> V_{1/2}$) at its own resonance frequency; damping is decreased.

The same can happen if identical speakers in series are loaded differently acoustically, for example, if damping material is more densely packed around one speaker; or in a vented enclosure, if one speaker is significantly closer to the vent.

It is for such reasons that parallel speaker connection is preferable; only then is constant-voltage drive assured with dissimilar drivers, loading, and so on.

Electrical elements in series driven by a constant-voltage source (or the parallel/current source dual) are actually a form of feedback stabilizing, if you consider the time delay of reactances (even what we call "resistors" have parasitic L and C). Consider a 1Ω resistor with one end connected to a +2V source (with reference to some defined ground point). Initially, the resistor's other end is floating—zero current. Then, this end is connected to a second 1Ω resistor whose other end is grounded.

Now we have 2V across two series 1Ω resistors. The steady-state 1A of current doesn't flow instantly; parasitic L and C cause a build-up delay, possibly with damped oscillations (at RF frequencies, most likely). With identical resistor parasitics, each resistor would see an immediate and constant voltage of 1V across it (regardless of transient current oscillations) due to the symmetry.

But with dissimilar parasitics, of sufficient magnitude, the resistor midpoint voltage would oscillate about 1V until (theoretically never fully) decayed to zero. In the steady-state, the resistors' *resistance* values determine the final

JFETS

ULTRA LOW NOISE

LS843 - 3nV/Hz typ

TIGHT MATCHING

LS843 - 1 mV max

- ◇ N & P Channel
- ◇ Duals & Singles
- ◇ Custom Screening
- ◇ Spice Model Library
- ◇ Die, SMT, Thru-Hole
- ◇ No Order Minimum

Second Source for Domestic & Foreign JFETs & Bipolars

Full Service U.S. Manufacturer of Specialty Linear Products

LINEAR SYSTEMS

4042 Clipper Court

Fremont, CA 94538

510-490-9160/510-353-0261 (Fax)

E-mail: Sales@Linearsystems.com


WWW.LINEARSYSTEMS.COM



RF PARTSTM

COMPANY

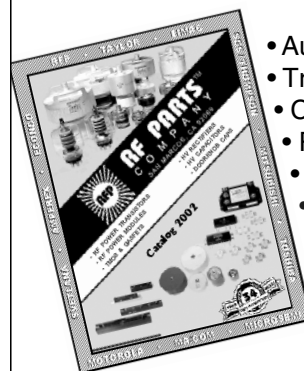- Audio
- Broadcast
- Industrial
- Communications



- Audio Tubes
- Transistors
- Capacitors
- Rectifiers
- Modules
- Gasfets
- Coax

Catalog available

Svetlana • Taylor • RFP • Eimac
Amperex • MA/Com • Motorola
Toshiba • Thompson • Mitsubishi
Se Habla Español • We Export

800-737-2787

760-744-0700 • 800-737-2787

Fax: 760-744-1943

E-mail: rfp@rfparts.com

www.rfparts.com

voltage division. So considering the oscillations due to reactances, it is interaction between currents and voltages, damped by resistance, that stabilizes the final result. And any self-regulating interaction process is, analytically speaking, negative feedback. (So, fellow audiophiles, technically there's no such thing as a zero-feedback amplifier!)

A fellow engineer once witnessed positive feedback with resistors, producing sustained oscillation. Actually, this is unfair; the resistors were temperature-dependent; the circuit was an attempt to compensate some voltage-controlled RF device. One "resistor" had a strong positive temperature coefficient (TC); the other a strong negative one. The supplied voltage fed to these two in series was enough to significantly heat at least one element, thus changing its resistance. This changed the current, and therefore the heating of both itself and the other element.

The result was an oscillation of current and mid point voltage, frequency of about one cycle every 15 minutes (0.0011Hz), which lasted longer than the engineer's patience! The world's simplest ultra-low frequency oscillator—no transistors, no tubes! (You could call it a thermo-parametric oscillator.)

This example of unexpected feedback interaction with assumed-to-be-passive elements is not as remote from normal audio design as you may think—with high driving power, voice coils heat up and their resistance increases—oh, the possibilities!

Dennis Colin
Gilmanton, I.W., N.H.

Dick Pierce responds:

Oh, the possibilities indeed! The possibilities are endless.

Fortunately for us, the realities are far more limited.

First, a general comment on Mr. Colin's alternate explanation involving the notion of symmetry. It is certainly another valid approach to describing the situation, and is one that I am fully aware of and alluded to in the final section of my article in describing the in-consequence of identical non-resistive attenuators in series. The same holds for his comment about the electrical dual of a series connection driven by a voltage source versus par-

allel connection driven by a current source. My choice for the path taken was that it used the familiar Thiele-Small parameter set, the lingua franca of loudspeaker drivers.

However, the remainder of his comments take the discussion quite a ways away from reality in several aspects. Let's examine several of the flawed assumptions in his reply, because those assumptions are quite crucial to his premise.

Let's specifically examine one very important assumption, where he states "acoustic interactions are ignored." Unfortunately, the acoustic interactions cannot be ignored: at the frequencies we are talking about, these interactions not only cannot be ignored, they are important to the understanding of the situation.

Beyond that, Mr. Colin makes other assumptions that are physically difficult or impossible to realize. Take his example of two speakers in a sealed box having two different resonances. The resonant frequency arises from the interaction of the moving mass of the cone and the total compliance as seen by the cone: that includes the suspension compliance and the enclosure compliance. Moving mass is one of the easiest-to-control parameters in a loudspeaker: the variation in resonant frequency between otherwise identical drivers is due overwhelmingly to the variations in driver compliance.

Yet, Mr. Colin's example completely ignores the fact that in most cases today it is the enclosure compliance that is the controlling factor: thus, it is quite difficult to obtain the situation he describes, with two nearly identical masses seeing a common total system compliance. Expecting a sealed box with two drivers of the same model to have resonant frequency one-third octave apart is difficult to imagine, much less take as a serious challenge to the analysis presented. Indeed, I would say with all due respect, his example is highly unrealistic and at substantial variance with the actual behavior of multi-driver sealed box systems.

His example further purposely discards the mutual coupling between the drivers, which is significant at the resonant frequency of the system, unless Mr. Colin is suggesting placing these two drivers in a sufficiently large enclosure that the drivers are essentially uncoupled. That would suggest an enclosure size of a few yards for reasonable low-resonance woofers.

Other assumptions made by Mr. Colin bear some note. Take, for example, the notion that the difference in distance between

the ports and the drivers, as a significant agent is, to be perfectly frank, far-fetched at best. At the frequency where the driver motional impedance is at its greatest, i.e., damping is significant, the wavelengths are substantially longer than the dimensions of the enclosure, the enclosure is working in pressure mode, and there, essentially, is no such distance issue.

Similarly, his comment about the difference that might arise because "damping material is more densely packed around one speaker" is highly unrealistic. First, as I am sure everyone is aware, the most significant mechanism for damping is the electrical loss in the speaker, followed by the mechanical losses, smaller by a factor of from 2 to 20. A very small part of the total dissipative mechanism that would have an effect on the driver are acoustic losses, suggesting that there would have to be a huge difference, more than would be realizable without someone being painfully aware of the difference when assembling the speaker, in the damping between the two speakers. Realize also the effects of such damping at the frequencies of interest: substantially less than at high frequencies. Lastly, who on earth would want to do such a thing purposely? Or what manufacturer would have such poor control over its assembly to allow such to happen?

Mr. Colin's comment that "electrical elements in series driven by a constant voltage source are actually a form of feedback stabilizing" is simply wrong. Feedback and feedback stabilization require effective power gain which is simply not relevant to the case at hand. The concept of "feedback" is one which is poorly understood in some corners of the hi-fi community, and is used as a bogeyman for explaining, inappropriately, all manner of problems, real and imagined. Indeed, you might even hazard to suggest that these wrong-headed notions of feedback are, in some respects, a cornerstone of high-end audio mythology.

His further comments on this topic once again ignore the reality that in the loudspeakers we use, the losses by far dominate and overwhelm the reactances, and the notion of coupled "active" oscillators, which his hypothesis implies, depends first upon the invalid assumptions of his feedback model and second on mechanical oscillators whose Q at resonance exceeds those of real drivers by orders of magnitude. In place of his RF parasitics, which can, in magnitude, exceed the bulk resistance of the resistors in his example, consider instead effective sizes of the reactive components represented by the mechanical

"parasitics" of real drivers and systems.

Mr. Colin's hypothesis can be tested in practice: it leads to a set of behaviors that can be observed. In this sense, his hypothesis, no more or less than mine, is falsifiable: the proof is in the observational pudding. Probably the one example in my article that is the best candidate to support his hypothesis is the two separate speaker systems that are hooked in series: there is no common mutual capacitance and, if desired, the speaker can be separated by a distance to minimize the effects of mutual coupling. You do not, as a result, observe behavior other than what the model I presented predicts. This might suggest that some of the assumptions behind Mr. Colin's model need to be addressed. Occam, on the other hand, remains clean-shaven as always.

Yes, indeed, the possibilities. Physics has a way of winnowing the possibilities to manageable numbers, though.

OUTPUT BIASING

In response to a recent inquiry in this column regarding the use of individual versus common-cathode bias resistors in self-biased power amplifiers employing multiple output tubes, I

would always use individual resistors and bypass capacitors on each tube. Use of a common-cathode resistor for two or, even worse, four tubes would aggravate mismatch between the tubes. With a common resistor, both or all four tubes are forced to operate at the same bias voltage, and if they are closely matched—meaning each tube draws the same cathode current at the same grid bias voltage—the total current would divide equally among them and everything would be fine.

However, if the tubes are not closely matched, one tube may draw considerably more current at the same bias voltage than the others, or conversely, need more bias voltage to reduce its current to that of the other tube(s). This tube would draw more than its share of current and force the voltage dropped across the resistor to be higher than normal. This, in turn, would bias the other tube(s) to a lower than normal current. Furthermore, since the value of the cathode resistor is one half (for two tubes) or one fourth (for four tubes) the resistance it would be for each tube individually, the tube drawing the high-



MILLEN GENUINE QUALITY COMPONENTS

ALL OF OUR COMPONENTS
ARE DOMESTIC MADE

CERAMIC SOCKETS
4 PIN, 5 PIN & 8 PIN
33004, 33005, 33008
GIANT 5 PIN 33405 & 33505
CAPS FOR PLATE OR GRID
36001, 36002 - 36004
COUNTER DIALS
SHAFT COUPLINGS
SHAFT LOCKS
DIAL LOCKS
RIGHT ANGLE DRIVES
HIGH VOLTAGE TERMINALS:
RED, BLACK, YELLOW LOW LOSS

HARD TO FIND AND OBSOLETE PARTS

MILLEN HARDWARE INC.

78 STONE PLACE, MELROSE, MA 02176

781-665-0452 fax: 781 665-0453

www.millenhardware.com


email: info@millenhardware.com

The CLIO system

Turns your PC into the most complete easy-to-use electrical and acoustical measurement system ...



The CLIO system PCI

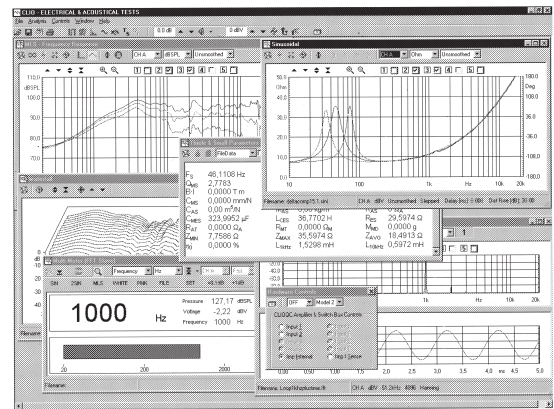

CLIOwin software

The **CLIO** system is a PC-based system for electrical and acoustical measurements. **CLIO** offers several measurement software, related measurement hardware and accessories. **A CLIO system is a complete test instrument**, 100% warranted by **Audiomatica**; all you need is to supply a compatible computer. **No Soundcards involved!**



CLIO is produced by **AUDIOMATICA** and is available also from



www.cliowin.com
www.audiomatica.com

er current would be less able to obtain the bias it needs.

As a result, in extreme cases, especially with four tubes on one resistor, the plate on the hog tube may glow red-hot, while the other(s) will be almost cut off. Providing a means to measure or compare the current drawn by each tube and adjust or balance these currents would be a solution to this problem, but it would be more complex than the individual resistors and bypass capacitors, and occasional measurement and readjustment would be needed.

With individual resistors, each tube could set its own bias independently and, to some extent, self-equalize. Imbalances can still occur, but not as much as with all tubes tied together, and you can easily detect these imbalances by measuring the cathode voltage on each tube. This also applies to push-pull drivers and other voltage amplifier stages, too.

The only time I use common-cathode resistors is in cathode-coupled long-tailed phase inverter and differential stages, where it is fundamental to the operation of the stage. Common-cathode resistors were generally used in the days when tubes were the cheapest (or only) way to amplify audio mainly for cost competitive reasons, but today, when tube amplifiers are a specialty, the added cost of a few extra resistors and capacitors is negligible.

Actually, fixed bias would be superior to self bias for power amplifiers, because the operating point will not shift with changes in signal level and tube current; more of the total B+ voltage would be available to the output tubes, resulting in more power with less distortion, and some electrolytic capacitors (the cathode bypass capacitors) would be eliminated from the signal path. However, the need to monitor the current and adjust the bias voltage of each tube is even more important for fixed bias than for self bias. For small (under 15 or so watts per channel) units intended for moderate volume levels in homes and other small spaces and where cost and minimal maintenance are important, individually self-biased output tubes would be a good choice.

Michael Kiley
Crestwood, Ill.

PAST AND PRESENT

While browsing through a copy of *audioXpress* several days ago, some thoughts crossed my mind. Current U.S. audiophile publications seem entirely devoted to reviewing equipment on the market and presenting little technical material beyond performance specifications plus reviewer comments. While *audioXpress* has some of this, it seems to me to be unique in having do-it-yourself construction and tutorial articles of interest to the serious hobbyist. There were past U.S. radio publications that devoted part of some issues to audio equipment construction, but to my knowledge they are no longer around. I believe the greatest contribution Audio Amateur Publications may have made—and is now making—is keeping interest in audio alive as a technical hobby.

My interest in audio goes back to my teen years, which began about 1940 when I built an amplifier using a pair of 45s in the output with parts mostly salvaged (scrounged) from old radios. My career as an engineer began in 1948 when I designed some components of a guided missile. Needless to say, design in the beginning involved vacuum tubes; later it involved solid state. Overall, I was at it for more than 40 years in one engineering capacity or another.

It is interesting to me to see renewed interest in vacuum tube amplifiers, and I believe that some opinions are not all on solid technical ground, but as hobbyists we are entitled to hear things that others may not, or may not exist at all. I am a little nostalgic, however. Tubes, unlike transistors, are forgiving even when operated so far above their ratings that the plates run a little red, but they usually survive.

I find it interesting that the audio hobby seems to have followed a path similar to that of ham radio. In the early days each was almost entirely a do-it-yourself hobby with high technical interest on the part of the builder. Kits appeared later, and became popular among those with little or no technical knowledge as well as those with experience; enjoyment probably came from having successfully built an operating system.

Currently audio equipment, like amateur radio equipment, is almost exclu-

sively of commercial systems and components involving no more than interconnecting the parts. Interest seems not in the internal workings of the gear but enjoyment in listening (audio) or in communicating (ham radio). As hobbies, both have greatly changed from the early days.

I have subscribed to Audio Amateur publications since the 1970s and am privileged to have had articles published in them. I was an avid reader of *Audio Engineering* and at one time had issues going back to 1949. I don't have them anymore, but I now have each of the seven *Audio Anthologies*, obtained as they became available. The articles were by audio professionals and serious hobbyists, including C.G. McProud, the publisher.

When the publication name was later changed to *AUDIO*, it became somewhat less do-it-yourself and less technical, but I remember it having good equipment reviews and test reports and a quasi-technical article or two; I believe do-it-yourself was dropped later. I think *audioXpress* is much like *Audio Engineering*.

I am glad to see some of the great audio publications of the past such as Olson's *Acoustical Engineering* and Langford-Smith's *Radiotron Designers Handbook* and others being brought back by Audio Amateur Publications. Individuals interested in vacuum tube applications in audio would benefit from the latter.

The anthologies present a good panorama of audio as it developed over more than a decade. I obtained some of these publications, and others, about the time when they came out. I treasure my collection. I hope Audio Amateur Publications can get the rights to other great ones.

I think you and your staff are doing a fine job and wish you the best in the future.

J. Laurence Markwalter, Jr.
Port Charlotte, Fla.

THOR UPDATE

Since reading your article in the Sept. '02 issue ("Building the THORS," p. 14), I'm interested in how the THOR speakers sound now that they've settled in. The very favorable

review by Dennis Colin (May '02) initially steered me towards this design (I've since noted there has been a mixed reaction from DIYers on the web). My problem is that I do not know of a finished pair here in Adelaide, South Australia, to audition. Your views would be immensely helpful.

Ross Yannis
Adelaide, South Australia

Edward T. Dell responds:

The THORs have improved, if anything, over the months since I completed building them. If the fact that this design was based on new, unprecedented transmission line research by G. L. Augspurger, the expert who evaluates speaker patents for both the Journal of the Audio Engineering Society and for The Acoustical Society of America, and who for many years was production director for a very large speaker manufacturer, and that the design for THOR was done by one of the most well-known speaker designers on the planet, then I don't know what kind of pedigree you need to have confidence in a system. I do not, generally, put very much confidence in what I read on the web. At best it is a mixed bag ranging from genuine experts to totally uninformed folks who like to hear themselves talk.

What I do put confidence in is the hour I spend each lunchtime since building the THORs, listening to CDs and for the last month to SACDs from a new Sony DVD player. This includes some 200 CDs so far. I have never heard this quality and resolution from any speaker system, either commercial or those I have built myself. The width of the frequency response—both at the top end and the bass—is without any competitors that I have listened to.

It is the most revealing speaker system I have ever heard. I am constantly surprised by what I hear. This is true for many CDs where the difference in recording methods is evident, sometimes painfully. I am beginning to note differences in microphone techniques. The regular CD issues from Nimbus, EMI, and Decca/London sound much better than many other brands. Only issues in the last year or two from DG sound worth listening to.

I very rarely use the cliché "awesome" about anything, and especially speakers. But the SACD reissue of Stravinsky's Rite of Spring by Telarc rates that adjective, as does

the Hohvanness "Mt. St. Helen's Symphony." The drums in both those recordings, as reproduced by the THORs and without a supplemental sub, are nearly overwhelming.

I think highly enough of the THOR performance that I have plans in place to build another pair for an ambient system, powered by bi-amped Pass Zens.

Why not look for the Australian distributor for SEAS products and ask for any dealers who sell to DIY people who may have built the THORs. It is early days for this, since we published the original tests in May of 2002. However, I confidently predict that any DIY speaker enthusiast who carefully builds the THORs according to our published plans and uses decent power—even as low as 20W per channel—will be more than satisfied.


DIGITAL RIAA PLAYBACK

I wish to respond to a statement in Gary Galo's review (audioXpress Oct. '02) of the KAB preamp, which I quote from page 46:

"... Among the virtues of digital equalization is the lack of nasty phase shifts inherent in analog filters. In the case of playback curves, the lack of frequency-

Build your own

\$50 audio burn-in generator!

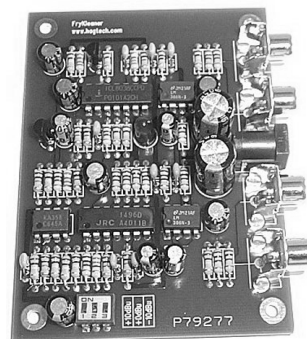

- Break-in your own equipment
- Three output levels
- Four outputs (both polarities)
- Built-in power amplifiers
- Runs on ac




www.frykleaner.com

FREE SAMPLE

IF YOU BUY,
SELL, OR COLLECT

OLD RADIOS, YOU NEED...

ANTIQUE RADIO CLASSIFIED

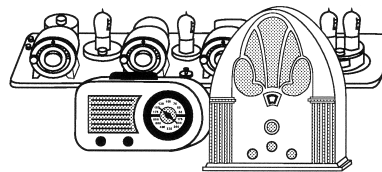

Antique Radio's Largest Monthly Magazine
100 Page Issues!

Classifieds - Ads for Parts & Services - Articles
Auction Prices - Meet & Flea Market Info. Also: Early TV, Art Deco,
Audio, Ham Equip., Books, Telegraph, 40's & 50's Radios & More...
Free 20-word ad each month for subscribers.

Subscriptions: \$19.95 for 6-month trial.
\$39.49 for 1 year (\$57.95 for 1st Class Mail).
Call or write for foreign rates.

Collector's Price Guide books by Bunis:

Antique Radios, 4th Ed. 8500 prices, 400 color photos\$18.95
Transistor Radios, 2nd Ed. 2900 prices, 375 color photos\$16.95
Payment required with order. Add \$3.00 per book order for shipping. In Mass. add 5% tax.



A.R.C., P.O. Box 802-A16, Carlisle, MA 01741
Phone: (978) 371-0512 — Fax: (978) 371-7129



Web: www.antiqueradio.com — E-mail: ARC@antiqueradio.com

dependent phase shifts presents a problem.”

He goes on to say,

“... It should certainly be possible to design digital filters to mimic both the phase and frequency characteristics of analog filters, but no one has done this commercially for playback equalization of disc records, as far as I know.”

In my experience, the usual way of designing digital filters actually does mimic both the phase and amplitude characteristics of an analog filter as a function of frequency. So, it is quite easy to design a digital RIAA filter that does a highly precise job of compensating for this recording equalization on an LP.

The only issue is that the bass boost, combined with the treble rolloff, is likely to use up 40dB of the 90dB dynamic range available in 16-bit audio, leaving about 50dB with which to represent the signal after digital RIAA compensation. To work around this, it is preferable to convert the analog LP to digital form using a 24-bit digitizer, leaving about 60dB for representing the signal using commercial 24-bit sound cards.

The digital filter designer could probably adjust the digital equalizer's gain to preserve more than 50dB dynamic






range with 16-bit recording, but you get the idea.

As for phase shift, I have designed a digital RIAA filter to be used on 44.1kHz audio samples in software, and I present graphs of only the error between the actual response and the ideal RIAA response.

Figure 1 shows the amplitude error, where the ideal response in dB was subtracted from the digital filter response in dB. The error is negligible up to a frequency of 10kHz, and by 20kHz the error is only +1dB. Since this is the range where most tweeters roll off, I

don't consider this much of an error. The purist would sample at 96kHz, and the amplitude error up to 20kHz in this case would be effectively zero.

As for the phase error, this is shown in Fig. 2. There actually is a noticeable phase error because of the way digital filters behave as you approach the sampling frequency (even with pre-warping during the design). However, the curve of phase error is so close to a straight line that it looks like a pure delay, which is inaudible. The excess delay is about 15° at 20kHz, which I doubt is audible. Again, redesigning for 96kHz

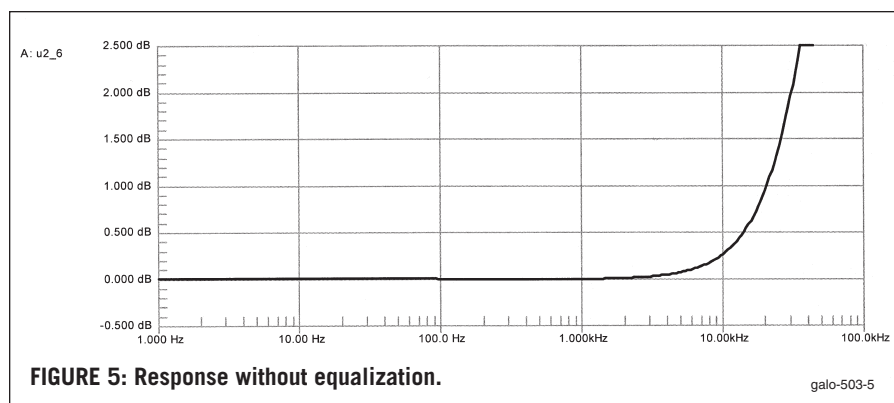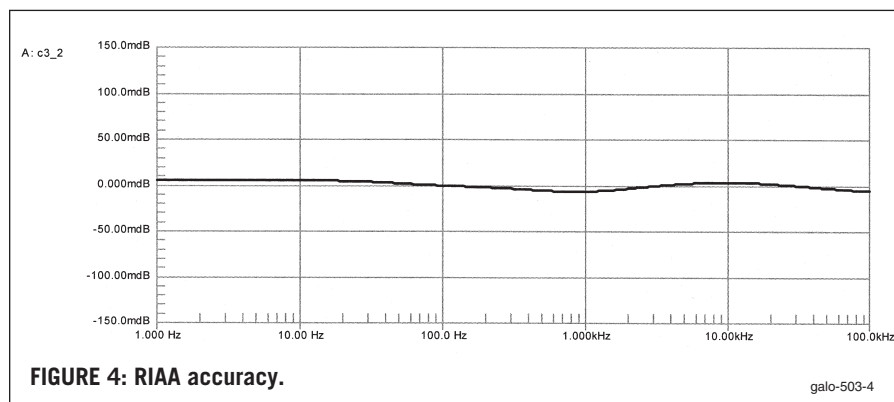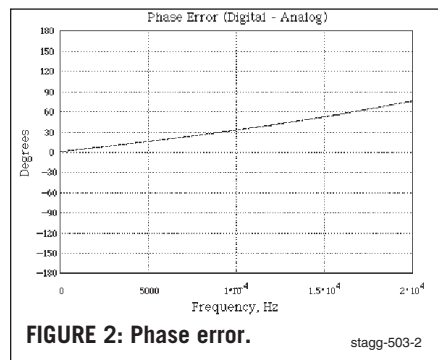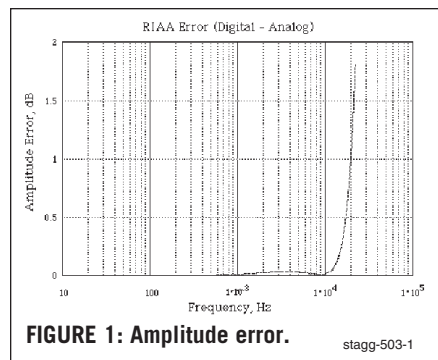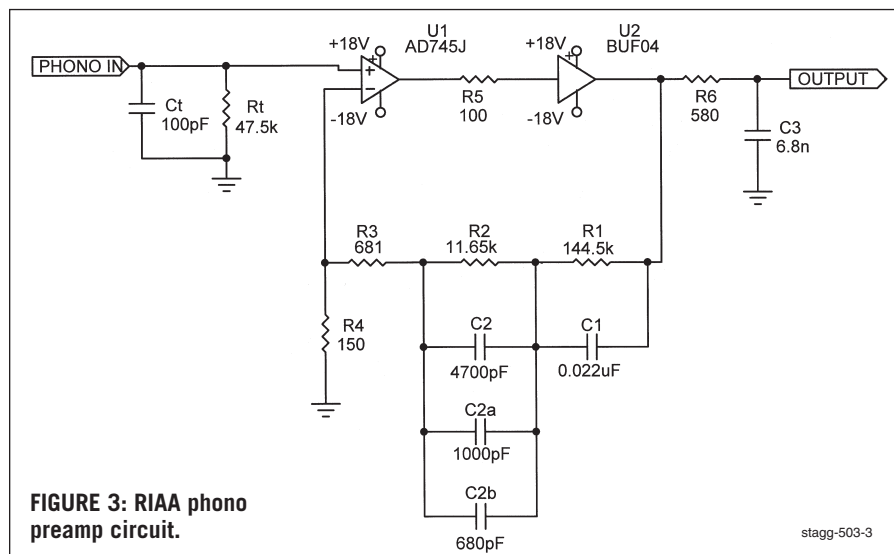

sampling will reduce even this error to effectively zero.

The only way to get non-analog phase response from a digital filter is to use non-analog design techniques. This is typically done in the antialias filters built into analog-to-digital converters in order to eliminate the large excess group delay inherent in steep filters, and similarly in the reconstruction filters in CD players.

It is even possible to use phase equalization techniques (without altering the amplitude response) on digitized LP tracks in order to improve the sound captured from some LPs, and I have done so. However, that is beyond the scope of this letter.

Victor Staggs
Torrance, Calif.

* Since I wrote this letter, a company has made a commercial software RIAA digital filter. The Griffin Technology Company, which makes monitor and sound adapters for the Macintosh computers, has released an RIAA equalizer digital filter to be used when importing LP recordings directly from a turntable, without any phono preamp. If you own their iMic sound input digitizer, the recording and equalization software is a free download at this date.

Gary Galo responds:

After receiving Victor Staggs' letter, I made inquiries to three of the leading manufacturers of digital editing equipment; namely, Sadie, Sonic Solutions, and Cedar. I asked them whether the algorithms for their digital equalization would mimic both the frequency and phase characteristics of analog filters. I also explained that I was specifically interested in phono equalization. I received no response from Cedar.

Ron Rigler of Sonic Solutions noted that they manufacture an equalization system specifically for RIAA de-emphasis. He further stated: "My understanding is that the filters are designed to mimic the phase response of an analog filter. You can use Desk Events or Complex Filtering in the background to produce any set of filters you desire."

Mike Porter of Sadie replied as follows: "The truthful answer is that we aren't 100% sure that the EQ does follow typical analog phasing characteristics. The EQ was de-

signed several years ago before the "Linear Phase" phrase became a popular topic of discussion. We are fairly certain that "Linear Phase" was not designed in as a principal characteristic of our EQ. The gentleman who was the design engineer with Sadie at that time left the company a few years ago and we were not able to contact him."

So the answer to this question would seem to vary from one manufacturer to the next. I caution against using any digital equalization system for phono equalization without a guarantee from the manufacturer that their digital equalizers duplicate both the amplitude and phase characteristics of analog filters.

I agree with Dr. Staggs regarding the dynamic limitations of 16-bit digital audio. In professional workstations, and the best sound cards, 24-bit is now the norm, so this shouldn't be a concern.

However, I do not agree with Staggs on what constitutes sufficient accuracy in an RIAA equalizer. Long-time readers of these pages (I refer to the predecessor of aX, The Audio Amateur) will recall the debates of the late 1970s and early 1980s regarding the audibility of differences between phono preamps. The view among some engineers was

Microphone preamps
Phono preamps
Amplifiers, filters, more...
Data sheets by mail or FAX
All User Guides on our web
site in Adobe® format
(All instruments are built in the USA)




ALSO DOING AUDIO
RESTORATION, DETAILS
ON WEB SITE

www.zianet.com/tld

TDL® Technology, Inc.
5260 Cochise Trail
Las Cruces, NM 88012 USA
505-382-3173
FAX 505-382-8810

It is not enough to put oil
into a Capacitor to make
it musical....

**KRISTALL
CAP**

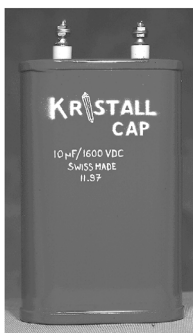

Forget about resistive devices
for the volume setting.
We offer a silver wired
transformer approach

**Silver Rock
Transformer-
Potentiometer**



It is not enough
to use silver wire
for a good SE-OPT...

**Silver Rock
Output transformer**



**There is only one optimum solution
for a given problem.**

Audio Consulting / 14B chemin des Vignes / 1291 Commugny / Switzerland
Fax: 00-41-22-960-12-59 / e-mail: serge.schmidlin@span.ch
<http://www.audio-consulting.ch>

that the only audible differences between phono preamps were those caused by errors in frequency response, phase, and absolute polarity. Those on the "golden-ear" side of the debate insisted that other, less easily quantifiable differences were also audible.

One thing that most audiophiles in both camps agreed on was the necessity of extremely accurate RIAA equalization, eliminating RIAA errors as a factor in LP reproduction. Errors of $\pm 0.25\text{dB}$ are at the edge of acceptability, and for well over 20 years the better RIAA phono preamplifiers have generally offered accuracy to within $\pm 0.1\text{dB}$. Since Stanley Lipshitz published his paper "On RIAA Equalization" in the June 1979 issue of the Journal of the Audio Engineering Society, the mathematics for designing extremely accurate RIAA networks has been readily available.

As Lipshitz pointed out in his opening paragraph: "One fact, however, is indisputable, and that is that frequency response differences exceeding a few tenths of a decibel in magnitude between disk preamplifiers are audible. Such deviations tend to be broad band in extent, since they arise from gain and component errors within the RIAA deemphasis circuit." Lipshitz also points out

that the additional high frequency time-constant, T_6 , inherent in feedback-based RIAA preamplifiers, can cause an audible rise in high-frequency response if not properly compensated.

I consider Dr. Staggs' RIAA accuracy to be unacceptable by either "scientific" or "golden-ear" standards. I doubt that very many audiophiles in either camp would consider the gradual rise in response in the top octave—a full 1dB at 20kHz—to be inaudible or otherwise of no consequence. In fact, it is an error very similar to what you can get if you ignore Lipshitz's T_6 in a conventional analog RIAA de-emphasis circuit.

Figure 3 is an RIAA phono preamplifier I designed a while back, using Analog Devices' AD745J op-amp as the gain block, buffered by their BUF04 closed-loop, current-feedback buffer. I designed the circuit for a 1kHz gain of 40dB. R_3 satisfies the stability requirement of the AD745 (minimum voltage gain of 5), and I calculated the RIAA values using a spreadsheet I designed to do the Lipshitz math for all four RIAA topologies. The network R_6/C_3 compensates for T_6 . I have not dealt with the DC-offset issues here. Either a servo or an output coupling capacitor will be necessary. I have

shown the parallel capacitor values necessary to make up C_2 , from available E12 values. R_1 and R_2 can easily be made from series or parallel combinations of E96 values.

Figure 4 shows a SPICE computer simulation of the RIAA accuracy, using a mathematically ideal RIAA emphasis model. As you can see, the circuit is capable of excellent RIAA accuracy, better than $\pm 0.012\text{dB}$. Figure 5 shows what happens to the RIAA accuracy when the R_6/C_3 network is eliminated. The RIAA response is up 1dB at 20kHz. If I were to publish such a circuit in these pages, I would probably be taken to task for a serious design oversight, and rightly so.

I admit to being a purist, and agree with Staggs that a 96kHz sampling rate is probably a minimum requirement if RIAA EQ is to be done properly in the digital domain.

REVIEW AFTERWORD

I read and enjoyed your review of the K-12M stereo amplifier by S-5 Electronics. Your review was thorough and honest.

I was concerned about the part on the K-12M's muddy bass, which would probably be solved by an upgrade of the output transformers. Substituting those supplied with Hammond P-T1609s

REPRINTED IN BOOK FORM!

Audiocraft Magazine by Audio Amateur Inc.

Published from November 1955 until its untimely demise in November 1958, *Audiocraft* magazine served the DIY audio community with a wealth of information from some of the greatest experts in the early audio industry. Regular offerings included Joseph Marshall's "The Grounded Ear," J. Gordon Holt's monthly articles on tape recording, and Norman Crowhurst's articles on amplifier design. Other highlights include Roy Allison's "Basic Electronics" columns, and a host of authors including Paul Klipsch, George L. Augspurger, and Dr. John D. Seagrave, as well as independent equipment tests from the Hirsch Houck Laboratories.



Order today by calling
1-888-924-9465
or e-mail custserv@audioXpress.com.

<i>Audiocraft: The First Fourteen Issues</i>	LAC1	\$49.95*
<i>Audiocraft: The Second Twelve Issues</i>	LAC2	\$49.95*
<i>Audiocraft: The Final Eleven Issues</i>	LAC3	\$49.95*

*Shipping for each volume add \$8.00 in the US; \$11.00 in Canada; \$13.75, other surface; \$28.25 other air.



Old Colony Sound Laboratory
PO Box 876 Dept WTD3
Peterborough, NH 03458-0876 USA
Phone: 603-924-9464 Fax: 603-924-9467
E-mail: custserv@audioXpress.com

ORDER THESE OR ANY OF OUR BOOKS & PRODUCTS ON-LINE AT www.audioXpress.com

(10KCT: 4/8/16Ω) would clean up the bass.

It's also important to note that the 11MS8 is not a high-fidelity tube per se. It's a variation of 11BM8 (an 11-volt 6BM8). The 11MS8 and 11BM8/6BM8 were intended for single-end use in portable phonographs and tape recorders where chassis space is extremely limited. In this type of application, small speakers with limited frequency response were used anyway, so the 6/11BM8 filled the bill.

You had reported that the 11MS8 was made in Japan. Tubes produced in Japan have rated poorly in *VTV* (Vacuum Tube Valley) magazine's tube shootouts. It might help to replace those furnished with some purchased from Antique Electronic Supply—providing they're not just Japanese jobbers.

A similar kit, using 11BM8s, as opposed to 11MS8s, is available from AES for \$140. While it costs \$10 more, I would go with it. In addition to the earlier-mentioned opt upgrade, the 11BM8 is probably easier to obtain under additional brands names, making further experimenting possible.

Neal A. Haight
Castro Valley, Calif.

Duncan and Nancy MacArthur respond:

Thanks for your thoughtful comments on the S-5 amplifier.

We tend to agree with many of your ideas about parts with the caveat that sometimes parts choices are synergistic, and changing one may upset the balance of the whole. In the final analysis, it's the results that matter.

In particular, the transformer set would appear to be a weak point in this design. But good iron costs money, and each consumer will need to make decisions based on his or her own budget.

Our only experience with the AES kit is the description and small picture on their web page. It appears to be extremely similar to the S-5 and has the same designer. At any rate, the AES amplifier looks worth investigating if you're in the market for an amplifier in this price range.

We note that S-5 is now selling a case for the amplifier that appears to address many of our ergonomic concerns. As of now the existence of this case and the fact that we've heard it would tip the scales slightly towards

the S-5 for us. (If you audition the AES, we'd be interested in hearing about your reaction.)

For more information, the websites are located at <http://s5electronics.com/index.html> and <http://www.tubesandmore.com/>.

SOFTWARE IDENTIFIED

Can you please tell me what software was used for circuit simulation in "A Passive, Low Level Crossover" (Nov. '02 aX, p. 16)? If it is not too much trouble, could you direct me to a vendor that sells this or a similar product to run these simulations.

David Miles
MilesAudio@aol.com

Cornelius Morton responds:

I used B² Spice by Beige Bag Software (www.beigebag.com, 734-332-0487, info@beigebag.com) for the simulation. Typing in "spice simulation" in the Google search window will bring up a ton of information and sites on SPICE simulators. A good start is the following link to a site listing numerous SPICE sources: <http://www.et1.tu-harburg.de/private/kb/download.html>.

PASS DIY

Printed Circuit Boards

Key Components

Plans

Zen Variations

Pearl Phono

and more...

PO Box 12878
Reno, NV 89510

www.passdiy.com



velleman Inc.

**MONO 65W
PURE CLASS A
TUBE POWER
AMPLIFIER
WITH KT88
TUBES**

K8010



**600W
MONO/
STEREO
MOSFET AMPLIFIER**

call or email for the NEW Velleman catalog & distributor list

7415 WHITEHALL STREET SUITE 117,
FORT WORTH, TX 76118
www.vellemanusa.com

TEL: (817) 284-7785
FAX: (817) 284-7712
email: Info@VellemanUSA.com

Test CDs From OLD COLONY SOUND LAB

CBS Records Standard Test Disc Pro Series CD-1



For measuring CD player performance with E.I.A. standard signals. 21 tracks including separation, frequency response, linearity, and other signals.

CD1\$45.00

CD-CHECK®

Easily ensure your CD-player delivers the complete range of digital sound.

CDDR2\$24.95

AUDIO-CD®

An easy and inexpensive way to detect hearing loss early—allowing you to take preventive and corrective action.

CDDR1\$24.95

Mix Reference Disc-Deluxe Edition

Expanded collection of audio test signals for pro audio or multimedia applications.

CDMX1\$39.95

"My Disc"-The Sheffield/A2TB Test Disc

For critical evaluation of audio components, listening environments, and your critical listening ability. 86 tracks including musical selections.

CDSH3\$29.95

EIA-426-B Loudspeaker Power Rating Test CD

from ALMA International

Developed as a companion to the written standard, the CD contains the calibration and test signals for all tests defined in the standard and outlines the procedures for making best use of the disk in setting the power ratings of loudspeakers and the amplifiers that drive them. Also includes a number of test-signal tracks, including additional higher-frequency pure tones and shaped tone bursts, not a part of the standard. 2001.

CDAL2\$99.00

NEW! CARA Test CD for Room Acoustics

ELAC Technische Software GmbH

The CARA Test CD is designed to help you test the acoustics of your listening room. Tracks 1–28 contain Pure Sine Wave Tones (70 seconds per track). Tracks 29–55 reproduce narrowband ($\frac{1}{8}$ octave) and pink noise (70 seconds per track). The last four tracks on the disc provide coloration, polarity, and phase testing.




CDCARA\$19.95

Auditory Demonstrations Test Disc


Philips

79 tracks featuring demonstrations of cancelled harmonics, decibel scale, masking, virtual patch, logarithmic and linear frequency scales, effect of echoes, and more.

CDAC\$37.95

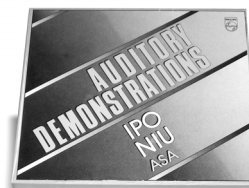

Studio Reference CD

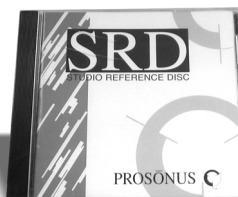

Prosonus

Developed especially to allow high-quality test and evaluation procedures to be made easily and quickly. 62 bands of test signals.

CDSA1\$69.95

Stereophile Test CD Three

From the publishers of *Stereophile* magazine, contains 27 tracks which include musical selections and signals for testing loudspeakers and rooms, electronic components, amplifiers and CD players.

CDSTPH3\$9.95



Shipping weight of all CDs is 1 lb. each.

TO ORDER:

call **1-888-924-9465**
or fax **603-924-9467**

Order On-line at
www.audioXpress.com


Check out more test CDs and track listings for these products on-line at
www.audioXpress.com

Old Colony Sound Lab, PO Box 876 Dept. V3, Peterborough, NH 03458-0876 USA
Phone: 603-924-9464 **Fax:** 603-924-9467 **E-mail:** custserv@audioXpress.com

New Chips on the Block

AKM AK4363 and AK4364

By Charles Hansen

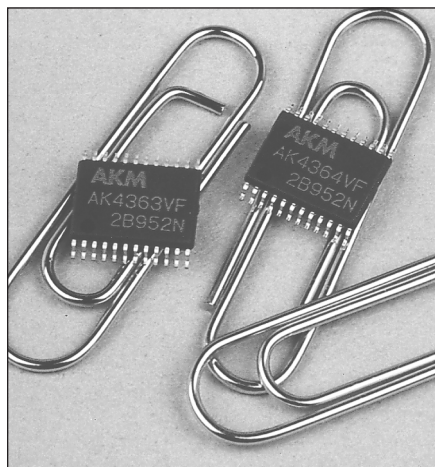

AKM Semiconductor has introduced the AK4363/AK4364 96kHz 24-bit, 2-channel stereo $\Sigma\Delta$ DAC with integrated programmable phase-locked loop (PLL), for MPEG/AC-3 audio playback. In an MPEG video system, the video and audio signals must be synchronized, which requires an audio DAC that operates at 27MHz, the MPEG clock standard. These chips are designed to solve integration problems for Set Box designers. The AK4364 also has a SPDIF digital audio interface transmitter (DIT) that simplifies transmission of digital audio to an external A/V receiver.

FEATURES INCLUDE:

S/(N+D): 90dB @ 5V

DR: 102dB @ 5V

S/N: 102dB @ 5V

Multiple sampling frequencies:

16kHz, 22.05kHz, 24kHz (half rate)

32kHz, 44.1kHz, 48kHz (normal rate)
64kHz, 88.2kHz, 96kHz (double rate)

On-chip low jitter analog PLL:

Multiple master clock frequencies generated from 27MHz

128fs/192fs for double rate

256fs/384fs for half/normal/double rate

512fs/768fs for half/normal rate

1024fs/1536fs for half rate

Master clock: PLL/external

Data input formats:

LSB justified/MSB justified/I²S selectable

Selectable function:

Soft mute

Digital attenuator (256 steps)

Digital de-emphasis

(44.1kHz/48kHz/32kHz)

Output mode: Stereo, mono, reverse, mute

Input level: TTL/CMOS selectable

Output level: 3.0V pp @ 5V

Control mode: 3-wire serial/I²C Bus

Low power dissipation: 80mW

Small 24-pin VSOP package

Power supply: 2.7 to 5.5V

AK4364 on-chip DIT:

Compatible with S/PDIF, IEC958, AES/EBU, and EIAJ CP1201 mode

AKM Semiconductor, contact Richard Kulavik toll-free at 888-256-7364, or icinfo@akm.com for information and engineering samples. AK4363 pricing \$2.06 US (10k pieces), AK4364 pricing \$4.63 US (10k pieces). ♦

*Ready, willing
and*
AVEL



*offering an extensive
range of ready-to-go
toroidal transformers
to please the ear, but won't
take you for a ride.*

 Avel Lindberg Inc.

47 South End Plaza
New Milford, CT 06776
tel: 860-355-4711
fax: 860-354-8597
www.avellindberg.com

LAST

Record Preservative



Hear Ye – Hear Ye

LAST®

THE LAST FACTORY

2015 RESEARCH DRIVE
LIVERMORE, CA 94550-3803
925-449-9449 • FAX 925-447-0662
www.lastfactory.com

Book Review

Loudspeaker and Headphone Handbook

Reviewed by Richard Honeycutt

Loudspeaker and Headphone Handbook, John Borwick, Ed., Focal Press, an Imprint of Butterworth-Heinemann, Linacre House, Jordan Hill, Oxford, OX2 8DP, UK; 225 Wildwood Ave., Woburn, MA 01801-2041, USA. \$120.

Perhaps the first in-depth book on loudspeakers was *Loudspeakers*, by N. W. McLachlan, published by Unwin Brothers in 1934. Since then, high-quality additions to the genre have been few and far between. Beranek's *Acoustics* and Olson's *Acoustical Engineering* each contained a treasure-trove of information, but neither was wholly dedicated to loudspeakers. Good books on headphones have been—to my knowledge—nonexistent, and even good papers on the subject in professional journals are not common.

First published in 1988, the *Loudspeaker and Headphone Handbook* jumps into the breach quite nicely. The current third edition contains the following chapters: Principles of Sound Radiation, Transducer Drive Mechanisms, Electrostatic Speakers, The Distributed Mode Loudspeaker (new to this edition), Multiple Driver Loudspeaker Systems, The Amplifier/Loudspeaker Interface, Loudspeaker Enclosures, The Room Environment: Basic Theory, The Room Environment: Problems and Solutions (these last two were a single chapter in the previous edition), Sound Reinforcement and Public Address, Loudspeakers for Studio Monitoring and Public Address, Loudspeaker Measurements, Subjective Evaluation, Headphones, International Standards, and Terminology. The third edition contains 718 pages, as compared to 592 for the second.


No single person could write equally well on all these subjects, so the *Hand-*

book is the product of specialists, each contributing one or more chapters. All are names well-known in the industry, including the late Peter J. Baxandall, Graham Bank, Mark Gander, Martin Collops, Floyd Toole, and John Woodgate, to name a few.

This book covers principles, and it falls somewhere between being a design text and a general acoustics text. While it provides more depth and detail than the hobbyist books on the subject, it is certainly not a cookbook.

One example is the first chapter, which describes the principles of sound radiation, using an appropriate level of math (complex differential equations). The discussion is limited to mathematical models applicable to loudspeakers, and includes mention of the frequency range in which each model is useful. The chapter examines the effects of mutual coupling on frequency response and diaphragm loading, and discusses edge diffraction. It explains the function of a horn both as an impedance transformer and as a means of directional control, and discusses nonlinear propagation of sound in intense sound fields.

The chapter on transducer drive mechanisms begins with a short history of loudspeakers, then proceeds to discuss cone behavior, magnetism, several different magnetic field structures, interaction between the voice coil and the stationary magnetic field in a loudspeaker, the chassis, efficiency, power handling and dissipation, the dome driver, the horn driver, the ribbon speaker, modeling the motor, the com-

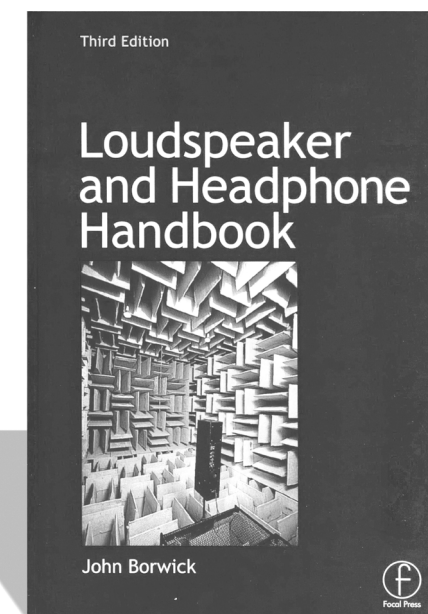

pound loudspeaker, and motional feedback. As you can see, this chapter packs quite a bit of information into its 62 pages. So do the other chapters.

Another example is the chapter on headphones. On the one hand, it is only one chapter, but on the other, it is 108 pages long! Far from just cataloging the many ways that you can mount speakers in cans and strap them to your head, this chapter begins with a thorough discussion of the ways in which the acoustics of headphones differ from those of a loudspeaker—both from a design and a usage standpoint.

Next comes a section on modeling headphones, after which you are finally equipped to appreciate both the acoustical problems in headphone design and the ways in which the various realizations of headphones interact with the acoustic problems. This chapter presents sample low-frequency responses for closed circumaural, open foam circumaural, impermeable foam circumau-

ral with fixed acoustical resistance, and integrated open headphones, then compares isodynamic and moving-coil transducers. It examines anomalies in response due to resonances involving the cushion/flesh resilience and the mass of the earcup, and studies in-ear phones.

This chapter provides a good bit of detail concerning the human hearing mechanism, especially in relation to the behavior of headphones. It discusses special-purpose phones, and, finally, describes headphone testing. From these two examples, you can see how much depth is provided in the *Handbook*.

Now, given the generous topical coverage, is there anything left out? Actually, not much. One important aspect of professional loudspeaker performance that tends to receive little coverage in the general press is directivity.

In the *Handbook*, while the information on directivity is spread among several chapters, it all sums to a pretty good outline of the subject. In particular, Peter Mapp's chapter on sound reinforcement and PA touches on most of the important considerations regarding directivity. You might hope for a complete chapter in a future edition devoted entirely to directivity, beginning with principles, and then moving to a discussion of cone drivers, horns, and various types of arrays. This sort of material is available, but has not been collected into a single reference.

The *Loudspeaker and Headphone Handbook* lends itself to numerous uses. The engineer who specializes in general electrical or mechanical engineering will find this book an excellent entrée to speaker design.

To the practicing loudspeaker engineer, the book presents a helpful intro into the areas of speaker art and science with which (s)he may be unfamiliar. The engineer who designs electronic equipment that interfaces with loudspeakers, or the consultant whose work involves sound systems, can learn much that is important to their work. And the hobbyist (aren't most of us, really?) can develop a professional-like understanding. In addition, the generous end-of-chapter references lead you to information in further depth.

In short, this book should be in the library of every loudspeaker professional or enthusiast. ♦

AUDIO TRANSFORMERS

AMERICA'S PREMIER COIL WINDER

Engineering • Rewinding • Prototypes

**McINTOSH - MARANTZ - HARMAN-KARDON
WESTERN ELECTRIC - TRIAD - ACROSOUND
FISHER - CHICAGO - STANCOR - DYNACO
LANGEVIN - PEERLESS - FENDER - MARSHALL
ELECTROSTATIC SPEAKER TRANSFORMERS**

***Williamson Amplifier Transformer Specialist*
WE DESIGN AND BUILD TRANSFORMERS
FOR ANY POWER AMPLIFIER TUBE**

PHONE: [414] 774-6625 FAX: [414] 774-4425

AUDIO TRANSFORMERS


185 NORTH 85th STREET

WAUWATOSA, WI 53226-4601

E-mail: AUTRAN@AOL.com

NO CATALOG

CUSTOM WORK

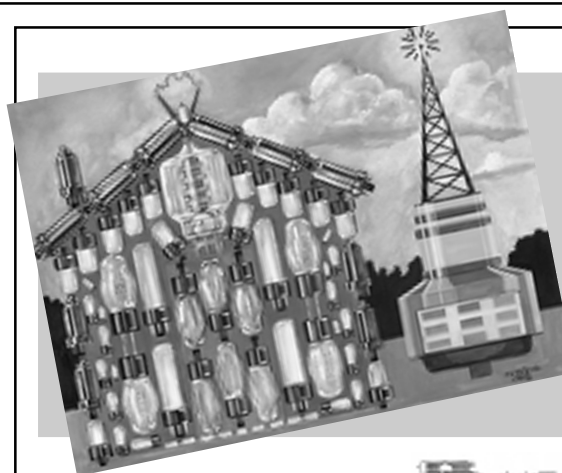

**Putting
the Glow
in Your
Audio
System!**

**THE HOUSE
OF TUBES**

We know that tubes are the heart of a transceiver and the soul of an amplifier. That's why we're dedicated to reliable tubes at excellent prices. We offer the finest in audio tubes and quality components, and we've made ordering convenient.

Visit us at:

www.houseoftubes.com

e-mail:

landlord@houseoftubes.com

TUBES—They're our foundation.

Classifieds

FOR SALE

Sale Western Electric Craftsman 500
845 211 Amplifier quality parts throughout,
will part out. All must go.
Daniel @ 917-218-7668

VENDORS

American Science & Surplus. Audio, electronic and mechanical components, connectors, wiring, kits, magnets, speakers, tools, hardware, and more! Call for a free catalog: 847-647-0011 or shop www.sciplus.com.

ALL-FET line amp, poweramp kits
www.borbelyaudio.com
Borbely Audio kits in USA:
www.audiokits.com

CONCRETE CABINET loudspeakers
www.faradaysound.co.uk
DIY instruction booklet \$15

DIY-ZEROs

Autoformers as seen in
Jan. 2003 of *audioXpress*

\$433/pair

PaulSpeltz@hotmail.com
651-735-0534

www.ZEROimpedance.com

Repairs and upgrades for audio equipment.
Let longtime *aX* contributor and VTV senior editor Eric Barbour make your system sound better.

METASONIX, PMB 109, 881 11th St., Lakeport, CA 95453, synth@metasonix.com, (707) 263-5343.

UNDERSTAND ELECTRONICS, THE EASY WAY. Read the book that received all 5-star reviews at both amazon.com and bn.com, saying it's unusually easy to read and understand. Explains what makes inductors and amplifiers work and so on. Hints about solder, oscillation, measurements. Write author's name, Shanefield, in any bookstore's search box. See also

<http://homepage.mac.com/shanefield>.

Sonic Craft is your high-end speaker source! Accuton, AudioCap, Axon, Alpha-Core, Black-hole 5, Cardas, Goertz, Mills, Sonicap, and kits are on the way! Call 940-689-9800, or see www.soniccraft.com

Principles of Power, tube audio books, kits, FAQ www.londonpower.com.

DIY HI-FI SUPPLY

www.diyhifisupply.com

Tubes: Valve Art, TJ Meshplate, Sovtek, Svetlana, China miltpec NOS

Kits: Billie 300B, Ella KT88, Joplin 2A3, Basie pre, Origin Live turntable kit, DAC

Accessories: XO Clock, S&B transformers, SSC isolation

Parts: Audionote copper and silver caps, Goldpoint, DACT, Seiden, Bullet plugs, Ultra-refined silver wire, SCR, Kiwame, etc

www.diyhifisupply.com
sales@diyhifisupply.com



gear racks, media drawers and more

Factory direct since 1984
Free brochure (mention audioXpress)
Per Madsen Design (800) 821-4883

www.rackittm.com



www.kleintechsys.com

ACOUSTIC INTERFACE PADS

COMPOSED OF SPACE-AGE POLYMERS

Improve sound clarity, optimize and expand tonal range. Isolate, reduce, and dampen cabinet distortion and vibration. Secure objects and furniture for stability. Eliminate the need for spikes, bolts, mounts. Fastens and adapts any speaker to any stand or surface. Great for center channel speakers, tile, wood, and linoleum floors. Stops vibration between amps, CD transports. Dealers encouraged!

p: 561-969-2298 f: 561-423-0388 e: support@kleintechsys.com



EUPHASE Audio

www.euphase.com
info@euphase.com

USHER AUDIO TECHNOLOGY Speaker Drivers

High Quality Products
Competitive Prices



Visit www.euphase.com for more information on the drivers and ordering.

Please contact for OEM and Quantity Purchase inquiries. Other models and customizations can be quoted upon request.

AD INDEX

ADVERTISER	PAGE
ACO Pacific Inc	35
Adire Audio	19
All Electronics	51
Alpha Electronics Corp of America	37
Antique Radio Classified	61
Audience	35
Audio Amateur Corp.	
<i>AudioCraft collection</i>	64
<i>audioXpress 2002 on CD</i>	48
Classifieds	70
Jensen Transformers	8
<i>Loudspeaker Design Cookbook 6th Edition</i>	71
Mitey Mike II	71
Test CDs	66
Audio Consulting	63
Audio Transformers	69
Audiogon.com	16, 20, 26, 44, 48
Audiomatica	59
Avel Lindberg Inc	67
Cardas Audio	7
Classified Audio-Video	47
DH Labs Audio Cables	CV2
Dynasonic Ltd	41
E-Speakers	72
EiFL	21
Electro-Harmonix/New Sensor	1
Emerald Physics	13
Grennan Audio	43

ADVERTISER	PAGE
Hagerman Technology	61
Hammond Manufacturing	17
Harris Technologies	19
Hi Fi Do Inc	27
House of Tubes	69
JENA Labs	37
KAB Electro-Acoustics	45
Kimber Cable/WBT-USA	5
K&K Audio	51
Langrex Supplies	47
Linear Integrated Systems	57
Madisound Speakers	24
Marchand Electronics	45
McFeelys	43
Millen Hardware	59
Mouser Electronics	33
Origin Live	25
Parts Connexion	15
Parts Express Int'l., Inc.	CV4
Pass Laboratories	65
Plitron Manufacturing	49
RF Parts Company	57
Selectronics	23
Sencore	29
Solen, Inc.	CV3
Speaker City USA	31
Speaker Works	39
Swans Speakers	11

ADVERTISER	PAGE
TDL Technology Inc	63
The Last Factory	67
Thetubestore.com	56
Usher Audio	9
Velleman Inc	65
Venus HiFi	39
Vidsonix	41
WBT-USA/Kimber Cable	5
World Audio Design	30
Zalytron Industries	31

CLASSIFIEDS

American Science & Surplus	70
Audio Upgrades	71
Billington Exports	71
Borbely Audio	70
DIY HiFi Supply	70
Euphase Audio	70
Faraday Sound	70
Klein Tech Systems	70
London Power	70
Metasonix	70
Daniel Ross	70
Daniel Shanefield	70
Paul Speltz	70
Per Madsen	70
Sonic Craft	70
Vintage Hi-Fi	71



Unique C.D. player & TUBE gear MOD'S!
Loudspeaker rebuilding!
fab audio high efficiency loudspeakers!
audio-upgrades@bellnet.ca

tubes?
www.tubes.it



All types of audio tubes. 300B 6DJ8
ECC81 ECC83 KT88 Mullard GEC
Sylvania. Discount for large quantity.
Billington UK. Tel (0)1403 784961.
Fax (0)1403 783519.
Email/website www.bel-tubes.co.uk

www.audioXpress.com

Yard Sale

FOR SALE

Assemblage L-1 preamp kit with chassis, no switches, pots, or faceplate, \$250; Sonic Frontiers SFL-1 preamp circuit board, only \$150; Anthem 1 all tube integrated amp (circuit board only) with all three transformers, \$250; Assemblage DAC 3.1 Signature, \$1000; D2D rate converter, \$350. dave.pitt@rogers.com or 905-819-8462.

Marantz 23 tuner; Philips CDC-875 changer; Proton 440 tuner; Dynaco FM-5; Philips CDB-560; Isodrive; Magnavox CDB-582; Byteline III digital cable; PS Audio 5.5 preamp with M500 power supply; VAC-poweramp-PA 100/100 (KT88 tubes). All mint. Dave, 724-274-8149.

Drivers, all new. Scanspeak, two Kevlar mids 13M8636 (\$115 ea), \$70 ea; two mid 13M8640 (\$85 ea), \$50 ea; Vifa, two tweeter D27TG45-06 (\$25 ea), \$15 ea; Scanspeak Automotive, two bass 21W555 (\$156 ea), \$95 ea; four tweeter D2904.60000 (\$110 ea), \$65 ea; Dynaudio, eight tweeter D260 with square frame, \$50 ea. 360-260-1147, weekends 509-586-9735, wrightt@gbaudio.com.

WANTED

Old/new hi-fi gear and speakers, tube/solid state, amps, preamps, tuners, tubes, tube testers, guitars, guitar amps, and so on—Altec, McIntosh, Audio Research, Marantz, Conrad Johnson, Western Electric, Electro-Voice, ASL, Hickok, Gibson, Fender, Vox, and so on, all considered, working or not. Call 850-314-0321 or e-mail sonnysound@aol.com.

Want to buy "as is": Quad ESL 57 or Quad ESL 63 speakers or parts for restoration project; NAD 3020 integrated amplifier or NAD 7020 receiver. Greg (519) 745-1579 or gnawrock@sympatico.ca.


Yard Sale Guidelines

For information on how you can publish your free personal ad in *audioXpress*, visit our website at www.audioXpress.com.

Classified Information

To find out how you can order an ad for the classified pages, see our website at www.audioXpress.com.

Now IN THE
6th
EDITION

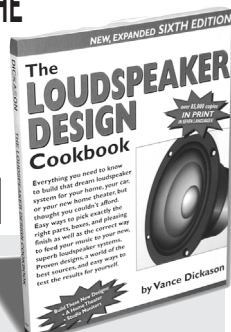

- More Pages
- More Graphs
- More References
- Brand New Chapters
- Explanations of New Technology

BKAA60
\$39.95

Order Your Copy
TODAY
by calling

1-888-924-9465

or order on-line at
www.audioXpress.com

Old Colony Sound Laboratory, PO Box 876
Dept. X3, Peterborough, NH 03458-0876 USA
Phone: 603-924-9464 Fax: 603-924-9467
E-mail: custserv@audioXpress.com

Shipping and
handling add
\$7.25, Canada
add \$11.00

Overseas sur-
face mail add
\$10.25, air mail
add \$22.25.

SMALLER
QUIETER
USES LESS
POWER

MITEY MIKE II

"One seldom finds a low-cost microphone that provides high quality performance and yet can be used with confidence in so many different circumstances." Daniel Queen, *Voice Coil*

MITEY MIKE II—SPECIFICATIONS:

Response (rel. 1 kHz)	± 1 dB, 20Hz-10kHz ± 2 dB, 10kHz-20kHz
Sensitivity @ 1 kHz	25 mv/Pa, ± 2 dB
Max. SPL (at 3% THD)	130 dB
Wide Band Noise Level	
Flat Weighting	≤ 40 dB
"A" Weighting	≤ 36 dB
Mid band dynamic range	≥ 120 dB

Price

MIKE AND WAND
\$139.00 per channel
\$179.00 calibrated per channel

PREAMP

\$159.00 assembled single channel
\$249.95 assembled two channel

Buy this microphone system for any application where you need a compact low-distortion, self-powered microphone.

- Loudspeaker Testing
- Sound Reinforcement
- Performance
- Field Recording
- Acoustical measurements

CALL 1-888-924-9465 TO ORDER
OR E-MAIL TO CUSTSERV@AUDIOXPRESS.COM
ORDER MITEY MIKE II ON-LINE AT
www.audioXpress.com!

Old Colony Sound Laboratory, PO Box 876 Dept X3,
Peterborough, NH 03458-0876 USA
Phone: 603-924-9464 Fax: 603-924-9467
E-mail: custserv@audioXpress.com


Vintage Glass

Merit Output Transformer

Output transformer designed for the Norman Crowhurst twin-coupled amplifier featured in the November 1957


issue of *Radio Electronics* magazine. (From Merit Coil & Transformer Corp. A-2997 instruction sheet issued Nov.

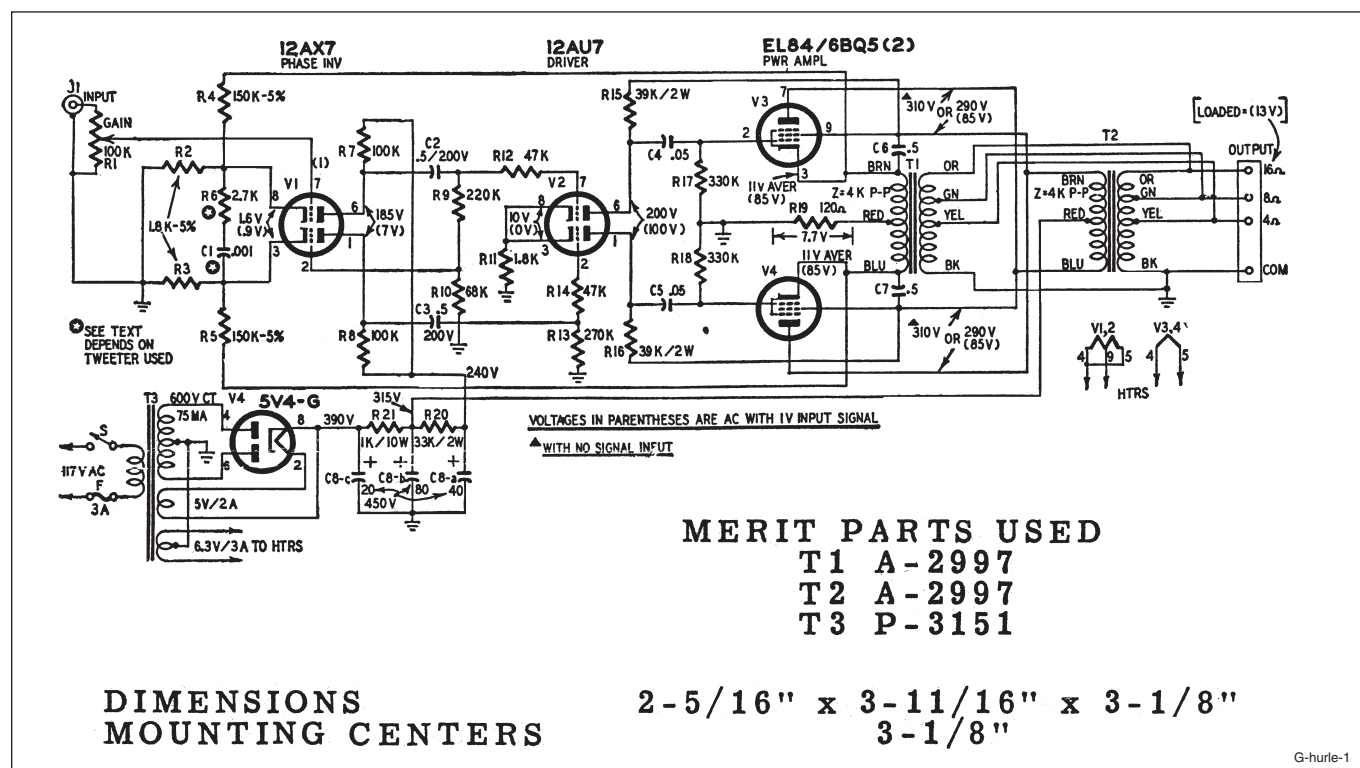1957.) Courtesy of Reed Hurley, Stockbridge, Ga. ❖



MANGER Bending wave transducer

"Natural accuracy"

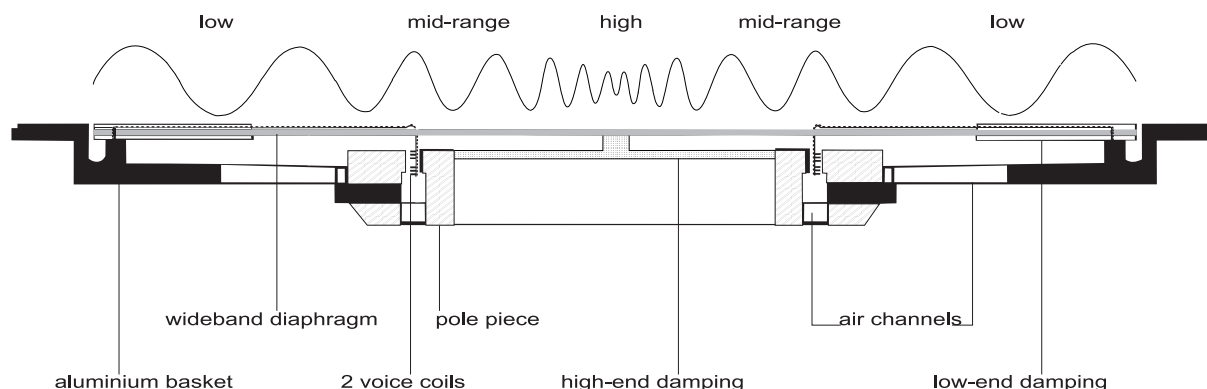

E-Speakers.com

Los Angeles, California. 818 907-8942 / www.e-speakers.com