

A High-Quality Solid-State Headphone Amp

By Dennis Colin



PHOTO 1: Headphone amp.

This compact unit, powered by an external 24V DC "wall wart" or battery, provides very high sonic fidelity, no audible noise, and switchable loudness compensation.

The maximum output power of this phone amp is 137mW into 300Ω phones, and 218mW into 32Ω phones. With the (most excellent; see sidebar) Sennheiser HD 650 300Ω phones, maximum undistorted SPL is 119dB sine wave, corresponding to


about 105–108dB music waveform average, which is about the SPL of a large orchestra playing full blast.

AMPLIFIER CIRCUIT

The output stage Q3-Q4, biased by constant-current sources Q1-Q2 (and asso-

ciated diodes and resistors), is a unity voltage gain power amplifier with a BW (bandwidth) of about 1.5MHz (Fig. 1). Q3-Q4 bias is about 30mA, enough to ensure Class A operation up to full power with 300Ω phones. With 32Ω phones, operation will be class AB at

FIGURE 1: Headphone amp (L channel shown).

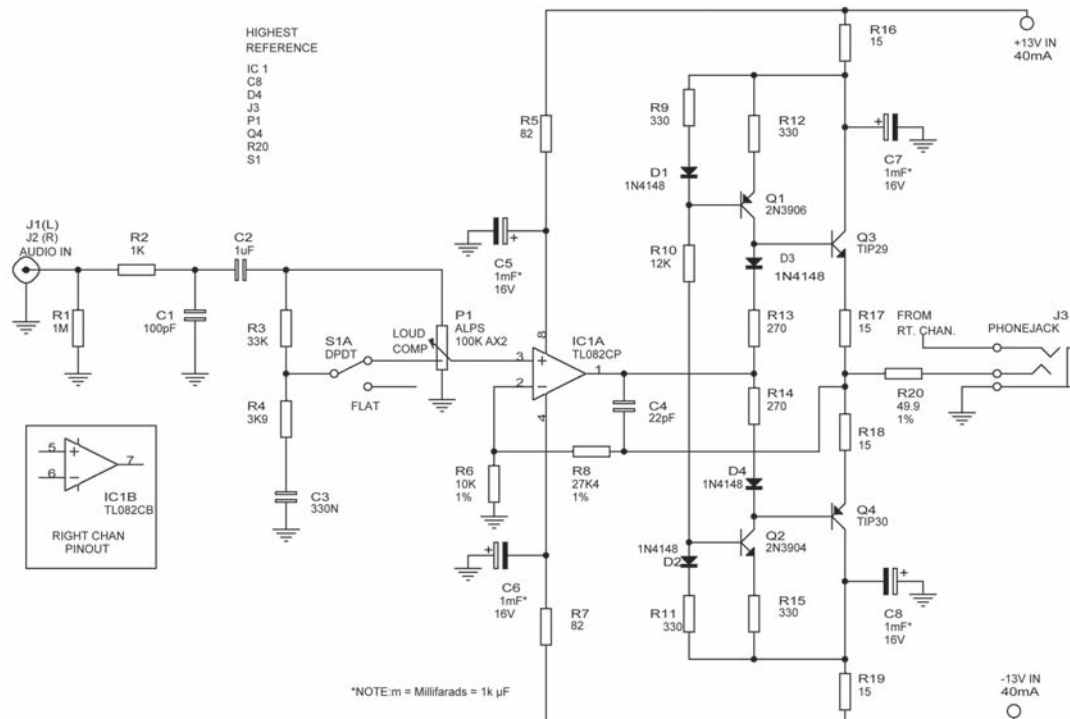

A-2512-01

high power, but distortion will still likely be inaudible. But you can obtain full Class A with 32Ω phones by increasing Q3-Q4 bias to about 120mA, by changing R13, R14 to 1.2kΩ. This, though, increases the dissipation of Q3 and Q4 from 0.36W to 1.1W, so you should use small TO-220 heatsinks (or insulated chassis heatsinking).

The TL082 input stage has a Class AB output. However, measurements involving supply current monitoring established that the TL082 output bias is 0.62mA, and its operation is Class A up to a load current of about ±1.2mA peak. The application here draws only about ±0.5mA peak, so the TL082 is always in Class A. This, plus a 1.3MHz available BW (reduced to 230kHz by C4), ensures high-purity amplification by the TL082.

INPUT STAGE AND FEEDBACK

The (half per channel) TL082, operating in Class A as described, provides stable gain, low DC offset, and low noise (inaudible; about 4dB SPL with the most sensitive phones). Feedback resistors R6, R8 precisely set the gain. C4 applies negative feedback locally around the op amp, above about 230kHz (the -3dB roll-off frequency of the overall amplifier). This cap is not necessary for stability; without C4 the amp's -3dB bandwidth is 1.26MHz and stable, but this invites AM radio interference, and so on.


50Ω OUTPUT IMPEDANCE

The feedback is taken from emitter resistors R17, R18, giving this junction a very low output impedance (<1Ω). So why the series 50Ω R20? This, of course, sets the amp's output impedance at 50Ω. The reasons for this are:

1. Output is unconditionally stable—open, short, pure reactance.

FIGURE1a: Transistor Pinouts.

A-2512-01a

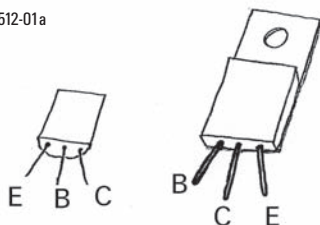

2N3904
2N3906

TIP 29
TIP 30

Precision Acoustic Measurements Require Precision Microphones



PS9200KIT™ USD

A complete IEC and ANSI traceable Type 1 Measurement Microphone System 2 Hz to 40 kHz, 15 dBA to 160 dB SPL
 *½ inch capsule *4012 Preamp *PS9200 2 Channel PS
 *AC adaptor *WS1 windscreen *SC1 die cut storage case.
 Options: 511E Calibrator; 1 & ¼ inch mics; and Gain for DRA's MLSSA and other board level products.

ACO Pacific, Inc.

2604 Read Ave. Belmont, CA 94002 USA
 Tel: (650) 595-8588 FAX: (650) 591-2891
 e-mail acopac@acopacific.com

ACOustics Begins With ACO™

Impeccable sound quality in a small package! **YES, Less is More** with

THE LITTLE WALLY

Clever Design & Minimum Parts Count = **BIG SOUND** in an Amp that Should cost more ... but **Mojo is included Free**



High Performance-to-Cost Ratio with a No-Compromise Attitude combined with Upgradeability—so if you want to go faster, the already great-sounding Lil'

Wally can be tweaked to perfection with just a little guidance from the designer. Amaze yourself & your friends by revealing what good sound is, and how to get it. How? The Little Wally is available in kit form as a module for your personal & custom modifications for \$150 US, or as a fully assembled amplifier.

Contact us at www.audiofyle.com to order a pair of modules or for a price for a pair of fully assembled mono-blocks.

At KICKWOOD AUDIO we design for optimal provable test results

Then we final tune under real listening conditions with recordings we are very familiar with so we can extract the last little nuances which are present in the medium, but often masked by imperfections in the playback chain.



We have Trapezoidal cabinet designs for the 10inch, 12inch, and 15inch Tannoy Gold & Tannoy Royal Tannoy HPD transducers.

We will also build cabinets to your specs.
 Contact us at www.audiofyle.com

Audio-Phyle Options

TABLE 1. Characteristics of Sennheiser Headphones.

Sennheiser HD 650 • Sound: Extremely Excellent • \$449
 $Z = 287\Omega + 1.227mH$ (both channels very well matched)
 Sens. = 103dB SPL at 1V RMS (manufacturer's data; confirmed by test) (3.3mW)

L-Chan		R-Chan.	
F	Z(Ω)	F	Z(Ω)
DC	287	DC	287
10Hz	296	10Hz	296
33.5	390	41.8	394
43.5	429	51.4	428
78Hz	481 LF Res.	100Hz	481 LF Res.
132	429	146	428
180	390	187	394
1kHz	307	1kHz	310
1.8kHz	304	1.8kHz	302
20kHz	356	20kHz	360

Comparing the HD650 with the Grado RS-2 (both about \$450), the Grado had some upper midrange roughness, while the Sennheiser sounded exceptionally smooth and tonally neutral.

2. Output is short-circuit proof.

3. Power delivered to 300 Ω and 32 Ω phones is approximately equal (about 3dB higher with 32 Ω phones, but they tend to be less efficient).

But what about "damping factor"? Unlike speakers, whose bass resonance might show a 10 $\times$ impedance rise,

phones have a nearly constant, nearly resistive impedance. The Sennheiser HD 650 (see **Table 1**) has a resonance Z of 481 Ω (re 300 Ω nominal). With a 50 Ω amplifier output Z , the signal increase to the phones at their LF resonance is only 0.5dB. If this concerns you, you can delete R20. But then a clipping signal level into 32 Ω phones could deliver about 2W, blowing the phones and perhaps your ears!

POWER SUPPLY

To eliminate concerns about AC line pollution, I decided on an external "wall wart" DC supply. The unit specified in **Fig. 2** works perfectly and causes no audible hum, or other noise (**Photo 4**). The circuit comprising Q1, 2 derives a stable voltage that's very close to the midpoint of the incoming single-ended DC supply voltage.


Basically a push-pull Class AB buffer amp, the output (R5-R6 junction) serves as the circuit ground, to which is then referenced the desired bipolar (about $\pm 13V$) supply. You could add voltage regulators, but they are not necessary because the amplifier has a very high power supply rejection ratio (PSRR). Including regulators would lower the supply voltage, and therefore the amplifier's maximum output power.

INPUT CIRCUIT

The ALPS 100KAX2 100k Ω stereo volume control pot (**Fig. 1**) is, as of this writing, available at Radio Shack for about \$3. This is a bargain—buy all you can. Quality appears to be excellent, and they have a 10% tap which I used for switchable (low) loudness compensation. Of seven units, I measured attenuation tracking (L/R), from 0 to -40dB, to be between about $\pm 0.2dB$ and $\pm 1dB$ (this does not depend on full-R matching, but rather on matching of the ratios of wiper-to-ground R to the full R). I suggest purchasing a number of units and selecting for best attenuation tracking.


R2 and C1 filter HF interference, such as AM radio stations. C2, the only cap in the audio path, removes any source DC offset that would cause noisy attenuator operation. I used a 1.0 μF 100V metal poly cap from Digi-Key (EF1105), 10 for \$7.36. Or, you can spend whatever you like on the audiophile cap of your choice. R1 keeps C2 discharged with no

FIGURE 2: Power supply for HA-2 headphone amp.

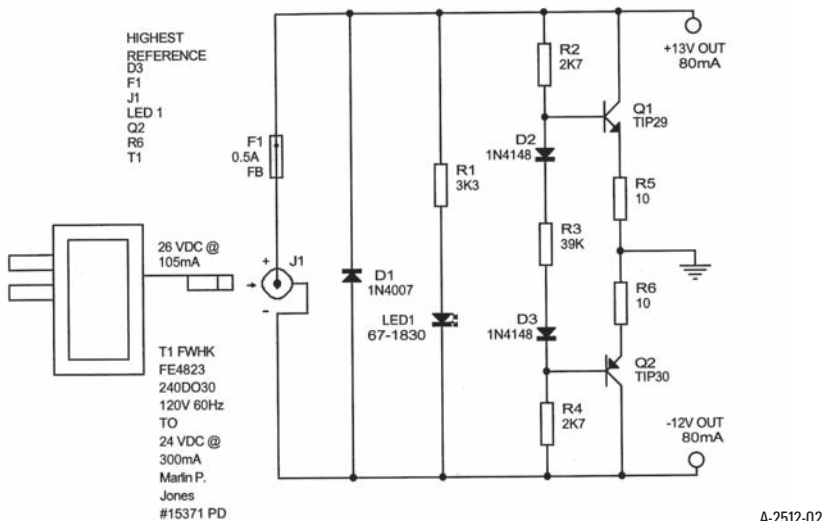

A-2512-02

FIGURE 3: Loudness compensation responses—attenuator setting = 0 to -25dB in 5dB steps.

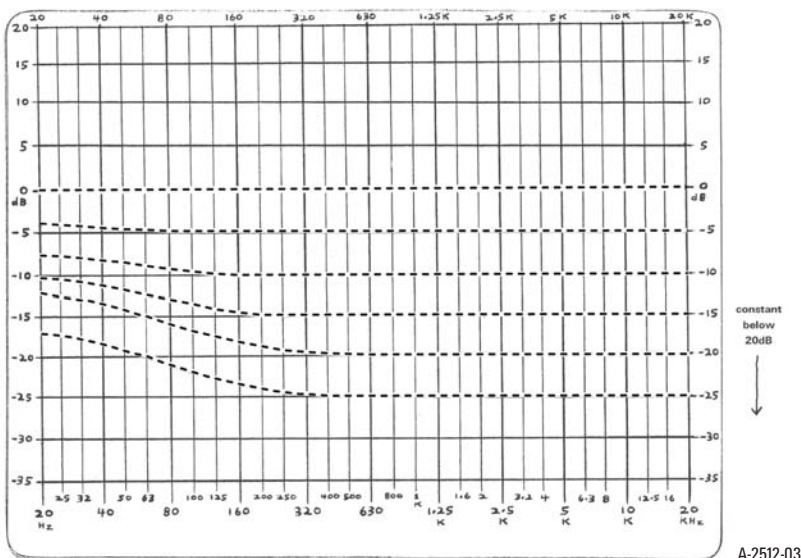

A-2512-03

input connected.

The gain (3.2W/300Ω phones) is such that at full volume (attenuation at 0dB), a 2.0V RMS input (Red Book CD 0dBFS = full scale) drives the amp to full power, producing 119dB SPL peaks, and about 107dB average music SPL—about that of a large orchestra playing full-blast—on the Sennheiser HD650 phones. But you can easily change the gain (with R6); the circuit maintains stability and adequate HF response over a gain range of at least 1 to 10.

LOUDNESS COMPENSATION

When S1 activates this, R3, R4, and C3 provide the LF boosts versus attenuation shown in **Fig. 3**. Maximum boost occurs at 20dB attenuation and then stays constant below that level. Down to about -30dB (re full volume), the boost nicely compensates the loss in LF hearing sensitivity (Fletcher-Munson contours) from ≥100dB SPL down to 70dB SPL, within about 2dB to 20Hz. The compensation is not adequate for much lower than 70dB SPL, but with good headphones why listen at lower volume?

Unlike many attempts at such compensation, that used here does not sound “boomy” or “muddy.” With a maximum boost of only 3dB at 100Hz, 7dB at 36Hz, and that only at and below -20dB volume, the compensation simply maintains natural bass fullness as the volume is decreased.

Note: If you use the ALPS 100k AX2 pot, you can use **Photo 2** as a calibrated dB template. These pots are very unit-to-unit consistent regarding attenuation versus rotation angle.

CONSTRUCTION

Don't do what I did—I (barely) stuffed everything into a 5 1/8" × 2 7/8" × 2 1/8" aluminum “Bud Box Clone” from Radio Shack (**Photo 5**). Fabricating a PC board, as opposed to the “rat's nest on balsa wood, lots of glue” construction I used, might save space, but I think the enclosure should be at least 6" × 3" × 3" in size*.

The DC supply input jack *must* be insulated from the metal enclosure. As **Photo 3** shows, I cut a 3/4" hole (with a Greenlee chassis punch—very precise and burr-free), then mounted over

How do *your* capacitors sound?

Doing a restoration, pooging, repair or upgrade? Fact: The quality of capacitors in the audio path or power supply affect the sound you hear more than any other component in the circuit.

What a great reason to use this most highly recommended *in-circuit* cap tester to check the capacitor's ability to pass dynamic signals by measuring the ESR (Equivalent Series resistance) with a guaranteed 100% accuracy* in 3 seconds.



CapAnalyzer 88A series II by EDS

Measures ESR from 0.1 to 20 ohms @ 120kHz
Color chart indicates good-fair-bad readings
One-handed tweezer test probe
Checks any cap from 0.47uF to 2200uF
Beeps one to five beeps for quality of cap ESR
Checks DCR to 500 ohms with *Set Alert*
Checks both through-hole or surface mount
Automatically and safely discharges cap first
Battery operated; optional AC adapter

Used and recommended by engineers and technicians from ABC, NBC, CBS, and by professional/commercial broadcast equipment technicians from JVC, Panasonic, and Sony, and government agencies including NASA and the CIA.

\$199

3-year warranty

Made in the USA

***60-day satisfaction or money-back guarantee**

Electronic Design Specialists www.eds-inc.com 561-487-6103

ATTENTION! ELECTRONICS TECHNICIANS



EARN YOUR B.S.E.E. DEGREE THROUGH HOME STUDY

Our Highly Effective Advanced-Placement Program for experienced Electronic Technicians grants credit for previous Schooling and Professional Experience, and can greatly reduce the time required to complete the program and reach graduation. No residence schooling required for qualified Electronic Technicians. Through our Special Program you can pull all of those loose ends of your electronics background together and earn your B.S.E.E. Degree. Upgrade your status and pay to the engineering level. Advance rapidly! Many finish in 12 months or less! Students and graduates in all 50 states and throughout the world! Established Over 50 Years! Write or call for free Descriptive Literature. (601) 371- 1351

COOK'S INSTITUTE OF ELECTRONICS ENGINEERING

 4251 Cypress Drive
Jackson, Mississippi 39212

PHOTO 2: Attenuator dB scale.



PHOTO 3: Insulated 24V DC jack.

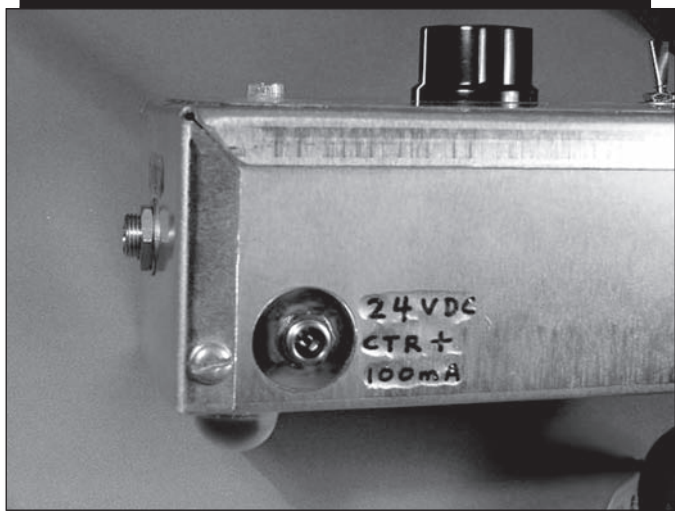


TABLE 2 HA-2 Headphone Amp Measurements.

Maximum Gain: 3.705 = 11.4dB, no load
3.176 = 10.0dB, 300Ω load
1.428 = 3.1dB, 32Ω load
At maximum gain, 0dBFS = 2.0V RMS (Red Book CD Full Scale Signal) drives amplifier to full output.
Maximum Output: 6.41V RMS = 137mW, 300Ω load
2.64V RMS = 218mW, 32Ω load
Maximum SPL with Sennheiser HD 650 phones = 119dB
Frequency Response: -3dB, 3.3Hz-230kHz
Half-Power Bandwidth: 360kHz, Slew Rate = 13.6V/μS (300Ω load)
Input Impedance: 27kΩ Output Impedance: 51Ω
Equivalent Input Noise: 31nV/√Hz density, flat spectrum (white)
(maximum with 4.38μV RMS unweighted, 20Hz-20kHz attenuator at -6dB;
3.42μV RMS "A" weighted, 20Hz-20kHz noise is 2.6dB lower with
attenuation at 0dB)
"A" weighted signal to noise ratio: 115dB re full output
Noise Level with Sennheiser HD650 phones: 4dB SPL (maximum with attenuation at
-6dB); 1dB SPL with attenuation at 0dB
Crosstalk: -66dB at 20kHz, -92dB at 1kHz (attenuation at 0dB, inputs term. in ≤1kΩ)
Output DC Offset: +2.1mV (left), +19.7mV (right), 300Ω load +0.9mV (left), +8.9mV
(right), 32Ω load
Loudness Compensation (switchable): Maximum at attenuator = -20dB; constant
below -20dB; +3dB at 100Hz, +7dB at 36Hz (close to equal-loudness contours for
80dB SPL re ≥100dB SPL)

the hole a piece of thick plastic, on which the DC jack was mounted.

I didn't use any shielded cables for the audio input paths, hence the 20kHz crosstalk of -66dB (not that anyone would notice it). But coax cable input connections would certainly improve 20kHz crosstalk, if only for the sake of impressive numbers.

Regarding **Photo 5**, I didn't use the transistor types specified in

the schematics; I used OHS (on-hand stock) types, similar enough to those specified. The circuit is very insensitive to transistor parameters (I've verified this by trying very different transistors; no noticeable degradation).


ADDING A SECOND PAIR OF OUTPUTS

You can connect a second 50Ω resistor to the R17/R18/R20 junction to drive a second output. If driving two pairs of 300Ω phones, the output stage Q3-Q4 will go into Class AB above about half the full voltage output. I've found that such Class AB loading appears clean (no visible crossover distortion nor obvious sonic anomalies). But you can achieve full Class A operation with two pairs of 300Ω phones by increasing the bias to 60mA (change R13, R14 to 560Ω). Small heatsinks on Q3, Q4 may or may not be needed; if Q3, Q4 are not too hot

PHOTO 4: 24V DC wall supply.



PHOTO 5: Balsa wood and glue construction.

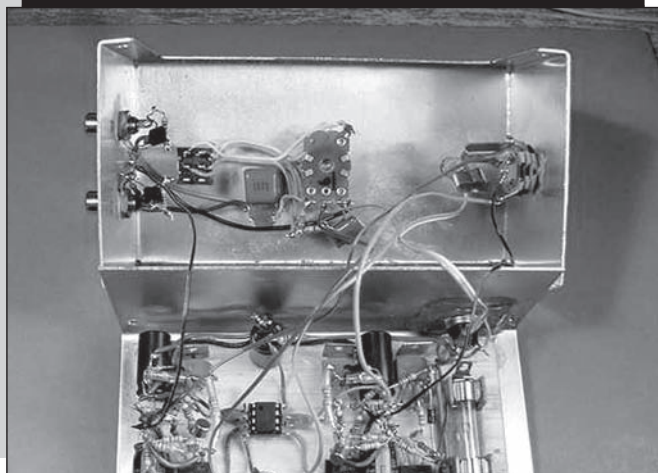



SENNHEISER HD 650 PHONES

Is \$450 expensive for headphones? Well, to quote the Chuck Mangione song title, "Compared To What?" Most audiophiles wouldn't blink at spending \$450 for a good pair of speakers, especially if they were almost ruler flat from 20Hz to 20kHz, could produce 120dB SPL, and reproduced clean 16Hz at 100dB SPL. Not on this planet for \$450!

But these headphones do all of the above, plus they have razor-sharp, time-adjusted, pristine transient response (not to mention the obvious freedom from room acoustics). Tonal reproduction is effortlessly and extremely natural. "Coloration" doesn't appear to be in these phones' vocabulary.

As wonderful as this is, there's something beyond, difficult to describe, when these phones are driven by a highly transparent, sonically noiseless amplifier, fed directly from a player, particularly an SACD or DVD-A unit: You will be repeatedly startled into instinctively looking around as you hear quiet but clearly-revealed background noises, such as the conductor's footsteps, musicians' motions, distant glasses clinking, and everyone breathing. Every subtle sonic nuance produced by the instruments is revealed with crystal clarity. If an unexpected, well-recorded xylophone is played, for example, you'll swear the resonating metal is right in front of you—downright spooky. ■

AUDIO TRANSFORMERS

AMERICA'S PREMIER COIL WINDER

Engineering • Rewinding • Prototypes

McINTOSH - MARANTZ - HARMAN-KARDON
WESTERN ELECTRIC - TRIAD - ACROSOUND
FISHER - CHICAGO - STANCOR - DYNACO
LANGEVIN - PEERLESS - FENDER - MARSHALL
ELECTROSTATIC SPEAKER TRANSFORMERS

Williamson Amplifier Transformer Specialist

WE DESIGN AND BUILD TRANSFORMERS
FOR ANY POWER AMPLIFIER TUBE

PHONE: [414] 774-6625 FAX: [414] 774-4425

AUDIO TRANSFORMERS

185 NORTH 85th STREET

WAUWATOSA, WI 53226-4601

E-mail: AUTRAN@AOL.com

NO CATALOG

CUSTOM WORK

NEW Products
NEW Technologies
NEW Suppliers



NEW CATALOG
EVERY 90 DAYS

Delivering the latest with the greatest.

SEMICONDUCTORS | PASSIVES | INTERCONNECTS | POWER | ELECTROMECHANICAL | TEST, TOOLS & SUPPLIES



New Products
New Technologies
New Suppliers
New Catalog Every 90 Days!



a tti company

(800) 346-6873

www.mouser.com

Mouser and Mouser Electronics are trademarks of Mouser Electronics, Inc.

FIGURE 4: Square-wave responses; phones = Sennheiser HD650 (300Ω); SPL = 109dB.

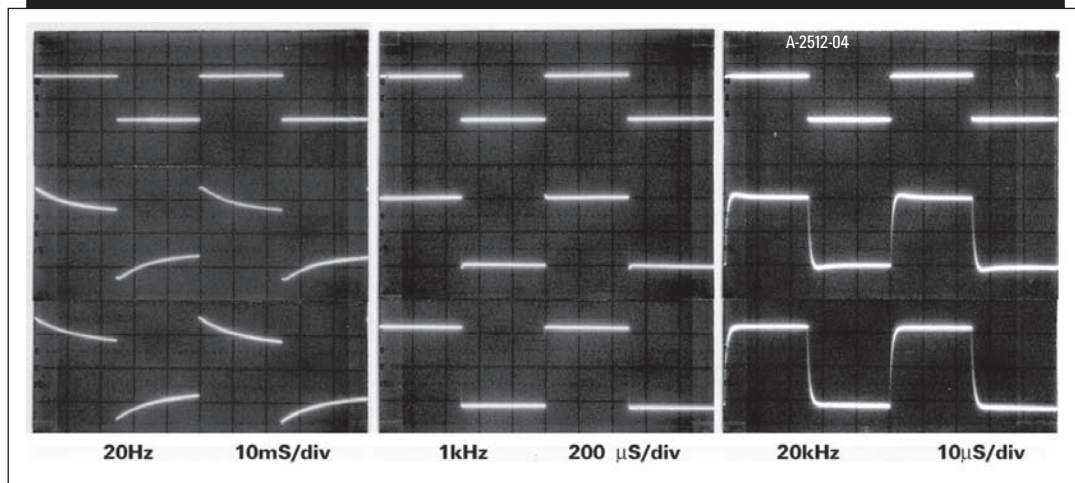


Figure 4 shows square-wave responses (20Hz, 1kHz, 20kHz) while driving the HD650 phones to 109dB SPL, and also with no load. The 20Hz exponential decay, and the 20kHz exponential rise time, reflect the -3dB bandwidth of 3.3Hz to 230kHz.

SONIC TRANSPARENCY

I compared various SACDs (1) with the HD650 phones direct-

to touch, they'll be fine.

The amp (with the pair of 50Ω output resistors) can drive two pairs of 32Ω phones, but since it's not recommended to increase Q3, Q4 bias above 120mA (the level for full Class A driving one pair of 32Ω phones), operation about half the full voltage output will be Class AB. But the 120mA bias is more than enough to ensure the absence of crossover dis-

tortion; the sound will still be very clean.

ELECTRICAL PERFORMANCE

Table 2 summarizes the measurements. I don't have a distortion analyzer, but THD up to just below clipping is probably no more than the 0.004% typical of the TL082 (that figure is with its output stage Class AB loaded; here everything is Class A).

ly connected to the player output (the 300Ω phone impedance and high sensitivity allow that) and (2) with the headphone amp inserted into the path (loudness compensation off, volume control set to match the direct connection). I heard no difference. Some might prefer a headphone amp that imparts a pleasing (euphonic) "sound"—warm, "romantic," and so on—but this unit

NOW YOU CAN BECOME A SPEAKER BUILDER


with Speaker Building 201 by Ray Alden

Whether you're a beginner eager to get into speaker building, an intermediate builder who wants to improve his skills, or a speaker building fanatic who's looking for projects to build, author Ray Alden has written this book for you!

You don't need an elaborate workshop, expensive analytical equipment, or sophisticated software. Alden walks you through the steps to design and construct a first-rate system—one that surpasses higher-cost commercial products.

Features 11 proven projects to build, many of which have been tested by loudspeaker expert, Joseph D'Appolito.

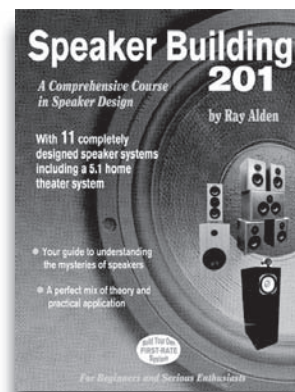2004, 8½ × 11, softbound, ISBN 1-882580-45-1. Shipping weight: 2 lbs. **BKAA66 — \$34.95**



■ To order call 1-888-924-9465 or order on-line at www.audioXpress.com ■

*"This is the book I've been waiting for all my life.... In the future, when I'm asked to recommend a book to someone who wants to 'learn about speaker design,' I'll be recommending Ray Alden's **Speaker Building 201**. It's an outstanding achievement."* — Jutta Dziwnik, *Australian Hi-Fi Magazine*, June/July 2005



Old Colony Sound Laboratory
PO Box 876, Peterborough, NH 03458-0876 USA
Toll-free: 888-924-9465 Phone: 603-924-9464 Fax: 603-924-9467
E-mail: custserv@audioXpress.com • www.audioXpress.com

Headphone Amp Parts List

Total Qty.	Schematic Ref Amp	Supply	Description	Source
1	A1		Dual opamp, TL082CP	
2	C4		Cap, 22pF	
2	C1		Cap, 100pF	
2	C3		Cap, 0.33μF 100V poly	Digi-Key EF1334
2	C2		Cap, 1.0μF 100V ply	Digi-Key EF1105
8	C5, 6, 7, 8		Cap, 1000μF 16V	
10	D1, 2, 3, 4	D2, 3	Diode, 1N4148	
1		D1	Diode, 1N4007	
1		F1	Fuse, 0.5A	
1			Fuse Holder	
2	J1, 2		Jack, RCA	Digi-Key SC1094
1	J3		Jack, 1/4" stereo	Digi-Key SC1048
1		J1	Jack for T1 (DC IN)	Digi-Key 67-1830
1		LED1	LED, Violet	ALPS 100K AX2
1	P1		POT, 100k stereo	Radio Shack 271-1732
2	Q1		PNP, 2N3906	Digi-Key 2N3906RLRAOSCT
2	Q2		NPN, 2N3904	Digi-Key 2N3904RLRAOSCT
3	Q3	Q1	NPN, TIP29	Digi-Key TIP29BOS
3	Q4	Q2	PNP, TIP30	Digi-Key TIP30COS
2	R20		RES, 1/4W, 1% 49.9Ω	
2	R6		RES, 1/4W, 1% 10.0k	
2	R8		RES, 1/4W, 1% 27.4k	
2		R5, 6	RES, 1/4W, 5% 10Ω	
8	R16, 17, 18, 19		RES, 1/4W, 5% 15Ω	
1		R3	RES, 1/4W, 5% 39Ω	
4	R5, 7		RES, 1/4W, 5% 82Ω	
4	R13, 14		RES, 1/4W, 5% 270Ω	
8	R9, 11, 12, 15		RES, 1/4W, 5% 330Ω	
2	R2		RES, 1/4W, 5% 1k	
2		R2, 4	RES, 1/4W, 5% 2.7k	
1		R1	RES, 1/4W, 5% 3.3k	
2	R4		RES, 1/4W, 5% 3.9k	
2	R10		RES, 1/4W, 5% 12k	
2	R3		RES, 1/4W, 5% 33k	
2	R1		RES, 1/4W, 5% 1M	
1	S1		Switch, DPDT	Digi-Key 360-1156
1		T1	"Wall Wart" 24V DC 300mA Alternate T1 →	Marlin P. Jones 15371PD
1			Suggested Enclosure Hammond 1590E (7.4" × 4.7" × 3.1")	Digi-Key T520-P6P Digi-Key HM155

isn't one of them. If the recording has *natural* warmth, you'll hear it clearly (with good headphones). *aX*

* The Hammond 1590 E aluminum enclosure, 7.4" × 4.7" × 3.1", Digi-Key HM155, is a good choice.


VACUUM STATE




Tube Preamp & DIY Cables books



MC & MM Phono Stage kit

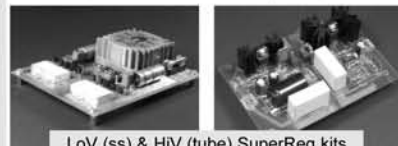

LoV (ss) & HiV (tube) SuperReg kits

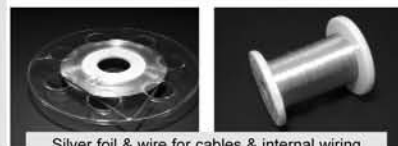

Silver foil & wire for cables & internal wiring

Full info on these kits & DIY essentials:

www.vacuumstate.com

Vacuum State GmbH
Büfingerstr. 5 8203 Schaffhausen
Switzerland Ph + 41 52 620 35 81
Questions? aw@vacuumstate.com

VTV AUDIO VIDEO MUSIC EXPO



Pasadena Embassy Suites
211 Huntington Dr. , Arcadia, CA
November 19-20, 2005
10AM TO 6 PM

Celebrating 75 Years of High Fidelity Sound in Motion Pictures

Modern & Vintage Hi-Fi, Home Theater, Speakers, Musical Instrument Amps

Rare Guitars, Records, CDs, Parts, Vintage Books, NOS Tubes.

John Atwood's **Tube School-Practical Tube Audio 8 Hour Class**

\$10 Admission - Open to the General Public

Very Reasonable Rate Vendor Space Still Available

Sponsored by: **Vacuum Tube Valley Magazine**

Contact: Charlie Kittleson PH:(707) 349-3009 FAX: (707) 263-7648

triode@vacuumtube.com www.vacuumtube.com

