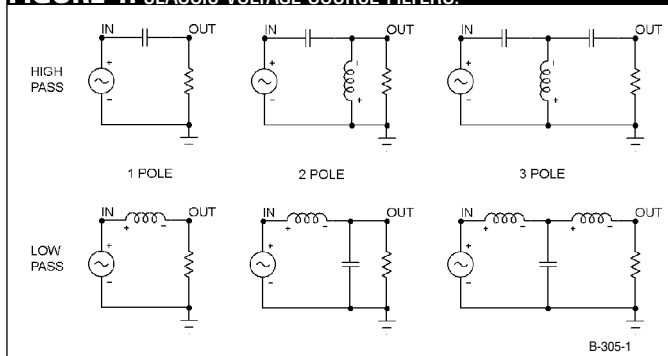


speakers

Current Source Crossover Filters

By Nelson Pass

Tips from a pro about designing filter networks—
for both voltage and current sources.

FIGURE 1: CLASSIC VOLTAGE SOURCE FILTERS.

In today's marketplace, audio power amplifiers are conventionally viewed as voltage sources, delivering a given voltage at the output that is a multiple of an input voltage. To the extent that they are truly voltage sources, having a very low output impedance, they simply deliver whatever current happens to reflect the response of the loudspeaker to the defined output voltage.

I have recently been playing with current source power amplifiers that have high output impedances and deliver a specific current to the load in response to an input voltage. The voltage across the loudspeaker reflects its response to this defined current. You could say that we have swapped the words voltage and current.

In a previous article, "Current Source Amps and Sensitive/Full-Range Drivers" (aX 10/04), I discussed some advantages of these amplifiers for Lowther, Fostex,

and these drivers typically appreciated a finite source impedance and often benefit from some equalization in the upper midrange and high frequencies.

With a voltage source, amplifier equalization is usually applied by a network in series with the driver. With a current source it is usually applied by elements placed in parallel, leaving the driver directly connected to the output terminals of the amplifier.

Of course, we don't want to limit ourselves strictly to one-driver loudspeaker systems (attractive as they may be), so we need to consider a means of filtering the signal to divide it between the drivers. We certainly can make life easy by using an electronic crossover network that does the filtering before multiple amplifiers. This way each driver gets an amplifier to itself. This has real performance advantages, but is generally more complex and expensive than a passive crossover between the amplifier and speaker.


VOLTAGE SOURCE NETWORKS

The classic crossover networks of Fig. 1 work very well if you have a voltage

source. Here you see both high-pass (tweeter) and low-pass (woofer) filters with a resistor representing the loudspeaker. Of course, a real loudspeaker is not exactly a resistor, but I don't want to get confusing here. A low-pass network gradually attenuates the high frequencies as the frequency goes higher than a particular transition point called the crossover frequency. Similarly, a high-pass network gradually rolls off the frequencies lower than the crossover frequency. The shapes of both types of filters can be characterized by numbers in addition to the crossover frequency, but here we will limit ourselves to discussing just the slope.

The examples of Fig. 1 show three different filters for both the high-pass and the low-pass filters. The first is a one-pole filter, corresponding to a rolloff slope of 6dB/octave. The second is a two-pole filter, which rolls off at 12dB/octave. The third is a three-pole filter, which rolls off at 18dB/octave.

There are, of course, filters with even more poles, and the exact shape of these filter curves can vary from sharply peaked at the "knee" of the crossover frequency to very gentle transitions. They all have different phase characteristics as well. There is no such thing as an ideal crossover network for all loud-

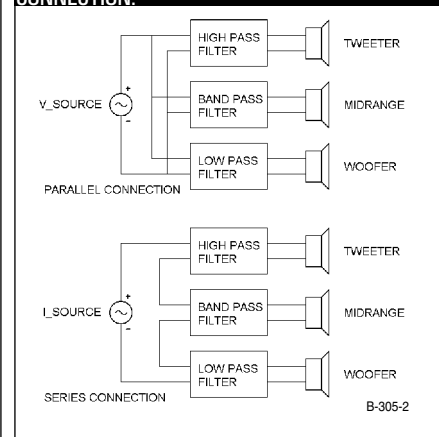FIGURE 2: PARALLEL AND SERIES FILTER CONNECTION.**ABOUT THE AUTHOR**

Nelson Pass, the proprietor of Pass Laboratories and a frequent collaborator to *audioXpress*, enjoys creating trouble.

speaker drivers, and considerable differences of opinion exist as to the best network for any given set of drivers.

CAUTIONARY COMMENTS

Everything you read here should be taken as approximate examples to help you arrive at your own filter types and values. It is rare for a textbook filter example to be the best in any particular real-life case. The best-sounding crossover networks—whether active or passive—are usually the result of painstaking experimentation, measurement, and listening. Remember also that the typical loudspeaker driver only approximates a resistor as a load, and additionally has an acoustic output to be considered, which is not very flat or phase perfect.

The decisions about what frequency or slope are your own, and you can mix and match them as you please. Occasionally you must consider protecting a tweeter or midrange from too much power at lower frequencies, but after that you can play as you like.

INSIDE OUT

When you switch from designing filter networks for voltage sources to networks with current sources, you will find that everything is suddenly turned

inside out. Capacitors become inductors and vice versa, and “T” networks become “pi” networks and vice versa. Multiple filters that used to be placed in parallel off the amplifier’s output terminals are now strung in series. Don’t worry, we’ll get you straightened out.

Figure 2 shows part of this difference. At the top is a voltage source amplifier driving three filters and speakers in parallel to divide the audio for a woofer, midrange, and tweeter. They all share the same voltage and the same ground. At the bottom is a current source amplifier where the filters and speakers are wired in series. They all share the same amount of current.

This is a key item—that just as voltage source filters can assume a given equal input voltage, current source filters can assume equal input current. In this way, both types of filters can be designed independently so that the characteristic of one filter does not alter the characteristic of another. You can’t say the same thing about voltage source filters strung in series or current source filters run in parallel—in those cases, the specifics of each filter will influence the others, as we will see in some band-pass filter examples later.

Consider some filter examples, which have been constructed for matching –3dB points at the crossover frequency, so that they present a nearly constant impedance to the source. Having a constant total impedance allows use with voltage sources equally well. Keep in mind that with a voltage source driving networks in series, when you adjust one filter, you affect the response of the others. With a current source, the response of other filters in series is not affected.

SINGLE-POLE TWO-WAY FILTER

Figure 3A shows a simple current source crossover where the woofer and tweeter are each crossed over at 1kHz and at a slope of 6dB/octave. The values of the inductor L and capacitor C are determined by the formulas:

$$L = R1 / (6.28 * F) \quad \text{and} \quad C = 1 / (6.28 * R2 * F)$$

L is the inductance in henries, R is the load resistance in ohms, C is the capacitance in farads, F is the transition frequency in hertz. By the way, the “T” and “W” in Fig. 3A indicate tweeter and woofer. When you see an “M” later, it will mean midrange.

Figure 3B shows the resulting response of this, the simplest filter we will see. As will be the case of all curves, the vertical axis is in decibels (dB) and the horizontal axis is frequency.

SINGLE-POLE THREE-WAY FILTER

You can produce a one-pole three-way filter easily by simply adding an additional filter in the middle for the midrange driver (Fig. 4A). The formulas

FIGURE 3A: ONE-POLE TWO-WAY FILTER.

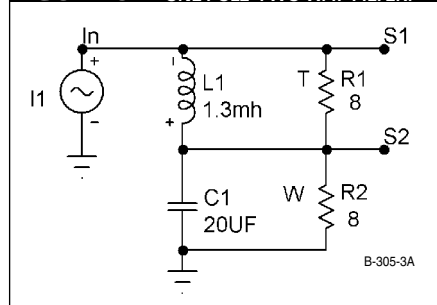


FIGURE 3B: ONE-POLE TWO-WAY FILTER RESPONSE.

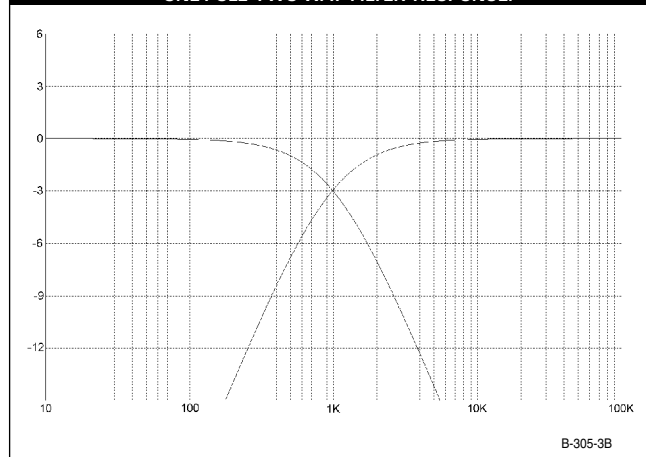


FIGURE 4A: ONE-POLE THREE-WAY FILTER.

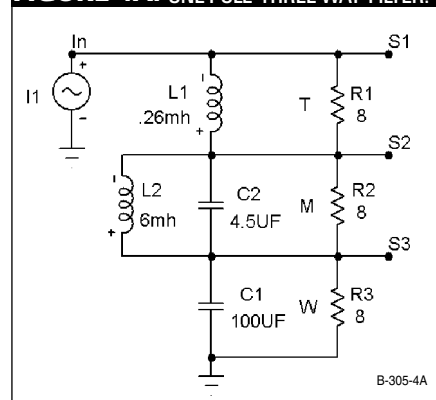


FIGURE 4B: ONE-POLE THREE-WAY RESPONSE.

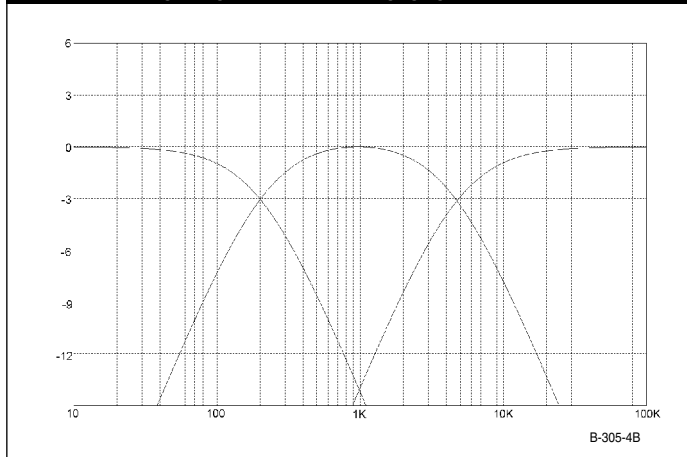
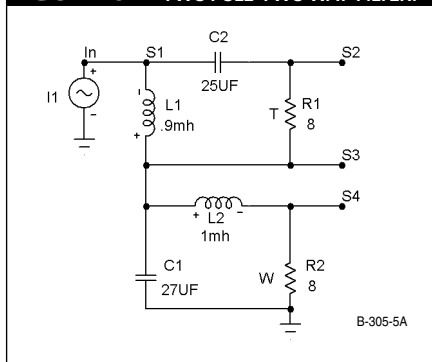
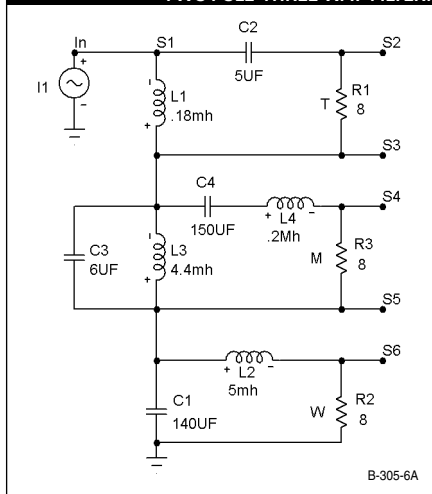
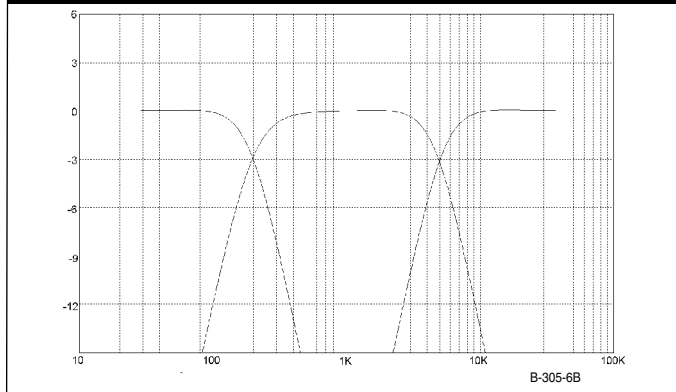
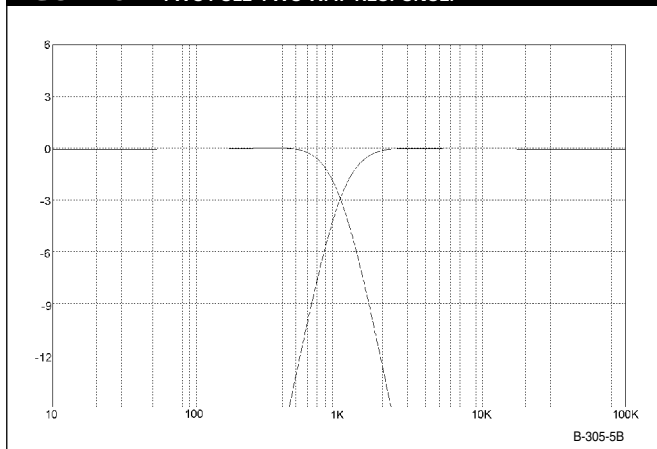


FIGURE 5A: TWO-POLE TWO-WAY FILTER.

applying to the previous example will work perfectly for the woofer and tweeter, but the midrange filters L2 and C2 will be off slightly, depending on the proximity of the two crossover points, which in this case are 200Hz and 5kHz. Here the coil needs to be about 10% lower than suggested by the calculation, and the capacitance needs to be about 10% higher. This is due to the loading influence of each of these elements on the other, and the variation increases as the crossover frequencies get closer.

You can calculate this if you're mathematically gifted, run a computer pro-

FIGURE 6A: TWO-POLE THREE-WAY FILTER.**FIGURE 6B: TWO-POLE THREE-WAY RESPONSE.****FIGURE 5B: TWO-POLE TWO-WAY RESPONSE.**

gram if you can follow instructions, or try wiring in different values if you're good with your hands. All three approaches are likely to end up with the "wiring in different values" when it comes time to evaluate the results. In this case the results are in Fig. 4B.

TWO-POLE TWO-WAY FILTER



In Fig. 5A we add another pole to each filter in the form of C2 on the high pass and L2 on the low pass, and we get the curves of Fig. 5B. The formulas have changed a bit, but you can scale from the examples. Remember that the high and low pass are independently adjustable. As you vary the frequency and resistance of the load, use the following rules:

- All examples of C are inversely proportional to the variation in frequency and load impedance.
- If you double the value of R, then you will halve the value of C.
- If you double the value of the frequency, you will halve the value of C.
- If you double the

TWO-POLE THREE-WAY FILTER

As with the one-pole three-way filter, we simply sandwich in a midrange filter in series with the high-pass and low-pass systems. The rules for the L and C values are the same as the two-pole two-way example, and of course don't work as well for the midrange depending on the proximity of the two crossover frequencies. Like I said before, you can calculate it out exactly, but you'll still end up fooling around with it when you actually adjust the speaker, so don't become too excited.

Figures 6A and 6B show the circuit and the resulting curves. As in all the

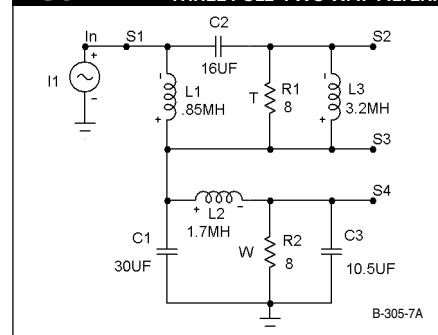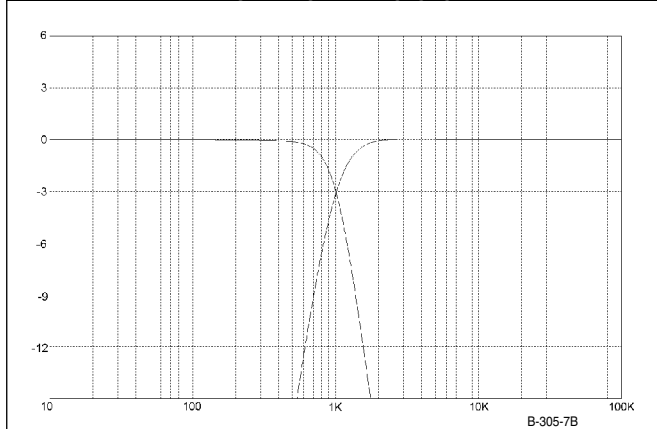FIGURE 7A: THREE-POLE TWO-WAY FILTER.**FIGURE 7B: THREE-POLE TWO-WAY RESPONSE.**

resistance and the frequency of both, you will quarter the value of C.

• All examples of L are inversely proportional to the variation in frequency, as with C, but they are proportional to the resistance.

• If you double the value of R, then you double L also.

other examples, the values of L and C scale with load resistance and frequency. Again, L is proportional to R and inversely proportional to F. C is inversely proportional to R and F.

THREE-POLE TWO-WAY FILTER

Now we're starting to get into some complicated stuff (Figs. 7A and 7B). All the rules of the preceding examples apply, such as they are. For scaling, L is proportional to R and inversely proportional to F. C is inversely proportional to R and F.

This is a good time to note that there is no rule that says you must pick the same frequencies and slopes for adjacent elements. More often than not, I use single-pole slopes for midranges, one or two poles for tweeters, and two or three poles for woofers. Also more often than not, I set the high- and low-pass portions at different frequencies. It's strictly a matter of what works best, and that is usually not exactly the textbook version.

THREE-POLE THREE-WAY FILTER

This is the most complex example we will look at. The high-pass (tweeter) por-

tion and the low-pass (woofer) portion are L C and R scalable as previously, and as long as the midrange filter frequencies are at a ratio of 5000Hz / 200Hz (25 to 1), then you can scale it as well. If they're not at that ratio and you really want those slopes, be prepared for some work.

Figures 8A and 8B show the result of my labors in this regard.

CONCLUSION

The concept of filter networks in series is not new, but it is not that popular because with a voltage source, anytime you adjust one filter you affect the response of the others. With a voltage source amplifier this is avoided by placing the filter systems in parallel, so that they all share the same input voltage independently of each other.

With a current source amplifier, you can use filters in series easily because they all share the same current, and adjusting the filter values in one network does not alter the response of the other filters. You can run networks in parallel off a current source, just as you can series filters with a voltage source.

As pointed out previously, the filter examples I have given have a fairly constant aggregate impedance, so you can use them as is equally well with a voltage source, however, the moment you adjust one of the filters, you'll find yourself re-adjusting the others.

Current source amplifiers aren't for everybody, although the great Malcolm Hawksford might effectively argue the case. I have certainly found that they have real charm with high-efficiency full-range loudspeakers as I have detailed elsewhere. Of course, the definition of "full-range" varies, and there are quite a

few cases where users—myself included—have attached a subwoofer and/or a tweeter to extend this range. If you do, you have the choice of using active electronic crossovers or passively filtering these pieces into the system.

I have successfully driven Lowthers, Fostexes, and their cousins with current source amplifiers while applying a passive single-pole low-pass filter to them. From there I can easily bring in a tweeter (such as the TAD PT-R9 ribbon) with a passive two-pole filter, usually at 10kHz and above. Generally it's been my experience that a big subwoofer such as El Pipe-O (May '03 aX) prefers a voltage source for high damping, so I have used an active filter to divide it from the full-range speaker in the range below 100Hz.

The more general category of limited-bandwidth high-efficiency drivers can benefit from current source amplification as well, particularly examples of high-efficiency woofers coupled with horn-loaded compression drivers. This article was an outgrowth of that investigation, which is still progressing.

In any case, we have seen that constructing crossover filters for current source amplifiers is not particularly difficult, or at least not more difficult than for voltage amplifiers. For that matter, we shall soon see that constructing a current source amplifier is not more difficult than a voltage source.

Copyright 2004 Nelson Pass.

aX

FIGURE 8A: THREE-POLE THREE-WAY FILTER.


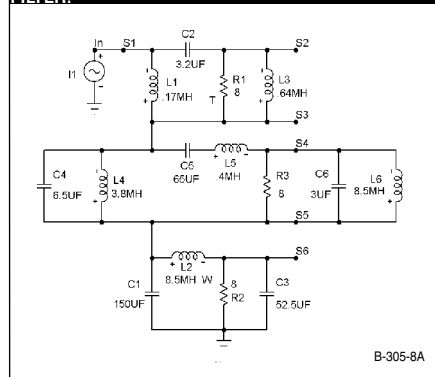


FIGURE 8B: THREE-POLE THREE-WAY RESPONSE.

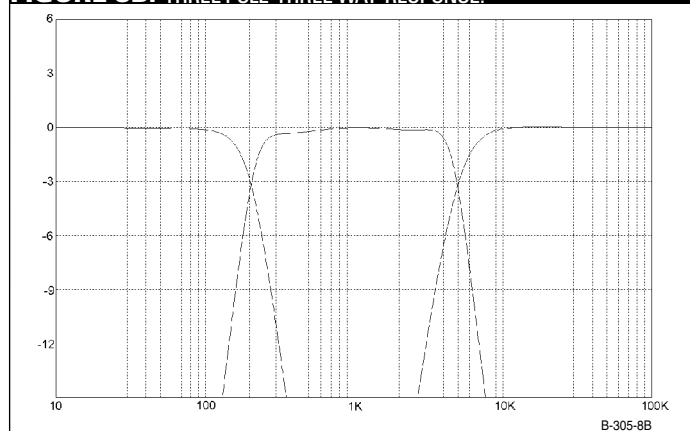

PASS DIY

Printed Circuit Boards

Key Components

Plans

Zen Variations

Pearl Phono

and more...

PO Box 12878
Reno, NV 89510

www.passdiy.com