

solid state

A Hybrid Tube/MOSFET Headphone Amplifier

By Erno Borbely

This noted audio expert makes his popular hybrid amp design available for headphone use.

In the 1/98 issue of *Glass Audio*, I wrote about a hybrid tube/MOSFET line amp, which, because of its musical sound, became a very popular amplifier ("Low-Voltage Tube/MOSFET Line Amp," which also appears on www.borbelyaudio.com under Special Articles). DIY amateurs wished to use it in many different applications, such as CD buffer, I/V converter, power amplifier, and headphone amplifier. It worked very well in all line-level applications, but the second stage was not laid out for high-current operation, so driving headphones was not possible. I have therefore redesigned the circuit to allow high-current operation.

The result is the EB-804/421, a single-ended (SE) pure Class-A amplifier, capable of driving headphones between 32 and 600Ω. The amplifiers need ± 15 to ± 24 V regulated supplies at 160/100mA and 6.3V DC at 300mA for the tube heater. I recommend feeding the amps from

separate supplies. The PCB for one amp is 90 × 80mm.

CIRCUIT DESCRIPTION


The schematic is shown in Fig. 1. The topology is the same as the hybrid tube/MOSFET line amp. Q1 is a double triode that operates as a differential amplifier, with approximately 2mA in each of the triodes. A constant-current diode D1, which supplies the source current to the differential amp, includes two J508 or E-202 diodes in parallel. You can also use a single J511, which delivers 4.7mA.

The two anodes, which produce out-of-phase signals, are converted to a single-ended signal using a current mirror composed of Q2, D2, and resistors R3/R4. Q3, a P-channel MOSFET in TO-220 package, is used in common-source mode as a Class-A single-ended second stage. I replaced its drain resistor with a second constant-current source, sup-

plying the Class-A current of 100 or 160mA.

The constant-current source, which increases the gain and improves the linearity of the second stage, is made up of Q4, an N-channel MOSFET in TO-220 package, and its associated components. I used the Hitachi 2SJ79 and

PHOTO 1: EB-804/421 PC BOARD.

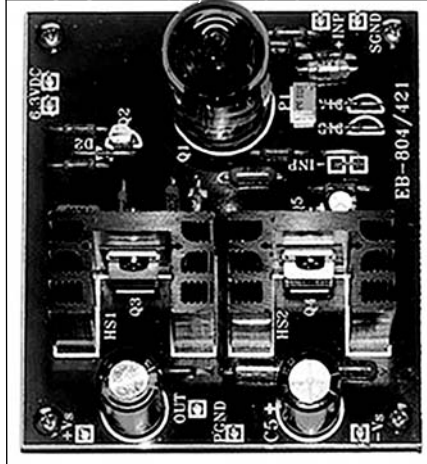

2SK216 for Q3 and Q4, respectively. You can also use the Toshiba 2SJ313 and 2SK2013, but note that the pinout is different from the Hitachi (GDS versus GSD).

The amplifier can work with a ± 15 V to ± 24 V supply. The maximum dissipation allowed for Q3 and Q4 is 2.4W each, so the supply voltage determines the maximum current. At ± 24 V the current is 100mA and at ± 15 V it is 160mA. Resistor R13 sets the current: it is 6R8 for 100mA and 3R9 for 160mA.


You must heatsink Q3 and Q4. I am using the SK76-37.5 with 8K/W thermal resistance. The temperature on the heatsinks is about 55° C, so proper ventilation is absolutely necessary! The PS/regulator I recommend for the hybrid tube/MOSFET headphone amplifier is the EB-802/243.

The input tube requires a 6.3V/350mA heater supply. Use a well-regulated/low-ripple supply for this (EB-793/204 is recommended). I recommend that you ground the negative side of the heater supply to the PGND on the PCB.

LINEARITY NOTES

The input tube dominates the overall distortion characteristics of the amplifier. Tubes of different manufactur-

FIGURE 1: EB-804/421 SE CLASS-A HEADPHONE AMPLIFIER.

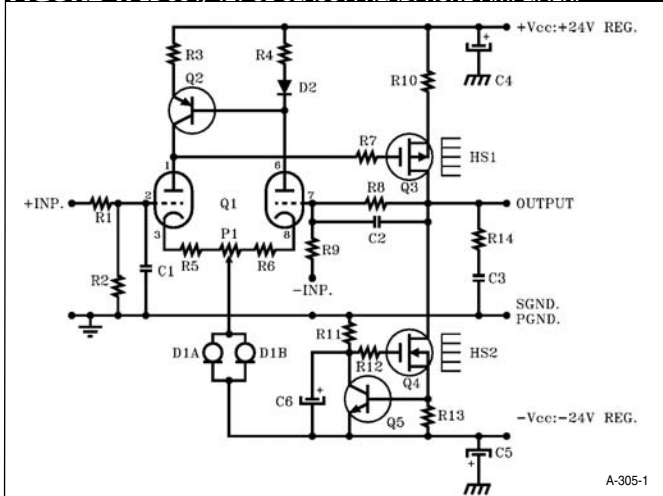


output stabilize to 0V. Alternatively, you can leave the heater on all the time or in a stand-by mode with—say—4V, in which case you can apply the full heater voltage and the supply voltage

simultaneously.

The feedback resistors R8 and R9 set the closed loop (CL) gain of the amp. Normal gain is 10×, or 20dB. Changing R9 can change this gain. CL output

FIGURE 2: STUFFING GUIDE FOR THE HYBRID TUBE/MOSFET HEADPHONE AMP (90 × 80MM).

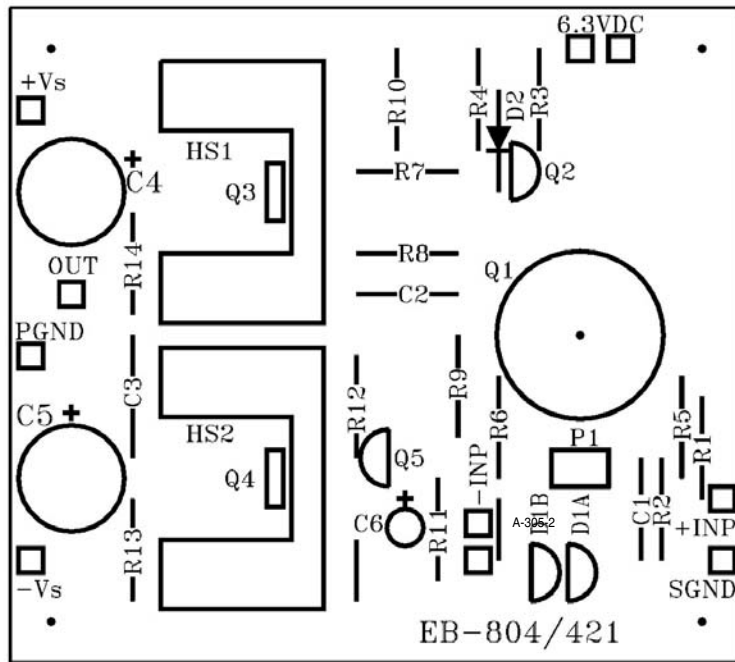

impedance is 15Ω. Equivalent input noise depends on the tube used and is 1.2–1.5μV!

The maximum output power into different loads depends on the supply voltage and the available current from Q4. With ±24V and 100mA in the second stage, the amp delivers >100mW into 32Ω and >250mW into 600Ω at 1% THD. With ±15V and 160mA the power into 32Ω increases to 300mW at 1% THD.

The maximum power is limited by the available current at low load impedances and by the available voltage swing at high impedances. If your headphones are low impedance, you should operate the amplifier at ±15V with 160mA in the second stage, and if they are high impedance, use a ±24V supply with 100mA. Since high impedance headphones require less power than the low impedance ones, the ±15V operation will probably give more than enough power for ear-shattering SPL over the whole impedance range.

ASSEMBLY

Figure 2 shows the stuffing guide for the hybrid tube/MOSFET headphone amplifier. Start the assembly by installing the solder pins, jumpers, and then

taking into consideration the rest of the electronics.

And this is not the end of the story. The Walkman-type devices are usually operating with two 1.5V batteries, for a supply of 3V total. Assuming that the audio amp would be able to work “rail-to-rail,” the equivalent audio signal would be $3/2.82 = 1.06V$ RMS, and you could generate a maximum current of:

$$I = 1.06/40\Omega = 26.5mA$$

This would give a maximum power of:

$$P = U \times I = 1.06V \times 26.5mA = 28.1mW$$

And SPL difference would be:

$$SPL_{diff.} = 10 \log 28.1 = 14.5dB$$

And the maximum SPL: 100dB + 14.5dB = 114.5dB, which is actually “only” 10dB less than the maximum. However, remember that in most cases the audio signal would be less than the one calculated, or the amp would already be clipping at a lower value. In a 32Ω headphone with 100dB SPL for 1mW input, the maximum power would be 35mW and the maximum SPL would be 115dB!

Real-life ICs, made specifically for low-voltage operation, will usually deliver less than this. Look up the National LM4911, which is a stereo headphone amp—it delivers 25mW into 32Ω at 1% THD from a 3V battery (12mW from 2.4V). This means that just a bit over 80% of the battery voltage is “converted” into audio! I bet most of the Walkman-type devices don’t deliver much more than 10–15mW of “clean” audio!

What would happen if you connected a 600Ω headphone to this amp? The maximum current would be: $1.06/600 = 1.77mA$, the maximum power: $1.06V \times 1.77mA = 1.88mW$. The SPL difference is:

$$10 \log 1.88 = 2.74dB \text{ and the maximum SPL is } 98dB + 2.74dB = 100.74dB.$$

Obviously, 600Ω headphones are less suited for this kind of application. For amps with low supply voltage, you need to use low-impedance headphones, assuming, of course, that the amp can deliver the necessary current.

Headphone amps operating from ±9V batteries fare much better in terms of maximum power. Assuming an 80% ratio between battery voltage and audio signal, such an amp could deliver over 600mW into a 40Ω headphone. Of course, the battery would also need to deliver the necessary current (over 120mA!), and the question is how long it would be able to do that? The same amp would manage only about 40mW into a 600Ω headphone, so even an amp working with ±9V power supply cannot cover the whole impedance range.


In addition to the problem of available power, most of the low-voltage, battery-operated headphone amps are working with very low bias current to save battery life. This means in most cases Class-B operation. Now it’s well known that Class-B is far from ideal in terms of sound quality due to crossover distortion, but there is really not much you can do when the amp must be portable and operate from low-voltage batteries. Still, there are many people listening to portable devices, so it cannot be all that bad!—EB

output stabilize to 0V. Alternatively, you can leave the heater on all the time or in a stand-by mode with—say—4V, in which case you can apply the full heater voltage and the supply voltage

simultaneously.

The feedback resistors R8 and R9 set the closed loop (CL) gain of the amp. Normal gain is 10×, or 20dB. Changing R9 can change this gain. CL output

FIGURE 2: STUFFING GUIDE FOR THE HYBRID TUBE/MOSFET HEADPHONE AMP (90 × 80MM).

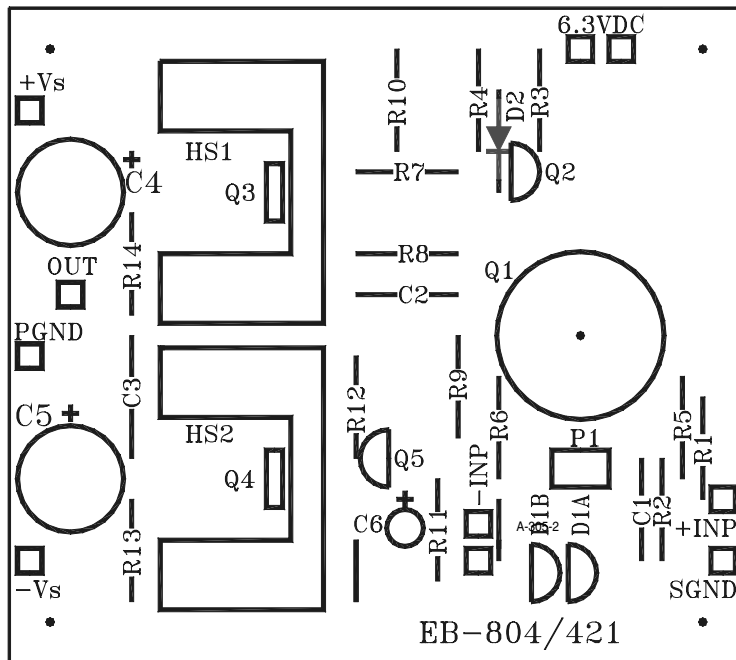

impedance is 15Ω. Equivalent input noise depends on the tube used and is 1.2–1.5μV!

The maximum output power into different loads depends on the supply voltage and the available current from Q4. With ±24V and 100mA in the second stage, the amp delivers >100mW into 32Ω and >250mW into 600Ω at 1% THD. With ±15V and 160mA the power into 32Ω increases to 300mW at 1% THD.

The maximum power is limited by the available current at low load impedances and by the available voltage swing at high impedances. If your headphones are low impedance, you should operate the amplifier at ±15V with 160mA in the second stage, and if they are high impedance, use a ±24V supply with 100mA. Since high impedance headphones require less power than the low impedance ones, the ±15V operation will probably give more than enough power for ear-shattering SPL over the whole impedance range.

ASSEMBLY

Figure 2 shows the stuffing guide for the hybrid tube/MOSFET headphone amplifier. Start the assembly by installing the solder pins, jumpers, and then

taking into consideration the rest of the electronics.

And this is not the end of the story. The Walkman-type devices are usually operating with two 1.5V batteries, for a supply of 3V total. Assuming that the audio amp would be able to work “rail-to-rail,” the equivalent audio signal would be $3/2.82 = 1.06V$ RMS, and you could generate a maximum current of:

$$I = 1.06/40\Omega = 26.5mA$$

This would give a maximum power of:

$$P = U \times I = 1.06V \times 26.5mA = 28.1mW$$

And SPL difference would be:

$$SPL_{diff.} = 10 \log 28.1 = 14.5dB$$

And the maximum SPL: 100dB + 14.5dB = 114.5dB, which is actually “only” 10dB less than the maximum. However, remember that in most cases the audio signal would be less than the one calculated, or the amp would already be clipping at a lower value. In a 32Ω headphone with 100dB SPL for 1mW input, the maximum power would be 35mW and the maximum SPL would be 115dB!

Real-life ICs, made specifically for low-voltage operation, will usually deliver less than this. Look up the National LM4911, which is a stereo headphone amp—it delivers 25mW into 32Ω at 1% THD from a 3V battery (12mW from 2.4V). This means that just a bit over 80% of the battery voltage is “converted” into audio! I bet most of the Walkman-type devices don’t deliver much more than 10–15mW of “clean” audio!

What would happen if you connected a 600Ω headphone to this amp? The maximum current would be: $1.06/600 = 1.77mA$, the maximum power: $1.06V \times 1.77mA = 1.88mW$. The SPL difference is:

$$10 \log 1.88 = 2.74dB \text{ and the maximum SPL is } 98dB + 2.74dB = 100.74dB.$$

Obviously, 600Ω headphones are less suited for this kind of application. For amps with low supply voltage, you need to use low-impedance headphones, assuming, of course, that the amp can deliver the necessary current.

Headphone amps operating from ±9V batteries fare much better in terms of maximum power. Assuming an 80% ratio between battery voltage and audio signal, such an amp could deliver over 600mW into a 40Ω headphone. Of course, the battery would also need to deliver the necessary current (over 120mA!), and the question is how long it would be able to do that? The same amp would manage only about 40mW into a 600Ω headphone, so even an amp working with ±9V power supply cannot cover the whole impedance range.

In addition to the problem of available power, most of the low-voltage, battery-operated headphone amps are working with very low bias current to save battery life. This means in most cases Class-B operation. Now it’s well known that Class-B is far from ideal in terms of sound quality due to crossover distortion, but there is really not much you can do when the amp must be portable and operate from low-voltage batteries. Still, there are many people listening to portable devices, so it cannot be all that bad!—EB

all the resistors (including the trimpot P1). If you have selected $\pm 15V$ operation, then resistor R13 = 3R9 and R10 = 7R5. If the supply voltage is $\pm 24V$, then R13 = 6R8 and R10 = 33R.

Next install Q2, Q5 and diodes D1 (A/B). Mount Q3 and Q4 on the heat-sinks with insulator and install them on the board. Make sure the MOSFETs are properly tightened to the heatsink. Then install the tube socket and all the capacitors, with C4 and C5 being the last ones. Finally, plug the tube into the socket.

SETUP PROCEDURE

If possible, test each amplifier separately before installing it in the chassis. This simplifies measurements, adjustments, and, if necessary, component changes. If you have access to a scope, connect it to the output of the amp and check whether radio frequency (RF) oscillations are present. If you have a complete audio instrumentation in your workshop, perform the usual gain, frequency response, noise, total harmonic distortion (THD), and intermodulation

distortion (IM) measurements.

Connect the +INP and the -INP to SGND. Apply the appropriate supply voltage ($\pm 15V$ or $\pm 24V$) and the 6.3V DC heater voltage to the amplifier. Connect a digital voltmeter (DVM) across R13 and check the voltage drop. It should be 0.62–0.65V. This sets the current to approximately 100mA or 160mA in the second stage, depending on the value of R13.

Let the amp run for about 20 minutes before you adjust the offset. Connect the DVM to the output of the amplifier and set the offset voltage to 0V with P1. This

completes the DC adjustments.

The EB-804/421 kit is available from North American representative Larry Black; for US/Canadian customers, see www.audiokit.com. Other countries can order the kit directly from Borbely Audio, www.borbelyaudio.com. **ax**

A note on intellectual property rights. DIY amateurs may build this circuit for their own use; however, commercial use or duplication in any form is not authorized. Many of my published circuits have been copied without my permission—not just by Far-East, but also by reputable European and US companies, and used in commercial products. This is against the international intellectual property rights.—EB



Chelmer Valve Company Ltd

The Stables, Baddow Park, Great Baddow, Chelmsford
Essex, CM2 7SY, England.

email: sales@chelmervalue.com ** tel. 44 1245 241 300 fax. 44 1245 241 309 ** www.chelmervalue.com

for High Quality Audio Tubes

Everybody in the audio tube business knows that the justly famous brand names of yesteryear like Brimar, GEC, Mullard, RCA, Telefunken etc. etc. are scarce and often quite expensive. Although we supply all major brands as available (and we have many in stock) our policy is to offer a range of tubes, all new and mostly of current manufacture, the best we can find from factories around the world, which we process to suit audio applications. The result – CVC PREMIUM Brand. Our special processing includes selection for **low noise, hum & microphony** on pre-amp tubes and controlled **burn-in** on power tubes to improve **stability** avoid tubes with weaknesses etc.

***** A selection of CVC PREMIUM Audio Tubes *****

PRE-AMP TUBE	POWER TUBES	POWER TUBES cont.	RECTIFIERS cont.
ECC81 5.90	EL34G 8.30	6L6/ 5881 WXT 9.00	5Y3GT 4.80
ECC82 5.90	EL34 (JJ) 8.50	6V6GT 5.50	5Z4GT 5.80
ECC83 5.90	EL34(Large Dia) 11.00	6080 11.50	SOCKETS ETC.
ECC85 6.60	EL84 5.50	6146B 11.00	B9A (Ch or PCB) 1.60
ECC88 5.70	EL509/519 13.00	6336A 48.00	Ditto, Gold Pl. 3.00
ECF82 5.50	E84L/7189 7.50	6550WA/WB 15.00	Octal (Ch or PCB) 1.80
ECL82 6.00	KT66 11.00	7581A 12.00	Ditto, Gold Pl. 4.20
ECL86 6.30	KT66R 22.50	807 10.70	UX4 (4-Pin) 3.60
EF86 6.00	KT77 13.20	811A 11.80	Ditto, Gold Pl. 5.50
E80F Gold Pin 11.00	KT88 13.50	812A 31.00	4 Pin Jumbo 10.00
E81CC Gold 8.00	KT88 (Special) 17.00	845 (New des) 33.50	Ditto, Gold Pl. 13.00
E82CC Gold 9.00	KT88 (GL Type) 30.00	RECTIFIERS	5 Pin (For 807) 3.30
E83CC Gold 8.50	PL509/519 9.90	EZ80 5.10	7 Pin (For 6C33C) 4.70
E88CC Gold 8.80	2A3 (4 pin) 15.50	EZ81 6.00	9 Pin (For EL509) 5.00
6EU7 7.00	2A3 (8 Pin) 17.50	GZ32 15.50	Screen can B9A 2.20
6SL7GT 8.90	211 23.00	GZ33 15.50	Ditto, Gold Pl. 4.30
6SN7GT 5.30	300B 45.00	GZ34 7.20	Top Con. (For 807) 1.70
6922 6.40	6C33C-B 25.00	GZ37 15.50	Ditto, (For EL509) 2.00
7025 7.00	6L6GC 7.60	5U4G 6.30	Retainer (For 5881) 2.20
	6L6WGC/5881 8.90	5V4GT 5.00	

***** And a few 'Other Brands', inc. rare types *****

5R4GY Fivre/GE 8.50	6SL7GT STC 13.00	13E1 STC 100.00	6550C Svetlana 18.00
5R4WGY Chatham 10.50	6SN7GT Brimar 13.00	211/VT4C GE 120.00	6146B GE 18.50
5Y3WGT Sylv. 6.50	12AT7WA Mullard 6.00	300B JJ 56.00	A2900 GEC 15.00
6AS7GT Sylv. 12.00	12AU7 Mullard 12.50	300B Svetlana 80.00	E88CC Mullard 14.60
6AU6WC Sylv. 5.10	12AY7 GE / RCA 8.40	300B WE 195.00	F2a Siemens 145.00
6B4G Sylv. 27.00	12AZ7 West'h. 8.00	805 USA 52.00	KT66 GEC 69.00
6BW6 Brimar 5.40	12BH7A RCA 14.00	5842A GEC 15.00	KT88 JJ 17.40
6BX7GT GE / RCA 9.00	12BY7A GE 9.50	6080 Telefunken 13.30	KT88 Svetlana 35.00
6CG7/6FQ7 8.50	12E1 STC 12.50	6550A GE 31.50	PX25 KR 128.00

ALL PRICES IN U. K. POUNDS £

Please note extras: carriage charge (£3.00 in U.K.) & in EEC VAT (17.50%). When ordering please state if matching required (add £1.00 per tube). Payment by credit card (VISA, AMEX etc.) or TRANSFER or CHEQUE (UK only).

FAX email or POST your ORDER for immediate attention – We will send PROFORMA INVOICE if required.

MILLIONS OF OTHER TUBES & SEMICONDUCTORS IN STOCK!

**** Valve Amplifiers sound better still with CVC PREMIUM Valves! ****

**

PRICE VALIDITY TO END APRIL 2002 – ASK ABOUT ANY TYPES NOT ON THIS LIST

PARTS LIST

EB-804/421

Resistors, Trimpot

R1,R7,R12	100R
R2	1MEG
R3,R4	499R
R5,R6	47R5
R8	10k, RN60
R9	1k1, RN60
R10	33R, RN60 ($\pm 24V$)
	7R5, RN60 ($\pm 15V$)
R11	10k
R13	6R8, RN60 ($\pm 24V$)
	3R9, RN60 ($\pm 15V$)
R14	47R5
P1	100R Copal
All resistors non-magnetic Dale CMF 135 and RN 60.	

Capacitors

C1	100pF, 160V PS
(Optional)	
C2	10pF, 160V PS
C3	1000pF, 160V PS
C4,C5	220µF, 35V
C6	100µF, 25V ROE EKO

Tube, Semiconductors

Q1	ECC86/6GM8, ECC88/6DJ8, E88CC/6922, 6H23T-EB
Q2	2SA872
Q3	2SJ79 INS.
Q4	2SK216 INS.
Q5	2SC1775
D1	J508 or E-202 (two in parallel)
D2	1N4148

Miscellaneous

PCB	EB-804/421
HS1,HS2	SK76-37.5
12 x 1mm solder pins	
4 x M3 screws, nuts	
2 x 9-pin PCB tube socket	
Mounting hardware	