

WHAT'S IN A CAPACITOR?


Theoretically, a capacitor is nothing but a pair of plates with a dielectric material between them—a device that holds an electric charge that can pass alternating current but not direct current. A pure capacitor contains nothing but capacitance.

Real-world capacitors, however, include parasitic elements produced by the physical construction of the device. First and foremost, there is inductance (L), which resonates with the capacitance to produce an impedance curve such as in *Fig. 1*. At low frequencies, including the ones you typically want to filter out of a power supply, the capacitor acts like a capacitor: its impedance decreases as the frequency goes up. This is the *capacitive region*.

At higher frequencies, the impedance levels off, then begins going up with increasing frequency, as the capacitor's inherent inductance takes over. This is, logically enough, the *inductive region*. Meanwhile, at the resonance frequency, the impedance does not drop to zero, as it would with a perfect capacitor and inductor. Instead, there is some residual impedance, which is known as the *equivalent series resistance* (usually abbreviated ESR).

A real-world capacitor, therefore, can be represented by three components in series (*Fig. 2*). There are other parasitic elements as well, most notably a network representing a phenomenon called “dielectric absorption” and a resistor representing leakage current, but I’ll save those for another time.

FIGURE 2: SIMPLIFIED EQUIVALENT CIRCUIT FOR REAL-WORLD ELECTROLYTIC CAPACITOR. NOT SHOWN: ADDITIONAL ELEMENTS REPRESENTING LEAKAGE CURRENT AND DIELECTRIC ABSORPTION.

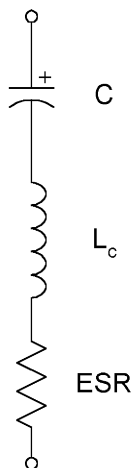

A-2437-2

WHAT IS IT FOR, ANYWAY?

Most of the time, we use electrolytic capacitors in electronic audio projects for two purposes: filtering ripple and other noise out of power supplies, and bypassing voltage regulators. (They’re sometimes used as audio coupling caps too, but we never do that, right? In any case, that’s also a topic for another time.)

Arguably, the most important role electrolytics play in our designs is filtering raw supplies. With the typical full-wave rectifier, this ripple is at 100 or 120Hz, depending where in the world you live. If you’re using a half-wave rec-

tifier, the ripple will be 50 or 60Hz.

The caps have more to do, though. Silicon diodes ring as they switch the current on and off;¹ this radio-frequency ringing can propagate through the audio system, perhaps causing intermodulation distortion and other ill effects. Power-supply caps can help shunt this high-frequency energy away from audio circuits—if they have a low-enough impedance at high frequencies. (It’s best, of course, if you generate as little high-frequency crud as possible; to this end, fast, soft-switching diodes and perhaps snubber circuits supply the requisite ounce of prevention.)

Do you suffer from Audiophilia Nervosa?



Audio Asylum - an institution for the care of audiophools.

Audio Asylum is a free and independent resource staffed by a small, volunteer group of audio lunatics. Our mission is to create a unique community for stimulating discussion and helpful interchange without the flame wars and slow load times often found at other sites.

Here's what inmates have to say:

"This is what the Asylum actually is: USEFUL."

"... the Asylum has taken me to a higher level of knowledge than I ever could have acquired on my own."

"I have saved hundreds...maybe thousands of dollars on equipment through the good advice received here. And not a banner ad in sight!"

"...the best return on your audio dollar will be the Asylum!"

Get committed today.


Audio**Asylum**.com

PASS DIY

Printed Circuit Boards

Key Components

Plans

Zen Variations

Pearl Phono

and more...

PO Box 12878
Reno, NV 89510

www.passdiy.com

You can build these amps!

Discover the magic of vacuum tubes. Join the thousands who have successfully built their own high-end audio equipment. Feel the satisfaction of accomplishment, save big.



Matching all-tube phono and linestages available. Check out our full line of DIY projects, including the new UFO turntable strobe.



www.hagtech.com

Supply capacitors can help filter out radio-frequency interference (RFI) that sneaks into the system by various routes, including the umbilicus connecting a main chassis to a separate supply box.


We also use electrolytic capacitors in voltage-regulator circuits. Typically, integrated-circuit regulators require a certain amount of capacitance at the output for stability. Adjustable regulators also need capacitors shunting the voltage-setting resistor, to minimize both noise and

output impedance. Complex regulators, such as the Sulzer² or Jung³ circuits, use electrolytics in several places, including the outputs, feedback networks, and reference voltage sources.

In short (well, in shunt), electrolytic capacitors and their behavior are central to the job of designing power supplies and the regulators they feed.

I decided to buy a pile of capacitors and see what they did.

FIGURE 3: TEST SETUP (NOT TO SCALE).

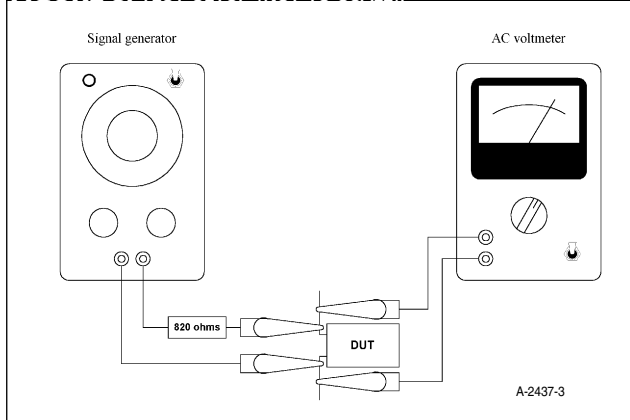

EXPERIMENTAL DESIGN

For the most part, I limited my study to capacitors that are easy to obtain, almost anywhere in the world. That meant Panasonic electrolytics, made by the giant and multinational Matsushita Corp., and available in the US from Digi-Key

TABLE 2

Two 1000µF electrolytics, with various bypasses. In all part numbers, the suffix “-ND” is assumed.

ELECTROLYTIC (µF/V)	ELECTROLYTIC P/N (SERIES)	BYPASS 1 (µF/V)	BYPASS 1 P/N	BYPASS 2 (µF/V)
1000/50	P11263 (FC)	None	None	
1000/50	P11263 (FC)	0.1/400	P3488	
1000/50	P11263 (FC)	0.47/50	P3474	
1000/50	P11263 (FC)	1.0/63	BC2076	
1000/50	P11263 (FC)	0.1/400	P3488	0.47/50
1000/35	P5555 (NHG)	None	None	
1000/35	P5555 (NHG)	0.1/400	P3488	
1000/35	P5555 (NHG)	0.47/50	P3474	
1000/35	P5555 (NHG)	1.0/63	BC2076	
1000/35	P5555 (NHG)	0.1/400	P3488	0.47/50
1000/35	P5555 (NHG)	0.1/400	P3488	1.0/35
1000/35	P5555 (NHG)	0.47/50	P3474	1.0/35
1000/35	P5555 (NHG)	0.1/400	P3488	100/50
1000/35	P5555 (NHG)	0.47/50	P3474	100/50
1000/35	P5555 (NHG)	0.1/400	P3488	100/50+1/35
1000/35	P5555 (NHG)	0.1/400	P3488	10/400
1000/35	P5555 (NHG)	0.47/50	P3474	10/400
BYPASS 2 P/N (SERIES)	F (MIN Z) (KHZ)	Z (MIN) (OHMS)	Z @ 1MHZ (OHMS)	Z @ 10MHZ (OHMS)
	10	0.157	1.600	15.90
	10	0.157	1.410	9.69
	10	0.157	1.300	10.36
	10	0.157	1.290	9.54
P3474	10	0.157	1.100	7.30
	13	0.203	0.995	9.74
	13	0.203	0.911	7.00
	14	0.203	0.865	7.33
	29	0.201	0.859	6.92
P3474	14	0.203	0.774	5.66
Generic Ta	25	0.200	0.817	5.43
Generic Ta	34	0.200	0.783	5.63
P5571 (NHG)	21	0.144	0.561	4.64
P5571 (NHG)	25	0.144	0.543	4.79
P5571 + G. Ta	25	0.410	0.471	3.87
GE surplus	46	0.171	0.608	4.89
GE surplus	54	0.170	0.588	5.05

Electronics (www.digikey.com) as well as many other suppliers. I ordered caps in common sizes, increasing roughly geometrically (100µF, 330µF, 1000µF, 3300µF), and in common low voltages (35, 50, and a few 100V units), plus a couple of high-voltage devices suitable for tube designs. For bypass caps, I mostly stuck with polypropylenes from Panasonic, plus a selection of B&C units and a couple of miscellaneous polypropylene, ceramic disc, and tantalum caps from my parts drawers.

My test hookup is shown in Fig. 3. I connected a GW GAG-808A audio generator to a non-inductive 820Ω resistor, which fed the device under test (DUT). (I soldered a clip-lead directly to the business end of the resistor to minimize the effect of stray inductance.) I measured the voltage across the DUT with a Hewlett-Packard 400H AC voltmeter, clipping its input leads directly over the leads feeding the DUT. (Thanks to Wylie Williams, of the Speaker and Stereo Store in St. Louis, for lending me the measuring gear.)

I calibrated the whole setup by inserting a 10Ω resistor as the DUT and setting the oscillator so that the meter read full-scale (on the 0–10 scale, although the actual sensitivity was 30mV) at 1kHz. This enabled me to read impedances directly without calculations.

Once I was calibrated, I measured each capacitor by twiddling the oscillator dial until I found the resonant frequency, where the impedance dipped to its lowest level. (This often required looking at the meter's needle with a magnifying glass to catch its small movements near the minimum point.) I then recorded the frequency and impedance. Knowing the frequency and the capacitance of the DUT, I calculated the inductance on a spreadsheet, using the formula:

$$L = 1/4\pi^2 \text{fres}^2 C$$

where fres is the resonant frequency in Hz and C is the capacitor's value in farads.

WORDS OF CAUTION

It's worth noting a few caveats and limitations in this experiment. For the lowest impedances, particularly with the 3300µF caps, I was working close to the noise-limited resolution of the system. That means that the impedance figures

for those caps should be taken with several grains of salt; I think the data reliably ranks which devices have higher or lower impedances, but the absolute ESR levels for these caps may be off. This doesn't affect the actual frequencies of resonance, though, from which I calculated the inductances.

I was curious to see whether the electrolytics' behavior would change when the capacitors were charged and the dielectrics were "formed." Accordingly, I jury-rigged a setup to charge the DUT from my 15V bench supply via a 10k resistor, and measured its resonant fre-

quency and ESR cold (never charged) a minute or so after turn-on and again an hour after turn-on.

For the two caps on which I tried this, the result was straightforward: no change at all in the resonance characteristics, either in frequency or ESR. (There was, however, a big change in leakage current, as measured by voltage drop across the 10k resistor, after the system had been on for an hour. Those folks who tell you to let your gear warm up for a while before you listen aren't just whistling Dixie.)

Be warned, though: I made this com-

J.C. Verdier

LA PLATINE MAGNUM



Now
the dream
is available



LABORATOIRE J.C. VERDIER
5/7, RUE D'ORMESSON - 93800 ÉPINAY/SEINE FRANCE
PHONE: 00 (33) 01 48 41 89 74
FAX: 00 (33) 01 48 41 69 28
WEBSITE: WWW.JCVERDIER.COM

Precision Acoustic Measurements Require Precision Microphones



PS9200KIT™ USD

A complete IEC and ANSI traceable Type 1 Measurement Microphone System 2 Hz to 40 kHz, 15 dBA to 160 dB SPL

*1/2 inch capsule *4012 Preamp *PS9200 2 Channel PS
*AC adaptor *WS1 windscreen *SC1 die cut storage case.
Options: 511E Calibrator; 1 & 1/4 inch mics; and Gain for DRA's MLSSA and other board level products.

ACO Pacific, Inc.

2604 Read Ave. Belmont, CA 94002 USA
Tel: (650) 595-8588 FAX: (650) 591-2891
e-mail acopac@acopacific.com

ACoustics Begins With ACO™

parison on only two capacitors out of the several dozen in the stack. While I can't see any reason why the rest of them should behave differently, I admit that I took the easy route and didn't try. Instead, I did all of my tests with the capacitors cold and unused.

As I took my measurements, I entered them into the spreadsheet, along with various specs gleaned from the manufacturers' datasheets, since I wanted to see whether any of them correlated with the results of my tests.

RAW RESULTS

The test data is summarized in *Table 1a (included here)* and in Tables 1b–e, which are posted at www.audioXpress.com (once there, click on the current issue and follow the link title "articles and addenda"). Each group of capacitors is ranked by increasing resonance frequency (corresponding to decreasing inductance). Looking at the data, several things jump out.

1. I had rather expected the low-ESR electrolytics (FC series) to have lower inductance than their higher-ESR counterparts, and thus lower impedance at high frequencies. They didn't.
2. I had similarly expected that, within a given series, capacitors with higher working voltages would have lower inductance, lower ESR, or both. Mostly, they didn't.
3. Looking at correlations between published specs and measurements, I found few. The specs for tan theta seemed to be only weakly correlated with measured ESR. There was no apparent correlation between inductance and price. On the other hand, there did seem to be a connection between inductance and size: the lower-inductance caps within a group of electrolytics had shorter bodies. (Makes sense.)
4. Among electrolytics, the larger the cap's value, the lower the resonant frequency. For example, the highest f_{res} among the 330 μ F caps was lower than the lowest one among the 100 μ F. (The high-voltage devices were an exception; they really should be considered separately.)
5. I expected the one Multicap® I had in the group, which is advertised as having a "self-bypassed" construction, to behave differently from a more conven-

AUDIO TRANSFORMERS

AMERICA'S PREMIER COIL WINDER

Engineering • Rewinding • Prototypes

McINTOSH - MARANTZ - HARMAN-KARDON
WESTERN ELECTRIC - TRIAD - ACROSOUND
FISHER - CHICAGO - STANCOR - DYNACO
LANGEVIN - PEERLESS - FENDER - MARSHALL
ELECTROSTATIC SPEAKER TRANSFORMERS

Williamson Amplifier Transformer Specialist

WE DESIGN AND BUILD TRANSFORMERS
FOR ANY POWER AMPLIFIER TUBE

PHONE: [414] 774-6625 FAX: [414] 774-4425

AUDIO TRANSFORMERS

185 NORTH 85th STREET

WAUWATOSA, WI 53226-4601

E-mail: AUTRAN@AOL.com

NO CATALOG

CUSTOM WORK

- tional cap of the same value. It didn't.
6. I expected the small-value film capacitors I tested to have extremely low ESRs. They didn't.
 7. Finally, it was clear that if you want a capacitor that remains capacitive beyond 1MHz, you should probably look at a ceramic disc or tantalum device. (OK, that's not really news. Nice to find data that confirms received wisdom, though.)

SIMULATIONS AND COMBINATIONS

What does all this information mean? And how does it relate to our stated topic, bypassing?

To find out, I ran simulations pairing likely-looking capacitors, using the venerable ECAP program available as shareware from www.cdquickcache.com/pccap.htm. I won't bore you with all of the results (if you're hungry to see them, I've posted them as a .txt file at www.audioXpress.com, but I've summarized one set of comparisons in Table 2).

This table shows a couple of promising 1000µF electrolytics, paired with popular 0.1µF and 0.47µF film caps, along with various other bypasses that came out well in the

Upgrade every component in your system without replacing any!

Make equipment you already own sound better! MANA ACOUSTICS Equipment Supports are revered for making dramatic improvements to turntables, CD players, tuners, tape decks, preamps, power amps, power supplies, speakers, DVD players, VCRs, even TVs! Just think... one multi-tier rack effectively upgrades each component you put on it. And it doesn't end there – MANA Supports are upgradable; each new level adds to the "MANA Effect." So stack 'em up, and believe your ears... the sound just gets better and better.



"Mana makes an important difference to the performance of a turntable but makes an equally big improvement to any component. The Mana Equipment table is not just good, it's fundamentally necessary for good sound... if you don't put Mana at the head of your shopping list you will never hear the true potential of your hi-fi system."
—Alan Sircom, HI-FI CHOICE

"The Mana stands are less an improvement in a system than a whole new system... I cannot recommend the Mana Acoustics Equipment Supports more strongly. They're a great investment themselves and a sure way to increase the value of the investment you've already made." —Steve Sullivan, FI



"I don't know of anything priced close to the [Mana Acoustics] Reference Table that could have improved my system so much." —Rob Doorack, LISTENER

BEST BUY Award —HI-FI CHOICE

★★★★★ —WHAT HI-FI?

Flat Earth Audio sells Mana Acoustics Equipment Supports direct to the public. Call toll-free:

888-653-5454

Tel: 203-888-3759

fax: 203-888-3769

www.flatearthaudio.com

FLAT EARTH AUDIO IMPORTERS



GRANDMOS The SMART amplifier



GRAND MOS
SILVER DESIGN

- ✓ Probably, the nearest approach to :
"A STRAIGHT WIRE WITH GAIN".
- ✓ High end 2 x 100 WRMS / 8 ohms MOS-FET amplifier.
- ✓ SILVER plated PTFE / fiberglass printed circuit boards.
- ✓ SILVER plated connections.
- ✓ Military grade components.
- ✓ Only J-FET and MOS-FET audio transistors.
- ✓ NO CAPACITOR in the sound path *.
- ✓ Minimum wiring and easy construction.
- ✓ Outstanding performances.
- ✓ Absolute Transparency and Sound.
- ✓ Extremely reliable.
- ✓ Steady performances over years.

* : under certain conditions

2 Audiophile Masterpieces for the DIYer

TRIPHON The ULTIMATE crossover system



To complete the GRANDMOS (or any good quality amplifier) we have designed the **TRIPHON system** :

- ✓ Musically neutral and transparent.
- ✓ 3-way electronic crossover.
- ✓ 6 or 12 dB/octave slope (true LINNKWITZ-RILEY filter).
- ✓ 4-channel Class A minimalist MOS-FET amplifier for MID and HIGH frequencies.
- ✓ Choice of cut-off frequency.
- ✓ PTFE / fiberglass printed circuit boards.
- ✓ Fully discrete component technology.
- ✓ SILVER plated connections.
- ✓ Minimal wiring.

by
Selectronic
L'UNIVERS ELECTRONIQUE

In U.S. : **VERASTARR**
3468 Cedar Valley Court, Smyrna, GA 30080
www.verastarr.com

>> Detailed information on www.selectronic.fr or by e-mail to : selectrocom@selectronic.fr <<


VACUUM STATE



The Winner of Bill Gaw's
Enjoy the Music.com
Best Of 2003 Award
and Best Of 2004 Award ...
Our dpa300B differential
monoblock poweramps!



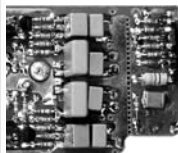RTP3C differential preamp
(MC phono & line):
*'Sounds like a Nightingale
that's fallen in love!'*



Our Upgrade modules for
SACD players have won
POSITIVE FEEDBACK ONLINE
2004 Brutus Awards
Best SACD Mods



Pure four nines
silverfoil & silverwire
interconnects and silverfoil
speaker cables.
*'I am really shocked by
their performance!'*

All products available finished or as KITS!

Showroom at: Vacuum State GmbH
Büsingerstr. 5 8203 Schaffhausen
Switzerland Ph + 41 52 620 35 81

www.vacuumstate.com

raw tests. I compared the lowest-inductance electrolytic (from the NHG series) with the lowest-ESR cap (FC series), looking particularly at behavior up in the megahertz region. This is a critical area for filtering out diode switching noise and RFI, not to mention possible decoupling of wideband op amps. Again, a few findings stand out:

1. The low-ESR FC caps inevitably had higher impedances at 1MHz and 10MHz, with a given bypass cap, than the lower-inductance NHG caps. This pattern held in every value of electrolytic I tested.
2. In general, using single bypass caps, the 0.47µF cap provided lower impedances at 1MHz than the 0.1µF; at 10MHz, though, the 0.1µF cap was usually lower. Using the 1.0µF B&C metallized cap provided slightly lower impedances at both frequencies. (It's nice and small, which often means lower inductance.)
3. Adding a third cap further improved performance. The 10µF GE polypropylene cap, which I obtained as surplus from Madisound a few years ago, had a distinctly salutary effect: high-frequency impedance was significantly lower with it than without it. (This

may be a finding of marginal usefulness, though, as these capacitors have vanished from the market, and I haven't found another tubular unit with similar characteristics.)

Similarly good results could be obtained by making the third cap a 100µF NHG-series electrolytic. Patching in a small tantalum device lowered high-frequency impedance still further. Variety, in this context, seems to be the spice of life.

HAVING YOUR CAKE AND EATING IT TOO

My tests imply a distinct trade-off in capacitor choice: For a given value of capacitance, you can design for the lowest possible ESR, or for the lowest possible impedance at high frequencies. Is it possible to get both at once? See Table 3 at www.audioXpress.com.

For this test, I compared a 3300µF low-ESR capacitor from the FC series with a composite unit made up of three 1000µF NHG-series caps, connected in parallel. Each was bypassed in various ways.

The composite cap produced an ESR that was about 40% that of the bypassed 3300µF cap, at a higher frequency, while its impedance at 1MHz and 10MHz was less than one-third of the larger unit's. Clearly, you can get the best of both worlds; as many designers have found, several little 'uns can outperform one big 'un—if your space and cash budgets don't mind.


It's been suggested—indeed, it's a common belief among designers—that parallel capacitors produce “multiple resonances,” or a single resonance with a sharp peak where the inductance of the large capacitor resonates with the capacitance of the small one. In my situations, I did not find this to be the case. The main reason is the high ESR of the small film capacitors; if I change the simulated ESR of the small cap to 0.1Ω, a peak does appear. With the actual ESRs of these capacitors, however, the curve is smooth, as shown in the dashed line of Fig. 1.

A HIGH-VOLTAGE INTERLUDE

For these experiments, I concentrated on lower-voltage capacitors, mostly because the projects I'm working on now happen to be op-amp based. However, I also design tubed circuits, which deserve at least a passing glance. Table 4 on www.audioXpress.com shows a few simulations I ran

FREE SAMPLE

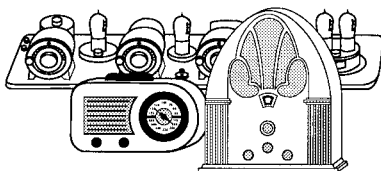IF YOU BUY,
SELL, OR COLLECT
OLD RADIOS, YOU NEED...



ANTIQUE RADIO CLASSIFIED

Antique Radio's Largest Monthly Magazine
100 Page Issues!

Classifieds - Ads for Parts & Services - Articles
Auction Prices - Meet & Flea Market Info. Also: Early TV, Art Deco,
Audio, Ham Equip., Books, Telegraph, 40's & 50's Radios & More...
Free 20-word ad each month for subscribers.

Subscriptions: \$19.95 for 6-month trial.
\$39.49 for 1 year (\$57.95 for 1st Class Mail).
Call or write for foreign rates.

Collector's Price Guide books by Bunis:

Antique Radios, 4th Ed. 8500 prices, 400 color photos\$18.95

Transistor Radios, 2nd Ed. 2900 prices, 375 color photos\$16.95

Payment required with order. Add \$3.00 per book order for shipping. In Mass. add 5% tax.



A.R.C., P.O. Box 802-A16, Carlisle, MA 01741

Phone: (978) 371-0512 — Fax: (978) 371-7129



Web: www.antiqueradio.com — E-mail: ARC@antiqueradio.com

using high-voltage capacitors. And, while I'm at it, *Table 5* on www.audioXpress.com shows the high-frequency performance of the various bypasses by themselves.

BACK ON THE GROUND

What do all these tests and data imply for our designs? I think a few conclusions can be drawn.

1. For a given application, you really need to run the calculations for the particular capacitors you're considering. If you simply plug in a randomly chosen electrolytic and whatever film cap seems inviting, you're likely to get less-than-optimal results (and you may spend more money than necessary). The tests aren't hard to do, and of course I've generated some numbers that you can use.
2. Don't assume! The results of combining capacitors are sometimes counter-intuitive, and you can't know until you try (or at least simulate).
3. Smaller caps, in multiples, may outperform their larger brethren.
4. Finally, the old and unfashionable ceramic disc cap has its place, particularly when you're trying to filter out

radio-frequency crud.

MAKING CHOICES

It's worth remembering, as I rattle on about comparative impedances, that there are other important criteria to look at when picking capacitors for a design. Temperature rating can be important—particularly in a box with limited ventilation—and projected lifetime is often an issue. When picking the first capacitor after a diode bridge, leakage current and ripple-current rating may be important. So may cost and size.

Electronic design is a balancing act; a good designer is always weighing one factor against another, knowing that it's impossible to optimize everything at once. I hope I've given you some information in this article that can help you juggle your way to better results. **aX**

REFERENCES

1. Jim Hagerman, "Calculating Optimum Snubbers," *Audio Electronics* January 1998, p. 26.
2. Michael Sulzer, "A High Quality Voltage Regulator for Operational Amplifier Preamplifiers," *Audio Amateur* 2/1998, p. 8.
3. Walt Jung, "Regulators for High-Performance Audio," *Audio Amateur* March 1995 and June 1995.



ELECTRA-PRINT
AUDIO CO.

S.E. OUTPUT TRANSFORMERS

- *Primaries to 10K
- *Power up to 100 watts
- *-1db 18hz to 40khz typical
- *Custom designs available

PUSH-PULL OUTPUTS

- *Built for triodes
- *Single output to load

INTERSTAGE TRANSFORMERS

- *Full bandwidth, up to 60ma
- *Single plate to P-P grids

LINE OUTPUTS

- *Full bandwidth, up to 60ma

POWER TRANSFORMERS

- *Custom built to your requirements

- *Power supply design advice

CHOKES/FILTER and AUDIO

- *Standard and custom HV filter chokes
- *High current filament chokes
- *High inductance audio plate chokes

specification and pricing catalog available
Visa, MC and Amex

ELECTRA-PRINT AUDIO CO.

4117 ROXANNE DR., LAS VEGAS, NV 89108

702-396-4909 FAX 702-396-4910

EMAIL electraaudio@aol.com

The Ultimate Acoustic Analysis System.

*For real-time testing of
Audio System performance!*

- 1/12th Octave Real-Time Analyzer (RTA)
- Energy-Time Graph (ETG)
with octave & 1/2 octave band filters
- Sound Pressure Level Meter
- Speaker Distortion Meter (THD+N)
- Signal to Noise Ratio
- Speaker Polarity Test
- Integrated Audio Signal Generator
- Handheld, Portable, Battery Operated
- Serial Data Download and Report Software



Powerful • Portable • Affordable

SENCORE

1-800-736-2673 • sencore.com • e-mail sales@sencore.com

Subscribe To The SENCORE News at www.sencore.com