

Dynamic Microphone Soundcard Amplifier

By Paul Loewenstein

This mike amp design expands computer and speech recognition capabilities.

This microphone amplifier is designed to interface the Shure SM10A dynamic microphone to a SoundBlaster card or other computer microphone input with a 5V through 2.2k Ω bias to the microphone connector ring. It enables speech recognition veterans of DOS DragonDictate to continue using the DragonDictate micro-


phone with Dragon NaturallySpeaking.

PRINCIPLE OF OPERATION

Referring to the schematic in Fig. 1, the open circuit voltage gain is provided by

the grounded emitter stage formed by Q1 and R2. This is followed by a unity-voltage-gain emitter-follower stage formed by Q2 and R4. R3 provides negative feedback to better define the gain,

FIGURE 1: Amplifier schematic.

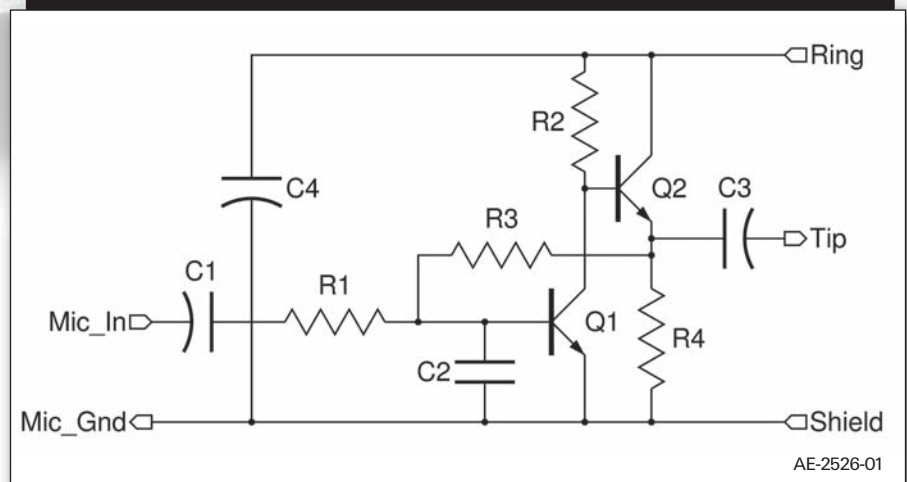

AE-2526-01

PHOTO 1: Amplifier in Radio Shack box.



VTV AUDIO VIDEO MUSIC EXPO



Pasadena Embassy Suites
211 Huntington Dr. , Arcadia, CA
November 19-20, 2005
10AM TO 6 PM

Celebrating 75 Years of High Fidelity Sound in Motion Pictures

Modern & Vintage Hi-Fi, Home Theater, Speakers, Musical Instrument Amps
 Rare Guitars, Records, CDs, Parts, Vintage Books, NOS Tubes.

John Atwood's **Tube School-Practical Tube Audio 8 Hour Class**


\$10 Admission - Open to the General Public

Very Reasonable Rate Vendor Space Still Available

Sponsored by: **Vacuum Tube Valley Magazine**

Contact: Charlie Kittleson PH:(707) 349-3009 FAX: (707) 263-7648

triode@vacuumtube.com www.vacuumtube.com

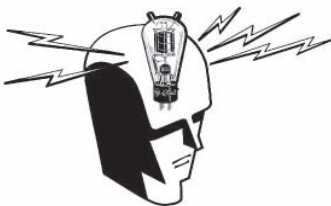

improve linearity, provide DC bias, and reduce the output impedance.

C2 rolls off the open-loop gain above audio frequencies to prevent oscillation. It also attenuates any radio frequencies picked up (see "Effects of Nonlinearities" section).

C1 and C3 provide DC isolation at the input and output, respectively. C4 reduces power rail excursions.

DC BIAS

Q1 base is one diode drop (about 0.6V) above ground, drawing current from Q2 emitter through R3, across which there is a negligible DC voltage. Q2 base is therefore about 1.2V above ground. Taking into account the 2.2kΩ in the soundcard between the ring and the 5V supply, the ring settles at about 3.5V.

OPEN-LOOP GAIN

The DC voltage across R2 is 3.5 - 1.2 = 1.3, so at room temperature the voltage gain of the grounded emitter stage is about $40 \times 1.3 = 52$.

CLOSED-LOOP GAIN

The model for calculating the closed-loop gain is shown in Fig. 2. It comprises:

- An ideal amplifier of gain -A representing the gain of the grounded-emitter stage with A = 52.
- Resistance x representing R1 in series with the microphone impedance; the impedance of an SM10A is 223Ω, so $x = 323\Omega$.
- Resistance z represents the input impedance of the grounded-emitter stage. This is $\beta \times$ the emitter impedance, which is $\frac{R2}{A}$. The lower bound on

β is 270, giving a lower bound on z of 29kΩ.

- Resistance y represents R3 (10kΩ).

Analysis of this circuit gives the closed-loop gain as:

$$\frac{-Ayz}{xy + yz + (1 + A)zx}$$

Substituting in for A, x, y, and z gives a (negative) closed-loop gain of 19.

NONLINEARITIES

The emitter impedance of a bipolar transistor is inversely proportional to the emitter current. This results in two sources of nonlinear gain:

1. The gain of the grounded-emitter stage.
2. The output impedance of the emitter follower, which results in nonlinear gain depending on how the output is loaded.

THE GROUNDED-EMITTER STAGE

The gain of a common emitter stage is proportional to the emitter current and therefore proportional to the voltage drop across R2. The gain when the output signal is high is less than when the

FIGURE 2: Closed-loop gain model.



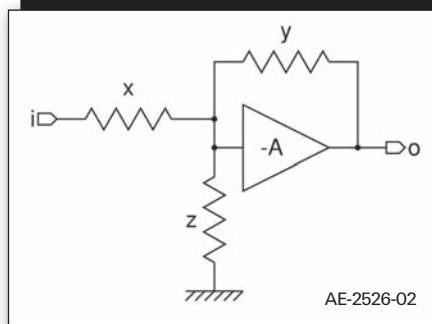


FIGURE 3: Printed circuit layout.

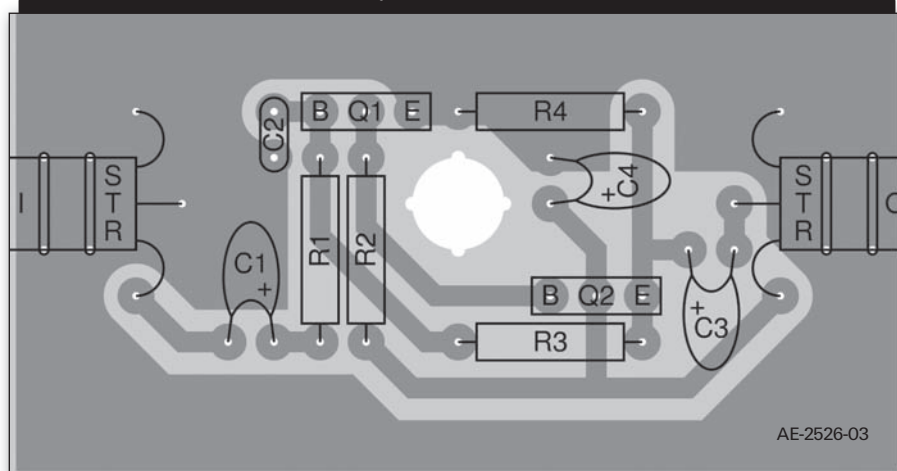

DSP Knowledge...Optional !

Signal Wizard II

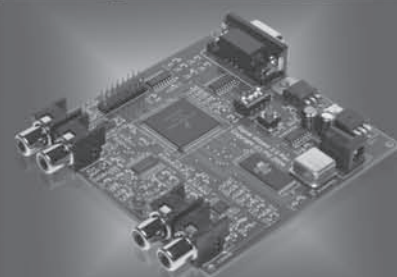

Want to create DSP crossovers & EQ without the learning curve?

With Signal Wizard you can !


Just specify your filter in the PC software, click to load DSP code into hardware, and then select the filter! Designers appreciate the ease of changing filters on the fly!

- FIR, IIR and adaptive filters.
- Butterworth, Chebyshev, LP-Brickwall.
- Low/high pass, bandpass/bandstop pole-zero placement.
- Spectrum analyzer and oscilloscope.
- Frequency response import (text file) allows precise loudspeaker equalization.
- Channel gain, mixing and inversion.
- Variable delay for precise LS alignment.
- Flash memory for standalone operation.
- Transparent audio - 24bit, 107dB SNR, range of sampling rates -4-48KHz
- High performance Freescale 56309 DSP

Applications:

- Loudspeaker crossover, equalization and room correction
- Acoustics research and development
- Sensor conditioning, and more...

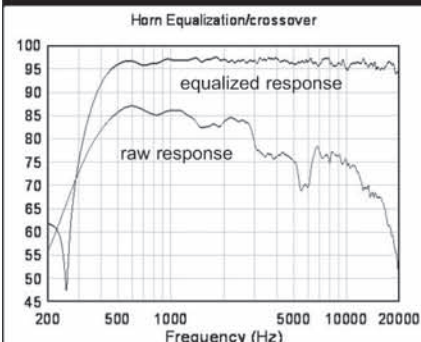Signal Wizard can equalize your loudspeaker!



Complete kit...everything you need \$399



Saelig Co Inc
European Technology

www.saelig.com
info@saelig.com
p: 585-385-1750
f: 585-385-1768

Visit the web at: www.saelig.com/Suppliers/ezfir/signalwizard2.htm



The Second Annual Rocky Mountain Audio Fest

The premiere audio show for music reproduction in the home

Stereo and Multi-Channel

90 Demonstration Rooms with Equipment from all over the World

Live Entertainment

Informative Seminars

Large Selection of Vinyl and CDs for Purchase

Ticket Prices

Online Pre-Registration (PayPal/Credit Cards only –

Pre-Registration ends 9/25/2005)

\$30 - Three-Day Pass

\$15 - One-Day Pass

\$20 - Three-Day Pass for students (ID required) and Audio

Society Members and Students (ID required)

\$7.50 - One-Day Pass for students and Audio Society members

Registration at the Door (cash or checks only with valid ID)

\$40 - Three-Day Pass

\$35 - Three-Day Pass with a coupon from selected retailers

\$20 - One-Day Pass

www.AudioFest.net • 303-393-7918

output signal is low. Assuming a 1mV signal from the microphone, the signal is about 20mV at Q1 collector, which means that the open-loop gain can deviate by almost 2%. However, the negative feedback limits the deviation of the closed-loop gain to about 0.7%.

THE EMITTER-FOLLOWER STAGE

The output impedance of the emitter-follower stage is inversely proportional to Q2 emitter current. With a 20mV signal, this can vary by about 6% around about 200Ω. However, the soundcard microphone input impedance is about 2.2kΩ, so the effect on open-loop gain is only about 0.3%. The effect on closed-loop gain is only about 0.1%. In addition, the nonlinearity is in the opposite sense to that of the grounded emitter stage, so it subtracts from the effect due to the grounded emitter stage.

Capacitively loading the output can introduce more nonlinear distortion. However, a significant effect would require several nanofarads of capacitance, much more than any likely parasitic.

EFFECT OF NONLINEARITIES

For variation of gain as a function of signal level introduces two components to the signal:

1. Frequencies double that of the original (0.6% deviation of gain introduces 0.3% second harmonic distortion). Given the high harmonic content of human speech, this is unlikely to adversely affect speech recognition.

2. A DC offset proportional to the signal level. At first sight this may seem inconsequential, but it turns the amplifier into a radio receiver un-

Parts List

C1	Tantalum capacitor	10μF 16V
C2	Ceramic capacitor	47nF 50V
C3	Tantalum capacitor	10μF 16V
C4	Tantalum capacitor	10μF 16V
R1	Carbon film resistor	100Ω 0.25W
R2	Carbon film resistor	5.6kΩ 0.25W
R3	Carbon film resistor	10kΩ 0.25W
R4	Carbon film resistor	2.2kΩ 0.25W
Q1	Silicon NPN transistor	NTE16
Q2	Silicon NPN transistor	NTE16

less steps are taken to attenuate radio frequencies¹.

MECHANICAL DESIGN

The printed circuit design is shown in Fig. 3.

To house the amplifier, you can use RadioShack's Mini Project Enclosure, part number 270-288, which has a convenient stud in the middle, providing a press-fit mount for a 0.1" pitch perforated board with one hole drilled out to 5mm.

Holes for the cables are drilled in each end with the box clamped tightly closed. The board is then inserted, cables attached, into the open box (**Photo 1**). The box is then closed and secured with a single self-tapping screw. The complete assembly with cables and connectors is shown in **Photo 2**. *aX*

PHOTO 2: Completed amplifier with cables.



Paul Loewenstein received a BA in 1971 from the University of Cambridge, an MA in 1974, and a Ph.D in 1994. His early career at Schlumberger in the UK and France involved analog systems from high-frequency IC amplifiers, vibrations of thin shells, and transients on high-voltage power lines. His professional activity has been purely digital since his move to the US in 1981, working for Schlumberger, National Semiconductor, Mitsubishi, and Sun Microsystems.

REFERENCE

1. The first version of this amplifier rolled off the loop gain using a capacitor to the collector of Q1. When conditions were right it happily picked up KGO at 810kHz AM, causing great confusion to the speech recognition.

Upgrade every component in your system without replacing any!

Make equipment you already own sound better! MANA ACOUSTICS Equipment Supports are revered for making dramatic improvements to turntables, CD players, tuners, tape decks, preamps, power amps, power supplies, speakers, DVD players, VCRs, even TVs! Just think... one multi-tier rack effectively upgrades each component you put on it. And it doesn't end there – MANA Supports are upgradable; each new level adds to the "MANA Effect." So stack 'em up, and believe your ears... the sound just gets better and better.



"Mana makes an important difference to the performance of a turntable but makes an equally big improvement to any component. The Mana Equipment table is not just good, it's fundamentally necessary for good sound... if you don't put Mana at the head of your shopping list you will never hear the true potential of your hi-fi system."
—Alan Sircom, HI-FI CHOICE

"The Mana stands are less an improvement in a system than a whole new system... I cannot recommend the Mana Acoustics Equipment Supports more strongly. They're a great investment themselves and a sure way to increase the value of the investment you've already made." —Steve Sullivan, FI



"I don't know of anything priced close to the [Mana Acoustics] Reference Table that could have improved my system so much." —Rob Doorack, LISTENER

BEST BUY Award —HI-FI CHOICE

★★★★★ —WHAT HI-FI?

Flat Earth Audio sells Mana Acoustics Equipment Supports direct to the public. Call toll-free:

888-653-5454

Tel: 203-888-3759

fax: 203-888-3769

www.flatearthaudio.com

FLAT EARTH AUDIO
IMPORTERS



Accuracy, Stability, Repeatability

Will your microphones be accurate tomorrow?



Next Week? Next Year? After baking them in the car???
ACO Pacific Microphones will!
Manufactured to meet IEC, ANSI and ASA standards.
Stainless and Titanium Diaphragms, Quartz insulators

Aged at 150°C.

Try that with a "calibrated" consumer electret mic!

ACO Pacific, Inc.

2604 Read Ave., Belmont, CA 94002

Tel: (650) 595-8588

FAX: (650) 591-2891

e-mail acopac@acopacific.com

ACOustics Begins With ACO™