

the two light bulbs with the supply filter and the constant-current source. Q4 is set up as a capacitance multiplier whose C3 and R8 time constant is set to 5 seconds. At this charge rate, the circuit will see minimal supply ripple and have a low turn-on transient.

The supply voltage appearing on the drain of Q3 enjoys some additional passive filtering from C2 and C6. Q4 drops about 4V off the supply, so that a 50V unregulated rail delivers about 46V at the drain of Q3 (*voltages in all schematics are approximate*). You could DC-stabilize the supply with zener diodes across C3, but that would make it more difficult to have such a slow turn-on, so use the constant-current source to DC-stabilize the bias current.

The constant-current source is formed by N channel MOSFET Q3 controlled by NPN transistor Q5. Make use of the physical constant of the PN junction of the base-emitter voltage of Q5 for a reference, and the circuit works to maintain about .66V across the resistors R4 through R6, which makes for a constant-current of 2A. R10 through R13

are there to provide a relatively constant bias current for the collector of Q5, with C4 bootstrapping from the output.

There are few other changes to the circuit of **Fig. 1**, but you will note the addition of an *audiophile-approved* bypass capacitor on the output, and variability in the value of R3. Later you will see that this value can be used to optimize the performance around the characteristics of individual JFETs.


In **Fig. 2** I trim the value of P1 for a drain voltage of one-half the supply voltage by adjusting the Vds of the JFET—if the voltage on the drain of Q3 is 46V, then you want about 23V on the drain of Q2. With the appropriate value for R3 (approximately 2Ω), you will see minimum distortion and a Vds across the JFET Q1 of 2 to 3V. This comes out to about 4 to 6W dissipation for the device.

This particular circuit is a transconductance amplifier; that is to say, a current source whose output impedance is mostly determined by the 100Ω output resistor R7. To lower the output impedance you will later apply some negative

feedback.

Figure 3 shows the comparative performance of the circuits of **Figs. 1** and **2**, and you see an immediate distortion reduction by about half. What is less clear is that the light bulb version is clipping at about 10% distortion at 10W, while the current-source circuit clips comparably at about 20W.

FIGURE 3: Light bulbs vs. current source.

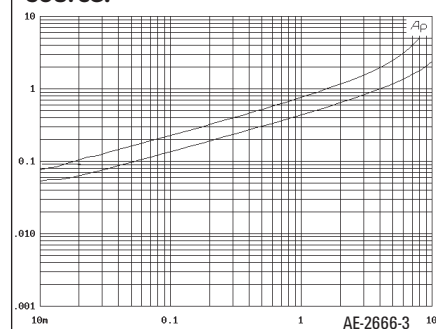

INSTALLMENT 2—CASCODE MODULATION

In ZV#8 I spent some time discussing the triode-like character of the power JFET at low voltages, where both the transconductance and “plate” (Vds) char-



LCY tweeters

Visit us online!



E-Speakers.com

Very High End Components and Kits

Los Angeles, California. toll free/fax 888.349.9419



Alian Tweeters



VISATON



Supreme Tweeter

Ribbon Tweeter is the best among all tweeters
LCY is the best of all Ribbon Tweeters

LCY-100K

Black Aluminium Casing and Stand



Manufacturer: YING TAI TRADING CO., LTD.
Director and Chief Designer: Lam Chin Yin
Rm. B, 1/F, Shumson Court, 214-216, Ap Lei Yeh, Sham Shui Po, Kowloon, Hong Kong
Tel: 852-25615152 Fax: 852-25615156 E-mail: info@yingtaihk.com

Frequency Response: 7K-100KHz (-18dB/oct crossover inside)
Crossover Fc: 10KHz/96dB/2.83V/1M (300W)
13KHz/92dB/2.83V/1M (300W)
Impedance: 8 ohm / 12 ohm Ribbon Size: 15 x 25 x 0.006mm

van den Hul[®]



DEQX PDC



CLIO win




ATD

acteristics show exponential behavior. With such a device, you can exploit distortion cancellation by carefully choosing the load line of operation so that the variation in gain versus current is cancelled against the gain versus voltage so that the distortion of the device is dramatically reduced.

This phenomenon was only discussed in ZV8, and here is where you will put it to use. In many examples, correctly varying the V_{ds} versus I_{ds} (drain-source current) in the JFET would involve more complex circuitry, but on this rare occasion Mother Nature does us a favor. The optimal voltage variation can be had across resistors R1–R3, which are coincidentally close to the value selected to give the JFET the correct DC self-biased value at 2A.

In **Fig. 2**, C5 is placed so that the AC voltage at the source of Q2 tracks the source of Q1, holding the V_{ds} of Q1 at a relatively constant DC value of about 2 to 3V. This is classic cascode operation.

FIGURE 5: Constant vs. modulated cascode.

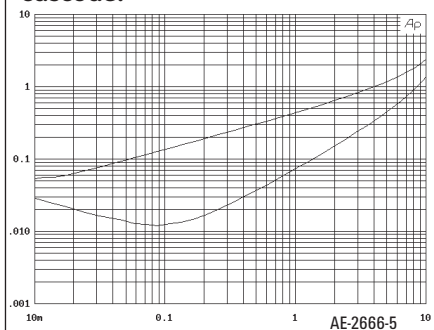

But a truly constant V_{ds} for Q1 is not the lowest distortion load line for the device. Because you want to cancel two nonlinear characteristics, the optimal V_{ds} across Q1 will be DC plus a finite AC voltage at around -600mV per amp, which was determined by testing at 1W. In **Fig. 4** you achieve this by grounding one leg of C5—the simplest change imaginable. **Figure 5** shows the difference.

INSTALLMENT 3—NEGATIVE FEEDBACK

The first two alterations improve the 1W performance by an order of magnitude, but it's still a current source. You might elect to stop here if a current source meets your needs. If you want a damping factor, apply some loop feedback, as seen in **Fig. 6**.

Figure 6 is different from **Fig. 4** with R16, R17, and C8 forming a negative feedback loop. Like most of its Zen predecessors, ZV#9 uses feedback to lower the output impedance. Roughly, R17 divided by R16 determines the gain and R16 determines the input impedance.

With the values shown you use about 10dB of feedback to get a damping factor of about 3 and a distortion reduction of about half. C8 imposes a small amount of compensation that makes the square wave look good. **Figure 7** shows the comparison with and without feedback. Note that the improvement is

FIGURE 4: Cascode modulation.

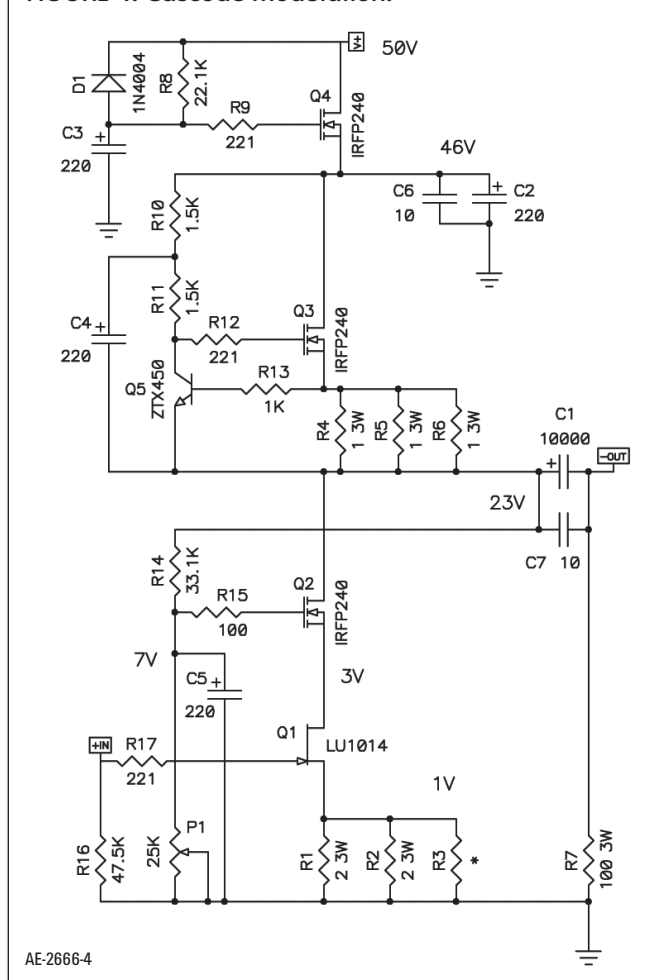


FIGURE 6: Negative feedback.


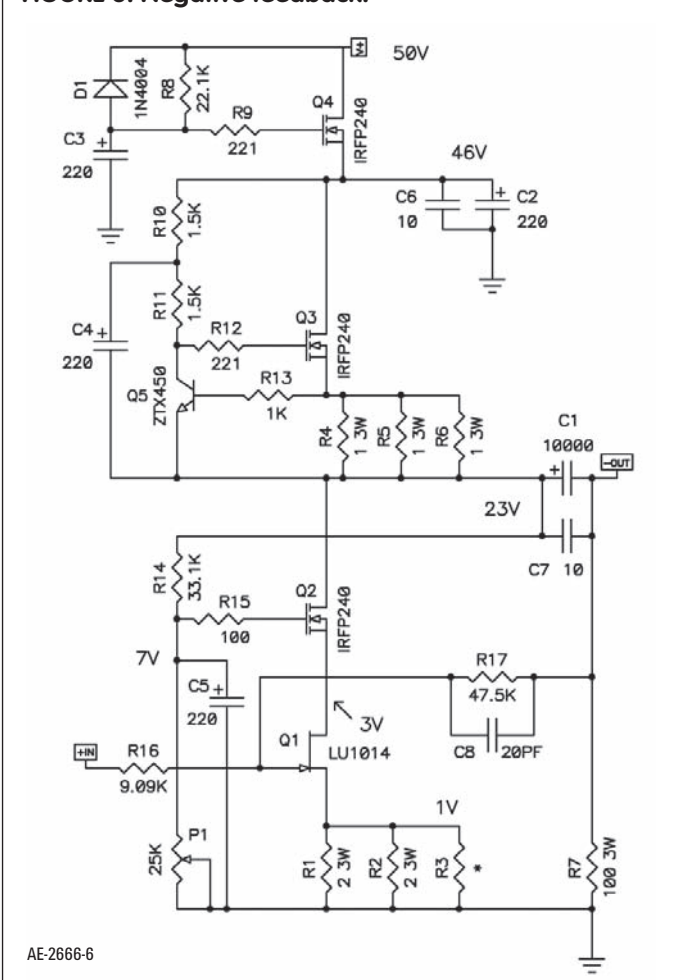


FIGURE 7: Feedback vs. no feedback.

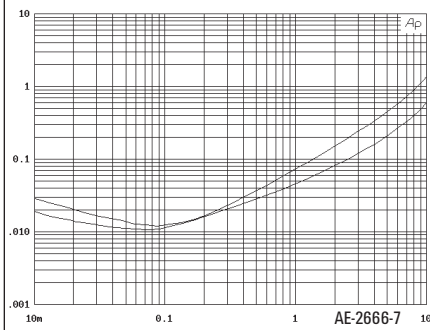

not uniform—with simple low feedback circuits it often is not.

INSTALLMENT 4—THE ALEPH CURRENT SOURCE


Those familiar with ZV#4 (“The Penultimate Zen,” Dec. ’02 *aX*) will probably figure out why I chose the particular current source of **Fig. 2**—it easily converts to the non-constant-current source used in the Aleph series of amplifiers and as described in patent # 5,710,522. ZV4 describes this current source in greater detail, but referring to **Fig. 8**, the current source has the addition of C9, R18, and R19 that set the current source AC value to track an arbitrary fraction of the output. Usually you set this value around 50%, and you can use it to “ghost” the complex load impedance at a negative multiple of the load value.

With the values chosen in **Fig. 8**, an 8Ω load would

look like 16Ω to the JFET gain device. By raising the apparent load impedance, the current source lowers the distortion of Q1 while still leaving it in control of the output. With tubes, variations of this idea have been called SRPP and SEPP output stages, although the distinction between an input and output stage is somewhat blurred in a single-stage amplifier.

At 1W, the improvement is a factor of about 5, and at 10W, a factor of about 10. Because the current source increases the open loop gain by about 6dB, the damping factor jumps up to about 6, and the output gain goes up about a decibel or so. As the open loop gain is still finite,

FIGURE 8: Aleph current source.

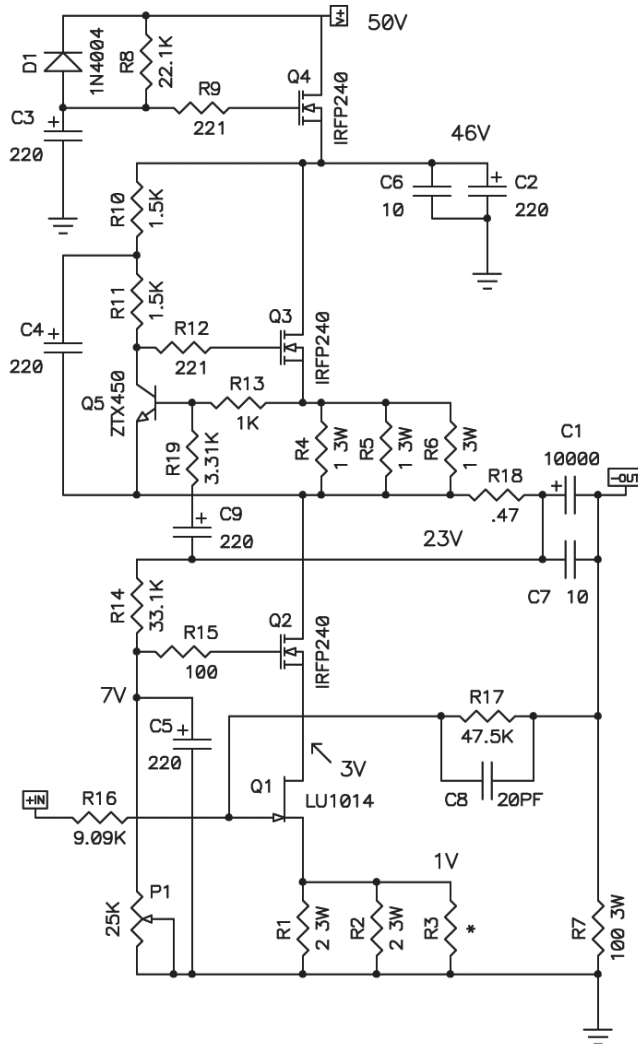

AE-2666-8



DRIVERS:

- ATC
- AUDAX
- ETON
- FOSTEX
- LPG
- MAX FIDELITY
- MOREL
- PEERLESS
- SCAN-SPEAK
- SEAS
- SILVER FLUTE
- VIFA
- VISATON
- VOLT

CUSTOM
COMPUTER AIDED
CROSSOVER AND
CABINET DESIGN

SOLEN CAPACITORS
AND INDUCTORS -
USED BY THE MOST
DISCRIMINATING
LOUDSPEAKER
MANUFACTURERS.

HARDWARE

HOW TO BOOKS

Contact us for the free
Solen CDROM Catalog.



SOLEN
4470 Avenue Thibault
St-Hubert, QC, J3Y 7T9
Canada

Tel: 450.656.2759
Fax: 450.443.4949
Email: solen@solen.ca
Web: www.solen.ca


TRIPHAZER.COM CD Remastering 29\$

Send us your 44.1 16 bit CD and We will remaster your original recording for incredible sound. Now for the very first time you can hear the AMAZING sonic benefits of Tritium Electronics Tri-Phazer audio processors on any recording regardless of age or quality.

Tri-phazers remove the SKEW and distortion your recordings have accumulated on the long journey from mind to master. 1 day turn around, priority shipping included. See our site for further information.

Send to: Tritium Electronics
8301A Lapham st. West Allis
WI 53214, tritium@execpc.com
Limited time offer 44.1 CDs only.
WELCOME TO THE FUTURE
OF RECORDING

FIGURE 9: Constant-current source vs. Aleph.

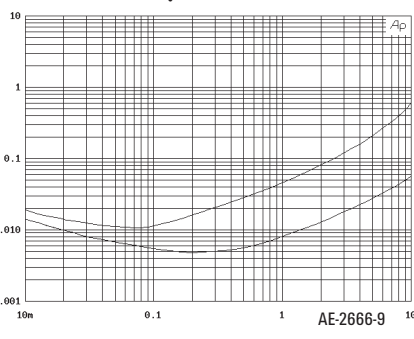


the input impedance is higher than the input resistor R16 at about 10kΩ. The -3dB bandwidth of the circuit is about 1Hz to 80kHz.

Figure 9 shows the performance difference with and without the two resistors and capacitor that enable the Aleph current source at about 50% gain.

A FEW CONSTRUCTION NOTES

I referred to choosing the value of R3 to get the lowest distortion. The best way to do this is to use a 5Ω power

FIGURE 10: Vgs test and value of R3 vs. Vgs.

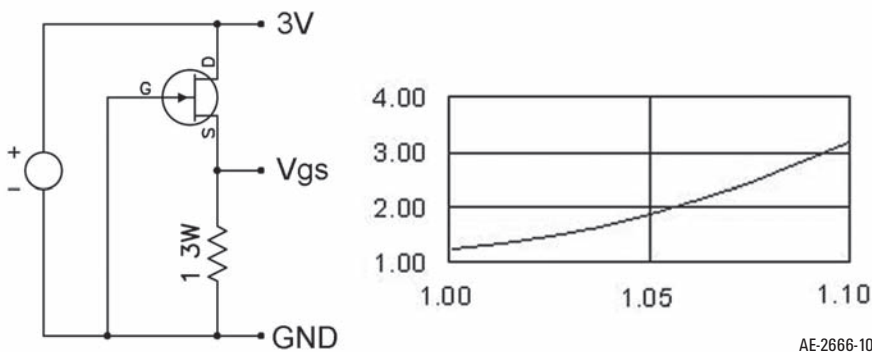

Reg's LP Rejuvenator Kit by Reg Williamson

Knock out static charges and deep clean your records with this classic two-step method still in demand by high-end audiophiles and LP lovers. Destatic compound supplies molecules which attract and retain static charges—one treatment usually lasts for the life of the record. The deep cleaner dissolves and flushes dirt out of the grooves—and then holds it in a film you simply peel away. You need to supply isopropyl alcohol, distilled water, and glycerin. Full instructions and Williamson's original articles are included.

KM-9 \$19.95*

*SHIPPING & HANDLING ADDITIONAL

To order call 1-888-924-9465
or order on-line at www.audioXpress.com

Old Colony Sound Laboratory PO Box 876 Peterborough NH 03458-0876 USA
Toll-free: 888-924-9465 Phone: 603-924-9464 Fax: 603-924-9467

E-mail: custserv@audioXpress.com www.audioXpress.com



potentiometer and measure the distortion for lowest possible value while adjusting P1 for output DC. This requires a distortion analyzer. Tweaking the various resistor values in the amplifier, I have seen distortion as low as .003% at 1W.

Since most of you don't have a distortion analyzer, I have an alternate method of determining the value of R3 based on the V_{gs} value of the Lovoltech LU1014 JFET in the test setup of **Fig. 10**. Using a 3V supply capable of greater than an amp, measure the V_{gs} of the device while the transistor case is still near room temperature. Most of them will sit between 1.0 and 1.1V, and you can use the graph to estimate the best value of R3—usually between 1 and 3Ω .

As yet another alternative if you don't want to test the devices, I recommend that you simply select R3 so that the V_d of the JFET in the amplifier is 2.5V with the output DC figure of 23V. More often than not, this is close to the sweet spot.

This amplifier idles at about 100W per channel, which means that each channel needs a heatsink rated at $.25^\circ\text{C}$ per watt. The Lovoltech LU1014D requires significant heatsinking also, and will operate at 4 to 6W continuously. Because of the high dissipation on Q2 and Q3, I recommend mica insulators with thermal grease.

The characteristics of all the semiconductor devices in the circuit will drift a bit with temperature, so you will find yourself readjusting values as the circuit warms up to a steady state. This also indicates a short warmup time for the amplifier, which is generally less than an hour.

Unless otherwise specified, the schematics use $\frac{1}{4}\text{W}$ metal film resistors and 50V capacitors, but you will note the 3W power resistors (I used the Panasonics from Digi-key). The Lovoltech devices are not yet in common distribution, and currently the best source for small quantities is the group buys arranged on www.diyaudio.com.

CONCLUSION

When the first Zen amplifier was published 12 years ago, I did not particularly imagine the course the exploration would take. A single-stage amplifier is attractive on a number of levels—it serves as an excellent base for tutorial projects, partly because it isolates concepts involved in amplification, but mostly because the simplicity invites beginners to try it.

Of course, a single gain stage amplifier has a purely esthetic value. The challenge is to make the best simple amplifier possible and hope that the minimalist character of the signal chain allows the most information through with the least coloration.

Remarkably, we seem to have made real progress. With the original Zen amplifier we measured .6% harmonic distortion at 1W, and here you see about 1/100 of that figure. I believe that the best correlation between measured performance and subjective listening occurs with simple circuits, giving rise to the obvious question: Does this sound 100 times better?

No, only about 10 times better. *ax*



"Cap of The Year!"



MCap® Supreme Silver/Gold

Launched in 2005, the Supreme Silver/Gold instantly achieved highest tribute from both our clients and reviewers.

Please visit www.humblehomemadehifi.com and find "The Great Capacitor Test" featuring a listening comparison of 20 caps. Aurally the very best: MCap® Supreme Silver/Gold followed by MCap® Supreme Silver/Oil on 2nd place.

The superior performance is based on our specially laid out capacitor-foil and its metallisation of pure silver added with 1% gold.



More audiophile innovations on www.mundorf.com

info@mundorf.com
OEM and dealer inquiries invited

- **Furthermore** - probably the largest range of various coils, capacitors and resistors available.
- **TubeCap** - as compact as an electrolytic capacitor, as fast and voltage-proof as a film capacitor. Due to its considerable low ESR and lower residual inductivity the TubeCap contributes to a finer, livelier sound. Advanced no drying out and self-healing properties.
- **M-Lytic HV** - electrolytic capacitor with the latest technology and best characteristics. Following many classic designs, these capacitors are offered as double capacity and are perfectly suitable for repair and upgrading.
- **M-Lytic Audio Grade** - compact electrolytic capacitor providing remarkable low ESR and ESL values as well a low inner-sound development.
- **Binding Posts** - of pure copper with exceptional torque. Also, various silver/gold wires for quality internal wiring.

Recommended US Dealer
MADISOUND SPEAKER COMPONENTS
www.madisound.com

Exclusive Canadian Distributor
AUDIYO INC.
www.audioyo.com

Exclusive Australian Distributor
SOUNDLABS GROUP PTY LTM
www.soundlabsgroup.com.au