



Grounding and System Interfacing

It's time to clear up some misconceptions regarding grounding and audio gear.

By Gary Galo

The annual conventions of the Audio Engineering Society are packed with technical papers, tutorials, seminars, and exhibits. Press coverage of the convention has become increasingly difficult due to the sheer size of the event. This year, rather than attempting an overview of the convention's proceedings, I decided to highlight one session that stood out as being particularly outstanding. On October 7, 2005, at the Jacob Javits Convention Center in New York City, Bill Whitlock, President of Jensen Transformers, Inc., gave a three-hour tutorial seminar titled *Audio System Grounding and Shielding: An Overview*. (Whitlock became President of Jensen following the untimely death of company founder Deane Jensen in 1989.)

Whitlock sought to dispel many of the myths surrounding grounding and system interfacing, noting that the subject abounds in black art and myths. Basic rules of physics are routinely ignored, and even many manufacturers "don't know ground loops from Froot Loops" (the last comment was typical of the touches of humor that Whitlock brought to his presentation, though there was serious intent behind each of them). If a system contains two or more pieces of grounded equipment, a ground loop may be formed if the chassis of the connected equipment are at different potentials. This will typically happen if the various pieces of equipment are powered by different AC branch circuits.

The most common approach to solving hum problems due to ground loops is by lifting safety grounds with "ground lifters" sold in any hardware store. Whitlock warned against this approach, noting that safety grounding keeps AC line voltages between equipment safe even if equipment fails. His view is that you

should never use ground lifters even if a manufacturer's instructions tell you that it's OK to do so.

Whitlock noted that the ground adapters sold in hardware stores, while superficially appearing as ground lifters, are actually intended to provide a safety ground when grounded (3-pin) power cords are used with 2-prong receptacles. They are designed to *add* a ground, *not* remove one, by putting the outlet plate screw through the ground tab on the adapter! If ungrounded equipment suffers an internal failure of insulation or components at the AC line input, the equipment chassis can turn live with 120V AC if the safety ground is not connected (**Fig. 1**; I thank Bill Whitlock for granting permission to use slides from his Power Point presentation for these illustrations).

Whitlock also recommends GFCI (Ground Fault Circuit Interrupter) outlets for safety. These outlets sense differences between line current and neutral current (fault currents). Any difference between line and neutral current may be current flowing through a human, which can be a deadly problem. GFCI outlets trip at 4 to 7mA of current, protecting the individual in contact with the "live" equipment.


He also dispelled some of the myths

surrounding earth grounds, noting that earth grounds are for lightning protection. The safety ground in a modern electrical system is tied to neutral at the entrance panel, and earth ground plays no role in protecting people from electrocution. Earth grounds are invariably *not* at 0V, and two earth grounds will rarely be at the same potential. Earth ground rods are useless for protection against fault currents, and are equally useless for reducing noise.

HUM CAUSES

Myths abound regarding the causes of hum in audio systems, and hum is rarely caused by bad audio cable shielding or AC distribution. You can trace the vast majority of hum problems to faulty system interfacing. Pro sound engineers routinely engage in dangerous practices in the field—adding ground lifters to AC power cords—in order to quickly eliminate hum problems. Defeating safety grounds is dangerous and illegal, and makes the person who did it legally liable. Whitlock emphasized that such practices have resulted in people being killed and companies forced out of business because of lawsuits.

The only safe way to solve hum prob-

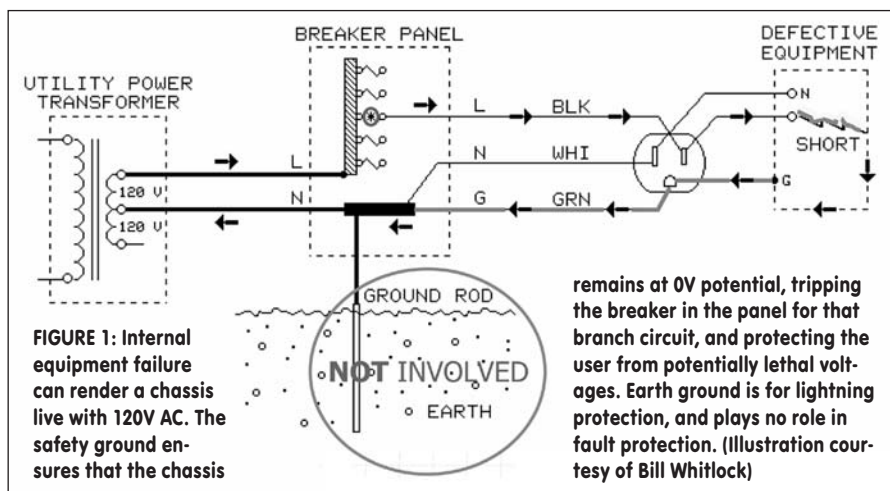

lems is through proper system interfacing. Whitlock provided a great deal of useful background on the causes of hum in unbalanced interfaces, and gave an excellent overview of the requirements for balanced interfaces.

Balanced lines are not balanced because they carry audio signals of equal level but opposite polarity (though they normally do). They are balanced because of careful impedance matching of the two signal carriers with respect to ground, especially the source (driving) impedances. If the impedances of balanced lines are not carefully matched, by definition they are not truly balanced. Common-mode rejection will be compromised, which reduces the system's ability to reject noise coupled to the signal carriers.

In unbalanced interfaces, leakage currents flowing in signal cables are the root cause of most hum problems (Fig. 2). Leakage currents are normally carried by the grounded conductor—the shield—which does not have a zero ohm impedance. Ohm's law tells us that the resistance of the shield generates noise voltage over the length of the cable. This

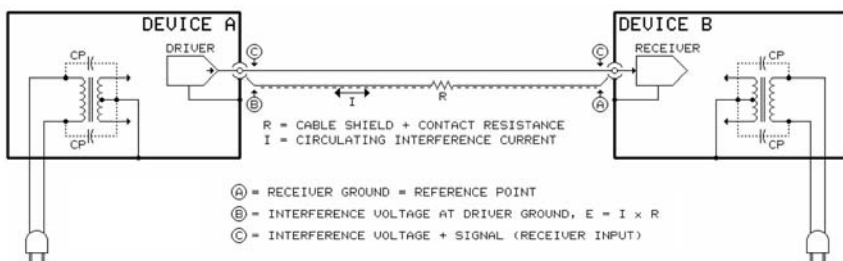


FIGURE 2: When two grounded chassis are at different AC potentials, circulating interference current will be carried by the interconnecting shield. Noise voltage will be generated over the length of the shield due to the shield's resistance. This noise voltage is added to the signal arriving at the receiver due to common-impedance coupling. (Illustration courtesy of Bill Whitlock)


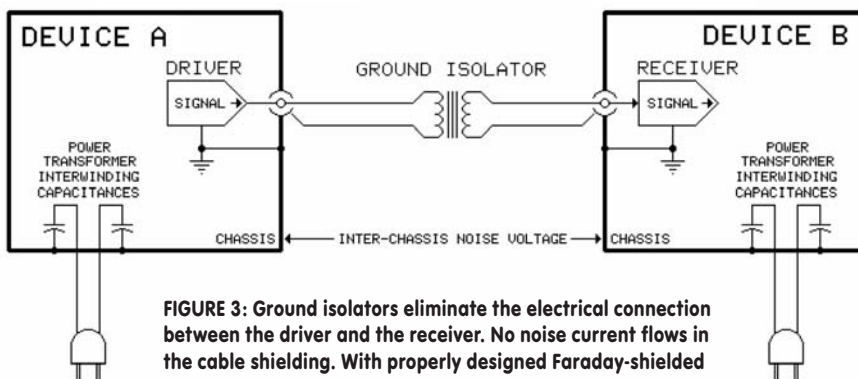


FIGURE 3: Ground isolators eliminate the electrical connection between the driver and the receiver. No noise current flows in the cable shielding. With properly designed Faraday-shielded input transformers, noise coupling is effectively eliminated. (Illustration courtesy of Bill Whitlock)

CLIO win 7


AUDIOMATICA news

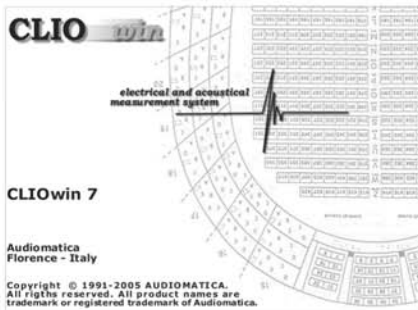Turns your PC into the most complete easy-to-use electrical and acoustical measurement system



www.cliowin.com
www.audiomatica.com

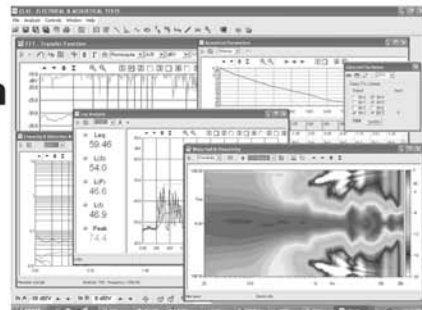■ **CLIOwin 7**, by Audiomatica, is the new measurement software for **CLIO**. We are proud to announce that several new features have been added to a measurement system that was already a reference.



Distortion & Linearity Analysis ■
 FFT Live Transfer Function ■
 Color Waterfall Analysis ■
 ISO 3382 Acoustical Parameters ■

**NEW
FEATURES!**

■ **Directivity Analysis Color Map**
 ■ **Directivity Polar Pattern**
 ■ **IEC 61672 Leq Analysis**
 ■ **Wow & Flutter Analysis**

■ **Powerful hardware control.** **CLIOwin 7** fully exploits the capabilities of the SC-01 Signal Conditioner and of the QCBox Model 4 Amplifier&SwitchBox. This measuring instrument excels for signal interfacing, precision and reliability.



Two channels separate input monitor and control up to +40 dBV (280 Vpp) Programmable AC output generator with DC voltage

Input A dBfs 10 dBV Input B dBfs -40 dBV Out 10.0 dBu 46.1°C

noise, in turn, is added to the signal at the receiver.

The correct way to eliminate hum problems in audio interfacing is with transformer isolation (**Fig. 3**). Transformers transfer the signal voltage from the primary to the secondary windings without any electrical connection between them. So, there are no noise currents flowing between the connected devices. With a properly designed transformer, hum is eliminated while safety grounds remain intact.

Reducing ground noise in a transformer-coupled interface depends on the type of transformer used. *Output* transformers typically have closely spaced primary and secondary windings. This increases the capacitance between the windings allowing efficient high-frequency noise coupling between the windings, which is undesirable. *Input* transformers typically employ a Faraday shield between the windings, which virtually eliminates capacitive coupling. This, in turn, greatly improves noise rejection of a transformer-coupled interface, including RF and ultrasonic interference.

Many transformer-based “black boxes” sold to eliminate noise caused by ground loop problems employ output transformers. Their low output Z allows these devices to be placed anywhere in the signal path, because their outputs are not sensitive to the capacitive loading caused by long cable runs. Input transformers, on the other hand, offer a 30dB improvement in noise rejection over output

types. But, their relatively high output Z requires that they be placed within 2 or 3' of the receiver in order to prevent degradation of their high-frequency response by the output cabling.

Whitlock noted that normally an unbalanced interface using a single isolation transformer close to the load will solve the noise problem. Only in unusual circumstances is a balanced interface necessary. Converting the entire interface to balanced is necessarily more complicated because it requires an unbalanced to balanced conversion at the source, and a balanced to unbalanced conversion at the load. In other words, two transformers rather than one.

One pet peeve of mine is the notion that professional audio systems should be designed to operate at matched impedances of 600 Ω . Naturally, I was delighted when Whitlock dispelled this nonsense. He correctly noted that 600 Ω impedances are holdovers from early telephone practice, but are not applicable to modern audio systems that are driven by signal voltage.

Modern audio circuitry is designed with low output impedances and high input impedances. This way, audio circuits are not subject to unnecessarily low Z loads. He also correctly noted that signal level, impedance, and line balance are three *independent* parameters. Impedance has nothing to do with level, and only its matching in the two signal conductors has anything to do with whether the line is balanced or unbalanced.



INGENIUS ICS

The near-infinite common-mode input impedance of a transformer-coupled line receiver gives it a huge noise-rejection advantage in real-world systems, but transformers have fallen out of favor in some pro audio circles. Transformer-less, actively-balanced circuitry has become increasingly popular over the past 20 years. **Figure 4** shows a typical op-amp based, instrumentation-type of active differential input. This type of circuit has a disadvantage over transformers because the bias return resistors for A1 and A2 also lower the common-mode input impedance. You could raise the values of R1 and R2, but this would compromise the noise performance.

Bill Whitlock has designed an elegant solution to this problem (**Fig. 5**). The common-mode voltage is extracted at the junction of R3 and R4. A4 buffers the common-mode voltage and bootstraps R1 and R2 via capacitor C. This patented technique is being used in the InGenius® line integrated circuit differential line receivers manufactured by THAT Corporation (**Photo 1**). Common-mode input impedance for this circuit is 10M Ω at 60Hz and 3.2M Ω at 20kHz, without the noise penalty that raising the resistor values would produce.

Whitlock noted a number of features of the InGenius chips:

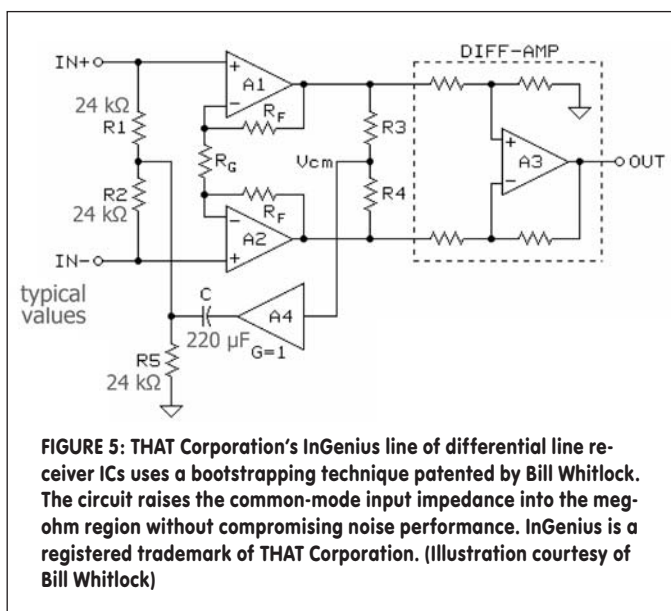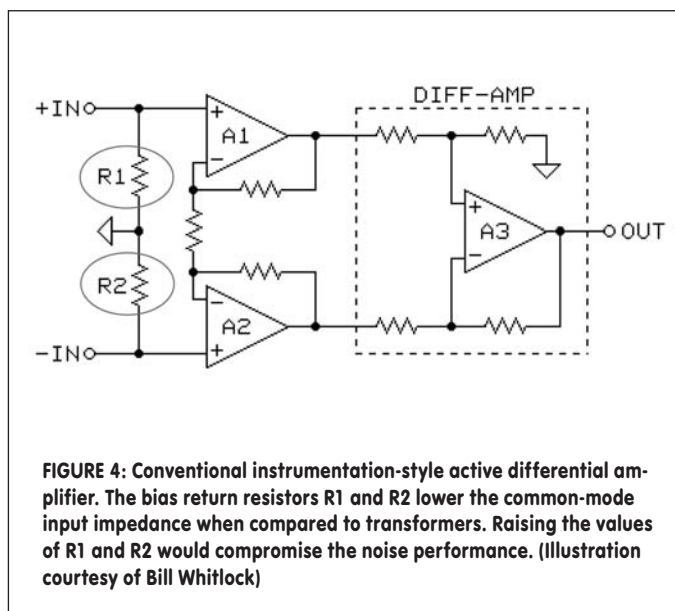- Thin-film silicon-chromium resistors are used, which yield better stability over time and temperature compared to nickel-chromium or tantalum-nitride types.



- 90dB common-mode rejection ratio and gain accuracy are achieved by careful resistor matching, typically 0.005%. Laser trimming is used in the manufacturing, which keeps cost reasonable.
- Chips are manufactured using a 40V complementary bipolar Dielectric Isolation (DI) process, which allows NPN and PNP transistors with performance as good as discrete circuits. Isolation between transistors is high, with no substrate connection. Stray capacitances are low, yielding high bandwidth and slew rates.
- Front ends use a folded-cascode, PNP design, yielding superior noise performance, high gain with simple stability compensation, and greater input voltage range.

Whitlock also highlighted key performance specifications for the InGenius chips:

- High CMRR maintained with real-world sources:
- 90dB at 60Hz, 85dB at 20kHz with zero imbalance source
- 90dB at 60Hz, 85dB at 20kHz with IEC $\pm 10\Omega$ imbalances
- 70dB at 60Hz, 65dB at 20kHz with 600 Ω unbalanced source!
- THD 0.0005% typical at 1kHz and +10dBu input
- Slew rate 12V/ μ s typical with 2k Ω + 300pF load
- Small signal bandwidth 27MHz typical
- Gain error ± 0.05 dB maximum
- Maximum output +21.5dBu typical with ± 15 V rails
- Output short-circuit current ± 25 mA

typical

- 0dB, -3dB, -6dB gain versions = THAT 1200, 1203, 1206

He also summarized the performance advantages:

- Conventional ac-

tive receivers are far cheaper, smaller, and lighter than a quality transformer, but

- Transformers consistently outperform them for reasons that need to be widely understood and appreciated.
- The main transformer advantage stems from its inherently very high common-mode impedances.
- The InGenius IC exhibits the very high CM impedances previously associated only with transformers.
- Excellent noise rejection even with *unbalanced* sources!
- Its bootstrap feature lends itself to novel and very effective RF interference suppression.
- Its high-quality internal op amps give it *great sound*.

For further information on the InGenius chips, visit THAT Corporation's website at www.thatcorp.com.

Whitlock highlighted his seminar with a lengthy Power Point presentation of over 150 slides, which he offered to e-mail to any interested parties. He will also send his 40-page seminar handout *Understanding, Finding and Eliminating Ground Loops in Audio and Video Systems* on request. The preceding highlights only scratch the surface of

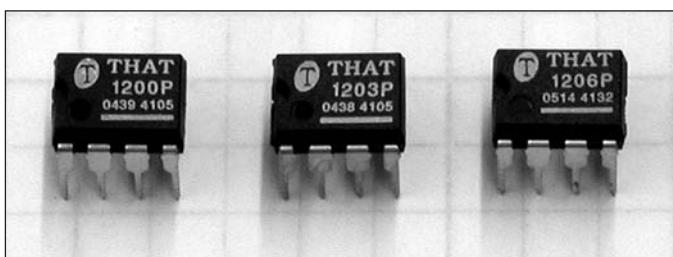


PHOTO 1: THAT Corporation's InGenius line of integrated circuit differential line receivers. The 1200, 1203, and 1206 have gains of 0dB, -3dB, and -6dB, respectively.



Dyna Clone Power Transformers

PA211 Upgrade and Replacement transformer for Dynaco PAS2, PAS3 and PAS3X preamplifiers.

PA522 International export version of PA211 with "universal" 120/240V 50/60 Hz primary.

PA774 Upgrade and Replacement for ST35 and SCA35

PA060S Improved replacement power transformer for ST70

PA135 replacement power transformer for Dynaco (tm) Mark 4.

P782S replacement power transformer for Mark 3 and Mark 2

C354 Exact replacement for chokes in ST70, Mk2, Mk3 and Mk4

Dyna^(tm) Clone Transformers... world's most popular and fastest selling Dynaco^(tm) replica transformers, priced competitively with generic massmarket transformers! Used by hobbyists, repairpersons and OEM's worldwide. Made in America's heartland by transformer professionals with over 50 years experience making private label and OEM transformers.

Dyna Clone output transformers are dimensionally identical and wound the same as the originals, with the same number of turns, sections and wire size, using the same patented Dynaco winding method, and made on the same core size and material. All have the requisite ultralinear screen taps.

Dyna Clone power transformers use improved insulation technology and 100% solids resin (no dripping wax!) impregnating to provide transformers that run cooler & quieter than the originals. Bolt in replacement installation, no cutting or drilling.

See and read more at www.triodeelectronics.com

Dyna Clone Output Transformers... compare price, quality, weight & specs to comparably priced mass market transformers. Why settle for generic when you can have a classic?

Z56548 Reproduction of the Z565 output transformer as used on the ST35 and SCA35 amplifiers, except that the output taps are **4 and 8 ohms**

A470S reproduction of the Dynaco A470 output transformer as used on the Dynaco (tm) ST70 and MkIV amplifiers

A431S a reproduction of the Dynaco A431 output transformer as used on the MkII and MkIII amplifiers and Sunn guitar/bass amplifiers.

Other stuff we sell: Tubes, Sockets, Other upgrade/replacement Parts.

Toroids for Audio



Tube Output

Toroidal transformers for tube output applications.

Electrostatic

Step-up toroidal transformers.

Solid State Power

Low noise, low inrush 500 to 2000VA.

Standard Power

Designed for general purpose applications. From 15 to 1500VA.



Part No. **PAT3025-SE**
Application **300B Single-ended**
Primary **2490 ohm**
Power **13W**
Secondary **4 & 8 ohm**
Ratio **24.96:1**
Pwr. Bandwidth **20Hz - 147kHz**
Insertion Loss **0.18dB**
Quality Factor **327,300**
Case **Aluminum**
Finish **Textured black**
Size **153 x 90mm**



8-601 Magnetic Drive
Toronto, ON M3J 3J2
Canada
416-667-9914
FAX 667-8928
1-800-PLITRON(754-8766)
www.plitron.com

www.plitron.com

his presentation, so these documents are required reading for anyone interested in this subject. Both are in PDF format, and encompass virtually everything discussed at the AES seminar. E-mail him at whitlock@jensen-transformers.com, and kindly mention this article.

ISO-MAX PRODUCTS

Jensen manufactures a multitude of transformers for every possible application, including microphone preamplification, moving coil phono cartridges, as well as balanced and unbalanced line-level usage (www.jensen-transformers.com). They also make a variety of transformer-based devices for audio interfacing. Perhaps the most useful for consumer applications is the CI-2RR Dual Ground Audio Isolator (Photo 2). You can download the .PDF datasheet for the CI-2RR at www.jensen-transformers.com/datashts/ci2rr.pdf.

This stereo device consists of a pair of their JT-11P-1HPC Line Input Transformers. You can download the .PDF datasheet for this transformer at www.jensen-transformers.com/datashts/11p1hpc.pdf.

[jensen-transformers.com/datashts/11p1hpc.pdf](http://www.jensen-transformers.com/datashts/11p1hpc.pdf).

Install the CI-2RR close to the load. In an audio/video application, a stereo RCA cable would be run from the video system's main audio output to the CI-2RR. The output of the CI-2RR is then fed to the preamp, integrated amplifier, or AV amplifier line input. Jensen notes that to avoid excessive high-frequency losses, the output cable lengths should be no more than 3'.

There may be cases where it is desirable to connect an audio/video system for both record and playback (Fig. 6). One possible application might be to use the audio recording capability of a Digital Video Recorder, DVD recorder, or VHS Hi-Fi recorder to capture an FM broadcast for delayed listening. For this application, use a pair of CI-2RR isolators, one in the record signal path, and one for playback. To keep output cabling as short as possible, place the CI-2RR used for the record signal path close to the video system's audio record inputs. Place the playback isolator close to the audio pre-



PHOTO 2: Jensen's Iso-Max CI-2RR transformer-coupled stereo audio ground isolator is ideal for interfacing audio and video systems. The transformers are among the world's finest, with very transparent sonics.

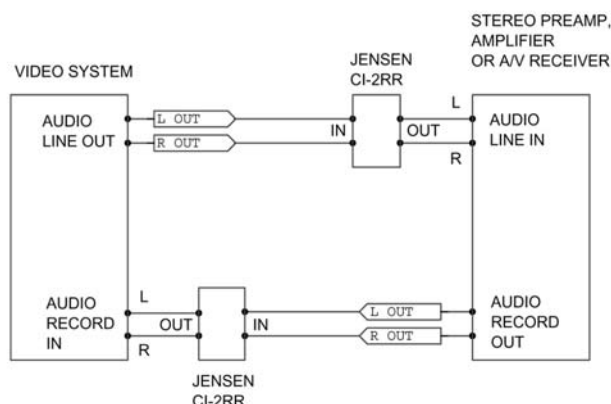


FIGURE 6: A typical audio/video application for recording and playback. A pair of Jensen CI-2RR stereo isolators are used in both the recording and playback signal path, providing ground isolation in both directions.

amp, amplifier, or A/V receiver.

In his review of the ISO-Max (Oct. '06 *aX*), Charles Hansen notes the high-frequency phase shift of the CI-2RR—about 35° at 20kHz—appears to be considerably higher than specified by Jensen. I made this measurement myself and got the same results. The graph in Jensen's datasheets for the CI-2RR and the JT-11P-1HPC shows essentially 0° deviation from linear phase at 20kHz.

It seems strange to me that Jensen would use the same graph for the transformer and the CI-2RR, because the CI-2RR has a series R/C damping network at its output, consisting of 13k in series with 680pF. The R/C network should introduce phase shift of its own, beyond that of the transformer. I disconnected the R/C network in one channel of one of the CI-2RR devices supplied by Jensen. This reduced the phase shift to around 10° at 20kHz.

The datasheet for the JT-11P-1HPC shows a schematic of a typical application for this transformer, with a series R/C network of 13k and 620pF (the capacitor is a slightly different value than the

680pF used in the CI-2RR). You would assume that the phase graph on this datasheet would be for the transformer as a standalone device, and not with the series R/C network, but Jensen doesn't really specify. None of the test circuits on page 2 of the datasheet show the series R/C network.

However, conventional phase measurements may not tell the whole story. Whitlock offered the following comments on the phase measurement:

"Regarding phase measurements on the Jensen samples, let me emphasize that 'phase shift' is not necessarily phase distortion! A totally benign time delay is represented in the phase domain as a phase shift that increases linearly with frequency. . . this is *not* distortion. Phase distortion occurs when there is a nonlinear relationship between frequency and phase—in other words, a time delay that changes with frequency. The widespread confusion about this subject is why Deane Jensen published a 1986 AES paper, *High-Frequency Phase Specifications—Useful or Misleading*, and why Jensen always

specifies Deviation from Linear Phase, or DLP, for our parts—*not* phase shift! DLP is the true measure of phase distortion. The secondary R-C networks specified for Jensen input transformers are chosen to provide two-pole Bessel high-frequency rolloff, which guarantees minimal DLP as evidenced by zero-overshoot and zero-ringing in square-wave response. This time-domain behavior is the hallmark of Jensen designs and a very important contributor to the sonic transparency of our products."

You can purchase the AES paper mentioned by Whitlock as a PDF download from the AES website www.aes.org/publications/preprints/search.cfm. Enter 2398 in the box labeled "Preprint/Paper Number." Cost is \$5 for AES members and \$20 for non-members. This paper is well worth reading.

Jensen uses standard PC-mount RCA jacks for the CI-2RR. The parts in the output R/C network appear to be Panasonic P-series polypropylene capacitors and 1% metal film resistors that look like

You can find the basics as well as the unusual at the Silicon Valley surplus source!

Power Resistors

8 ohm, 25W 1% Aluminum case	
HSC#20088	\$1.75
50 ohm, 5W Axial Ceramic case	
HSC#18282	\$.25
1K ohm, 50W 1% Aluminum case	
HSC#20991	\$2.50



Delta Electronics IEC Line Filter Input Module - 50 - 60 Hz, 10 A 115/250 VAC, part # 10DKG3S

HSC#19985 **\$2.95**



Gold-plated dual RCA jacks, PC-mount. (not color coded)

HSC#20448 **\$.65**

HSC Electronic Supply

Popular Film Caps

1 uF, 600V 5% Mylar Axial	
HSC#20996	\$2.95
2.2 uF, 250V Mylar Radial	
HSC#17297	\$.85
10 uF, 100V Mylar Axial	
HSC#20425	\$1.25

Handy wire & cable -- In Bulk!

20 ga Tinned Buss Wire, 1/4 lb.	HSC#WIR121	\$5.19
18 ga Tinned Buss Wire, 1/4 lb.	HSC#WIR120	\$3.69
16 ga Plain Speaker Wire, 50'	HSC#WIR082	\$10.95
14 ga Plain Speaker Wire, 50'	HSC#WIR084	\$14.95
12 ga Plain Speaker Wire, 50'	HSC#WIR087	\$18.29

This small sample of items and many, many more are available at our website...and we are adding more all the time. Due to the nature of surplus electronics however, when they are gone, they're usually gone for good! We also have computer parts, test equipment, IC's & components, tools, kits and books...everything for the electronics hobbyist. In addition we are a factory-authorized dealer for LMB chassis boxes, Littelfuse, Xcelite tools, Weller soldering equipment, HC Protek test equipment and lots of other products useful for most electronics manufacturing, repair, and prototyping.

For the Bench...



DMM with Capacitance (2nF to 20uF), Inductance (2mH to 20H), Frequency to 20KHz, Logic & Diode Test, Temperature as well as the usual Volts, Ohms & Amps!

HSC#MAS004 **\$49.95**



Weller WLC100 adjustable temperature soldering station with iron holder, sponge. Reg. price \$49.00!

HSC#WEL021 **\$39.00**

HSC Electronic Supply

Main Office - Mail Orders...

3500 Ryder St., Santa Clara, CA 95051

Three Retail Stores to serve you in

Northern California!

Local phones: Santa Clara 1-408-732-1573

Since 1964...

Silicon Valley's favorite place to shop for Electronics!

Order Toll-Free: 1-800-4-HALTED (442-5833)

or...ONLINE AT: www.halted.com

Sacramento 1-916-338-2545

Rohnert Park 1-707-585-7344



Time-Saving easy-to-use Solutions!

Signal Wizard



Signal Wizard - easy-use real-time DSP-based filter board for audio bandwidth signals. Design filters in seconds without any DSP knowledge!

Signal Wizard II

\$399

NEW! LCD Handheld Scope



HDS1022M - 20MHz 2-ch standalone scope with USB connection and 3.8" color LCD. Built-in meter - great for your tool kit. Volts, Amps, Resistance, Capacitance, Diode. Video Triggering. 100MS/s

HDS1022M

\$599

Low-Cost! LCD Bench Scope



PDS5022 - 25MHz 2-ch + trig. 100MS/s standalone bench scope with USB connection and 7.8" color LCD. Built-in meter - great for your service kit. Lowest cost available!

PDS5022

\$399

PicoScope 3224



PS3224 - new 2-ch PC adapter with 12bit resolution, 20MS/s sampling 512KS buffer. USB 2.0-powered, eliminates external power supply.

Small enough to carry anywhere you need. PS3244 is 4-ch version with the same performance.

PP300/PP298

\$626/\$1128

RF - Tight Testing



RF Testing - Economical benchtop RF test enclosure for troubleshooting, tuning, testing electronic devices in an RF-free environment. 8"H x 17"W x 10 1/2"D inside. Built-in illumination (RF-filtered supply).

STE3000B

\$1095

But Wait...There's More

USB to 24 I/O lines.....	\$69
USB to 8 Thermocouples.....	\$475
USB to 11 x A/D ch.....	\$181
USB 2ch 100MHz scope.....	\$1139
CANbus, VME, cPCI, etc.....	\$300+
easyRadio modules.....	\$40
USB-Serial adapters.....	\$35
USB-RS422 1/2/4ch.....	\$48+
USB Temperature Logger.....	\$60
Stepper Motor Controller.....	\$89

If you don't see what you need maybe we can find it for you? - Ask for sales!

1.888.7.SAELIG



the Yageo types sold by Digi-Key.

SUBJECTIVE TESTS

I evaluated the CI-2RR by inserting it in the signal path between my outboard D/A converter and my preamplifier. I use D.H. Labs' Air Matrix cables fitted with their Ultimate RCA Connector for all of my system interconnects, so I used an additional 1/2-meter pair of these cables to connect the CI-2RR to my preamp inputs. My procedure was to listen to a reference CD recording without the CI-2RR, then insert it in the signal path and listen to the same selection again. I compensated for the insertion loss of the CI-2RR when the device was in the signal path.

Sonic evaluation of the CI-2RR proved difficult, because the device is incredibly transparent. Sonic anomalies I normally associate with transformers simply didn't appear when I auditioned the CI-2RR. The important virtues of my audio system were left unscathed, including soundstage size and localization, ability to resolve subtle inner details, low-level resolution including hall ambience, and the overall clarity and purity of the sonic presentation.

There were times when I thought that the CI-2RR softened the treble slightly, but I could not verify this consistently. I did find that the CI-2RR seemed to make difficult CDs more listenable by softening the edge on these discs. The CI-2RR also maintained the weight and impact in the bass region. The only time I thought that the bass may have been degraded was on discs that have substantial energy below 20Hz, and this was more a matter of "feel" than audibility. But, the effect was very subtle.

Overall, the CI-2RR acquitted itself impressively in my listening tests, and it is no wonder that so many manufacturers of high-end consumer and professional audio equipment choose Jensen transformers for their designs. As examples, The Jeff Rowland Design group uses Jensen transformers for moving coil inputs, as well as for balanced line inputs and output on their multi-thousand dollar audiophile preamplifiers. The John Hardie Company, maker of some of the world's finest microphone preamplifiers, uses Jensen transformers for both microphone inputs and balanced line outputs.

The CI-2RR retails for \$177.95, but transformers of this quality are expensive to manufacture. Like all Jensen products, the CI-2RR is made in the USA, and is heartily recommended in any application requiring isolation of unbalanced lines. Jensen manufactures a sizable assortment of Iso-Max products for a wide variety of balanced and unbalanced applications, and you can purchase all of their transformers separately. Check their website for details. Iso-Max products are also available from Old Colony Sound Lab (www.audioXpress.com).

VIDEO ISOLATION

Many audio/video installers have encountered hum when interfacing video and audio systems. The hum usually appears when the cable TV coax is connected to the video system. Remove the CATV line and the hum disappears.

I first ran into this problem around 20 years ago, before CATV isolators were readily available. My solution was to connect the 300Ω ends of a pair of 75Ω to 300Ω balun transformers back-to-back. Garden-variety balun transformers typically have an insertion loss of around 3dB, so the total loss of this solution was around 6dB. But, it did cure the hum problem.

Anyone opting for this "cob job" approach should beware of certain devices being passed off as balun transformers. I have seen cheap ones that were actually nothing more than feed-through adapters—no transformer, no impedance matching, and no ground isolation. Some devices labeled "matching transformers" use an autotransformer. They are not baluns, and do not provide ground isolation. When in doubt, use an ohmmeter to check for continuity between the 300Ω and 75Ω sides, both signal and ground—resistance should be infinite.

A more elegant solution to CATV ground isolation is Xantech's model 63400 Ground Breaker. This 75Ω to 75Ω isolation transformer costs less than \$10 from Hometech.com: www.hometech.com/video/attn.html or Smarthome.com: www.smarthome.com/81285.html. Parts Express sells a similar device, the Dayton VIT-1, part no. 180-075, for also less than \$10. Subjectively, I find the picture a bit sharper with the Xantech Ground Breaker.

The Jensen VRD-1FF CATV isolator is unusual in that it is the only Jensen

product that does not use a transformer (**Photo 3**). The VRD-1FF is a capacitive isolator. According to my measurements, the device consists simply of two series capacitors, one in the signal path and one in the ground path. Both capacitors measure 2nF. At the power line frequency of 60Hz the device has extremely high isolation impedance, 1.3MΩ, but the impedance is very low in the RF region.

Jensen claims a bandwidth of 1MHz to 1.3GHz ± 3 dB. The VSWR (Voltage Standing Wave Ratio) is specified as 1.08:1 from 50MHz to 866MHz. One advantage of the capacitive isolator is extremely low insertion loss in the operating range. Jensen specifies the 50MHz insertion loss at 0.01dB typical and 0.1dB maximum. The device is compatible with analog, digital, and HD systems, as well as modems. You can download the VRD-1FF datasheet at www.jensen-transformers.com/datashts/vrd1ff.pdf.

According to the datasheet, the capacitors in the VRD-1FF are rated at 200V DC. However, Jensen notes that the VRD-1FF should not be used in situations where the DC or peak AC voltage between input

and output exceeds 34V. Check the voltage potential between your CATV line and the RF input to your video system. *If it exceeds 34V DC or peak AC, you have a grounding problem that must be corrected before using this or any other isolation device!*

Retailing at \$60, the VRD-1FF is not cheap, but it boasts the high-quality construction and performance I have come to expect of Jensen products. Because the VRD-1FF has female F-connectors on each end, Jensen also supplies the short jumper cable shown in **Photo 3**. No corners have been cut here either—the jumper uses Canare LV61S cable and Canare FP-C4 F-connectors. The LV61S is a flexible, high-quality RG-59 replacement, and the Canare F-connectors are the finest made. These connectors incorporate a gold-plated, crimped center pin, rather than relying on the cable's flimsy cen-

ter conductor.

Subjectively, the VRD-1FF yields the clearest, sharpest picture of all of the isolation devices I have tried. The capacitive isolation approach is superior to the cheaper transformer alternative, and is well worth the extra expense. I recommend using the VRD-1FF along with one or more CI-2RR isolators to provide complete effective ground isolation between video and audio systems. Note that you can't use the VRD-1FF between a DSS dish and receiver, because the capacitors can't pass the DC power that the receiver supplies to the dish. **ax**



PHOTO 3: The Iso-Max VRD-1FF is the only product made by Jensen that doesn't use a transformer. This CATV isolator is capacitive, resulting in extremely low losses over a wide bandwidth. Picture quality is visibly superior to transformer-coupled CATV isolators. The supplied pigtail cable uses high-quality Canare F-connectors and Canare LV61S cable.

PARTS CONNEXION

The Authority on Hi-fi D I Y !

No matter what your requirements are, pcX has what you need. Whether it be vacuum tubes (NEW, New Old Stock or OS), sockets, transformers, capacitors, resistors, connectors, hook-up wire, etc...we've got a world class selection of all the best brands...and more arriving every month!

Visit our website and sign up for our quarterly eConneXion Newsletter!

www.partsconneXion.com

Tel: 905-681-9602 Fax: 905-631-5777

1-866-681-9602

*USA & Canada only

order@partsconneXion.com

***Toll free order line**

International orders welcome!

SANYO OS-CON **audience** **KIWA ME** **NEURALGEAT** **nichicon** **ELNA**

LC Audio Technology **PEARL** **ALPS** **CERABALL**

MultiCap **InfraCap** **audioquest** **NEUTRIK** **EAR**

GOERZ **DISCOVERY CABLE** **DI LASS** **WATTAITE** **CADDOCK** **reizenham** **KIMBER KABLE** **Supra**

vacuum tube valley **vacuum tube valley** **vacuum tube valley** **vacuum tube valley** **vacuum tube valley**

2885 Sherwood Heights Drive, Unit #72, Oakville, Ontario, CANADA L6J 7H1 • NOTE: No "on-site/walk-in" business at this time