

A Home Theater Preamp

With this six-channel preamp, you'll be able to accommodate the latest audio formats.

Is it worthwhile for an audio hobbyist to try and build a multi-channel preamp in the age of multi-format digital audio? The answer is "yes," especially for those who relish separate amplifiers and active frequency dividing networks. Inexpensive home theater receivers do not likely contain multi-channel analog outputs to support a multi-amplifier system.

Obtaining an expensive home theater preamp limits you to the digital audio formats embedded therein at the time of purchase. The chipset used for decoding is often touted as an advantage for audio quality. However, if you wish to take advantage of newer formats such as multi-channel PCM, Dolby True-HD, or DTS-HD available on Blu-Ray and HD-DVD discs, the unit may not be able to decode these. Instead, you will need to resort to using a set of analog multi-channel inputs along with an audio decoder internal to the player or other source.

PREAMP OVERVIEW

The preamp contains inputs for four sources, three of which are six-channel inputs and one stereo input. In my system (Photo 1), these are connected to a Dolby Pro-logic decoder (for TV sound), a Blu-ray disc player, a DVD audio/video player, and a CD changer. The disc players decode multiple audio formats inter-

nally and deliver them via multi-channel RCA outputs.

The preamp contains five outputs (more on that later). The main channels are sent to a three-way active crossover network and then subsequently through separate MOSFET power amplifiers. The center channel and surround right/left channels are connected directly to respective amplifier channels.

The reason for including only five outputs is that the "subwoofer" input channel is summed with the main channels. This "subwoofer" signal is a combination of the Low Frequency Effects channel (Dolby 5.1 soundtracks) and low-frequency information that has been re-directed from the center and surround channels. This is a matter of personal preference because my system does not contain typical subwoofers, but rather a set of robust three-way main speakers. Should you choose to build your own preamp, you could modify the design to include a dedicated subwoofer output.

The front panel of the rack cabinet (Photo 2) contains a rocker power switch, three function push buttons, and a red bezel window. Mounted behind the bezel are an infrared detector and the seven-segment LED displays. The rear panel (Photo 3) contains 25 RCA connectors necessary for the audio component connections.

The LED display indicates which of



PHOTO 1: Author's audio/video system.

the four sources is currently selected. When the attenuation up or down command is given, the attenuation level is displayed (0 to -60dB in 2dB steps). For my application, a gain > 1 is not necessary given that digital audio players have sufficient output levels to drive the power amplifiers into clipping (overloaded). However, you may choose to modify the design for additional gain to suit your application.

The preamp is programmed to respond to NEC type IR commands that are generated by a "universal" TV remote. The attenuation level is controlled with arrow keys on the remote. Numbered buttons 1-4 set the input source selection. I also added a mute function ("0" key) that sets the attenuation level



PHOTO 2: Front panel.



PHOTO 3: Rear panel.

to >-100dB, which is great for dealing with annoying commercials. This mute feature is only available from the remote control.

Another added capability of the preamp is that relative levels of the individual channels may be set from within the software. This is useful when the internal decoding of your equipment does not allow for proper balancing of the surround system.

THE POWER SUPPLY/MICROCONTROLLER BOARD

The power supply board (Photo 4 far right) is a single-sided PCB that contains the power supply, the microcontroller IC with associated components, and the IR detector and seven-segment LED displays. The power supply is made up of a toroidal transformer T1, rectifier bridge D1, filter capacitors C1/C2, and four fixed-voltage regulators. Regulator output stability is ensured with the use of tantalum output caps. The $\pm 15V$ levels are used to supply the op amps on the

audio board. All other ICs use the $\pm 5V$ levels. Note: The four TO-220 package

com). The program decodes NEC 6121 IR commands, which are 32 bits in length and are derived from Pulse-Position Modulation. I used the 6121 encoding because it was available from an existing TV remote and not used by any other equipment that I own.

The 22 I/O pins of the PIC16F57 are fully used in the preamp design. Port A is connected to the input switches SW1-SW3 and pullup resistors R15-R17. The Sharp IR receiver U7 is also connected to

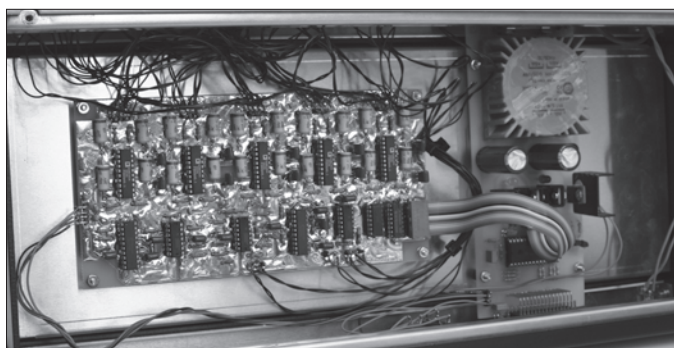


PHOTO 4: Preamp PC and power supply (right) boards.

regulators use small heatsinks; however, I used a slightly larger 5W rated heatsink for the +5V regulator due to the heavier current demand.

The PIC microcontroller contains 2K bytes of flash program memory, which is easily programmed using a PICSTART Plus development programmer. This PC-based application allows changes to be made in minutes. The program listing, along with a flowchart explaining the IR remote portion of the code, is posted on the *aX* website (www.audioXpress.com).

Port A. This three-terminal device contains the IR detector, amplifier, limiter, and 38kHz bandpass filter necessary to receive IR commands from across a room.

Port B I/O pins are connected to the multiplexed common-cathode LED displays (one overflow digit and a two-digit display). The LED displays are mounted on a 30-pin right-angle IC socket directly adjacent to the IR detector. Port C I/O pins control the function of the audio board via a 16-pin DIP header cable.

The schematic for the power supply

Ever needed an Audio Consultant in a pinch, and couldn't find one?

Call 1-800-**SENCORE**
(736-2673)

"The RaSTI and STI-PA functions of the SP495 help us get a better idea of the real-world performance in understanding speech for our digital signage applications."

Chris Osgood, Innovox Audio Factory,
Minneapolis, Minnesota



Take a test drive: www.sencore.com/products/sp495/sp495.html

Quality • Stability • Total Business Solutions

SENCORE

3200 Sencore Drive • Sioux Falls, SD 57107

sales@sencore.com

1-800-736-2673 or 1.605.339.0100

to the etch process used.) Construction of the PCB is fairly straightforward. I placed small circular pads in the pattern to locate the mounting holes.

The schematic diagram for the audio board (**Photo 4**) is shown in **Fig. 5**. The three sets of six-channel inputs (and single stereo input) are connected through DC blocking capacitors to quad analog switches. The SSM2404 is produced by Analog Devices and is designed especially for audio applications. Noise and distortion figures are negligible. Digital logic levels from the microcontroller select the input source.

FIGURE 1: Preamp power supply.

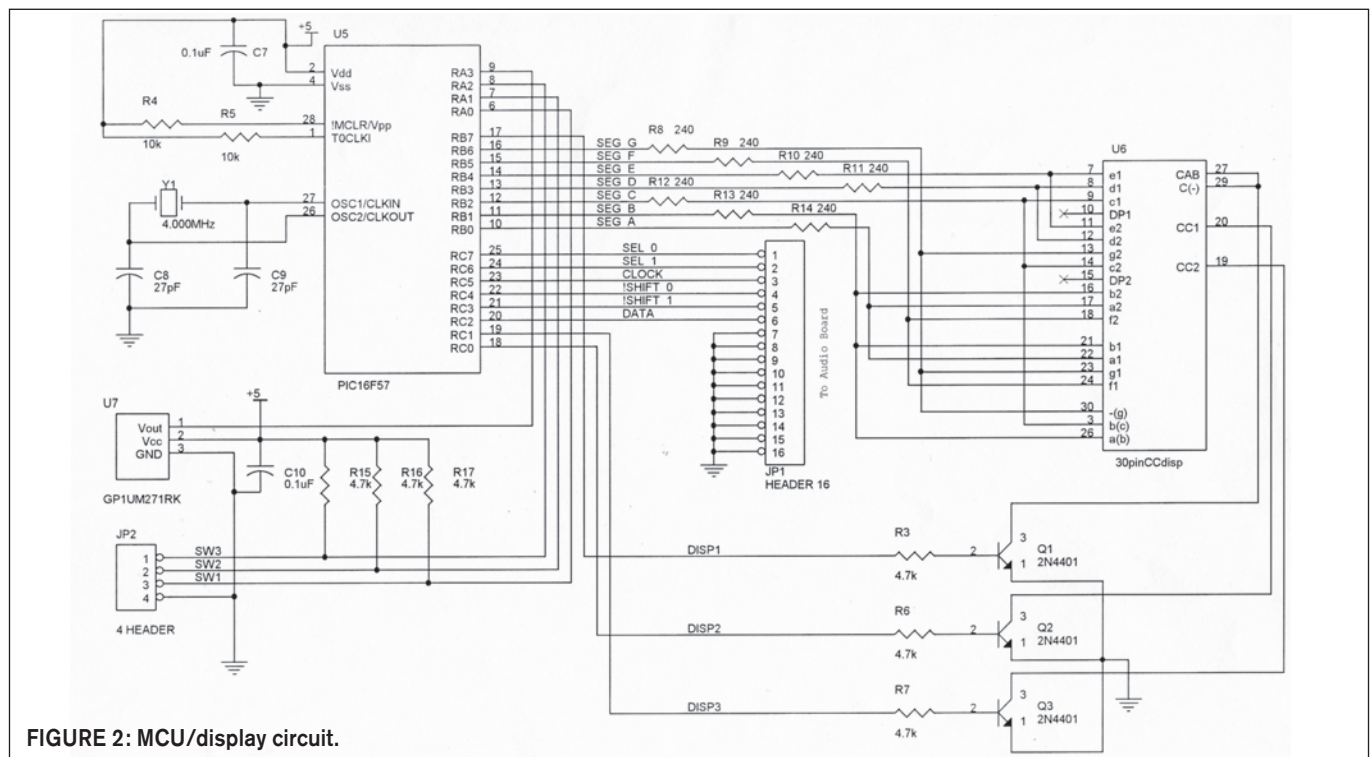


FIGURE 2: MCU/display circuit.

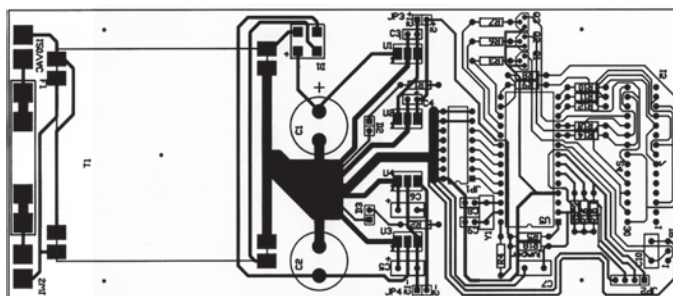


FIGURE 3: Component placement.

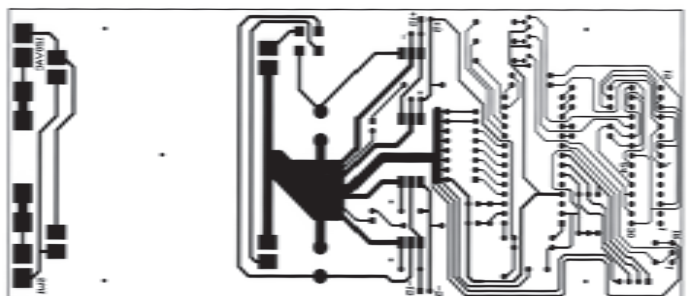


FIGURE 4: Printed circuit layout.

the six channels by the program, because each attenuator channel is individually addressable.

The outputs of the attenuators are buffered using LF347B bi-FET op amps. You may substitute more specialized devices; however, FET inputs are necessary to maintain clickless operation. The 100Ω series resistors prevent signal degradation when driving higher capacitance audio cables.

The purpose of op amp U5 is to sum the subwoofer channel with the main channels. Again, this has been done to suit a specific application (and admittedly a preference). You may modify the design to provide a dedicated subwoofer output if so desired.

The audio board is a double-sided PCB in which the top layer is designed primarily as ground plane. This feature, along

PARTS LIST

Power Supply/Microcontroller Board

Ref.	Value	Manufacturer	Digikey.com #
C1, 2	2700µF 35V	Panasonic	P11247-ND
C3-6	2.2µF tan	Kemet	399-3550-ND
C7, 10	0.1µF	Panasonic	P4593-ND
C8, 9	27pF	BC Components	1430PH-ND
D1	RB154, 1.5A 400V	Bridge	RB154MS-ND
D2	Red LED	Generic	
D3	Green LED	Generic	
F1	0.25A slow	Generic	
JP1	Header 16	16-pin IC socket	ED3116-ND
JP2	4 header	Generic	
JP3, 4	Header 2	Generic	
J1	120V AC	Generic	
Q1-3	2N4401	Fairchild	2N4401-ND
R1, 2	1k	Yageo	1.00KXBK-ND
R3, 6, 7, 15-17	4.7k	Yageo	4.75KXBK-ND
R4, 5	10k	Yageo	10.0KXBK-ND
R8-14	240	Yageo	240XBK-ND
S1	SW-339	CW	SW339-ND
T1	70054	Talema	TE70054-ND
U1	LM7815	National Semi	LM340T-15-ND
U2	LM7805	National Semi	LM7805CTFS-ND
U3	LM7915	National Semi	LM7915CT-ND
U4	LM7905	National Semi	LM7905CTFS-ND
U5	PIC16F57	Microchip	PIC16F57-I/P-ND
U6	30 pin CC disp	Stanley	404-1131-ND, 404-1136-ND
U7	GP1UM271RK	Sharp	425-1139-ND
Y1	4.000MHz	Abrakon	535-9057-ND

Preamp audio board

Ref.	Value	Manufacturer	Digikey.com #
C1-3, 5, 11-14, 21, 22, 27-30, 35-38, 43, 44	0.1µF	Panasonic	P4593-ND
C4, 10, 15, 20	10pF	BC Components	1426PH-ND
C6-9, 16-19, 23-26, 31-34, 39-42	10µF	BC Components	4211PHCT-ND
C45-48	2.2µF tan	Kemet	399-3550-ND
JP1	Header 16	16-pin DIP socket	ED3116-ND
JP2-15	4 header	Generic	
R1-3, 5, 6, 12-15, 17	100k	Yageo	100KXBK-ND
R4, 16, 28, 29, 35	100	Yageo	100XBK-ND
R7-11, 18-27, 30-34, 36-41	10k	Yageo	10.0KXBK-ND
U1	74LS00	TI	296-1626-5-ND
U2	74LS139	TI	DM74LS139-ND
U3-5	LF347B	TI	LF347B-ND
U6, 8-10, 12	SSM2404	Analog Devices	SSM2404P-ND
U7, 11	LM1973	National Semi	LM1973-ND

Miscellaneous

Item	Value	Manufacturer	Digikey.com #
Rack chassis	RMC19038, RMP1908	Hammond	HM738-ND, RMP1908-ND
LED Bezel		PRD	PRD180R-ND, PRD180B-ND
Selector switches (3)		E-switch	EG2041-ND
RCA connectors (25)		Switchcraft	SC1134-ND, SC1146-ND, SC1147-ND
30-pin display socket		MILLMAX	ED58427-ND
16-pin DIP cable		CW	C6PPG-1606M-ND

MCap® RXF Radial Xtra Flat Capacitor

NEW! MCap® RXF Oil

Featuring the ultimate winding geometry (edgewise) for

- extremely short, low-loss signal transmission,
- extremely reduced residual-resistance (ESR),
- remarkable low residual-inductivity (ESL).

Polypropylene capacitor-foil, alu metallized.

Grouted winding against microphonic effects.

- Fit-In-Adaptors now available.



TubeCap® - Optimized
High Voltage MKP



Audiophile Resitors



Silver/Gold
Internal Wirings



MSolder™ Silver/Gold
MSolder™ Supreme

MCap® Supreme



THE LATEST
MCap® Supreme Oil and
Supreme Silver/Gold/Oil

MCap® Supreme
MCap® Supreme Silver/Oil
MCap® Supreme Silver/Gold



Varied Foil Coils & Air Core Coils

Recommended US Dealer
MADISOUND SPEAKER COMPONENTS
www.madisound.com
Exclusive Canadian Distributor
AUDIO INC.
www.audiyo.com

See more audio innovations on
www.mundorf.com
and subscribe for our newsletter
info@mundorf.com
OEM and dealer inquiries invited



MUNDORF®

High End Components Made In Germany Since 1985

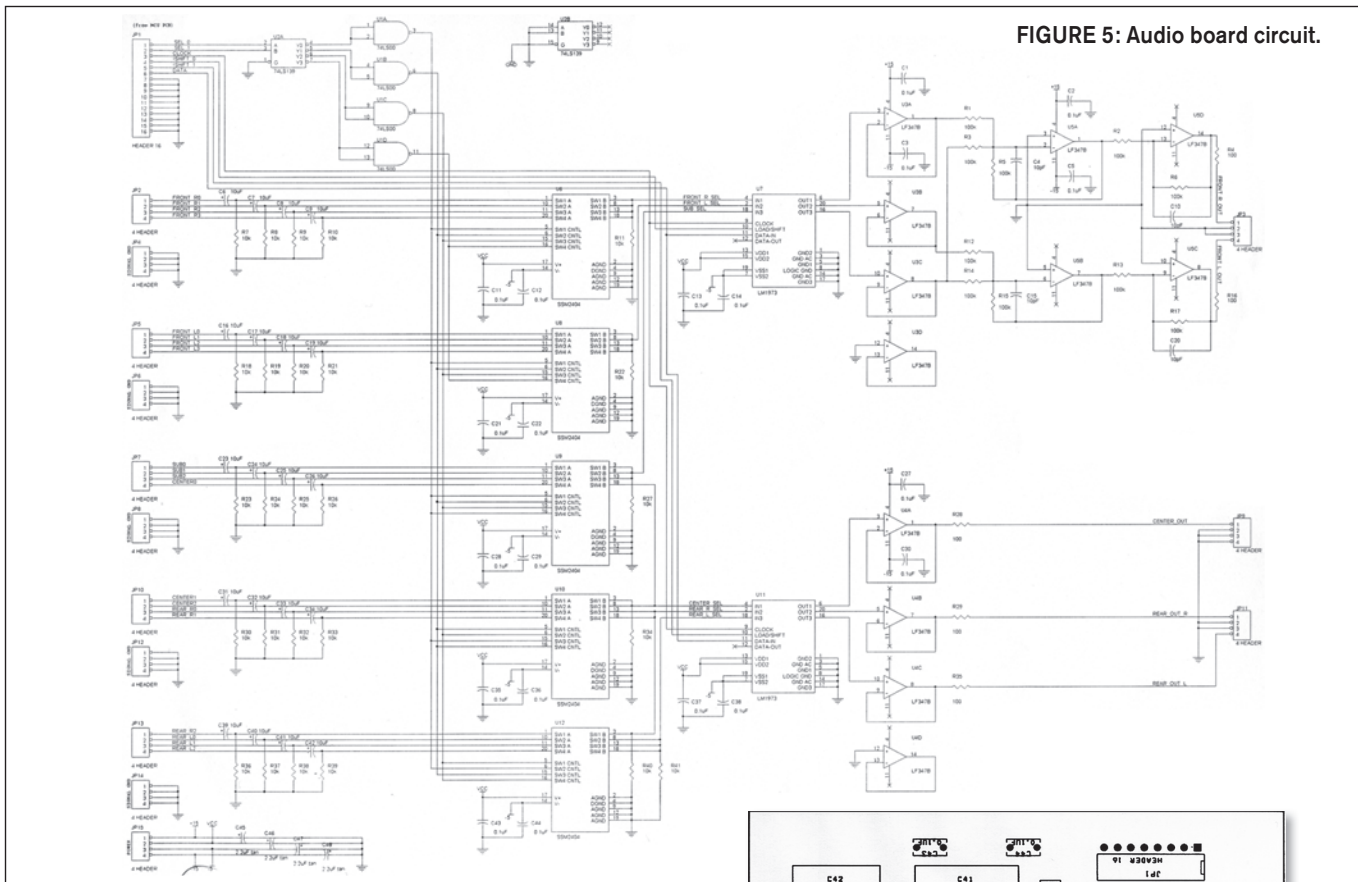


FIGURE 5: Audio board circuit.

with generous power supply bypass capacitors, helps ensure good electrical performance. The layout is available in **Figs. 6 and 7** (top and bottom side, respectively). The component layout is shown in **Fig. 8**.

The PCB has been designed

without any vias, such that all front-back connections are made with only component leads. Hint: I achieve better results drilling from the bottom (main routing) side of the PCB. This reduces the chance of damaging a pad-trace connection due to drill bit deflec-

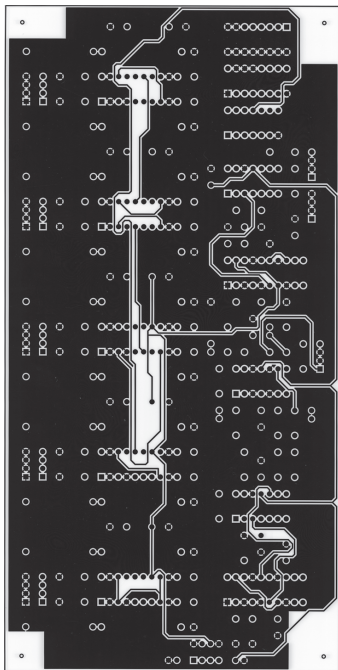


FIGURE 6: Audio board—top.

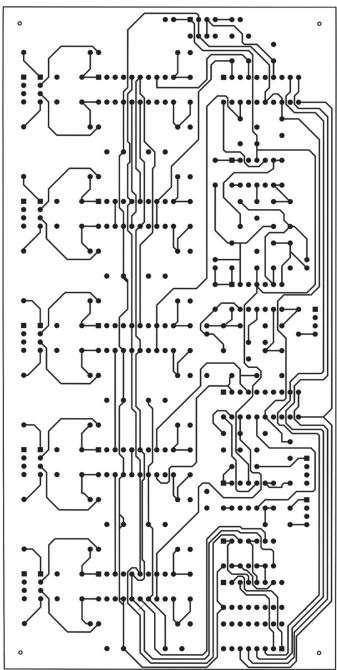


FIGURE 7: Audio board—bottom.

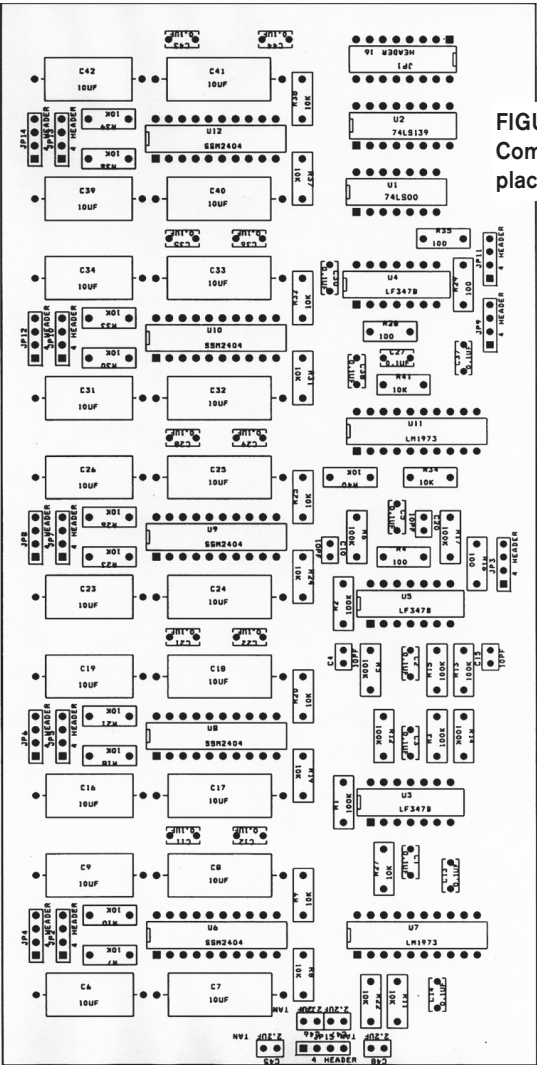


FIGURE 8: Component placement.

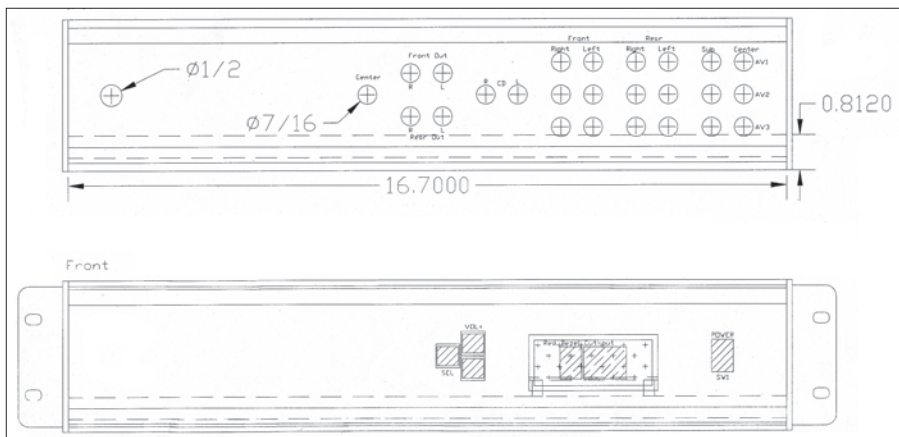


FIGURE 9: Template for front and back panels (45%).

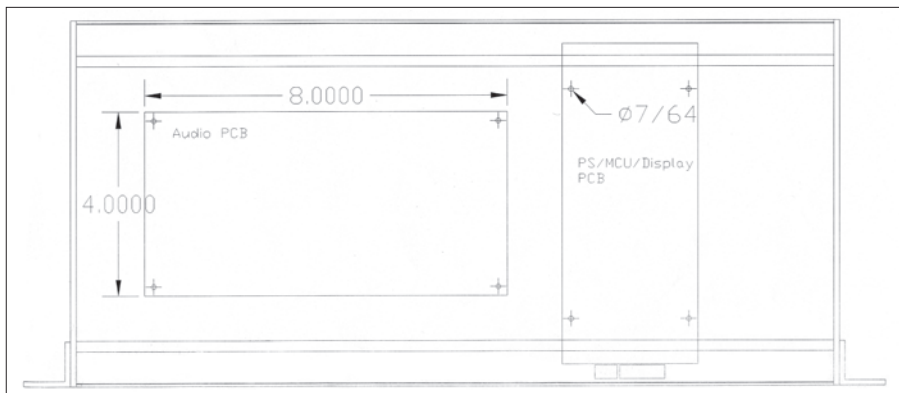


FIGURE 10: Top view template (43%).

tion or positioning error.

THE CHASSIS

The preamp was fabricated in a Hammond RMC19038 19" × 8" rack cabinet. I mounted the circuit boards on an optional RMC1908 chassis panel using 1/4" × 1/4" nylon spacers and 4-40 hardware.

I used an inkjet plotter to produce the [reduced as indicated] CAD drill-

ing templates (Figs. 9 and 10). Once you cut these to size and affix them to the proper surface, you can use them to locate the drilled holes for the RCA connectors, PCB mounting holes, switch cutouts, and so on. Cut the display openings using a nibble tool and some patience. Use draw filing to clean the edges after using the nibble device.

FINAL WIRING AND TESTING

During assembly, I first verified the testing of the power supply, display, and remote functions by using a simpler version of the final program and then installed the audio board. After wiring the power supply, DIP ribbon cable, and RCA connectors, I applied power without any ICs inserted into the sockets. Voltage and logic levels were verified for each of the functions prior to installing all ICs.

The power supply and input/output connections were made using 26 GA twisted-pairs to reduce any crosstalk. You could also use shielded audio cable; however, it proved too difficult to manage so many I/Os in a limited space.

The ground plane of the PCB is connected to the power through redundant wires in the ribbon cable between the two boards. As best practice, I purposely made the ground connection much shorter than other power supply connections. Also note: Each RCA connector is connected separately to the ground plane of the PCB to minimize the production of ground loops. Finally, to complete the testing, inject a 1kHz, 2V peak sine wave with a waveform generator and verify the proper outputs and levels with an oscilloscope.

The preamp described here has worked flawlessly for many hours of use since I installed it into my system. It is the link that integrates a multi-amplifier, home-grown audio system with the latest sources without necessitating the purchase of an expensive home theater preamp. *ax*



VACUUM TUBES, INC.

1080 Sligh Blvd

Orlando, FL 32806

Phone/Fax (407)481-9994

Email: jim@vacuumtubesinc.com



"Celebrating our 10th year in the tube business"

Decent NOS tubes without the hype - over 250,000 tubes in stock

Matching available - Good US and Western European brands available

Check out our website - www.vacuumtubesinc.com