

A Wide-Range Audio Sweep Oscillator

Build this versatile DIY oscillator.

By Dennis Colin

This oscillator unit is capable of 0.5Hz-30kHz in one exponential (1 octave/volt) sweep and provides sine and cosine outputs (90° quadrature) with THD low enough ($\approx 0.1\%$) for frequency response measurements and audible distortion evaluation.

ADDITIONAL FEATURES

1. THD is mostly 2nd and 3rd harmonic (inaudible).
2. Linear and exponential frequency control (and modulation) inputs respond cleanly with fractional-cycle response time.
3. Linear (sawtooth) sweep generator provides constant octave/second sweep $\pm 1\%$, 20Hz-20kHz.
4. Warble (FM) generator with 0.2-10Hz rate and 0 to ± 1 octave frequency deviation.
5. Stable amplitude and frequency.

OUTPUTS

Figure 1 shows the sine and cosine outputs (Fig. 1A), and their precise 90° relationship (Fig. 1B). Figure 4 shows how controlled distortion can be introduced by self-modulation (auto-FM).

CONSTRUCTION

Photos 1-3 show the unit in an 8" x 6" x

FIGURE 1A: Oscillator outputs, 1kHz.


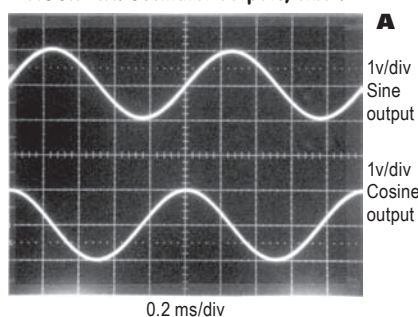


FIGURE 1B: $\tau = \sin(2\pi \times 1000\text{Hz} \times t)$
 $x = \cos(2\pi \times 1000\text{Hz} \times t)$
 $\text{radius} = \sqrt{(x^2 + y^2)} = 1$
 constant radius = circle; scope spot revolves with constant speed

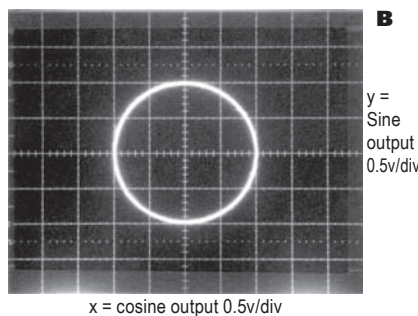

3" plastic Radio Shack project box. The circuitry (not shown) is on three solderless breadboards containing the oscillator and auxiliary functions. Also included (not essential to the features listed) are a sweep-position meter, sweep/manual

switch, $\frac{1}{3}$ octave step switch, 10-turn fine-tune pot, and Ni-Cd batteries (not used in 13 years).

OSCILLATOR CIRCUIT

The oscillator (Fig. 2) is basically a state-variable filter (biquad) using the method I described in a 1971 Audio Engineering Society paper ("A Combination—Filter"). The "filter" is made to oscillate by having controlled positive feedback (instead of the usual negative) around the (as a filter) bandpass loop. This positive FB initially gives the "filter" a "negative Q," but is then (quickly) exactly balanced by a variable amount of negative FB, proportional to the square of the output amplitude. Thus, the "Q" is made to effectively "hover at infinity," resulting in stable oscillation.

The active gain-control elements are in T1-3, each a dual "operational transconductance amplifier" (OTA), the Harris CA3280AE¹. Each section consists of an emitter-coupled bipolar diff-amp with current-mirrors, providing a push-pull Class A current source output. The transconductance (ratio of output current to base-to-base input voltage) is varied in proportion to a negative supply-referenced current input, which is "mirrored" to control the input diff-amp's combined emitter current.

PHOTO 1: Front.



PHOTO 2: Right side.



PHOTO 3: Left side.



This control current, called I_{ABC} (Amplifier Bias Current), at pins 3 and 6 (for the two independent sections), can vary the overall transconductance by over a million to one (120dB).

Normally, an emitter-coupled bipolar transistor has a nonlinear (hyperbolic tangent) and temperature-dependent transfer curve, its "S" shape similar to the transfer of a cathode-coupled ("long-tailed pair") tube stage. However, current applied to pins 1 and 8 (the two sections) biases on a pair of back-to-back "predistortion diodes," whose transfer curve and temperature dependence are inverse to those of the diff-amp (if the differential voltage inputs are sourced through a high resistance compared to 52mV/diode bias current). Then the overall transfer is very linear and temperature stable.

CIRCUIT OPERATION

OTA units T1-A and T1-B control the gains of integrators U1-D and U1-C, cascaded in a feedback loop. The polar-

ity appears negative, but is made positive at the oscillation frequency with unity gain by the -180° phase shift of the two cascaded integrators. The feedback is through R5 to T1-A pin 16.

In a perfect world this alone would generate a stable oscillation. But in the real world, stability must be enforced—humanity needs police, and oscillators need stabilizers (as do airplanes—they definitely don't want *them* to oscillate!).

STABILIZATION LOOP

Here's where things become interesting. Oscillators have used the variable resistance of light bulbs (slow response) or FETs, or diodes (distortion). I use T3-A, another OTA, to control negative FB around the first integrator (U1-D). A small amount of positive FB (to get things going at turn-on) is applied through R7 to T3-A pin 13 (remember that it has a current-source output, so a signal current can be summed into it to add to its load voltage).

Negative (damping, or in this case,


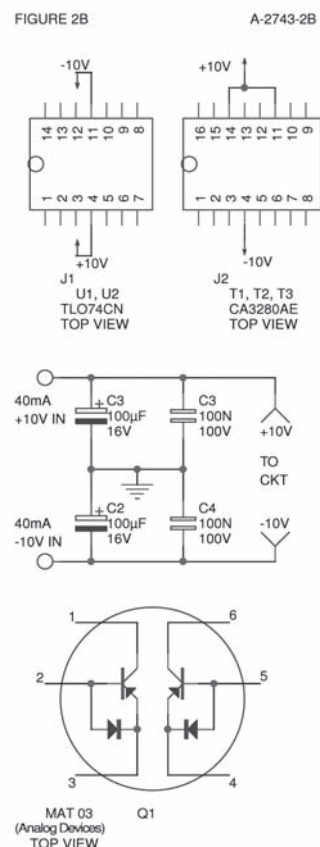


FIGURE 2: Oscillator schematic.

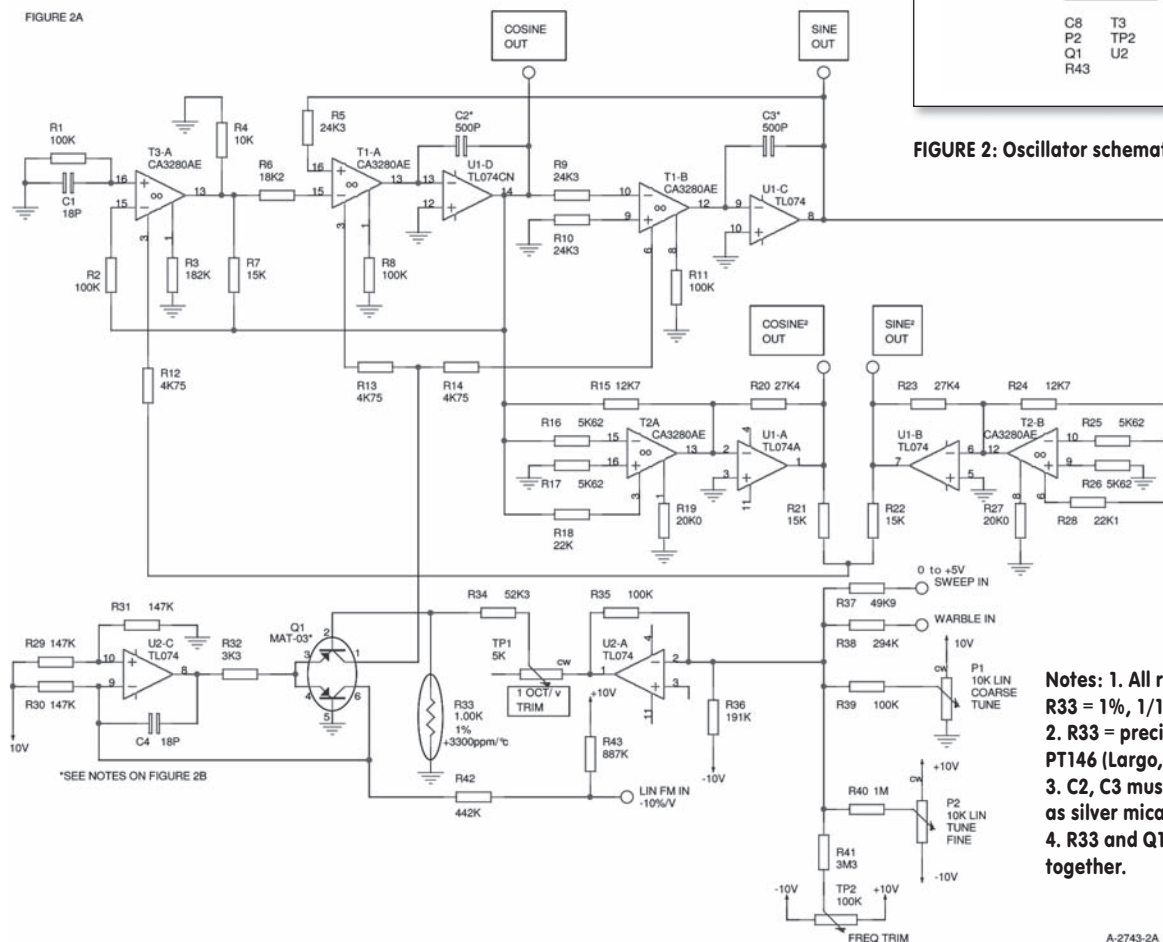

- Notes: 1. All resistors except R33 = 1%, 1/10W or more.
 2. R33 = precision resistor co. PT146 (Largo, Florida).
 3. C2, C3 must be high Q, such as silver mica (not ceramic).
 4. R33 and Q1 should be glued together.

growth-limiting) FB is controlled with the I_{ABC} input (pin 3) of T3-A. But how is the signal amplitude determined? Oscillators (the ones having a feedback-control element) often use a signal “envelope follower” such as a diode-capacitor peak detector. But their output ripple must be strongly lowpass-filtered to avoid modulation distortion introduced by the FB-controlling element. The required ripple filtering makes the amplitude-stabilizing response very slow, and its time lag can even make the loop unstable.

In this oscillator, the presence of 90° shifted sine and cosine outputs virtually “shouts out” a solution: Those who didn’t sleep through high school trigonometry might remember that the sum of a sine squared plus a cosine squared (if of the same amplitude and the same angle or time function) equals one (unity, or in this case, pure DC).

I use T2-A/U1-A and T2-B/U1-B as analog multipliers to square the cosine and sine outputs, respectively. Summing these squared outputs yields a signal (current in this case, feeding T3-A pin 3,

the NFB control input) that is 1) virtually ripple-free DC, and 2) proportional to the square of the signal amplitude. The constant radius (circle) in **Fig. 1B** demonstrates the trigonometric relationship, discovered by Pythagoras in ancient Greece.

It works very well: Upon power turn-on, the oscillator “warms up” (stabilizes) in a few cycles’ time. Once stabilized, the frequency can be square-wave modulated even from 20Hz to 20kHz, within a fraction of a cycle, without any transient “hiccupping,” and so on. The output amplitudes are about 1V RMS.

Note that the outputs of U1-A and U1-B provide, respectively, cosine squared and sine squared signals. These form a 180°-shifted pair of mostly double the oscillator frequency (with a small amount of its fundamental due to unavoidable imbalances), riding on a DC offset due to the squaring function.

OUTPUT LEVEL CONTROL

The sine and/or cosine outputs can drive a 10k to 100k log pot, with a knob that can be calibrated in V RMS, dBu, and so


on. I use a dual stereo 10k pot to equally attenuate the two outputs (quadrature stereo drive is described later in “oscillator applications,” no. 3).

EXPONENTIAL FREQUENCY CONTROL

In the lower left area of **Fig. 2A**, a matched PNP pair (Q1) is used to precisely implement the well-known exponential relation between a bipolar transistor’s collector current and base-emitter voltage. Through feedback, U2-C holds the current through the lower Q1 transistor constant, providing a 1st-order VBE matching reference for the upper transistor. The latter is fed, at its base, an attenuated and temperature-compensated (by R33) frequency-control voltage, proportional to the voltages summed by U2-A.

The exponential (uniform octave; doubling per summed control volt) output current from the upper Q1 unit is divided equally by R13, R14 to control, by means of T1-A and T1-B, the gains of integrators U1-D and U1-C. The oscillation frequency is proportional to

FIGURE 3: Sweep and warble generators.

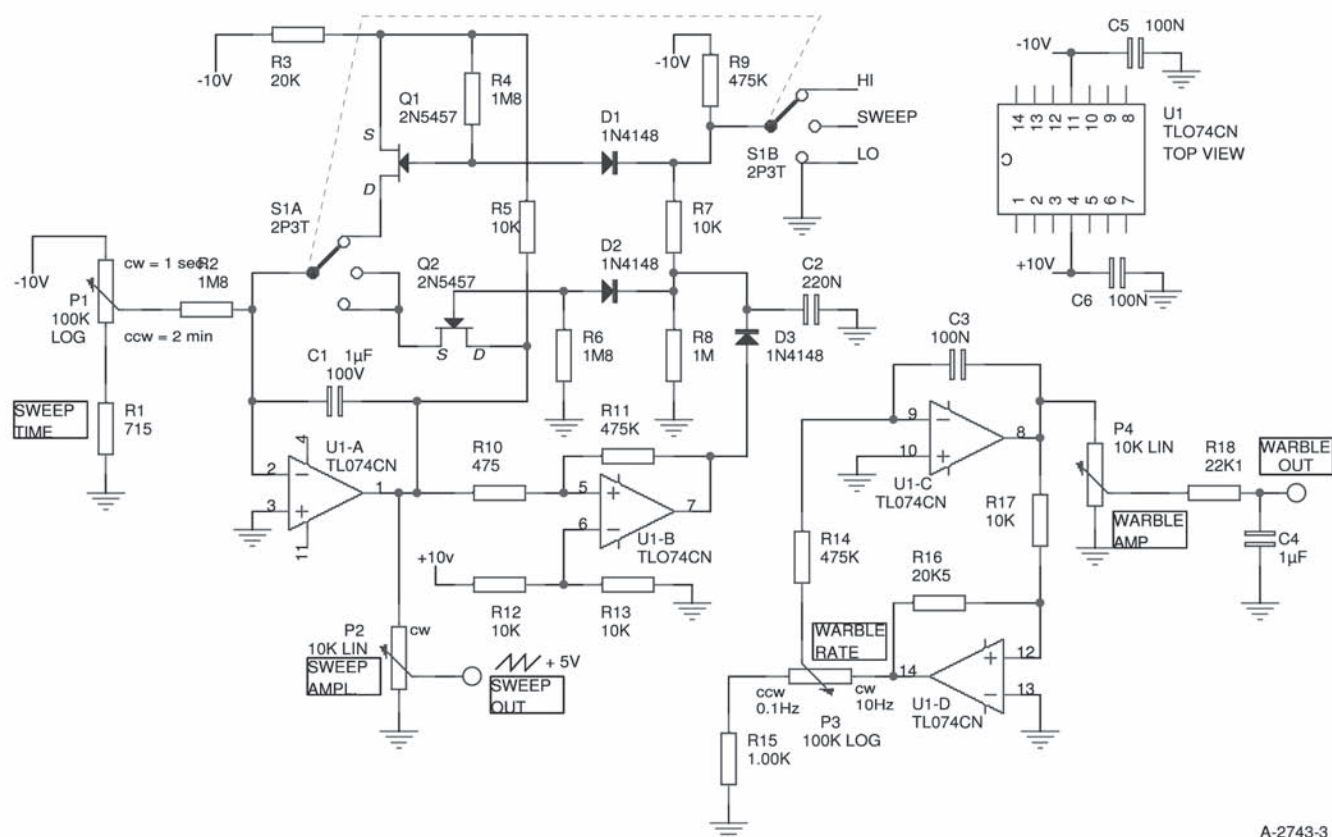

A-2743-3

the Q1 output current, and therefore is exponentially related to the summed frequency control voltages.

The 1 octave/volt scale factor has a nonlinear deviation of $\pm 3\%$, from 0.4Hz to 25kHz, a range of 16 octaves. The unit, if pushed, can sweep from 0.3Hz to 50kHz. Temperature drift is about $0.2\%/^{\circ}\text{C}$, meaning a temperature change of 30°C (54°F) causes a change of 6%, about one semitone (the 12th root of 2 = 1.059463094).

LINEAR FREQUENCY CONTROL

Applied through R42, a voltage applied here varies the collector current of the lower unit of Q1, the exponential generator's reference current. **Note:** For the best temperature stability, you should mount R33 next to Q1, preferably epoxied or glued together.

SWEEP GENERATOR

This provides a linear sawtooth ramp of zero to +5V, which when fed to the oscillator's sweep input (its R37) sweeps it 10 octaves, e.g., from 20Hz to 20kHz. In **Fig. 3**, U1-A is an integrator (with C1) which is fed an adjustable DC current from P1 and R2. In the center ("sweep") position of S1, the output of U1-A linearly rises from zero until it reaches +5V. Then, U1-B, a comparator with small positive FB (R10, 11) and biased to +5V (R12, R13), switches its output from about -9V to about +9V.

This turns on FET Q2, which quickly discharges C1, resetting the output of U1-A back to zero, and the cycle repeats.

With S1 in the "Lo" position, Q2 is held on, keeping U1-A output at zero, which keeps the oscillator frequency at its lowest frequency that was swept.

With S1 in the "HI" position, FET Q1 is switched across C1 through R3, R5. This keeps the output of U1-A at +5V, keeping the oscillator frequency at its highest frequency that was swept.

WARBLE GENERATOR

U1-C and U1-D make up the common triangle/square oscillator, with a range (selected by P3) of 0.1 to 10Hz. The triangle output (about $\pm 4.4\text{V}$) is adjustably attenuated by P4. The lowpass filter (R18, C4) rounds the triangle-wave peaks so that the waveform approaches

a sinusoidal shape above around 5Hz (a typically useful and musically pleasing vibrato rate).

In practice, I've found this variable (with warble rate) wave shaping to be very practical: at low rates—for example, 1Hz—the triangle shape provides a linear (on a per octave basis) up and down sweep, useful for listening to speaker response variations, standing waves, and so on. But for smoothed response RTA measurements (and listening), rates around 5Hz 1) sound musically pleasing, and 2) provide nice measurement smoothing when the oscillator's frequency deviation is $\frac{1}{6}$ or $\frac{1}{3}$ octave peak-to-peak, adjustable with P4.

OSCILLATOR APPLICATIONS

The THD of about 0.1% disqualifies it for distortion measurements. But the pure Class A analog methodology produces a "tube like" spectrum, mostly 2nd and 3rd harmonics. By all accounts this is inaudible, so the oscillator is perfectly acceptable for auditory evaluations and response measurements.

1. RTA (Real Time Analysis) Measurements

Using a sweep oscillator to display frequency response can produce accurate results, but there are two drawbacks. First, a log converter (linear voltage to dB) is needed, along with an X-Y storage scope or chart recorder. This is virtually obsolete and cumbersome compared to computer programs such as Mlssa, Clio, and so on. Second, for speaker responses, in-room measurements without software "windowing" are strongly influenced by room acoustics; furthermore, a flat in-room response is undesirable because narrowing speaker dispersion and increasing room absorption at high frequencies reduce integrated response, whereas (except in the bass) you judge spectral balance primarily on the speaker's direct, "first arrival" signal.

However, *listening* to a swept response, or a fixed center frequency with warble, is very revealing of standing wave patterns and speaker anomalies.

I'd like to mention that you can use a sound level meter close to a speaker (say 1m) and obtain a reasonable measurement. However, the popular Radio Shack 33-2055 meter has a broad 8dB

peak around 6kHz and a rapid rolloff above 12kHz. This meter (in "C" weighting) is flat within $\pm 1\text{dB}$ only from 60Hz to 1.6kHz. The Panasonic WM-60AY mike capsule, such as is used in *Speaker Builder's* "Mitey Mike," is very flat over the entire audio range. (See my article "A Purist Recording Mixer," *aX* Feb. '06 and "Mitey Mike II," *SB* 4/97.)

FREQUENCY TRIMMING

1. Connect either the sine or cosine output to a frequency counter. Set P1 (coarse tune) and P2 (fine tune) to approximately center. Connect a DC voltmeter to the output of U2-1 (pin 1), negative meter lead grounded.
2. Turn on the $\pm 10\text{V}$ power supply. The counter should show some midrange frequency (between 200Hz-2kHz). If not, something is wired wrong. If or when it oscillates, proceed.
3. Adjust the coarse- and fine-tune pots to obtain zero volts $\pm 0.01\text{V}$ at U2-1 pin 1.
4. Allow at least five minutes to stabilize warm-up drift. Then record the frequency.
5. Adjust the coarse- and fine-tune pots (clockwise initially) to obtain negative $2.00\text{V} \pm 0.01\text{V}$ at U2-1 pin 1.
6. Adjust TP1 (1 octave/V trim) to obtain a frequency that's four times that recorded in step 4, as closely as is practical.
7. Remove the DC voltmeter positive lead from U2-1 pin 1, and connect it to the wiper of P2 (fine tune).
8. Adjust P2 for zero volts $\pm 0.1\text{V}$ at the wiper.
9. Set P1 (coarse tune) fully CCW.
10. Adjust TP2 (frequency trim) for 20Hz, or any other sweep-starting frequency of your choice.
11. Set P1 (coarse tune) fully CW. The frequency should be close to 20kHz, or 1000 times the lowest frequency selected in step 10.
12. You can perform back-and-forth fine tuning of TP1 and TP2 to obtain more precision if needed.

2. Listening Tests

A pure sine wave, useful for amplifier tests and speaker power handling, and so on, sounds perfectly boring. However, things change radically when the tone is frequency modulated (FM, warble) at, say, a 3Hz rate with a deviation of 1 octave p-p. On good headphones, or listening right next to a good speaker, you simply hear the tone quickly sweep up and down with constant loudness.

But with a colored (resonant) speaker, or a good speaker in a room with overly live acoustics, the resonances and/or standing waves “pile up” at some swept frequency spots and cancel at others. The resulting sound is “choppy”; moreover, turning your head or moving about changes the “choppy” patterns. Sometimes you can hear all kinds of strange effects coming from different directions, similar to “The Sound Strobe” (aX, March '06).

3. Bass/Midrange In-Room Measurements and Listening Tests

At these frequencies where the aforementioned dispersion-narrowing and room absorption effects aren't significant, in-room listening and SPL measurements can be representative of musical playback sound quality.

To evaluate a two-channel stereo system, it's desirable to have both speakers driven. However, a mono-center signal will have a 6dB increase relative to one speaker driven (if the room and locations of the speakers and listener are reasonably symmetrical) in the bass. This is because the long wavelengths add pressure-wise (analogous to voltage) in phase. On the other hand, higher frequencies, with much shorter wavelengths, will add (or cancel) due to left/right phase randomness (unless everything is absolutely symmetrical, which is impossible except for one ear exactly centered).

This is where the 90° (quadrature) feature of the sine/cosine outputs solves the problem. Using these two outputs as a stereo pair, even the lowest bass sound sources have a relative 90° phase shift. This makes the stereo pair add up to only a 3dB increase over one speaker driven, equal to the average random power (not pressure) addition that unavoidable asymmetry imposes on

the higher frequencies.

4. Self-Modulation (Auto FM) For Controlled Distortion


Figure 4 shows interesting examples of “auto FM” waveshaping, sometimes used for tone generation in synthesizers. Here, the sine output was connected (in **Fig. 4B** and **4C**) to a frequency control input with 2 octave/V sensitivity (R37 labeled “sweep in” in **Fig. 2A**).

In **Fig. 4A** with no modulation (for reference), the frequency is 85Hz. Note that the X-Y (Lissajous) plot is not only a circle, but it's of uniform brightness, because the oscilloscope spot is revolving (counterclockwise) at a constant speed, 85 times per second (5100 RPM).

In **Fig. 4B**, note that the output ex-

cursion is $\pm 0.5V$, meaning that the “instantaneous frequency” is modulated up and down one octave. The actual (or “average”) frequency has dropped to 74.4Hz because of the “time stretched” negative waveform portion. A mechanical analogy: Driving 30 miles at 30mph obviously takes one hour. But suppose you drive the first half (15mi.) at 15mph (an “octave lower” speed), taking one hour, and then try to make up for lost time (obviously you can't; you've already used up the hour) by increasing your speed to an “octave higher” than the original 30mph; that is, to 60mph. The second 15 miles then takes a quarter hour, so the total trip time is 1.25 hours. Your “average frequency” (speed) is 24mph, a reduction of 20%; not the

Continues on p. 49

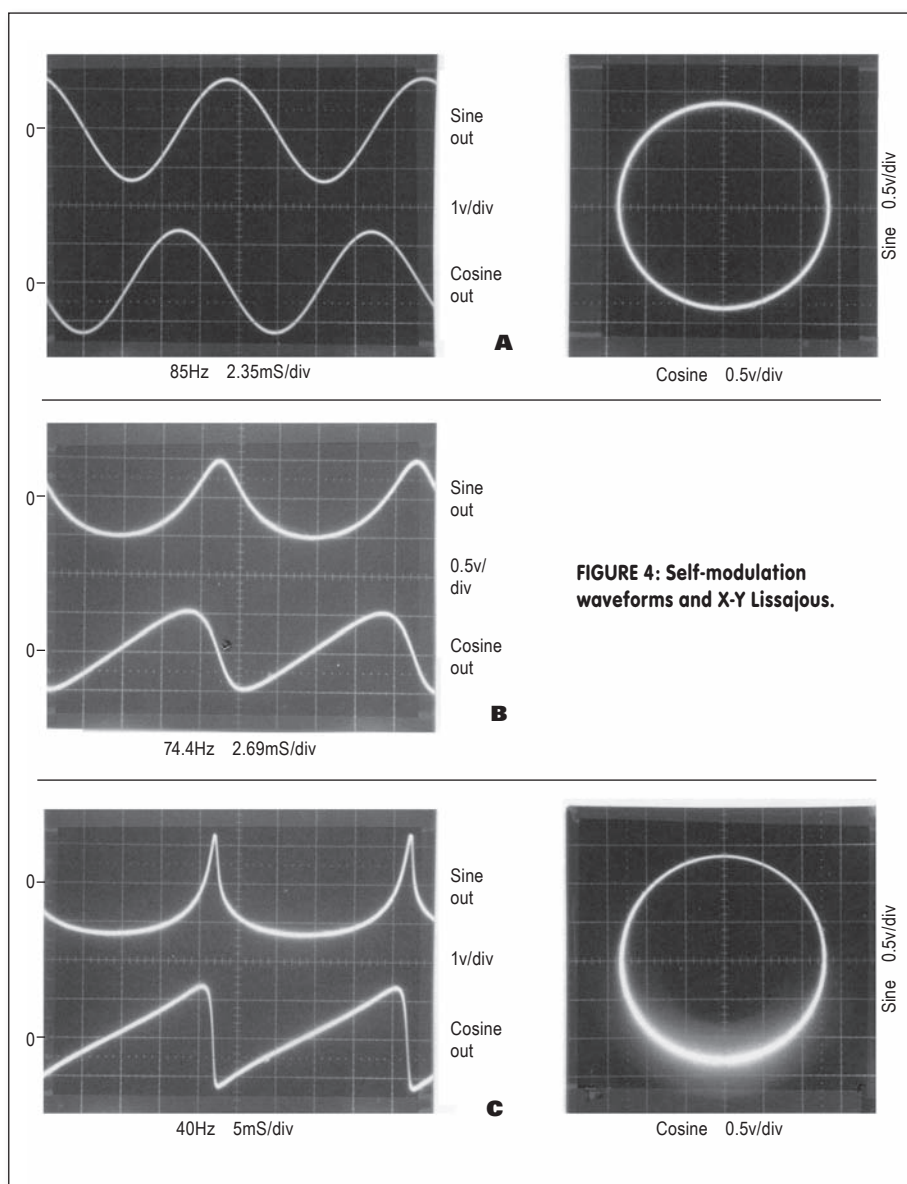

From p. 30

same as trying to average the 15mph and 60mph (which would erroneously give 37.5mph). With an auto-modulated exponential frequency versus voltage oscillator, the mechanism is more complicated than in the analogy, because nonlinear time-varying feedback is involved.

Figure 4C is a more extreme example; the waveform's $\pm 1.3V$ excursions generate ± 2.6 octave modulation peaks. This modulates the average 40Hz frequency (reduced as explained) for an "instantaneous frequency" excursion range of 6.6Hz to 242.5Hz, reflected in the "cuspy" shape of the (normally) sine output. There are several fascinating features of this result:

- The X-Y plot is still circular (meaning that the relative phases of fundamental and all harmonics in the two outputs are 90° ; the two output waveforms are mutual Hilbert transforms).
- The circle's brightness varies, being brightest at the bottom. This is because the "sine" output (vertical axis) spends a relatively long time at a negative voltage. Thus the scope spot revolves at an uneven ("jerky") speed, slowest at the bottom. Looks like an annular² solar eclipse, where the moon is farther away than normal from the earth, so its image is too small to completely cover the sun.
- The "sine" output has a negative DC offset ($-0.92V$); the AC component is 0.58V RMS; total AC + DC = 1.09V RMS.
- The "sine" output approaches a "tapered impulse" wave, while the "cosine" output approaches a linear sawtooth.
- The two outputs have identical harmonic amplitude spectra, and sound nearly identical, except on headphones or with very phase-coherent speakers in a dry-acoustic room. Hard to believe, but it's true.

For less extreme FM excursions, the harmonic spectrum is low-order, resembling (and sounding like) single-ended triode tube distortion; note the "sine" output in **Fig. 4B**. This provides a method of simulating various amounts of tube-like distortion for auditory evalua-

tions. At various frequencies, adjusting a pot (100k or so) between either oscillator output and the (normally connected to) warble input allows you to determine your distortion audibility threshold (for smooth tube-like distortion) by monitoring the output on a distortion meter or spectrum analyzer.

Table 1 is the parts list for the oscillator, while **Table 2** lists the parts for the

sweep and warble generators. A regulated $\pm 10V$ supply is required; current draw is about $\pm 40mA$. **ax**

REFERENCES

- originally designed by RCA.
- Not a misspelling of "annual." Means "ring-like."

TABLE 1

Reference	Description	Manufacturer	P/N	Distributor	P/N
C1, C2	cap, 18pF	Analog Devices Precision Resistor Co.	MAT-03 PT146	Digi-Key Largo, Fla.	EF1104
C2, 3	cap, 500pF mica				
C7, 8	cap, 100nF 100V				
C5, 6	cap, 100μF 16V				
P1, 2	pot, 10k Lin				
Q1	matched PNP				
R33	Res, 1k, +3500ppm/°C				
R32	Res, 1%, 1/8W, 3k32				
R12-14	Res, 1%, 4k75				
R16-17, 25-6	Res, 1%, 5K62				
R4	Res, 1%, 10k0				
R15, 24	Res, 1%, 12K7				
R7, 21, 22	Res, 1%, 15K0				
R6	Res, 1%, 18K2				
R19, 27	Res, 1%, 20K0				
R18, 28	Res, 1%, 22K1				
R5, 9, 10	Res, 1%, 24K3				
R20, 23	Res, 1%, 27K4				
R37	Res, 1%, 49K9	Harris	CA3280AE		
R34	Res, 1%, 52K3				
R1, 2, 8, 11, 35, 39	Res, 1%, 1/8W, 100k				
R29-31	Res, 1%, 147K				
R3	Res, 1%, 182K				
R36	Res, 1%, 191K				
R38	Res, 1%, 294K				
R42	Res, 1%, 442K				
R43	887K				
R40	Res, 5%, 1/8W, 1M				
R41	Res, 5%, 3M3				
T1-3	Transconductance Amp				
TP1	Trimpot, 20T, 5K				
TP2	Trimpot, 20T, 100K				
U1, 2	Quad op amp				

TABLE 2

Reference	Description	Manufacturer	P/N	Distributor	P/N
C3	cap, 100nF 100V		1N4148	Digi-Key	EF1104
C2	cap, 220nF 100V			Digi-Key	EF1224
C1, 4	cap, 1 μ F 100V			Digi-Key	EF1105
C5, 6	cap, 100 μ F 16V				
D1-3	diode				
P2, 4	pot, 10k lin				
P1, 3	pot, 100k log				
Q1, 2	JFET, N-channel				
R10	Res, 1%, 1/8W, 475 Ω				
R1	Res, 1%, 715 Ω				
R15	Res, 1%, 1k00				
R5, 7, 12, 13, 17	Ewam 1% m 10k0				
R3	Res, 1%, 20k0				
R16	Res, 1%, 20k5				
R18	Res, 1%, 22k1				
R9, 11, 14	Res, 1%, 475K				
R8	Res, 5%, 1/8W, 1M				
R2, 4, 6	Res, 5%, 1M8				
S1	Switch, DPDT				
U1	Quad op amp		TL074Cn		