



An Audio Isolation Box

This simple transformer-coupled unit allows you to send line-level audio 100' away, while isolating AC line ground-loop pickup by over 120dB. Audiophile quality is maintained.

By Dennis Colin

My wife wanted to make CD copies on her computer of LPs and tapes, whose players were about 70' from the computer. A direct cable feed caused audible 60Hz hum. A 2.4GHz wireless A/V link (Radio Shack, about \$100) was noisy at that distance. I quickly dismissed the idea of floating the AC line safety ground at one end as dangerous.

The unit I describe here uses a stereo pair of Hammond 850H audio line transformers, rightly described as broadcast quality: electrostatically shielded, hum-bucking windings, rugged metal case, 4Hz –90kHz BW at –1dB, < 2% THD at 20Hz at 2V RMS (0dB full-scale Red Book CD standard), probably less than 0.01% THD at normal line levels.

CONSTRUCTION

Photos 1–5 show the unit, built in an aluminum Hammond 1590S box, 4.35" × 3.21" × 1.57", Digi-Key P/N HM158.

The output RCA jacks must either be of ground-insulating type or floated from the metal box. I did this by punching four 3/4" holes in the box with a Greenlee chassis punch ("knock out punch unit," model 730BB-3/4), then epoxying a strip of 1/8" hardwood inside, covering the holes. Then I drilled 1/4" holes in the wood, centered in the 3/4" box holes, and mounted the RCA jacks. Before mounting the wood strip I painted it with enamel to prevent moisture absorption electrical leakage. As a testament to the box's overall insulation including the transformers, the input/output leakage resistance is 4000MΩ.

The input/output ground (cable shield) capacitance coupling is 436pF, which at 60Hz is a 6MΩ impedance. Therefore, even in the unlikely (and dangerous!) event that the audio equip-

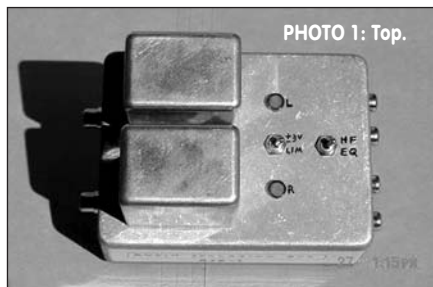


PHOTO 1: Top.

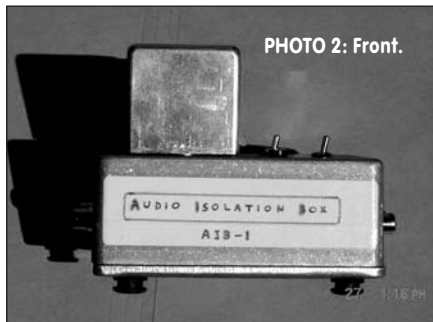


PHOTO 2: Front.

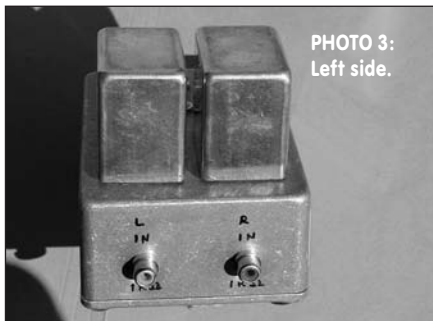


PHOTO 3: Left side.



PHOTO 4: Right side.

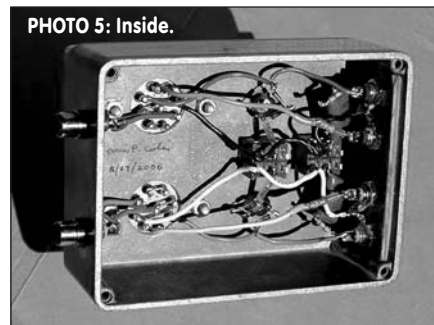


PHOTO 5: Inside.

ment being driven has its "ground" shorted to the hot 120V AC line, the 60Hz leakage current through the box would be only 20μA, not even enough to feel a tingle.

SAFETY WARNING: VERY IMPORTANT—Before you contact both source and receiving setup cables simultaneously (yes, people have been electrocuted by "only" 120V!), please measure the AC voltage between those two cable shields! If all is well, it shouldn't be more than 5V, the maximum drop expected between line grounds at opposite ends of a house.

My house originally had the safety "ground" of an outside outlet connected

to the hot 120V by some "electrician"—I discovered this when some contractors were using the outlet for some equipment, when someone started yelling about shocks! Thankfully, he lived—of course, I should have checked the wiring when moving in. I promptly had it fixed and tested it (and all the other outlets, inside and out). Whew!

I recommend reading Charles Hansen's excellent articles about the AC power grid and safety in this magazine. The reason I'm emphasizing this is that the box described here isolates two audio systems' (supposed) AC line grounds, and that it's all too easy to take "only 120V" for granted. OK, enough preaching.

SCHEMATIC

The transformers (**Fig. 1**) have a nominal stated impedance of 1200 to 600Ω, but will provide this 2:1 impedance transformation (1 to 0.707 voltage step-down) over a wide range of source and

load impedances. Most CD, SACD, and so on, players have a 1k Ω output impedance, which is optimum for the Hammond 850H units (T1, T2). The 3dB voltage reduction (I measured 3.25dB) is easily accommodated by preamps, power amps, and audio/video A/D converters used for computer disc recording.

Two stereo pairs of box ground-isolated RCA jack outputs are provided. J3 and J4 are the cable-driving outputs, while J5 and J6 are 300 Ω headphone-


monitoring outputs.

HIGH FREQUENCY EQUALIZER

With no load, or up to 100' of cable driving hi-Z loads, the transformers have a "ringing" resonance at between 200kHz (no load) and about 50kHz (driving 100' of Alpha 2466C twin-insulated pair cable). Source impedances below 1k Ω (such as headphone outputs) exacerbate this resonance. The resonance is between transformer leakage inductance and load capacitance

(the windings' shunt C as a minimum).

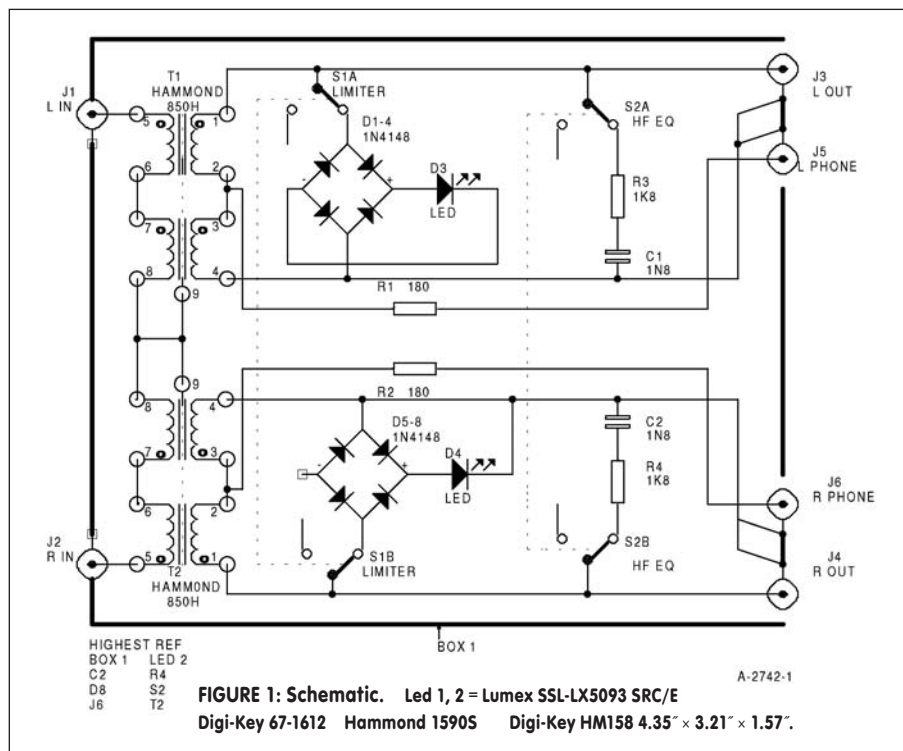While the resonance frequency is ultrasonic, SACDs can have content up to 100kHz, and vinyl records can also have ultrasonic content. R3/C1 and R4/C2, when switched on by S2 ("HF EQ"), form a resonance damping network.



The Woofer Tester 2

The most useful tool for building loudspeaker systems.

- Measures all Thiele/Small parameters including Rem/Xem Erm, Exm, Krm, Kxm
- Built-in Closed and Vented Box Simulator
- Fast, Accurate and Easy to Use
- R L C meter from 1 Hz to 20 kHz
- Accurate to .001 Hz
- Self-powered from a PC's USB port
- Line-out Signal Generator
- Export to BassBox 6 Pro
- Tune Sealed and Vented Box Systems
- Windows 98, ME, XP and 2000
- Save, Load and Print Results

Discounts bundled with BassBox
We have high-power subwoofer drivers



Smith and Larson Audio

www.woofertester.com

Email sales@woofertester.com

design enclosures

BassBox Pro

still only **\$129** plus S&H

Includes the world's largest driver database.

Accurate and fast software for Microsoft Windows.

HARRISTECH

P.O. Box 622
Edwardsburg, MI 49112-0622 U.S.A.

Tel: 269-641-5924
sales@ht-audio.com

For more information go to:
www.ht-audio.com

Create professional speaker designs quickly, easily and accurately. Includes user-friendly features like "Welcome" windows, "balloon" help, detailed on-screen manuals with tutorials, beautifully illustrated printed manuals and a huge driver database.

design crossovers

Xover Pro

still only **\$99** plus S&H

Includes the best printed manuals & help.

Design sophisticated closed, vented, bandpass and passive radiator speaker boxes for any space: car, truck, van, home hi-fi, home theater, pro sound, studio, stage, PA, outdoor, and musical instruments. Import the measured acoustic response to simulate the in-room and in-car response.

- 22 box shapes • view 10 designs at the same time •
- "expert" mode • advanced vent calculation • include leakage losses with any box type • 9 performance graphs • design "wizard" • analyze parameters.

Design 2-way and 3-way passive crossover networks, separate high-pass, band-pass and low-pass filters, impedance equalization, L-pads and series / parallel notch filters. Its Thiele-Small model produces professional results without complex driver testing.

- 1st, 2nd, 3rd and 4th-orders • "ladder" filter circuits • parallel crossover circuits • many filter slopes • full manual control • estimate ESR and DCR • 4 graphs • schematics.

Copyright © 2006 by Harris Technologies, Inc. All rights reserved worldwide. BassBox is a trademark of Harris Tech. Other trademarks belong to their respective companies. Harris Tech reserves the right to make changes without notice. All prices are in U.S. dollars.

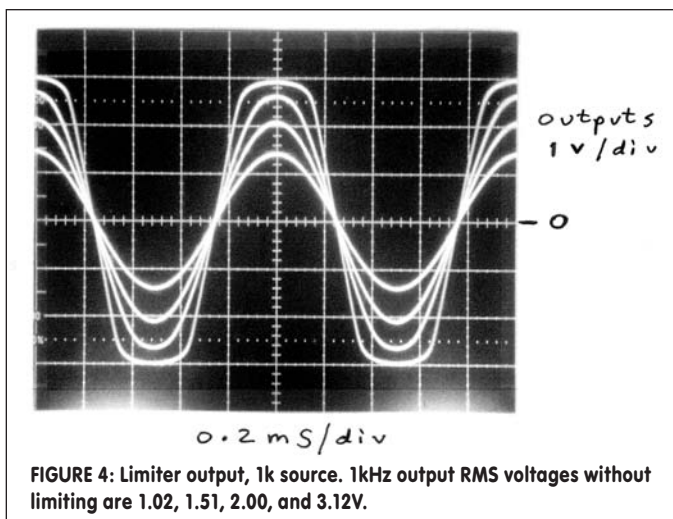
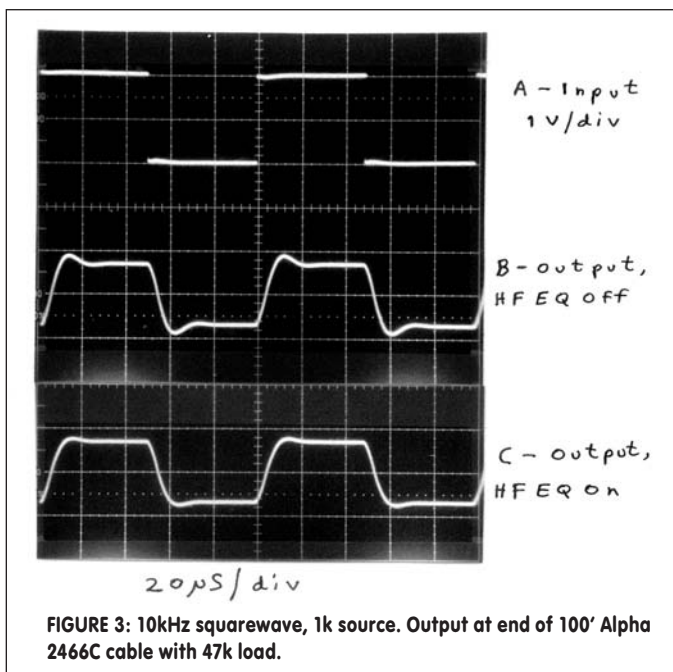
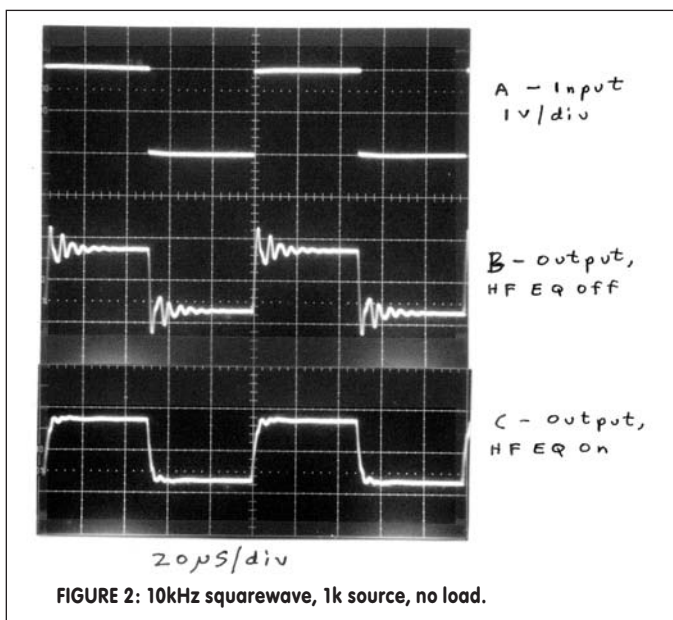


Figure 2 shows 10kHz squarewave responses with 1k source and no load, with (2C) and without (2B) the HF EQ.

The reason for including switch S2 is that depending on cable and load, there might be enough HF damping to not need the EQ.

Figure 3 shows the outputs at the end of 100' of Alpha 2466C cable (5.35nF capacitance) terminated in a 47kΩ resistive load. With HF EQ on (**Fig. 3C**) the overall frequency response reaches a "peak" (insignificant) of 0.07dB at 10kHz, and is -0.03dB at 20kHz. Above this the response monotonically falls (no peaks or dips) to -3.2dB at 50kHz, and -31dB at 250kHz. The latter provides good rejection of AM radio interference and the digital noise surrounding computers.

PEAK LIMITER

You do not want to ever overload the input to an A/D converter preceding a digital recording setup. Even momentary peak "digital clipping" produces a broken-glass-sounding "crunchy splash" of musically irritating wideband IM transients.

The Red Book CD standard defines 0dBFS (full scale) as 2V RMS for a sinusoidal peak, meaning a maximum peak voltage excursion of ±2.83V. Several CD/SACD players I've measured can output peaks (with some recordings) reaching about ±3.5V.

The -3dB voltage stepdown of this isolation box provides additional margin. Just in case (e.g., driving the box from a headphone output, or a phono preamp or tape recorder), switch S1 enables a diode bridge/LED peak limiter. The specified LEDs have a low drop (1.70V at 5mA) and high brightness, visible even with 0.1mA.

Figure 4 shows the limiting characteristic, which limits very smoothly, producing low-order odd harmonics similar to a push-pull tube amp without feedback. Much, much better than "digital clipping!"

MEASUREMENT SUMMARY

Table 1 shows data on the isolation box alone, **Table 2** is with the box driving 100' at Alpha 2466C cable, and **Table 3** shows characteristics of the cable. Parts cost for the isolation box is about \$220.

CABLE DATA

I purchased a 100' spool of Alpha 2466C SL 005 (SL for slate color) cable from Digi-Key, P/N A131-100, for \$43.52. It has two individually shielded pairs of 22-gauge conductors, plus an overall shield. I think the three shields are in contact, but I connected them and one conductor of each pair together. At each end I connected a red (right) and green (left) RCA stereo pair of plugs. The green plugs (Digi-Key CP-1452) connect to the cable's green wire (hot) and white wire plus all three shields (plug shell); the red plugs (Digi-Key CP-1448) connect to the cable's red wire (hot) and black wire plus three shields (plug shell).

This provides a nice convenient thin and flexible 100' stereo RCA cable, easy to use and roll up when not in use (wives don't like leaving long cables all over the floor, but

neither do I after having tripped on it).

Figure 5 shows 200' of this cable (left plus right looped back) responding to a 100kHz squarewave. At the cable input, you can see the delayed reflection (in phase with open load, **Fig. 5A**; out of phase cancellation with shorted load, **Fig. 5C**). **Figure 6** shows a time-expanded view of the cable's delayed and HF-attenuated response.

You may take such waveforms for granted, but **Fig. 6** shows a signal traveling at 449 million mph, which is 67% of the speed of light. Needless to say, with 100' of this cable having a delay of 0.3% of a 20kHz cycle period (1° of linear phase shift), there are no "wavelength effects" to influence sound quality! (Of course, you could spend \$30,000 for 100' of "audiophile interconnect.")

LOW FREQUENCY PERFORMANCE

With a 1kΩ source, the 850H transformer has an LF (-3dB) point of 1.7Hz, and is down only 0.32dB at 20Hz. But I wanted to determine its 20Hz signal-handling ability. Ham-

mond states +15dBm as maximum power, which is 4.36V RMS across 600Ω; I'm using the "600Ω nominal" winding as the output secondary. Hammond states 1.5% THD at 20Hz, +15dBm.

But that's with the windings each seeing their nominal impedances for source and load, equivalent to driving the 1200Ω winding (used here as primary) from a 600Ω source with no load, as far as magnetizing current distortion is concerned (more on this follows).

With my 1kΩ source/47kΩ load testing, the nonlinear magnetizing current will produce more distortion of the signal voltage. **Figure 7** shows 20Hz sine response. In **Fig. 8**, a 20Hz squarewave is used. **Figure 8A**, with an input of ±1V peak (1V RMS for a squarewave), shows only a slight tilt due to phase shift from the 1.7Hz 3dB rolloff.

But in **Fig. 8B** I increased the driving amplitude until core saturation became evident. The output, at each squarewave jump, starts with a large, fast overshoot, as the core "snaps" out of saturation from the previous half-cycle.

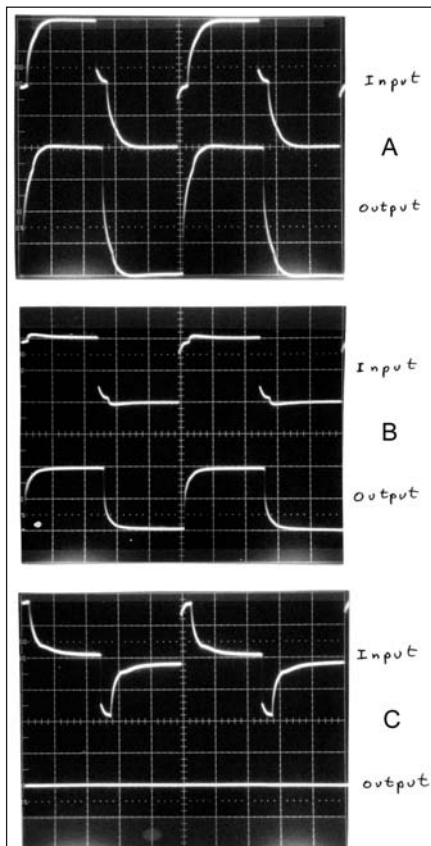


FIGURE 5: 200' Alpha 2466 cable, 100kHz squarewave from 50Ω source. 1V/div, 2μS/div.

TABLE 1: AIB-1 MEASUREMENTS.

In/out ground isolation: 126dB at 60Hz, 76dB at 20kHz
in/out ground coupling: 436pF, 4000MΩ
AC line pickup, 12" from an 80W power supply:
1.8μV RMS = -113dBu = -121dBFS (0dBFS = 2V RMS)
impedance stepdown ratio = 2:1
voltage transformation ratio = 0.688 = -3.25dB
insertion loss re stepdown ratio = 0.24dB
frequency response, 1kΩ source, 47kΩ load, HF EQ on:
-0.32dB at 20Hz, + 0.08dB at 20kHz
-1dB at 4Hz, 90kHz
-3dB at 1.7Hz, 150kHz
maximum input (2% THD): 2.0V RMS at 20Hz, 10V RMS at 100Hz
THD at 0dBu (0.775V RMS) input:
0.3% at 20Hz; approximately 0.01%, 100Hz - 20kHz


TABLE 2: AIB-1 DRIVING 100' OF ALPHA 2466C SL005 CABLE.

HF response w/47k//100pF load, 1k source to AIB-1:
+0.6dB at 20kHz (HF EQ off)
-0.03dB at 20kHz, -3dB at 48kHz (HF EQ on)

TABLE 3: CHARACTERISTICS OF 100' ALPHA 2466C SL005 CABLE.

(2 pair, shielded individually and overall; between one #22 conductor and other one connected to shield)
DCR: 1.61Ω (conductor), 1.57Ω (shield)
C = 5.35nF
L = 12.6μH round trip, measured at 50kHz
Zo (characteristic impedance) = 48.5Ω at 50kHz
fo (quarter-wave resonance) = 1.348MHz
propagation velocity = 67% speed of light

Test Equipment Depot

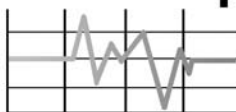

800.996.3837

The source for premium electronic testing equipment

New & Pre-Owned

- Oscilloscopes
- Power Supplies
- Spectrum Analyzers
- Signal Generators
- Digital Multimeters
- Network Analyzers
- Function Generators
- Impedance Analyzers
- Frequency Counters
- Audio Analyzers



Call now to speak to one of our knowledgeable salespeople or browse our extensive online catalog

www.testequipmentdepot.com

• Sales • Repair & Calibration • Rental • Leases • Buy Surplus

Then it maintains the desired 10V level for about 10mS, followed by saturation, gradual at first, then complete just before the next jump. At this point, the magnetic flux can't continue increasing (as needed to maintain an induced voltage) so the voltage collapses to zero.

The product of voltage and time duration is a constant for a given number of turns on an iron core; in this case that saturation constant is about 100 millivolt-seconds.

HYSTERESIS LOOP (B-H CURVE)

I saved the most interesting waveshapes for dessert (**Fig. 9**). "H" symbolizes magnetic driving force (magnetization), analogous to voltage or water pressure. It's proportional to current times the number of winding turns (ampere turns).

Iron atoms have an organized elec-

tron-spin effect, making the atoms microscopic magnets. In unmagnetized iron, the atoms are randomly oriented, so the individual magnetic fields cancel, averaging out to zero. But an applied external magnetic field makes these tiny magnets tend to align. In "hard" steel, they stay aligned after the external force is removed. This is called "remanence" (for "remaining") and is used in permanent magnets.

But in "soft" iron used for transformer cores, remanence is undesirable, causing energy to be wasted overcoming this magnetic "stickiness."

"B" symbolizes magnetic flux, analogous to electric current or water flow rate. In iron, and other magnetic materials, the permeability (ratio of flux to magnetic force, or B/H) is greater than that of a vacuum or air (defined as permeability = 1). This is because an

external magnetic field starts aligning the tiny iron atom magnets; this alignment increases the overall flux much more (by thousands) than in air. But as the externally applied field is increased, eventually the iron atoms are as aligned as the molecular structure allows; this is saturation. Beyond this point, only the vacuum permeability of 1 can add flux; beyond hard saturation you have an air-core transformer, useless except perhaps at radio frequencies.

Figure 9A shows the test setup for displaying B-H curves. Primary current, which is sensed by R1, is proportional to H, the magnetic driving force. The primary voltage, proportional to the rate of change of flux, could have been sensed, but I used the secondary voltage for two reasons: 1) the primary voltage has an additional component, the drop across its DC resistance, whereas the secondary current

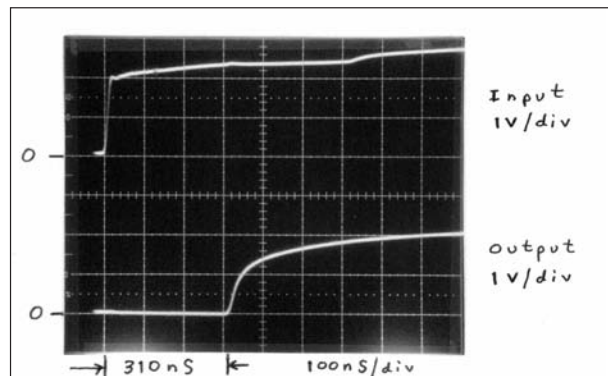


FIGURE 6: 200' Alpha 2466 cable + 5' RG58 C/V cable, 500kHz squarewave from 50Ω source. Cable load = 50Ω. 2466C cable $Z_0 = 48.5\Omega$. BW (-3dB) = 1.2MHz.

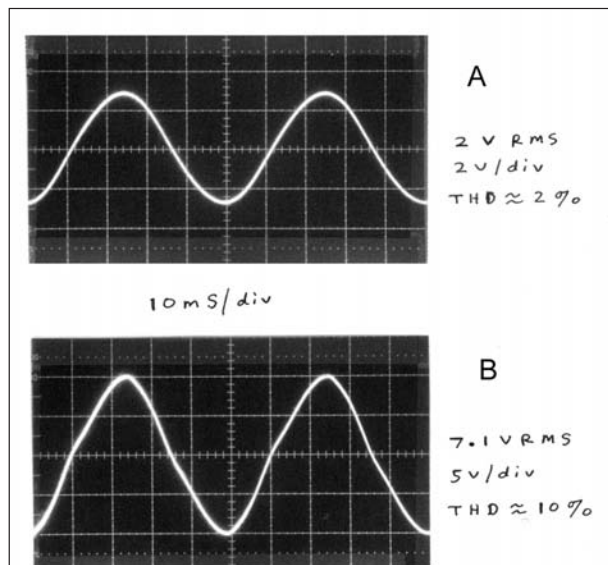


FIGURE 7: 20Hz output, 1kΩ sine wave source, 47kΩ load.

auricap
High Resolution
7.0r 10% 200V
Made in U.S.A.

Precision Wound-High Resolution Capacitors

Made in U.S.A.

**Top Performance
among exotic
capacitors at
reasonable
OEM prices**

*"Auricaps are precision-wound
in the US, and are considered
by many to be the finest
capacitors available."*

Stereophile - June '06 - Peter Breuninger

**OEM & dealer inquiries invited.
Call (800) 565-4390
www.audience-av.com**

**ELECTRA-PRINT
AUDIO CO.**

AUDIO TRANSFORMERS

- Single Ended
- Push-Pull
- Parafeed
- Cathode Follower
- Interstage
- Line Level Outputs
- Audio Chokes
- Moving Coil
- Step-up/down
- Low level input
- Phase splitting
- Silver windings
- Nickel core designs

POWER TRANSFORMERS

- High Voltage
- Filament
- Filter Chokes

Custom transformers built to your specifications.
Custom Amps and Pre-amps of our design.

Visa, MC & Amex

ELECTRA-PRINT AUDIO COMPANY
4117 Roxanne Dr., Las Vegas, NV 89108
702-396-4909 Fax 702-396-4910
electraaudio@cox.net www.electra-print.com

Because the induced voltage is proportional to the rate of change (time derivative) of flux B, the latter can be obtained by integrating (the inverse of the derivative) the winding voltage. R2 and C1 serve as an integrator. An op amp with feedback cap would form a virtually ideal integrator, but because the

2. The opening, or separation, of the

Fig. 9C shows the B-H curve with only 1V RMS applied, again at 18.9Hz. Here, the curve appears smooth and el-

FIGURE 8: 20Hz output, 1k Ω squarewave source, 47k Ω load.

FIGURE 9: Hammond 850H Primary B-H curves (hysteresis loops).

liptical. At this level, much below saturation, the elliptical shape is probably not from hysteresis, but rather from resistive losses, especially the 10k secondary load. A volt-amp X-Y plot of an ideal inductor would be an ellipse or circle (with equal X-Y excursions).

But here the R2/C1 integrator's 90° shift would cancel that of a pure inductor. However, any resistive losses (core loss, winding resistance, or most likely the secondary R2 load) will cause a net overall (including integrator) phase shift. That the shape of **Fig. 9C** is not due to nonlinearity is supported by the observed low distortion of this trans-

former with 1V RMS applied at 20Hz and 18.9Hz.

Figure 10 shows the locations of parts that I used on the box.

CONCLUSION

Table 4 is the parts list. While describing a simple isolation box, I've taken the liberty of graphically displaying some fundamental physical principles of cables and audio transformers, and also electrical safety regarding AC line grounding imperfections. One or more of these boxes will allow you to use your house as a low-noise recording studio. *ax*

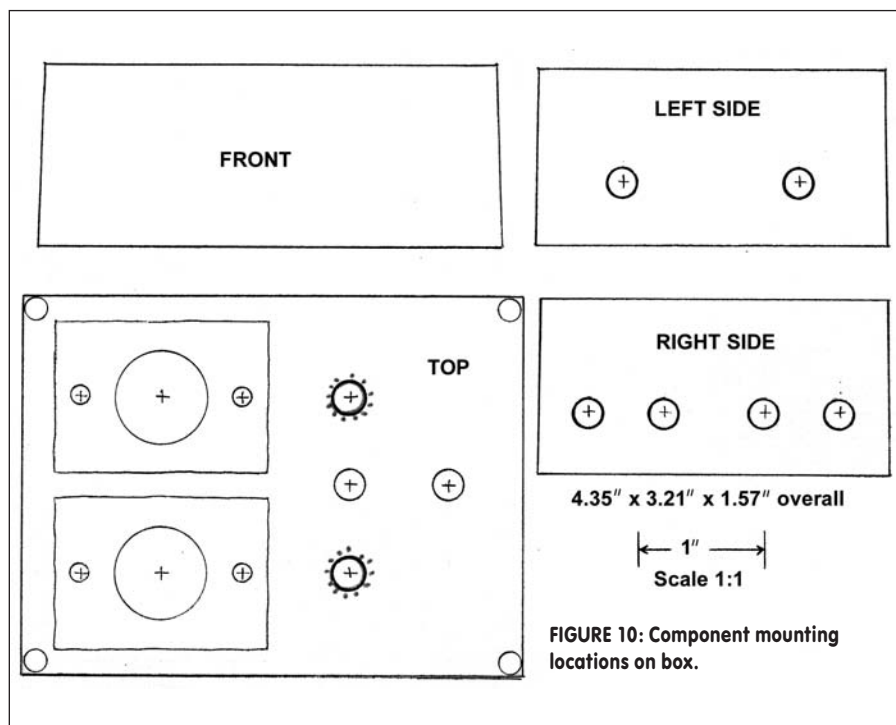


TABLE 4: PARTS LIST.

Ref	Description	Manufacturer	Part#	Distributor	Part#	Price
Box 1	box, 4.35" x 3.21" x 1.57"	Hammond	1590S	Digi-Key	HM158	\$10.88
C1, 2	cap, 1.8nF, 100V			Digi-Key	PS1182J	
D1-8	diode		1N4148			
J1, 3, 5	jack, RCA, green			Digi-Key	CP-1417	
J2, 4, 6	jack, RCA, red			Digi-Key	CP-1413	
LED1, 2	LED, red	Lumex		Digi-Key	67-1612	
R1, 2	Res, 180Ω ¼W					
R3, 4	Res, 1.8k, ¼W					
S1, 2	switch, toggle, DPDT			Digi-Key	360-1156	
T1, 2	transformer, 1.2k-600Ω	Hammond	850H	Spartan*		\$98.77ea
	cable, twin, 100'	Alpha	2466C SL005	Digi-Key	A131-100	\$43.52
	plug, RCA, green (2)			Digi-Key	CP-1452	
	plug, RCA, red (2)			Digi-Key	CP-1448	

* Haverhill, MA (978) 373-1200

Ready, willing and Avel



*offering an extensive
range of ready-to-go
toroidal transformers
to please the ear, but won't
take you for a ride.*

Avel Lindberg Inc.

47 South End Plaza
New Milford, CT 06776
tel: 860-355-4711
fax: 860-354-8597
www.avellindberg.com

www.Alltubetesters.com Tube Tester Repair



Repair, Calibration, Upgrades

- ☞ 35 + years experience
- ☞ All Makes and Models
- ☞ Circuit Upgrades/Improvements
- ☞ Testers sales
- ☞ Technical Support
- ☞ Bogey tubes available
- ☞ New Meters available
- ☞ Tester Refurbishing

6 month limited warranty on all work performed including calibration.

Roger Kennedy
21143 Hawthorne Blvd., #354
Torrance, CA 90503 USA
www.alltubetesters.com
Email: alltubetesters@msn.com
PH: (310) 323-3281