

A Hybrid High-Fidelity Power Amplifier

This patent-pending design features a National Semiconductor IC in a vacuum tube topology.

For years I have thought about building an amplifier with output tubes and transformer driven by a solid-state front end and driver stage. But I put the idea aside because I wanted to use integrated circuit operational amps to avoid the complexity of designing the driver stage with discrete components, and, to my knowledge, there wasn't a suitable IC op amp available. About a year and a half ago, that changed when National Semiconductor introduced the LM4702, a high voltage dual op amp intended for use in high-fidelity amps with solid-state output stages. In the commercial grade you can operate it from a $\pm 75V$ power supply, which is more than adequate for the driver stage of a tube amp.

When the output devices of a class AB power amp are properly biased, there is a small overlap in the signals delivered by these devices. Class AB amps that employ solid-state devices in their output stages generate extremely fast switching transients when one device switches off and the other switches on. Traditionally these transients are nulled out with large amounts of negative feedback.

But this can cause an effect called transient intermodulation distortion. This is because the input stage where the error correction takes place has a difficult time handling the slow rate of these transients. This effect is difficult to measure, but it is audible. It is my opinion that this phenomenon is what makes tube amps sound different from solid-state amps.

CIRCUIT DESIGN

Using the LM4702, I designed a hybrid audio amp that uses a solid-state input and phase-splitting driver stage feeding a push-pull vacuum tube output stage typical of conventional vacuum tube audio amps. The input stage is composed of a non-inverting operational amp that accepts the input signal and negative feedback signal. The driver stage uses the LM4702 with one amp inverting and the other non-inverting, thereby providing the phase-splitting function with sufficient voltage swing needed to drive the control grids of vacuum tubes in a push-pull output stage. The combined gain of the input and driver amps is set to emulate their counterparts in a conventional vacuum tube amp. The gain is set higher than the overall closed loop gain of the amp by a factor determined by the amount of negative feedback that you desire.

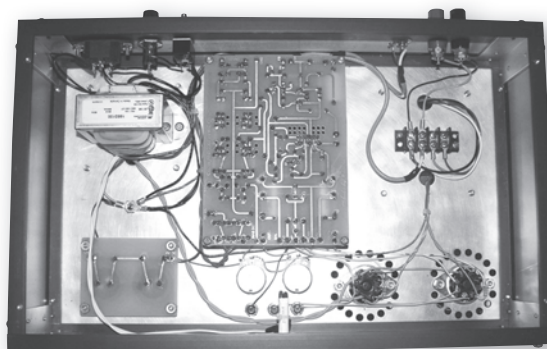


PHOTO 2: Hybrid amplifier chassis wiring.

For the solid-state operational amps I used Burr-Brown's (Texas Instruments) OPA134 for the input stage and National Instruments' LM4702 high voltage dual op amp for the driver stage. You can achieve much lower distortion in the

input and driver stages with these amps than you can typically achieve with input and driver stages using vacuum tubes. This combination takes advantage of the strengths of both technologies.

The basic topology of the hybrid amp is shown in Fig. 1. It is typical of the topology found in many conventional vacuum tube amps, with the exception that the input amp and phase-splitting amps are solid-state. The input is connected to the non-inverting input of op amp U1, and the output of the feedback network of R7 and C3 is connected to the inverting input of U1. Resistors R1 and R2 form a local feedback loop that sets the gain and stabilizes this stage of the amp.

The output of this stage feeds two operational amplifiers U2a and U2b. U2a is configured as an inverting amp with resistors R3 and R4 setting its gain. U2B is configured as a non-inverting amp with resistors R5 and R6 setting its gain. The gains of U2a and U2b are equal in magnitude but opposite in polarity, thereby producing the required phase-splitting function.

The DC voltage of this stage is isolated from the output stage by capacitors C1 and C2. This is necessary because the control grids of the output tubes must be negatively biased with respect to their cathodes. The DC bias network performs this function. The output tubes are connected to the primary winding of the output transformer.

The secondary winding of the transformer is connected to the load and to a feedback network of resistor R7 and

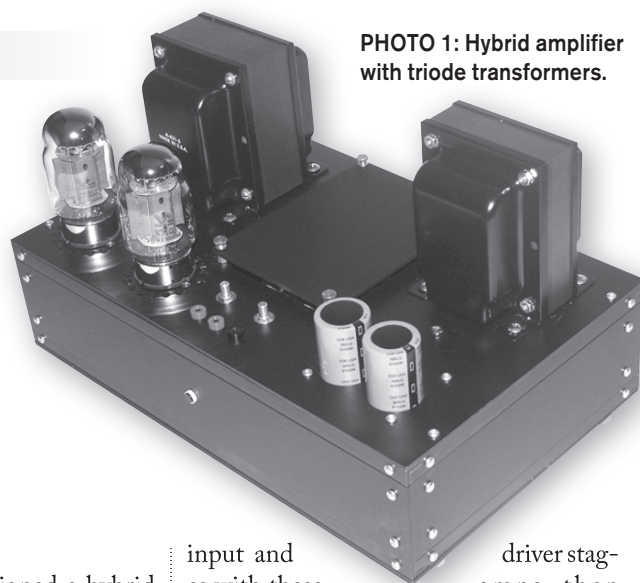


PHOTO 1: Hybrid amplifier with triode transformers.

THREE EXAMPLES

The second is a stereo amp that I built around Acrosound TO-330 output transformers, which I had from amps I built using Eico's HF-60 circuitry. I powered the amp with a Toroid of Maryland Transformer, P/N 326.5072, which was

The only problem these amps have is that the output transformers would be nearly impossible to duplicate. Therefore, I decided to build a third amp using readily available parts—transformers from Triode Electronics that are clones

Combined gain for the input and driver stage is set to 180. The gain of the driver stage is about 32 or 30dB (National Semiconductor specifies a minimum gain of 26dB for stability). The

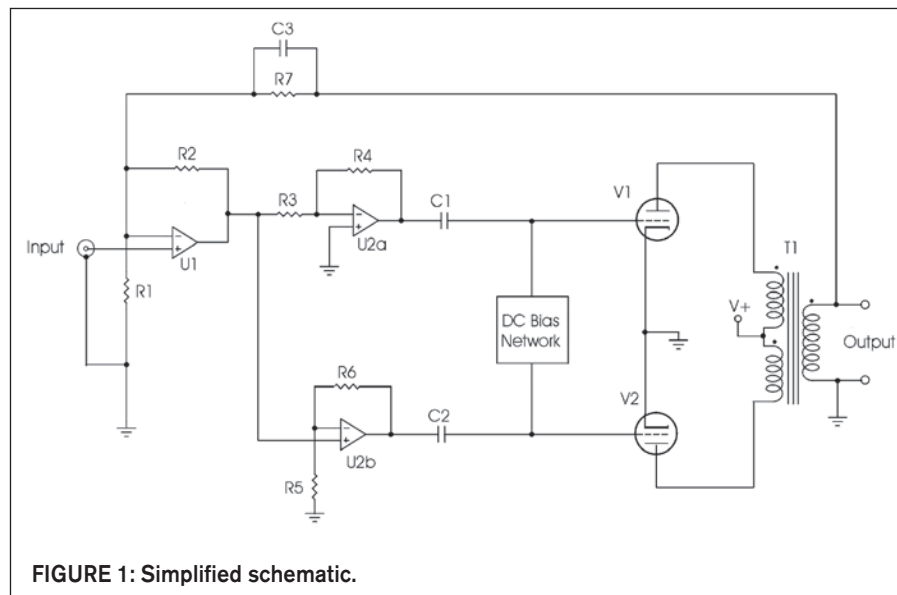


FIGURE 1: Simplified schematic.

Call 1-800-SENCORE
(736-2673)

SENCORE

Function Selection L signal Control R

7 [ETG] ms H 85.5 -40 H -40 0x N

100

15ms A: 100d RT60 0ms

dB

30

0.1 RT 0 0.1ms 6.3 dB 15

CHUM SSRG

Monitor Control Generator Control

SP495

Soundpro
Audio Consultant

Quality • Stability • Total Business Solutions

SENCORE

sales@sencore.com

audioXpress January 2008 **31**

$$VCC+ = 1.25 * (1+R32/R33) + 0.00005*R32$$

Similarly, the voltage from the negative regulator is:

$$VCC- = -1.25 * (1+R40/R39) - 0.00005*R40$$

The large filter capacitors preceding these regulators are necessary to keep ripple voltage low enough to ensure adequate headroom for the regulators.

MECHANICAL ASSEMBLY

I used a 1/8" thick aluminum plate for mounting everything. This is thick enough to drill and tap, which facilitates mounting parts under the transformers. I drilled a ring of ventilation holes around each output tube and cut a large hole in the plate where the main printed circuit is mounted. I mounted the lower voltage power transformer under the main power transformer and a terminal block to select the output impedance of the amp under the output transformer. If you do the same, make sure the screws are flush with the top of the plate before mounting the main power

and output transformers.

I like using dual banana plugs for connecting the speaker to a pair of 5-way binding posts, and using the terminal block to select the output impedance means that I have only two wires going to the back panel. The large hole has two

advantages. First, it allows access to both sides of the PC board, and, second, it allows for ample ventilation.

The PC board is mounted under the hole with spacers, and a cover plate is mounted with spacers above the hole. Mount a smaller PC board containing

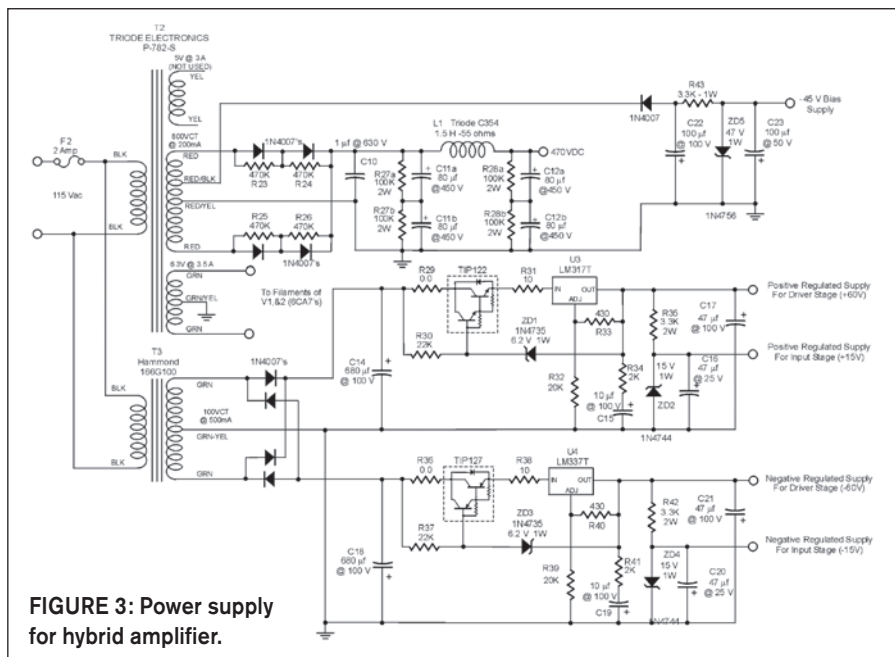


FIGURE 3: Power supply for hybrid amplifier.

AnTek Inc

The Reliable Power Solutions

Rack Mount Chassis

Power Transformers

Tube Amp Chassis

Output Transformers

Quality

Stock



Please visit our web site for more detail

25 Ewing Ave • N. Arlington • NJ 07031 • U. S. A. • Tel: 201-991-3300 • Email: antek1000@yahoo.com • Web: www.antekinc.com

THE audio engineer's hands-on X-over design & speaker voicing tool.

ATTENTION!
Audio professionals, hobbyists, installers
and University students/professors...

The Virtual Crossover BOX™
MODEL VCB-100

by **Vidsonix**
Reschitz-Madison



Shipping Wt:
7 lbs.
K-VCB100
\$249.95

Now includes our exclusive
Crossover Design Pocket
Slide Tool!

Old Colony Sound Laboratory
PO Box 876, Dept. US2
Peterborough, NH 03458-0876 USA
888-924-9465 Fax: 603-924-9467
E-mail: custserv@audioXpress.com

Call 1-888-924-9465
today or order on-line
at www.audioXpress.com!

OLD COLONY SOUND LAB

RAK K DAC
MOORESVILLE

We also design and manufacture home
theater, marine, and professional loud-
speakers and accessories. Individual
drivers, including all Thiele-Small
parameters, are also available on our website.

Vidsonix Design Works
508 Performance Rd., Mooresville, NC 28115
(704)658-9617

More info
at: **www.VIDSONIX.com**
©2008 VIDSONIX. All Rights Reserved

the high voltage filter capacitors in front of the power transformer and also mount a number 8 screw next to it to serve as a connection point for a star ground. All grounds are tied to this point.



You can mount this assembly in either a wood or metal base. A back panel is used for the main power connector, fuse, switch, and input and output connectors. I made the bottom plate out of 1/8" thick aluminum and put holes under the tubes and PC board.

FINAL ASSEMBLY AND ADJUSTMENTS

You should use a socket for the input op amp U1, and you need to solder the LM4702 driver IC directly to the PC board. Fully populate the board with the exception of jumpers J1 and J2 and don't insert the input op amp. This will allow checking out the power supplies without risking damage to the op amps.

With the amp otherwise fully wired and the output tubes not yet inserted,

FIGURE 4: PC board with component layout.

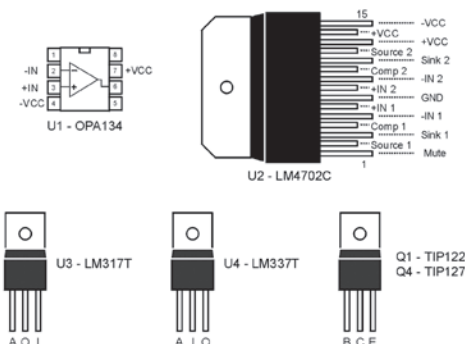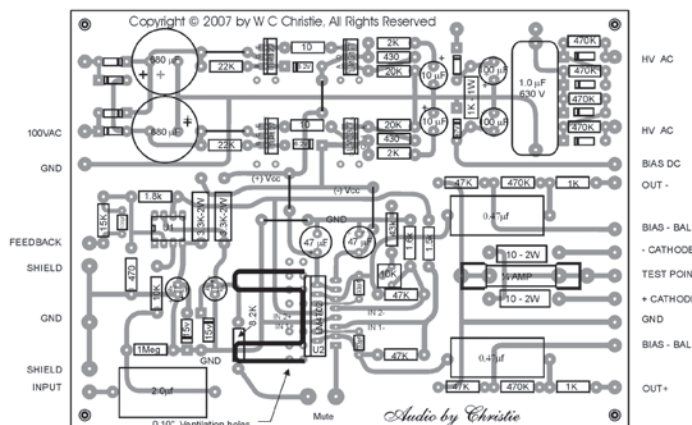

Lundahl Transformers in the U.S.

K&K Audio is now selling
the **premier European audio**
transformers in the U.S.

New Lundahl Products

- Amorphous core tube power output transformers – SE or PP
- Special SE 845 output transformer
- Compact high inductance power supply chokes
- Tube line output transformer

High-End Audio Kits

- RAKK DAC 24bit/192kHz D/A Converter w/ tube output stage
- MM/MC Phono Preamplifier
- MC Phono Step-up Unit
- Differential Line Stage Preamplifier
- Minimal Reactance Power Supply
- Tube Microphone Preamplifier

For more information on our products
and services please contact us at:

www.kandkaudio.com

info@kandkaudio.com voice/fax 919 387-0911

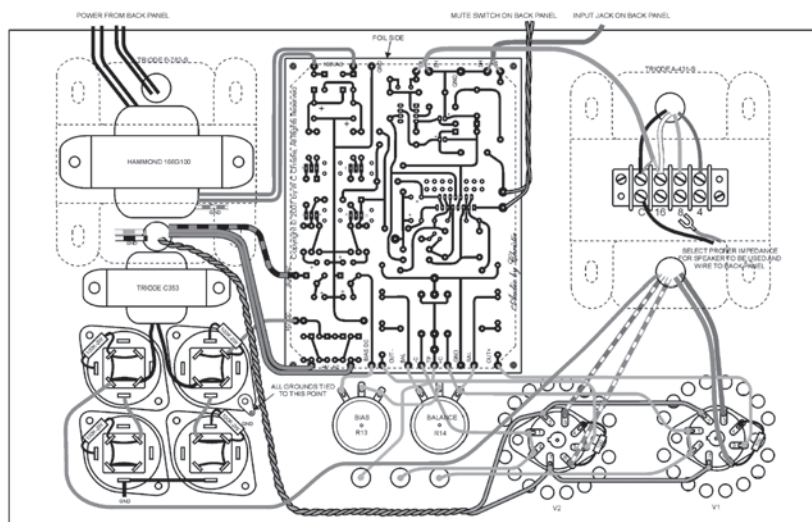


FIGURE 5: Chassis wiring for hybrid amplifier.

you can turn on the amp and measure the voltages. **Table 1** gives the voltages that you should find. Use extreme care when measuring high voltages, which, in this case, are high enough to be lethal.

Once you've checked out the power supplies, remove power and wait about five minutes for the filter capacitors to

PHOTO 3:
Hybrid amplifier
with cover off.

PHOTO 4:
Hybrid amplifier,
bottom view.

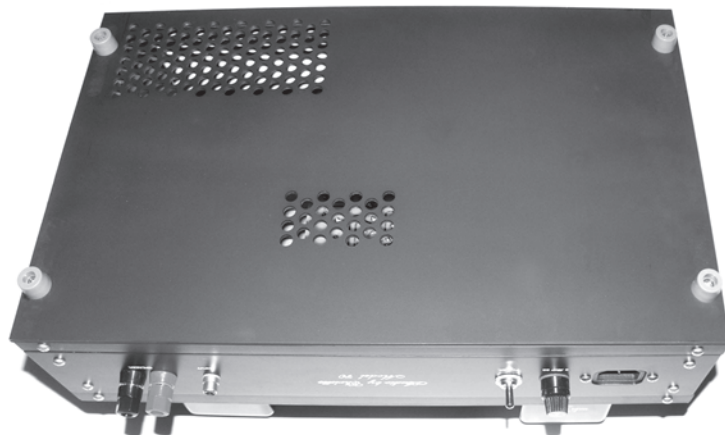
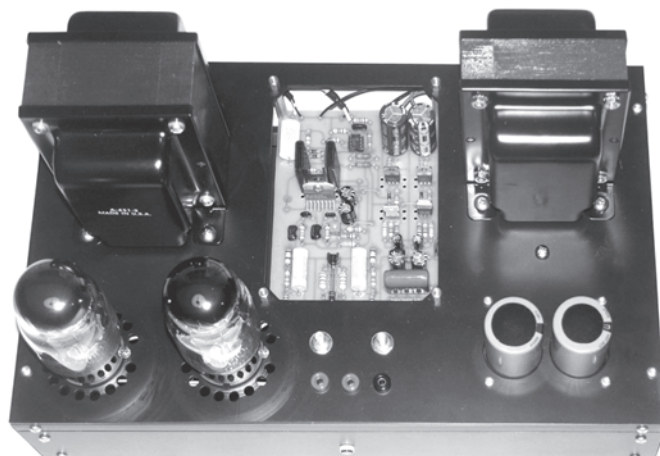


TABLE 1

Preliminary measurements before installing tubes

High voltage DC	+600V	From C10 to ground
+Vcc	+60V	From J1 to ground
-Vcc	-60V	From J2 to ground
U1+ supply	+15V	From U1 pin 7 to ground
U1- supply	-15V	From U1 pin 4 to ground
Raw bias voltage	-78V	From pot R13 to ground
Bias voltage at V1	-69V	From V1 pin 5 to ground (R13 ccw)
Bias voltage at V2	-69V	From V2 pin 5 to ground (R13 ccw)

Measurement with tubes installed and bias adjustments made

High voltage DC	+527V	From C10 to ground
+Vcc	+60V	From J1 to ground
-Vcc	-60V	From J2 to ground
U1+ supply	+15V	From U1 pin 7 to ground
U1- supply	-15V	From U1 pin 4 to ground
Raw bias voltage	-75V	From pot R13 to ground
Balance adjust	0V	From TP2 to TP3
V1 plate current	+70mA	+700mV from TP2 to TP1
V2 plate current	+70mA	+700mV from TP3 to TP1

Note: High voltage DC and raw bias voltage will vary with line voltage. Measurements in these tables were with line voltage at 120V AC and no input signal.

AKFEST 08

BECAUSE MUSIC MATTERS



5th Annual AKFEST

Dozens of Manufacturers & Exhibitors
50 listening rooms
Live music, door prizes
Food, fun and more...

May 3 - 4, 2008

The Plaza Hotel
Southfield, Michigan
PH: 248.552.8833
Special AKFEST 08 Room Rates

Snell

marantz

SALK
Signature Sound

MANLEY
LABORATORIES, INC.

McIntosh

Madisound Speaker Components, Inc.

Audio by Van Alstine

For more information please visit:
www.AKFEST.com

Exhibitors please contact David Goldstein
at ph: 248.200.9074 or info@akfest.com
Brought to you by AUDIOKARMA.ORG

Time-Saving easy-to-use Solutions!

NEW! High-end Testgear



2-ch 60-300MHz 2GSa/s high-end DSOs set a totally new price/performance level. USB, 2K wfm/sec, One-touch autoseup - especially easy to use! We have DVMs and ARBs too.

DS1000 series <\$1000 to \$2K

NEW! Bargain LCD Scopes



Owon - Low-cost 25 or 60MHz color LCD 2-channel benchtop scopes **OR** 20MHz handheld scope/meter. USB interface for printing waveforms. Includes scope probes! Battery versions available!
PDS5022S/PDS6062T \$329 / \$599
HDS1022M/HDS2062 \$499 / \$749

PenScope



PP315 - High-performance USB2.0-pwr scope-in-a-probe! Up to 100MS/s, 25MHz 24kS buffer. +/-

100mV to +/-20V. 20ns/div - 50s/div C/VB/Delphi/LabView/VEE drivers.

PP317 (10MHz) \$234

Mixed-Signal Scopes



100 MHz Scope, Spectrum/Logic Analyzer sweepgen. 4MSample storage! Easy A-B, math & filters! 2 ch x 10/12/14 bit; 8 logic inputs.

CS328A-4 (4MS Buffer) \$1149

CS328A-8 (8MS Buffer) \$1642

CS700A (signal generator) \$249

RF - Tight Testing



RF Testing - Economical benchtop RF test enclosure for troubleshooting, tuning, testing electronic devices in an RF-free environment. 8"H x

17"W x 10 1/2"D inside. Built-in illumination (RF-filtered supply).

STE3000B \$1095

But Wait...There's More

USB to 24 I/O lines.....\$69

USB to 8 Thermocouples.....\$466

USB to 11 x A/D ch.....\$178

CANbus, VME, cPCI, etc.....\$300+

easyRadio modules.....\$40

USB-Serial adapters.....\$20

USB-RS422 1/2/4ch.....\$48+

USB Temperature Logger.....\$60

Stepper Motor Controller.....\$84

Spectrum Analyzers to 7GHz.....\$299 - \$1999

Custom Switches.....from \$1

New products arriving daily!

Check our website for specials!

Saelig
unique electronics
1-888-75SAELIG info@saelig.com

TABLE 2

AMPLIFIER PERFORMANCE

Power output: 60W

IM distortion: Less than 0.1% at 1W

Less than 1.0% at 60W

TABLE 3 PARTS LIST

RESISTORS

R1	10K 1/2W
R2	1 Meg
R3	470 1/2W 1%
R4	15K 1/2W 1%
R5	3K3 1/2W 1%
R6	1K5 1/2W 1%
R7	1K6 1/2W
R8	10K trimpot
R8a	43k
R9, R10	47K 1/2W 1%
R11, R12, R24-27	470K 1/2W
R13, R14	25K chassis mount potentiometer
R15, R16	180K 1/2W
R17, R18	1K 1/2W
R19, R20	10 1W
R21, R22	100 1/2W
R23	8K2 1/2W
R28, R29	100K 2W
R30, R37	Jumper
R31, R38	22K 1/2W
R32, R39	10 1/2W
R33, R40	20K 1/2W
R34, R41	430 1/2W 1%
R35, R42	2K 1/2W 1%
R36, R43	3K3 - 2W
R44	3K3 1W

CAPACITORS

C1	2μF
C2	100pF
C3, C4	15pF
C5, C6	33pF
C7, C8	470pF
C9	1μF at 630V
C10, C11	820μF at 400V
C12, C16	680μF at 100V
C13, C17	10μF at 100V
C14, C18	47μF at 100V
C15, C19	47μF at 25V
C20, C21	100μF at 100V

TRANSFORMERS

T1	Triode Electronics A-431-S
T2	Triode Electronics P-782-S
T3	Hammond 546-166G100

DIODES

ZD1, ZD3	1N4735 (6.2V - 1W)
ZD2, ZD4	1N4744 (15V - 1W)
D1, D2, ...	1N4007 (1A - 1000 PIV)

TRANSISTORS

T1	TIP122 (Darlington) (NPN 100V, 3A, 40W)
T2	TIP127 (Darlington) (PNP 100V, 3A, 40W)

ICs

U1	OPA134PA (Single OP amplifier)
U2	LM4702C (Dual HV OP amplifier)
U3	LM317T (Pos. Adj., 1.5A)
U4	LM337T (Neg. Adj., 1.5A)

VACUUM TUBES

V1, V2	KT88 (Power Tetrode)
--------	----------------------

FUSES

F1	1/4A
F2	3A Slow Blow

discharge. Plug in the input op amp, install the jumpers installed, and then you can test the input and driver stages. With a small signal applied to the input—say 0.1V RMS at 1kHz—you can adjust the AC balance pot to get equal AC voltages from the output of the amps in the driver stage. (Note that the mute switch must be closed to get anything out of the LM4702.)

Once this is done, you should remove the signal and short the input. Prior to inserting the output tubes, preset the bias and balance pot. You should set the balance pot at its mid point and the bias pot fully counterclockwise (zero ohms). Pins 5 of all the output tube sockets should read -45V or more negative. If they don't, then something is wired wrong and needs to be fixed before proceeding. Output tubes, which are expensive, can easily be damaged if the bias voltage is not negative enough.

With the power supplies checked out and the input and driver stages working properly, and again waiting for the filter capacitors to discharge, you can install the output tubes. You need to put a dummy load across the output terminals before turning on the amp. Without it the amp will be unstable and damage to the output transformer can occur.

Now you can adjust the bias and balance pots. You should short the input jack for this procedure. While the tubes are warming up, monitor the voltage across one of the 10Ω cathode resistors (test points 1 and 2 or test points 1 and 3). If it exceeds 0.8V, turn the amp off and look for wiring problems.

After the tubes have had time to warm up—say 3 or 4 minutes—adjust the balance pot for equal voltage on the cathodes (zero volts between test points 2 and 3). Next measure the voltage between test points 1 and 2 and slowly turn the bias pot clockwise to get a 0.6V reading. Let the amp set this way for an hour or so and then readjust the balance as before, and then adjust the bias for a reading of 0.75V between test points 1 and 2.

The amp should now be functioning. The output tubes will change slightly during a burn-in period. After a few days or a week of use, recheck and adjust the bias and balance if necessary. **ax**