

A Multiple "Wall-Wart" Power Supply

Get organized with this handy device that can reduce the rat's nest of plugs and wires.

A power supply is perhaps not a very glamorous or exciting project, but this one is very useful. It replaces ten DC wall-wart supplies, thereby freeing up nine AC outlets. And this, in itself, is a worthwhile accomplishment.


Each output voltage is isolated from the others so there is no common return or ground. I have operated the prototype unit continuously for over three years with no problems. I chose to make nine of the outputs 24V DC, with the tenth

one at 14V. The output voltage is easily settable with two 1% resistors, so you can choose whatever voltages you need (up to about 30V) with the transformers in the parts list. If you set all the outputs to a lower voltage, using a transformer with a lower secondary voltage would minimize power dissipation in the regulators.

The circuit diagram is shown in **Fig. 1**. All ten circuits are identical, with the exception of the voltage set resistor values R3 and R4. The needed values are calculated from:

$V_{out} = 1.25 + (1.25 * (R3 + R4) / 240)$
For example, for 24V $(R3 + R4) = 4368\Omega$. This is closely approximated by choosing standard 1% resistors of 4120 and 249 Ω .

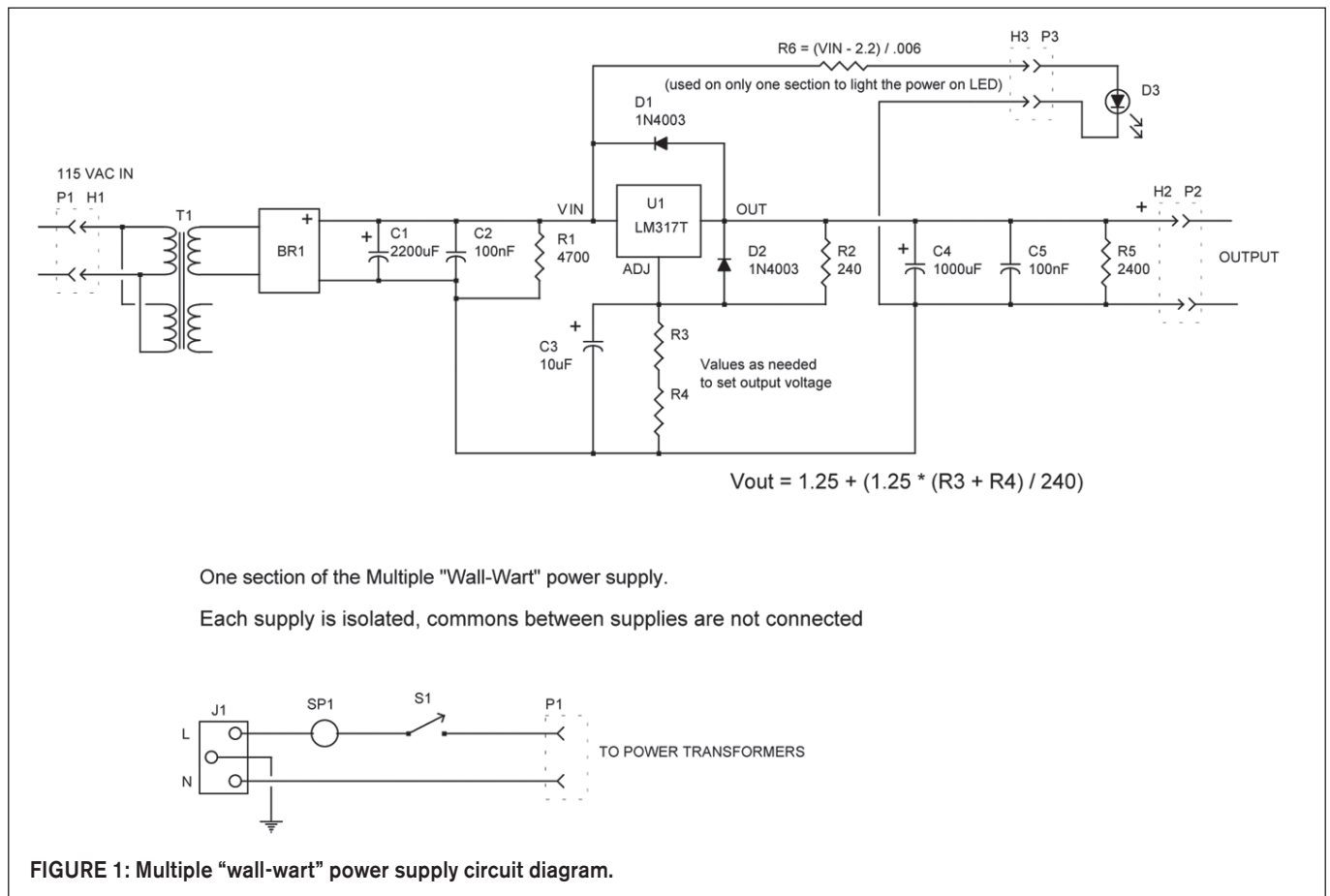Because there are two secondary windings on each transformer, two supplies share a transformer. I considered using one large circuit board, but on second thought this didn't seem like a practical idea. I settled for two different boards: one for four supplies (two boards needed), and the other single board for



two supplies. The circuit board layouts (single-sided) are shown in **Figs. 2 and 3**. (You can download the layout files from the TDL® website.¹) I named this supply a Model 701 (just to keep track of circuit boards and parts), but it is not a product, and I have built only the one prototype. Hence, the front panel has no labels.

CONSTRUCTION

The construction is straightforward and not critical. But because the circuit boards almost fill the enclosure, there isn't much room for variation (**Photos 1 and 2**).

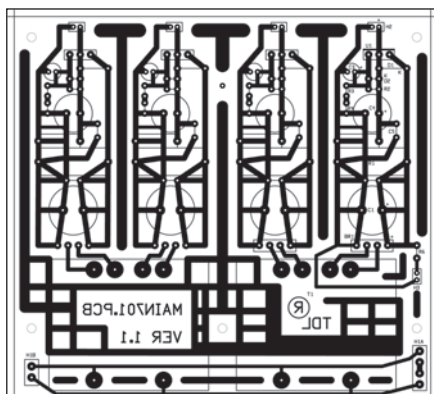


FIGURE 2: Four section supply circuit board. Note that H1B is used to connect AC power from board to board.

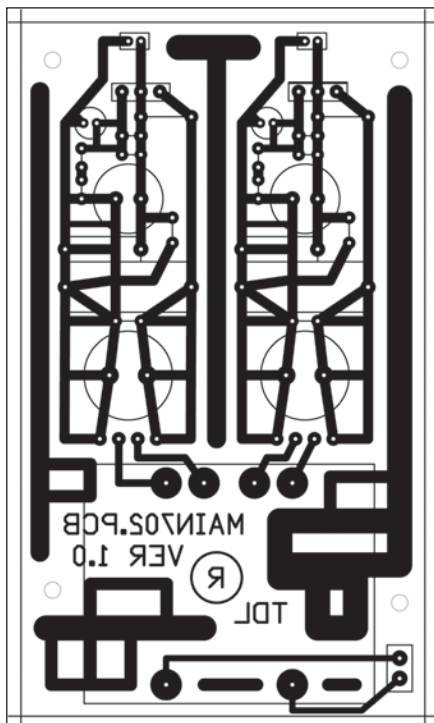


FIGURE 3: Two section supply circuit board.

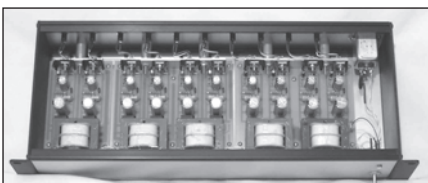


PHOTO 1: Multiple wall-wart power supply inside view. The inrush current limiter, SP1, is directly wired to the fused, IEC AC power input connector.

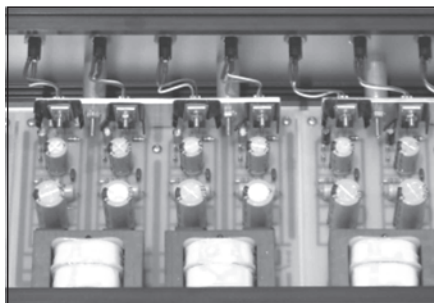


PHOTO 2: Multiple wall-wart power supply inside view. After mounting the circuit boards, measure the distance from the aluminum heatsink bar to the rear panel and cut the 1/2" diameter aluminum rod to this length.



In The 21st Century

Analog playback should be
More Technical
More Objective
More Affordable

The Technics SL-1200 SE
Five Base Models
Seven Genuine Upgrades
Starting At \$475


We Call it The
Audiophile Custom

KAB
Preserving The Sounds
Of A Lifetime
www.kabusa.com

FREE SAMPLE

IF YOU BUY,
SELL, OR COLLECT
OLD RADIOS, YOU NEED...

ANTIQUE RADIO CLASSIFIED

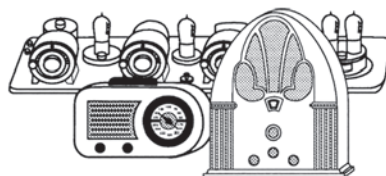

Antique Radio's Largest Monthly Magazine

68 Page Issues!

Classifieds - Ads for Parts & Services - Articles
Auction Prices - Meet & Flea Market Info. Also: Early TV, Art Deco,
Audio, Ham Equip., Books, Telegraph, 40's & 50's Radios & More...

Free 20-word ad each month for subscribers.

Subscriptions: \$24 for 6-month trial.

\$45 for 1 year (\$60 for 1st Class Mail).

Call or write for foreign rates.

The Collector's Guide to Antique Radios, 7th Edition by John Slusser & Radio Daze: 10,000+ prices, 1,200 color photos – \$24.95

Payment required with order. Free shipping! In Mass. add 5% tax.



A.R.C., P.O. Box 802-A16, Carlisle, MA 01741

Toll free: (866) 371-0512 — Fax: (978) 371-7129



Web: www.antiqueradio.com — E-mail: ARC@antiqueradio.com

PARTS LIST

Reference	value	description	source
R1	4700	5%, 3W carbon film	Xicon (Mouser) 283-4.7K-RC
R2	240	1%, 1/4W metal film	Xicon (Mouser) 271-value-RC
R3, R4		1%, 1/4W metal film	values set output voltage for example: for 24V out R3 = 4120 and R4 = 249, for 14V out R3 = 2400 and R4 = 475
R5	2400	5%, 1W metal oxide	Xicon (Mouser) 286-2.4K-RC
R6		1%, 1/2W metal film	value depends on input voltage R6 = (Vin - 2.2)/0.006 (medium bright)
C1	2200µF	50V radial electrolytic	Xicon (Mouser) 140-XRL50C2200-RC
C2, C5	100nF	50V polyester film	Panasonic (Digi-Key) P4525
C3	10µF	25V radial electrolytic	Xicon (Mouser) 140-XRL25V10-RC
C4	1000µF	50V radial electrolytic	Xicon (Mouser) 140-XRL50V1000-RC
D1, D2	1N4003	silicon diode	
D3		red LED, panel mount	Lumex (Mouser) SSH-LXR48161D
BR1		bridge rectifier, 2A 100 piv	MCC (Mouser) RS402L-BP
U1	LM317T	adjustable 3-terminal voltage regulator, TO-220	
J1		IEC power connector with built-in line fuse	
H1A		4-pin header, 0.156"	Molex KK-series 26-60-2040
H1B		2-pin header, 0.156"	Molex KK-series 26-60-2020
H2, H3		2-pin header, 0.1"	Molex KK-series 22-03-2021
P1A		(2) 2-pin shell with terminal pins	Molex KK-series 09-50-7021
P2, P3		2-pin shell with terminal pins	Molex KK-series 22-01-2027
SP1	CL40	inrush current limiter (thermistor)	Digi-Key or Mouser
T1		power transformer	depends on output voltage, for example: for 14 and 24V outputs, a good choice is Jameco # 209015 rCR, each secondary is 24V AC at 400mA. If lower output voltages are needed, using a transformer with lower secondary voltages minimizes power dissipation in the regulators.
		inside heatsinks	for example: Avid (Mouser) 530613B00000G
		rear panel heatsinks	for example: Avid (Mouser) 507002B00000G
		enclosure	rack mount 2RU7 (3.5" high) from Wolgram Engineered Plastics, LLC, 913-491-5414. www.wolgrammfg.com.

The Jameco 209015 is not in their current catalog (#281) but it is on their website, www.jameco.com. The single-quantity price is \$2.59

For reliable operation it's important to get the heat out of the regulators and into the air, preferably outside of the enclosure. Each group of regulators (either two or four) share a common 1" wide × 1/8" thick aluminum bar, which is thermally connected to the rear panel through a length of 1/2" aluminum rod drilled to pass a 6-32 machine screw. As you can see from the photos, each regulator has its own small finned aluminum heat dissipater between the regulator and the aluminum bar. These may not be necessary because the supply operates very cool. However, I prefer to err on the side of "overkill."

The rear panel (**Photo 3**) also has a finned dissipater held in place by each of the five machine screws passing through the aluminum rods. (The regulator mounting tabs are not isolated, so you also need a silicon rubber insulator between each tab and the aluminum bar as well as insulating washers.)

It is important not to omit the inrush current limiter, SP1, because all five transformers are powered on when S1 is closed and must charge a total of 22,000µF (ten times the value of C1) at turn-on. I used

Esoteric 3D-X

from Jena Technologies LLC

Specially formulated for polycarbonate, the new Esoteric 3D-X is designed to dramatically enhance surface transmittance and refractive characteristics of CDs and DVDs. It also protects discs from common contaminants such as oils from your hands and accidental contact with water.

When a disc is treated with Esoteric 3D-X, an optical coating is created that acts similarly to the lens coating of a fine camera. The optical signal-to-noise ratio is improved, and there is less jitter in the original datastream off the disc causing less frequent activation of your player's error-cancellation circuitry.

Although not designed to restore damaged discs, it will clean mild filth and most previously applied coatings from CDs, DVDs, and most SACDs.

Available in a 2 oz. Mini Kit for the home user, the Esoteric 3D-X is also available in a 4 oz. standard kit featuring a handy metal carry case. Both kits include disc enhancer cream, non-latex applicator sponges, lint-free optical quality polishing pads, and a plastic box to hold applicator sponge when not in use.

CD-SACD-DVD Optical Disc Enhancer



KE-3DX	2 oz. Mini Kit	Sh. wt: 1 lb.	\$40.00
KE-3DXS	4 oz. Standard Kit	Sh. wt: 2 lbs.	\$80.00

Old Colony Sound Laboratory PO Box 876
Peterborough NH 03458-0876 USA

Toll-free: 888-924-9465
Phone: 603-924-9464
Fax: 603-924-9467

E-mail: custserv@audioXpress.com
www.audioXpress.com

► To order call **1-888-924-9465**
or order on-line at
www.audioXpress.com

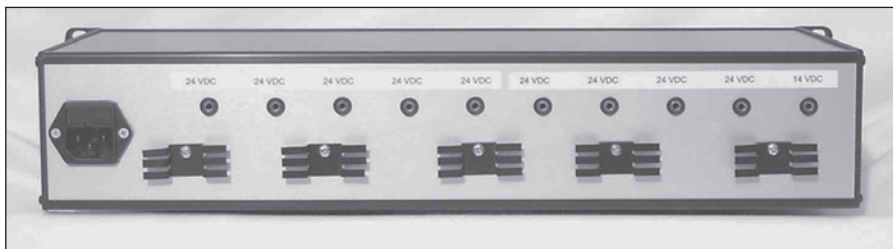


PHOTO 3: Multiple wall-wart power supply rear panel. During continuous operation, the panel is only slightly warm to the touch.



PHOTO 4: Multiple Wall-Wart power supply front panel.

3.5mm insulated mono phone jacks for output connectors because they provide a positive, locking connection and have sufficient current capacity. You could also use two-pin DIN or mini-DIN as well as 1/4" insulated mono phone jacks. The circuit boards are attached to the enclosure bottom panel using 1/2" long nylon spacers and 4-40 x 3/4" screws and 4-40 nuts.

If all the output voltages are the same, no rear panel labels would necessarily be needed. But I thought it would be useful to keep track of which one was 14V. I used a word processor to print two rows of voltages on an 8 1/2 x 11" sheet of sticky-back label, cut them into 1/2" wide strips, and stuck them to the rear panel over the output connectors. If you are going to build one of these with several different output voltages, it might also be helpful to use a different type output connector for each voltage.

FINAL WORDS

This supply is better than the wall-warts it replaces because all the outputs are regulated and have much less hum and noise. I would build another one if need-

ed, but so far the one prototype has been sufficient, although there are times when all ten outputs are in use.

REFERENCE

1. Download wallwart.zip from the downloads page at www.tdl-tech.com. They are in .pcb format and can be printed with a free version of CIRCAD from www.holophase.com. *aX*

*Ready, willing
and*
AVEL



*offering an extensive
range of ready-to-go
toroidal transformers
to please the ear, but won't
take you for a ride.*

Avel Lindberg Inc.
47 South End Plaza
New Milford, CT 06776
tel: 860-355-4711
fax: 860-354-8597
sales@avellindberg.com
www.avellindberg.com

Engineered for Engineers

www.mouser.com
Over 965,000 Products Online

- The ONLY New Catalog Every 90 Days
- NEWEST Products & Technologies
- More Than 335 Manufacturers
- No Minimum Order
- Fast Delivery, Same-day Shipping

(800) 346-6873

**MOUSER
ELECTRONICS**
a tti company
*The Newest Products
for Your Newest Designs*

Mouser and Mouser Electronics are registered trademarks of Mouser Electronics, Inc. Other products, logos, and company names mentioned herein, may be trademarks of their respective owners.

Old Colony Sound Lab often makes available printed circuit boards in support of magazine projects if there is sufficient reader interest. To indicate your interest level in PCBs for this power supply project, contact Old Colony Sound Lab at 603-924-9464, 603-924-9467 (fax), or custserv@audioXpress.com (e-mail). Availability decisions are usually made in about two-three months—watch Old Colony ads for further developments.