

# The Unnecessarily Complex 300B Amplifier

Rube Goldberg meets the directly heated triode.

By Pete Millett



**PHOTO 1: The amp.**

**I** have a confession to make. Even though I've been experimenting with and designing with tubes for many years, I've never designed or built a single-ended directly heated triode amplifier. Until now, that is.

Single-ended DHT amps have always seemed too fashionable. I've always been more interested in doing something out of the ordinary. The high price of triodes such as the 300B and the fact that I hadn't heard many of these amps that really sounded great to me were also major contributors to my prejudice against these amps.

But all along I had this nagging question in my mind: was I missing something? After a fortuitous trade netted me a pair of new 300B tubes, I decided that I really needed to give it a go.

## DESIGN GOALS

If I were to design and build a single-ended 300B amplifier, I decided that I should incorporate as many of the current

design details for this amp that I could. After all, how better to find out whether any of them were worthwhile?

To this end, I deemed the amp needed to use interstage transformer coupling, fixed bias, DC and/or CCS filament supplies, and mercury vapor rectification with a choke-input filter. Some of these design details have clear technical advantages associated with them—the advantages of others were not so clear to me. In any case, even if I wasn't sure what the amp would wind up sounding like, I *was* certain that it was going to *look cool!*

Being the engineer that I am, of course, this also meant that I needed to include circuitry to delay application of B+ until the mercury vapor tubes had sufficient time to heat. And fixed bias meant I needed to design a very clean bias supply, and provide protection so that if the bias supply were to fail, the output stage would be protected from excessive plate current.

The result (**Photo 1**) is an amplifier that I call the “unnecessarily complex”

300B amplifier, because you really don't need all of this complexity to build a good single-ended 300B amp. You could build the same amplifier circuit with a more conventional power supply with a lot fewer components. But, this is a hobby, not a business, and who says we need to be practical?

## THE AMPLIFIER

The amplifier circuitry itself—that is, the part that the audio signal passes through—is really not complex at all. The schematic is shown in **Fig. 1**. The 300B output tube is coupled to the speaker via a Tango XE-20S output transformer.

The 300B's grid is driven through a 1:1 interstage transformer (I used a Tango NC-14) by a two-stage amplifier using two sections of a 5687 or 7044 dual triode, DC-coupled to each other. I found both the 7044 and 5687 worked equally well, as should the 7119/E182CC tube. Power to the first stage needs to be decoupled with an RC filter; without it, I found that there is a considerable gain peak at low frequencies. Note that a large (and relatively high voltage) cathode bypass capacitor is required on the second stage to provide enough gain, and to keep the  $Z_{out}$  low enough to drive the interstage transformer, especially at high frequencies.

The negative grid bias voltage for the 300B is delivered through the interstage transformer. The bias voltage is adjustable via a pot, and is bypassed to ground with a 3.3 $\mu$ F polypropylene film capacitor.

My initial design used a single-stage driver, using a triode-connected EL802 tube, a very high-Gm pentode designed for video amplifier service. This design was simpler and actually performed slightly better than the two-stage design











pass capacitor on the first stage, increasing if a smaller capacitance is used.

Every attempt I made to tame this high-frequency nastiness resulted in an increase in HF distortion or an unacceptable drop in HF response, so I left it alone. As long as the input signal doesn't contain much energy at these frequencies—which normal, well-behaved audio sources

**Figure 9** shows a plot of THD + noise versus frequency at 1W output into 8Ω. As you normally see in this type of amp, THD rises at both low frequency (due to trans-


**Figure 10** shows an FFT spectrogram of the amplifier output at 1kHz and 1W. As expected of a single-ended amp, the distortion spectrum is dominated by the second and fourth harmonic. The third harmonic is over 90dB below the fundamental.

Finally, **Fig. 11** shows a plot of THD + noise versus output power. Due to the well-filtered power supplies and DC filament operation, this amplifier is very quiet; not much noise appears at the low end of the plot. THD increases as expected with increasing power. The onset of clipping occurs at approximately 7W, and the THD rises rapidly past 5% above about 8.5W. Note that this is with the output transformer connected with a 3.5k $\Omega$  load impedance on the 300B.


What does it sound like? Well, it sounds like a single-ended 300B amplifier!

I had much better results listening with my higher-efficiency Fostex-based speakers. Initially, I found the sound of this combo a little too wild—somewhat underdamped bass and a little rough on the high end. I re-wired the output transformers for a 5k plate load instead of 3.5k, which results in a little less power, but lower distortion and lower output impedance. This eliminated the problems, so I listened extensively to this combination.


As you might expect, some types of music sounded better on this system than others. Vocals, both female and male, were very special. There is a sense of realism that I don't get with many of my other amplifiers. The soundstage was also extended, and I noticed small details

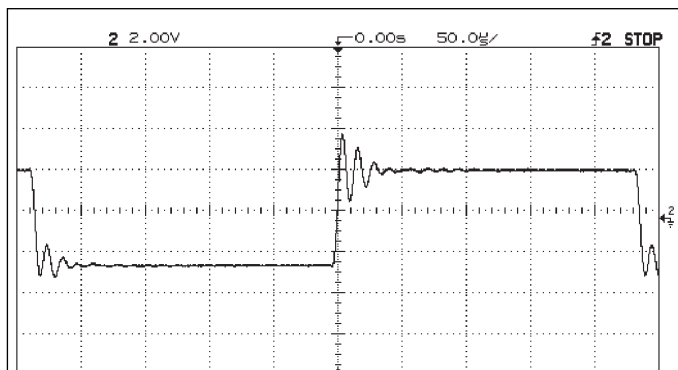


**FIGURE 8: Square-wave ringing.**

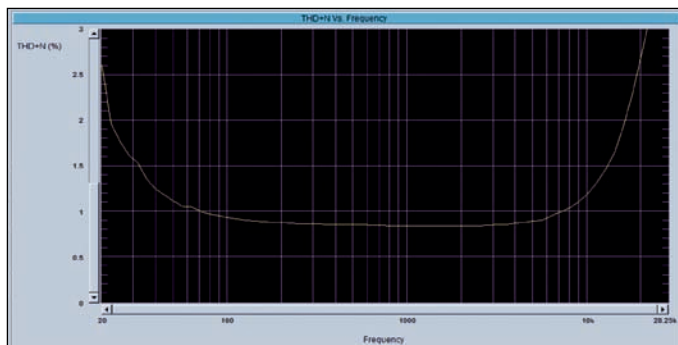

**FIGURE 9: Distortion vs. frequency.**

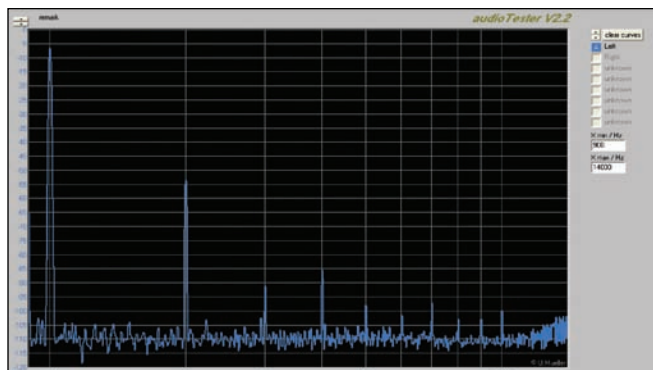

**FIGURE 10: FFT spectrogram of amp output at 1kHz and 1W.**

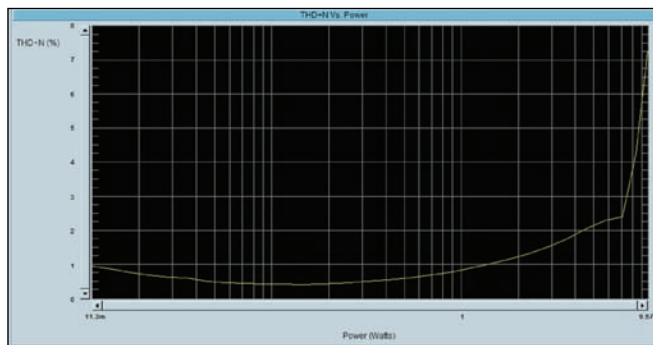

**FIGURE 11: THD + noise vs. output power.**





