

paX, Part 2

Continuing with the paX amp design, covering the voltage amplifier and input buffer stages.

Last month I discussed the principle of error correction and developed an error-correction power output stage. In this installment I will use H.ec in a voltage amplification stage and present the complete amplifier.

BACKGROUND

Let me back up to the conceptual circuit of error correction, as defined by Malcolm Hawksford, shown in **Fig. 1A**. You know that if the summers S1 and S2 are unity gain summers, you get $V_{out} = V_{in}$, an ideal gain-of-one amplifier stage. But for the voltage amplification stage (Vas) that drives the output stage, you need much more than unity gain.

Common amplifier gains are around 26 to 30dB, a gain of some 20 to 30 times. I like the lower value because it is better to have less gain in the power amp than to have a lot of unnecessary gain, only to need to turn down the volume control to get rid of it. It turns out you can use H.ec in voltage amplifiers quite easily if you insert an attenuator in the V_{out} sense leg, similar to what you would do in a regular negative feedback circuit.

I did that in **Fig. 1B**. The sums are slightly different: $V_c = (V_{out}/\beta) - V_e$, but still $V_e = V_{in} - V_c$. Substitution and rearranging shows that now $V_{out}/V_{in} = 1/\beta$. So, if you make β , as is customary, from a simple resistive 1:20 voltage divider, you now have an amp with gain, linearized by error correction.

One other very important note: When I found that the open-loop gain was no longer part of the amp transfer equation, I said that the gain of the amp block no longer had any bearing on the final result. That is true in theory, but

not in practice.

In the case of the power output stage, I said the gain is "about 1." A realistic value would be 0.98 at mid frequencies and light load, down to 0.95 at higher frequencies and higher loads. That means that the error-correction circuit needs to add 0.02 to 0.05 times the signal level to the input to straighten out the amp. Intuitively, I believe it is advantageous to have only small signals in the error-correction circuitry that helps it to work linear and with low distortion.

But in the case of the Vas, if the forward gain block has only a gain of 1, the error-correction circuit will need to add 19 times the signal level, and it would be much more difficult to design simple circuits that could handle those levels with high linearity. So, what you need is to make the open-loop gain of the Vas amplifier block such that the signal levels in the error-correction circuit are minimized. This will be the case when the open-loop gain is as close as possible to the closed-loop gain. Then, there will be quite small differences between the input of the actual amplifier and the scaled-down output (by β), and that small difference then is the error signal.

This, of course, is totally at odds with what you would do for a negative feed-

back amp. There, you would try to get the highest open-loop gain you can get away with, stability wise, to have a lot of excess gain for the feedback loop to work with. Not so with H.ec, and a corollary to this is that your V_{as} can now be a very simple gain-of-20 amp.

VOLTAGE AMPLIFIER

The particular topology I chose is in **Fig. 2**. It's very simple. U1 is a unity-gain buffer. V_{in} applied appears at the buffer output across R7.

The output current through R7 comes from the supplies, of course, so you find a signal current $V_{in}/R7$ in the current mirrors formed by Q1 and Q3. The DC quiescent current for the buffer (I'll tell you later which buffer type I used) happens to be about 7mA. With an R7 value of 220 Ω and a current of 14mA peak-to-peak available, this buffer can handle a little over 3V peak (about 2V RMS) before running out of class-A, which, of course, is good for linearity. With an amplifier gain of 20 that is enough to deliver 100W in 8 Ω .

That same signal current in Q1, Q3 is mirrored through Q2, Q4 and flows through R16 to generate the output voltage. As a first approximation, be-

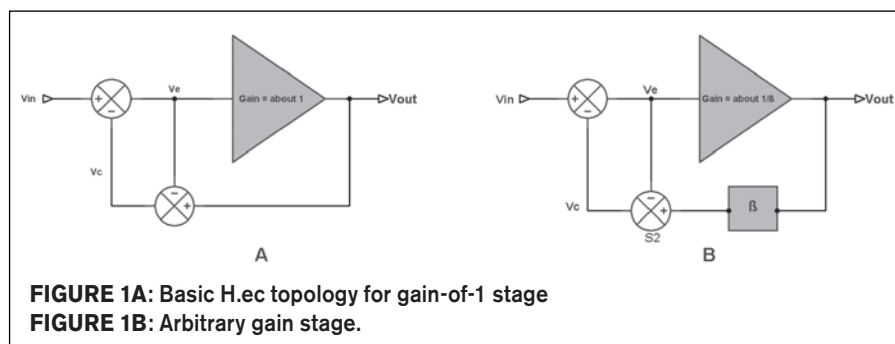


FIGURE 1A: Basic H.ec topology for gain-of-1 stage
FIGURE 1B: Arbitrary gain stage.

Now that you have the main gain block for the V_{as} , enclose it in an er-

audioXpress September 2009 **11**

ror-correction loop as you did with the output stage (Fig. 3). Note here, that, first, although both the EC sense and

the EC generation resistors are given as “R,” they are not equal. The sense resistance value at the right is the sum of resistor R plus the output resistance of the β -network (R_{11}/R_{12}). It is the total resistance of R plus R_{11}/R_{12} that determines the error current into the CCII. That same current generates the EC voltage when flowing through the left side R, and these voltages should be equal, so similarly, the left side “R”

is actually the series resistance of the nominal R and the output resistance of whatever V_{in} source will drive the V_{as} . I’ll come back to this issue later.

Second, note that the gain of this amp is not strictly $1/\beta$. Terminal Y is a virtual earth point. To calculate the exact attenuation from V_{out} to the node R_{11} , R_{12} and R, you need to account for the fact that for the attenuation, seen from the V_{as} output V_{drive} , R appears in parallel with R_{11} . So, the attenuation, and thus the gain, is slightly higher than $1/\beta$.

You need to consider both of these issues when you dimension the error-correction sense and generation resistors. Just as with the output stage, I use an AD844 current conveyor for the EC circuit, while the buffer is used in the amplifier input stage to drive R_7 . The complete V_{as} circuit is shown in Fig. 4.

I have yet to mention the diodes D_9 , D_{12} , D_{13} , and D_{14} . What happens if you overdrive the amp? The positive feedback loop is regenerative and will continue to increase the input signal until stopped by some physical limit such as the supply voltage or current or voltage limitations in the circuit. In the V_{as} stage, this is limited by the four diodes across the error-correction generation resistor R_{29} (Fig. 4).

When the amp is overdriven, the error correction current out of pin 5 of the AD844 CCII will increase considerably. This current will start to generate a large correction voltage across R_{29} , to the point where the threshold voltage of the diodes is reached. At that point, the effective impedance of R_{29} collapses to just the dynamic diode impedance that is only a few tens of ohms. Further increases in the error-correction current will not generate more error-correction voltage and the positive feedback loop is broken. This makes the clipping clean and recovery fast. But you run the risk that the diodes increase the distortion because they may already conduct small current before the threshold, which would upset the error-correction accuracy.

It turns out that because of the very small error-correction voltages across R_{29} , this can be avoided. In Fig. 6 you see that if you use a single pair of soft clipping diodes, the distortion starts to

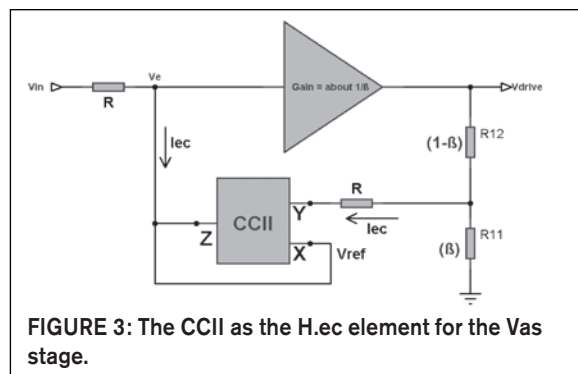


FIGURE 3: The CCII as the H.ec element for the V_{as} stage.

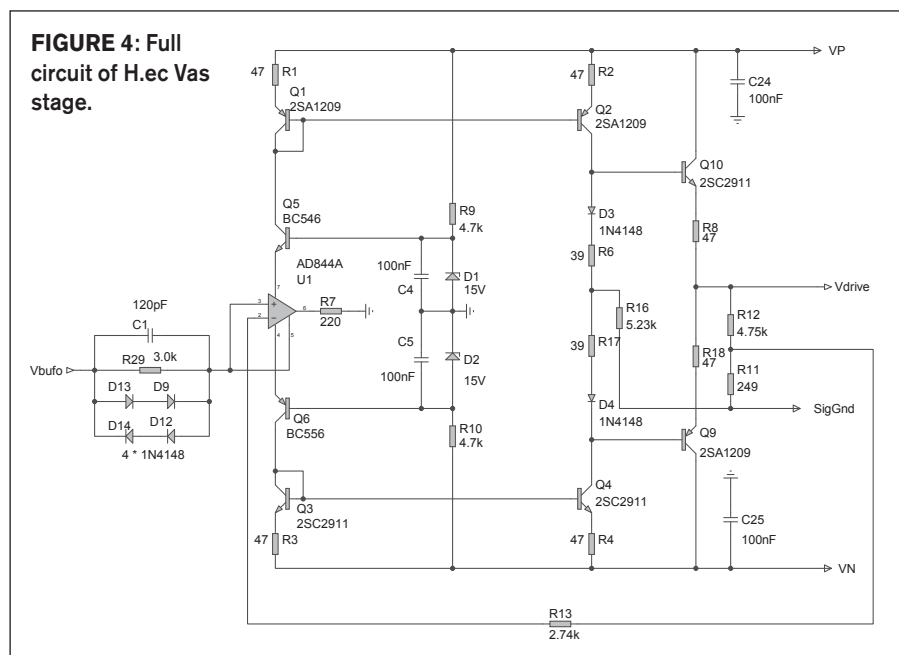


FIGURE 4: Full circuit of H.ec V_{as} stage.

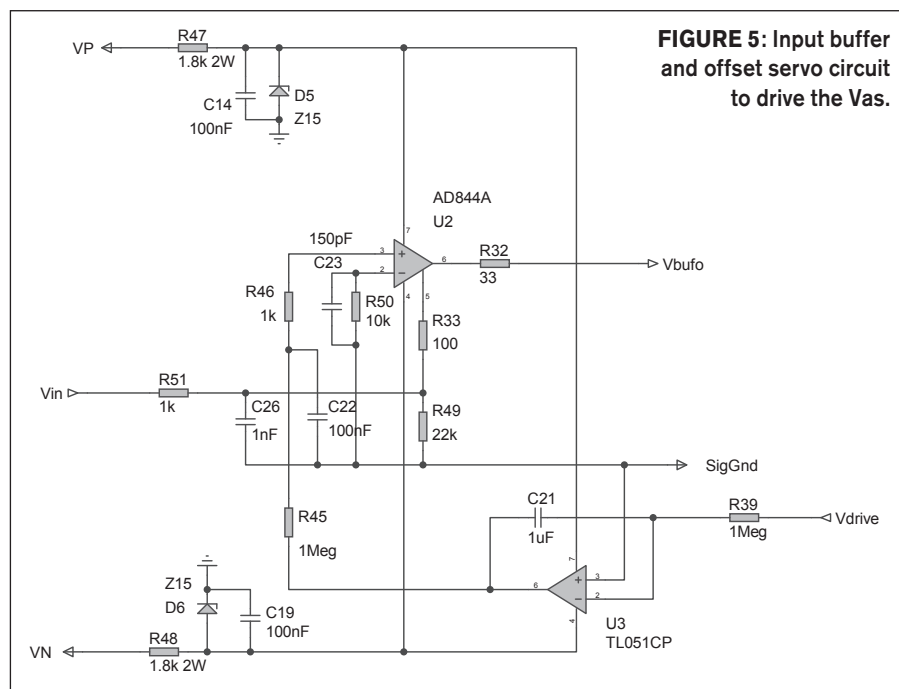


FIGURE 5: Input buffer and offset servo circuit to drive the V_{as} .

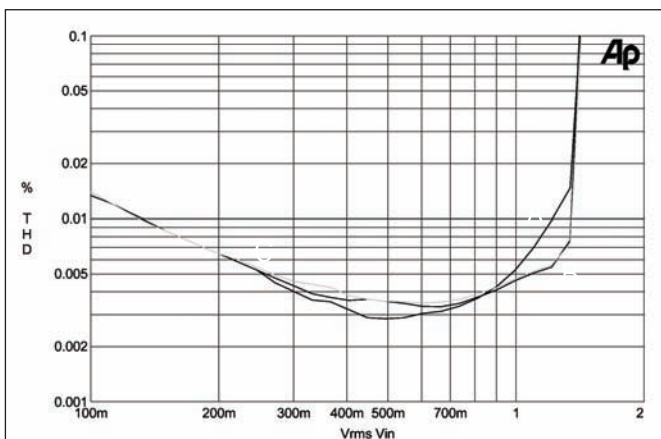


FIGURE 6: Amp distortion as a function of output level, with single diode (A), dual diode (B), and without soft-clipper diodes (C).

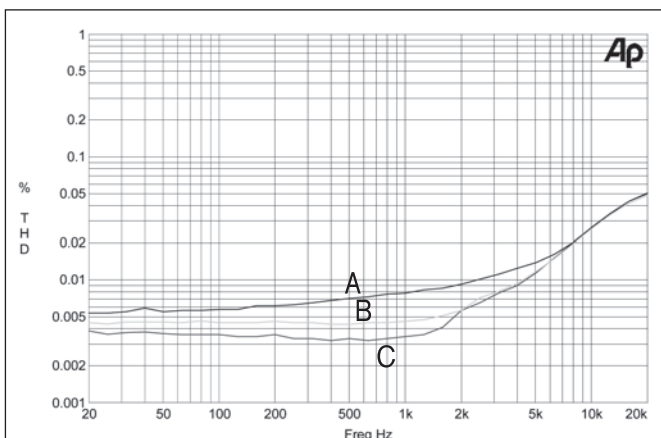


FIGURE 7: Amplifier distortion vs. frequency at 50W in 8Ω, with single diode soft clipper (A), dual diode soft clipper (B), no soft clipper (C).

rise before maximum output. With the dual pairs, no difference is apparent.

Figure 7 shows this effect from a different perspective. The soft clipping diodes for the negative signal part have been temporarily removed so only the positive signal is affected. You can see that without the diodes, clipping recovery is delayed (negative part), while with the diodes (positive part), there is only a hint of delay.

BUFFER STAGE AND DC OFFSET

All that is needed now for a complete amplifier is the input buffer and the DC offset servo (**Fig. 5**). Just as with the output stage, you need to drive the *Vas* input resistor, which develops the *EC* voltage (*R29*), with a low impedance source. You guessed it: I will again call upon the open-loop buffer in an AD844 to drive the *Vas* from *Vin*. The signal enters the buffer in *U2* through *R51* and *R33* at pin 5 and exits at pin 6.

The enemy of your speakers (and the amp as well) is DC offset at the output terminal. Most amps have some sort of means to avoid that. In this amplifier, the output stage itself doesn't need any additional measures: the error correction ideally duplicates the driving voltage (from the *Vas*) to the output terminal, with zero offset, although there will still be

MCap® RXF Radial Xtra Flat Capacitor

by MUNDORF
Made in Germany

MCap® RXF Oil

Featuring the ultimate winding geometry (edgewise) for

- extremely short, low-loss signal transmission,
- extremely reduced residual-resistance (ESR),
- remarkable low residual-inductivity (ESL).

Polypropylene capacitor-foil, alu metallized. Grouted winding against microphonic effects.

- Fit-In-Adaptors now available.



TubeCap® - Optimized High Voltage MKP

MCap® Supreme



MCap® Supreme Oil and Supreme Silver/Gold/Oil

MCap® Supreme
MCap® Supreme Silver/Oil
MCap® Supreme Silver/Gold



Audiophile Resitors



Silver/Gold Internal Wirings



MSolder™ Silver/Gold MSolder™ Supreme



Varied Foil Coils & Air Core Coils

Exclusive Argentinean Distributor
SK NATURAL SOUND
www.naturalsound.com.ar

See more audio innovations on
www.mundorf.com
and subscribe for our newsletter
info@mundorf.com
OEM and dealer inquiries invited



High End Components Made In Germany Since 1985

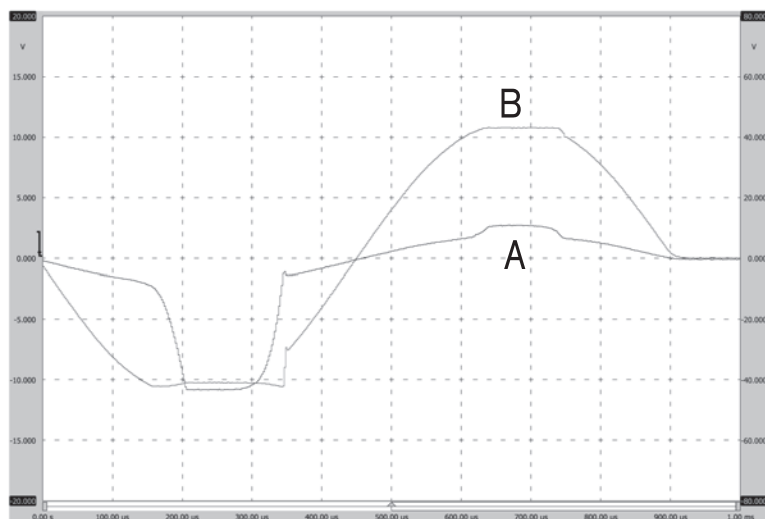


FIGURE 8: Error-correction current (A) and amplifier output clipping (B) with soft clipper (positive signal) and without soft clipper (negative signal).

TABLE 1: AMPLIFIER PARTS LIST

Category	Reference	Value	
Resistors 0.25W MF	R1-4, R8, R18	47	
	R6, R17	39	
	R7	220	
	R9, R10, R12	4.75k	
	R11	249	
	R13	2.74k	
	R16	5.23k	
	R19, R20, R30, R31	2.15k	
	R21-24, R33, R60	100	
	R25, R34	4.99k	
	R26, R27, R40-43, R46, R51	1k	
	R28	10	
	R29	3.0k	
	R32	33	
	R35, R36	619	
	R37, R38	680	
	R39, R45	1 Meg	
	R44	7.5k	
	R50	10k	
Resistors 5W ceramic	R52-R55	0.22E	
Resistors 2W MF	R47, R48	1.8k	
	R64	1.5E	
	R65	6.8E	
Capacitors	C1, C3, C23	150pF	polypropylene or mica 0.2" pitch
	C2, C4, C5, C9, C14-16, C19, C22, C24, C25	100nF ceramic	0.1" pitch
	C6-C8, C13, C21	1μF/63C foil	0.3" pitch
	C10	220nF/50V ceramic	0.2" pitch
	C11, C12, C17, C18	470μ/63V	0.2" pitch, 0.5" diameter
	C26	1nF foil	0.2" pitch
ICs	U1, U2, U4	AD844AN	
	U3	TL051CP	
Transistors	Q1, Q2, Q9	2SA1209	
	Q3, Q4, Q10	2SC2911	
	Q5, Q11, Q17, Q18	BC546B	
	Q6, Q14, Q19, Q20	BC556B	
	Q13, Q16	STD03N	(+ isolation pad and mounting hardware)
	Q12, Q15	STD03P	(+ isolation pad and mounting hardware)
Connectors	J9	Header 2*1 pin	signal input
	J10	Header 2*3 pin	to protection board
Diodes	D3, D4, D9, D12, D13, D14	1N4148	
	D1, D2, D5, D6, D10, D11	Z15 0.5W	
	D7, D8	1N4003	
Miscellaneous	L1	5μH	see construction guide
	RV1, RV2	200E trimmer	
	PCB		
	IC socket (4)	DIL08	

some offset of a few millivolts from the error-correcting AD844. The only requirement is that the Vas has negligible DC offset.

The Vas, however, has higher gain and will amplify its own AD844 offset with that gain. I decided to implement a DC servo to keep the Vas offset under control. The servo uses a standard low-offset op amp, a TL051CP. I will use the uncommitted current conveyor in that input AD844 (U2, Fig. 5) to couple the servo signal to the amplifier.

The way this works is as follows: Remember that whatever current flows in or out of the low impedance input pin 2, also flows (in opposite direction) out of or into pin 5. You also know that the voltage at pin 2 and 3 will track accurately. When you couple the servo signal to the reference input pin 3, it will cause a current in R50 to keep pin 2 at the same level. That same current will flow in R33, and in this way the offset correction will be added to Vin. R49 ensures that that current, which essentially is DC, can flow in R33 even if the Vin comes from a coupling capacitor.

Finally, this input buffer and servo amp have their own $\pm 15V$ supply from two zeners, D5 and D6. With this circuit, compound offset of the whole amp is just a few millivolts.

POWER SUPPLY

The power supply for this amp should deliver about $2 \times 42V$ DC. Although the output devices are rated for higher voltages, it is not advisable to increase the supply in trying to achieve more output power. The allowed dissipation at higher Vce is much less than the rated DC dissipation due to secondary breakdown limitations of the SOA (Safe Operation Area). With loads that dip substantially below 4Ω , even temporarily, the SOA may be exceeded and an output Darlington destroyed. The supply for the error-correction circuit in the output stage is bootstrapped from the output; that part of the circuit can actually drive the output devices beyond the supply voltage.

Consequently, it is the Vas that determines how close the output can

get to the supply rails. Because the Vas will clip first, there is no clipping overdrive and overdrive delay in the output stage. The output can swing within a few volts of the supply, which is better than in most amps (unless you use separate higher voltage Vas supplies).

The power supply is uncritical. The error correction not only corrects internal amp nonlinearities, but also any power supply ripple or noise that makes it into the circuits. (The supplies for the error-correction AD844s are stabilized separately with zener diodes.) Therefore, a classic rectifier-and-reservoir capacitor supply delivering 2 * 42V DC under load is sufficient for about 100W in 8Ω, 200W in 4Ω.

The power supply circuit details are given in **Figs. 9** and **10**. For a stereo version, a 300 or 400VA transformer should be sufficient; after all, you will not drive both channels at full power for a long period (except maybe on

the test bench). You can use the common transformer with a center-tapped secondary, but you can use other configurations.

One nice option for a stereo amp is to use two completely separated supplies, each with a 250 or 300VA transformer. Completely separated supplies for each channel make it easier to maintain strict star grounding.

It is important to get the grounding right. Ground currents back to the supply from the speaker, as well as from the reservoir caps, can be quite large and have all kinds of ripple and noise. Such ground currents generate voltages across the ground return wiring. If the ground for the signal is connected to this ground wire at another point, you have effectively produced a small ripple signal that appears in series with the input signal. This may seem far-fetched, but with very low distortion and very clean amplifiers, even a few mV of these

noise signals can be enough to ruin the linearity and distortion figures of an otherwise very good amplifier.

Usually you try to prevent this by using a star ground: All ground returns come together at a single point, and no signal return runs through the same ground wire with another return loop. The power connections to the PCB also get to a central star point. On the PCB itself, I've tried to maintain this. There are two or three separate traces that bring the returns for the regulator zeners and the decoupling capacitors to the same point.

The signal returns from the input network, the gain setting resistors R7, R16, and the attenuation network R11, R12 are brought to a separate point. All return wires from the supply, the transformer, and the speaker are returned to this point, the star ground.

The signal grounds are returned to this point via a low-value resistor R28, which is then by definition the "clean" ground point (pad J1 on the PCB is the clean ground and should be used

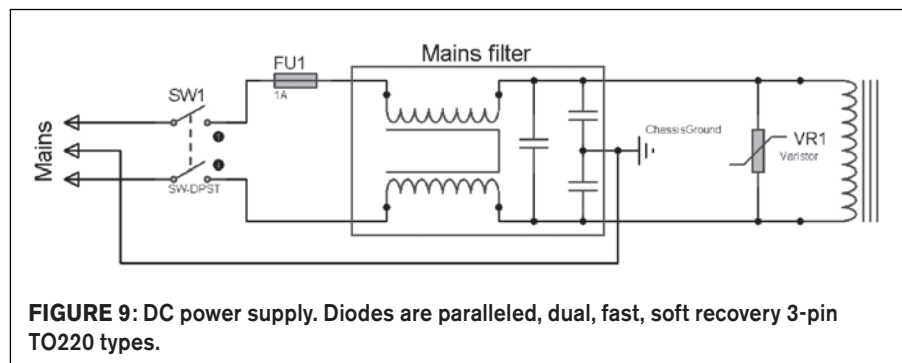


FIGURE 9: DC power supply. Diodes are paralleled, dual, fast, soft recovery 3-pin TO220 types.

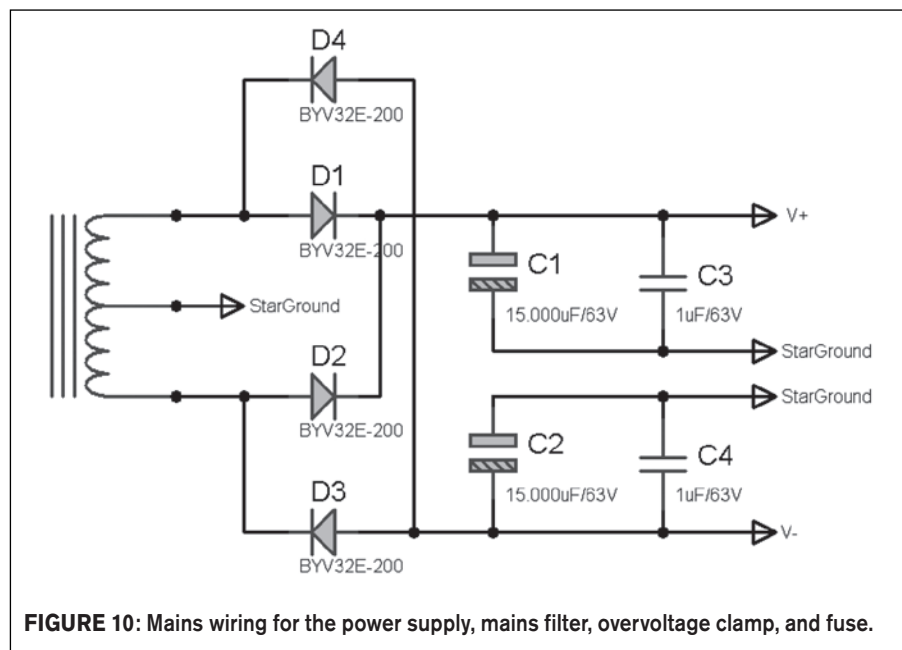


FIGURE 10: Mains wiring for the power supply, mains filter, overvoltage clamp, and fuse.

THE audio engineer's hands-on X-over design & speaker voicing tool.

ATTENTION!
Audio professionals, hobbyists, installers
and University students/professors...

The Virtual CROSSOVER BOX™
by **Vidsonix Professional**
MODEL VCB-100

Shipping Wt:
7 lbs.
K-VCB100
\$249.95

Now includes our exclusive
Crossover Design Pocket
Slide Tool!

Old Colony Sound Laboratory
PO Box 876, Dept. L152
Peterborough, NH 03458-0876 USA
888-924-9465 Fax: 603-924-9467
E-mail: custserv@audioXpress.com

Call 1-888-924-9465
today or order on-line
at www.audioXpress.com!

OLD COLONY SOUND LAB

We also design and manufacture home theater, marine, and professional loudspeakers and accessories. Individual drivers, including all Thiele-Small parameters, are also available on our website.

Vidsonix Design Works
508 Performance Rd., Mooresville, NC 28115
(704)658-9617
More info at: **www.VIDSONIX.com**
©2009 VIDSONIX. All Rights Reserved

as “ground” for measurements as well). Any error voltages generated by ripple and pulsating currents in the ground wires cannot end up in the signal, except through radiation. In turn, you can minimize this by making all high-current wires short and as far away from sensitive signal areas as possible.

Finally, the rectifier diodes should be types that recover quickly from voltage reversal when switching off, and do so “softly”—that is, without very sharp current steps. Diodes that take a long time to reverse themselves and in the process generate sharp current steps may cause high-frequency noise that is difficult to filter out. Fast, soft recovery types don’t need capacitors or snubbers; indeed, such capacitors would only increase the transmission of mains-borne noise to the amplifier.

I recommend you use Philips BYV32E-200 diodes, which are TO220 dual types with a common cathode; the two diodes should be paralleled. They have a relatively small threshold voltage, and are quite inexpensive. They don’t need to be

heatsinked, so you can put them on a PCB in free air. For the reservoir capacitors, you should use a minimum of 15,000 μ F per supply polarity. 63V rating is adequate.

You should use a mains filter (Fig. 10) to keep out high-frequency noise and switching pulses riding on the mains. Good mains filters are not cheap but worthwhile; use a type with at least 12A rating for US (120V) mains. Ground the filter ground lug as well as the mains safety ground wire to the chassis only. Use a slow-blow fuse of 6.3A for a stereo version, larger if you use larger reservoir capacitors. A 150V AC varistor clamps any high-level pulses that make it out of the filter.

CONCLUSION

So, there you have it, a complete, high-quality yet simple error-correction power amp. A complete parts list is in Table 1. Although harmonic distortion measurements do not always correlate with sound quality, they do give an indication of linearity and behavior of an amplifier. Therefore, a few performance

curves are given in Figs. 7 and 8.

If you want to build this amp, there is a detailed Construction Guide for the amp on the *audioXpress* website. Working step-by-step, checking your work after each major part will help to avoid errors and, if errors are made, to quickly isolate and fix them. Also check on my website for any last-minute information, additions, or corrections.

This is not a very difficult project, but will give you an excellent amplifier, which reproduces your source music faithfully—adding nothing, taking nothing away. This amplifier is stable and will happily drive a wide range of different speakers. In short, an amplifier that will let you enjoy your music for many years to come! **ax**

[This article originally appeared in the April and May '08 issues of *Elektor*—Eds.]


Further reading: A MOSFET Power Amplifier with Error Correction, Robert R. Cordell, *Journal of the Audio Eng. Soc.*, Vol.32, No.1/2, 1984 January/February; also available at www.cordellaudio.com.

D-4 PROTOTYPING PC-BOARD

designed by D.H. Labs

audioXpress author, Gary Galo, has this to say about the board. “The board is very ‘generic’ and should accommodate a variety of IC op-amp projects without needing any modifications. Power supply, ground and parts connection traces are laid out intelligently...The D-4 is now my first choice for small audio op-amp projects.” *audioXpress*, June 2007.

PCBD-4 \$5.00

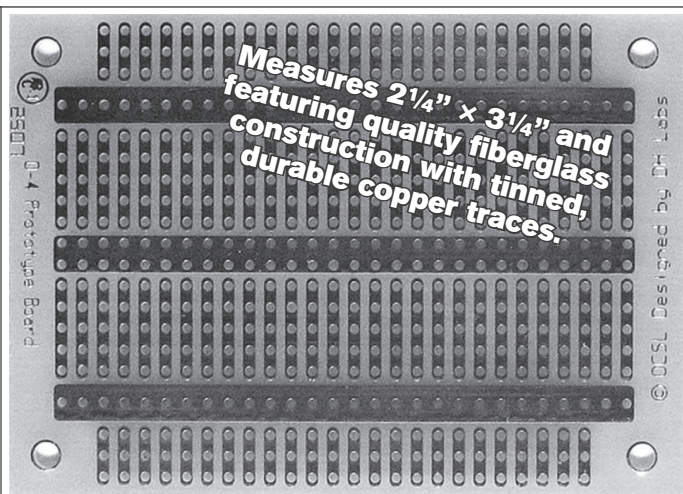

To order call 1-888-924-9465 or order on-line at www.audioXpress.com



Old Colony Sound Laboratory PO Box 876 Peterborough NH
03458-0876 USA
Toll-free: 888-924-9465 Phone: 603-924-9464
Fax: 603-924-9467
E-mail: custserv@audioXpress.com



www.audioXpress.com